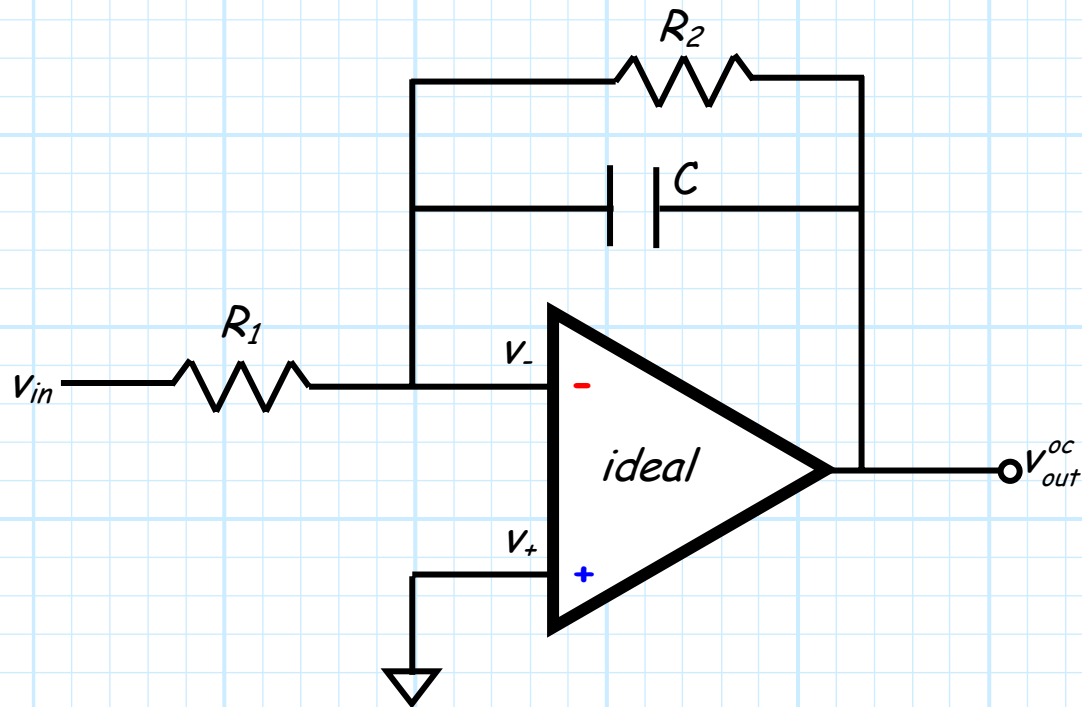


# Example: An Inverting Network

Now let's determine the complex transfer function of this circuit:



## It's the inverting configuration!

Note this circuit uses the **inverting** configuration, so that:

$$G(\omega) = -\frac{Z_2(\omega)}{Z_1(\omega)}$$

where  $Z_1 = R_1$ , and:

$$Z_2 = R_2 \parallel \frac{1}{j\omega C} = \frac{R_2}{1 + j\omega R_2 C}$$

Therefore, the **transfer function** of this circuit is:

$$G(\omega) = \frac{v_{out}^{oc}(\omega)}{v_{in}(\omega)} = -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_2 C}$$

## Another low-pass filter

Thus, the transfer function **magnitude** is:

$$|G(\omega)|^2 = \left(-\frac{R_2}{R_1}\right)^2 \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

where:

$$\omega_0 = \frac{1}{R_2 C}$$

Thus, just as with the previous example, this circuit is a **low-pass filter**, with **cutoff** frequency  $\omega_0$  and pass-band **gain**  $(R_2/R_1)^2$ .