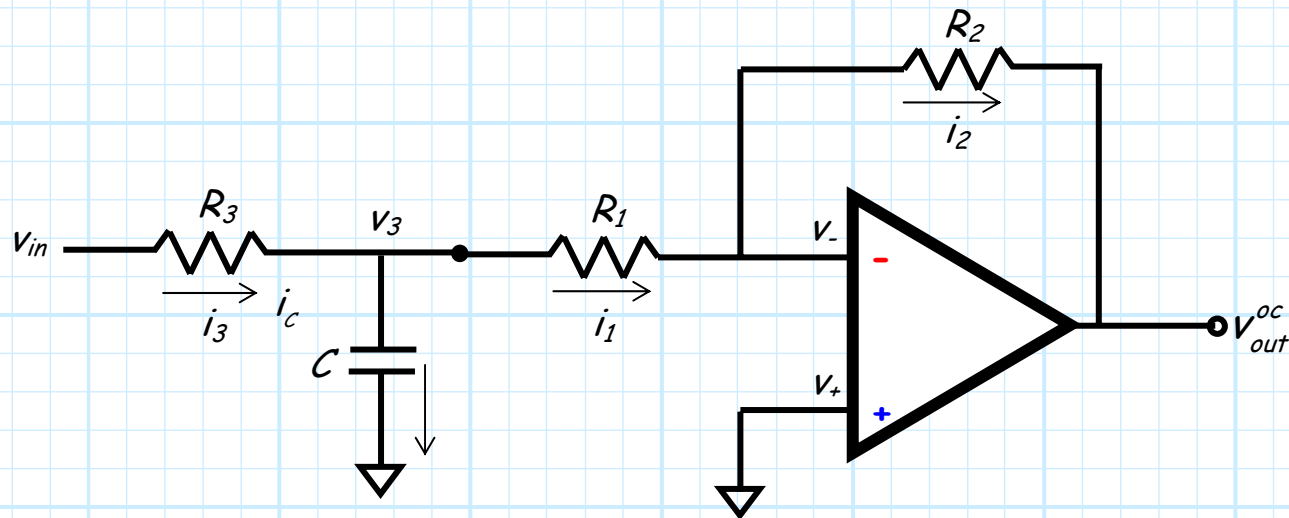


# Example: Another Inverting Network

Consider now the transfer function of this circuit:




## Some more enjoyable circuit analysis

To accomplish this analysis, we must first...

*Wait! You don't need to explain this to me.*

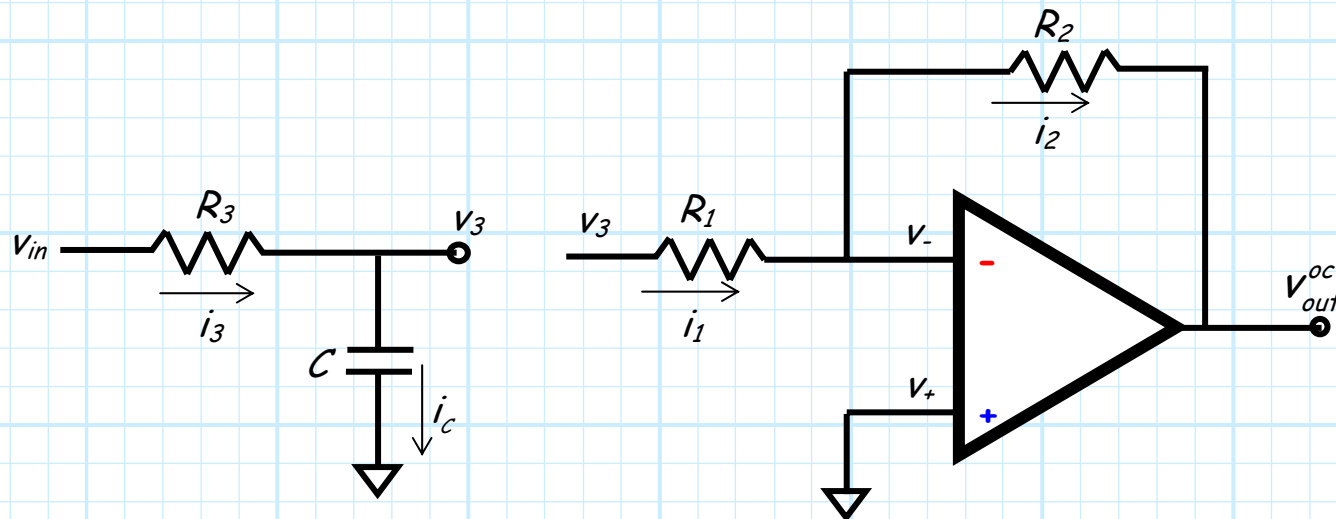*It is obvious that we can divide this is circuit into two pieces—the first being a complex **voltage divider** and the second a **non-inverting amplifier**.*



## Can we analyze the circuit this way?

The transfer function of the complex voltage divider is:

$$\frac{v_3(\omega)}{v_{in}(\omega)} = \frac{1/j\omega C}{R_3 + 1/j\omega C} = \frac{1}{1 + j\omega R_3 C}$$

and that of the inverting amplifier:

$$\frac{v_{out}^{oc}(\omega)}{v_3(\omega)} = -\frac{R_2}{R_1}$$

And so of course **I** have correctly determined that the transfer function of this circuit is:



Joe Marquette / AP file

$$\frac{v_{out}^{oc}(\omega)}{v_{in}(\omega)} = \frac{v_{out}^{oc}(\omega)}{v_3(\omega)} \frac{v_3(\omega)}{v_{in}(\omega)} = -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_3 C}$$

## No, we cannot

**NO!** This is **not** correct:

$$\frac{v_o(\omega)}{v_i(\omega)} \neq -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_3 C}$$


The problem with the above "analysis" is that we **cannot** apply **this** complex voltage divider equation to determine  $v_3(\omega)$ :

$$v_3(\omega) \neq \frac{\frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} v_{in}(\omega)$$

The reason of course is that the output of this voltage divider is **not** open-circuited, and thus current  $i_3(\omega) \neq i_C(\omega)$ .
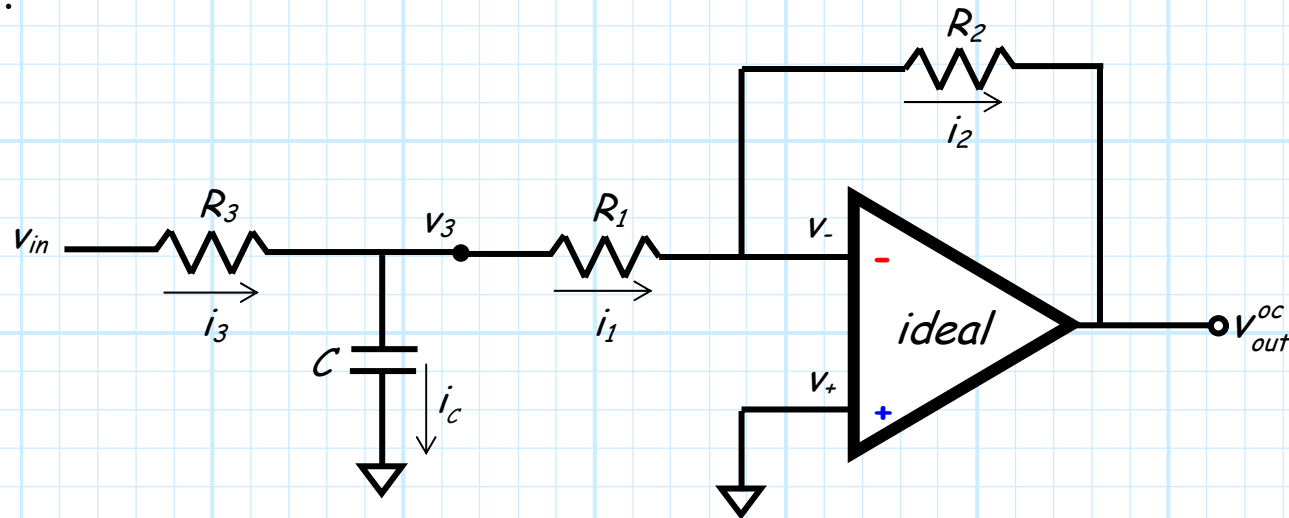
## My computer suspiciously crashed while writing this (really, it did!)

We **cannot** divide this circuit into two independent pieces, we must analyze it as **one** circuit.




*Of course what I meant to say was that we should determine the **impedance**  $Z_1$  of input network, and **then** use the inverting configuration equation  $T(\omega) = -Z_2/Z_1$ .*
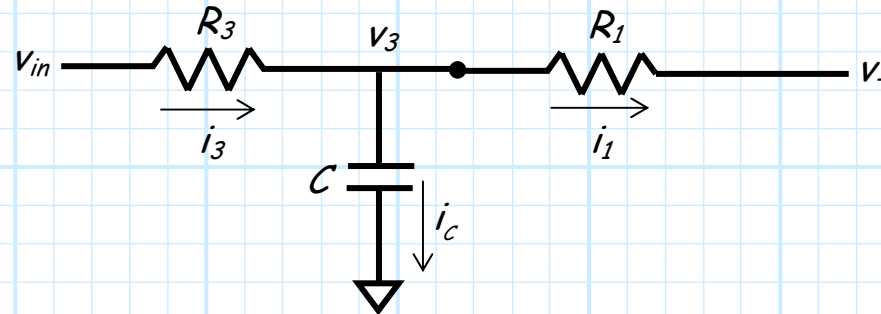
## An even worse idea than Vista

**NO!** This idea is as bad as the last one!

We cannot specify an impedance for the input network:



After all, would we define this impedance as:

$$Z_1 = \frac{v_{in} - v_-}{i_3} \quad \text{or} \quad Z_1 = \frac{v_{in} - v_-}{i_1} \quad ???$$




Windows Vista™
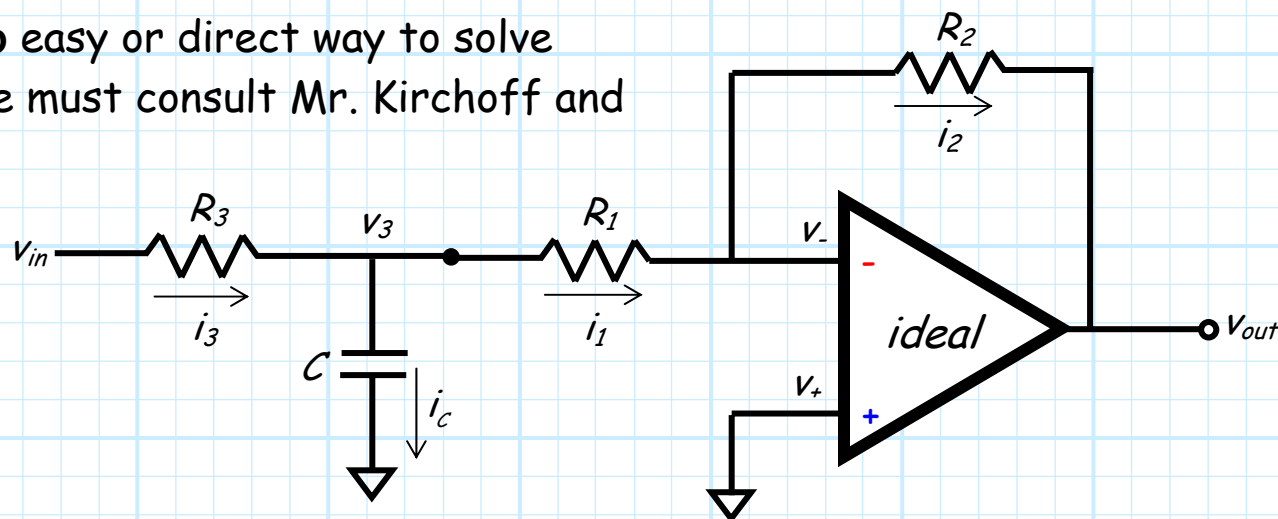
## Don't look for templates: trust what you know



So, there is **no** easy or direct way to solve this circuit, we must consult Mr. Kirchoff and his laws!



We know that  $i_1 = i_2$ , where:


$$i_1 = \frac{V_3 - V_-}{R_1} = \frac{V_3}{R_1} \quad \text{and} \quad i_2 = \frac{V_+ - V_{out}}{R_2} = \frac{-V_{out}}{R_2}$$

Combining these equations, we get the **expected** result:

$$V_{out} = -\frac{R_2}{R_1} V_3$$
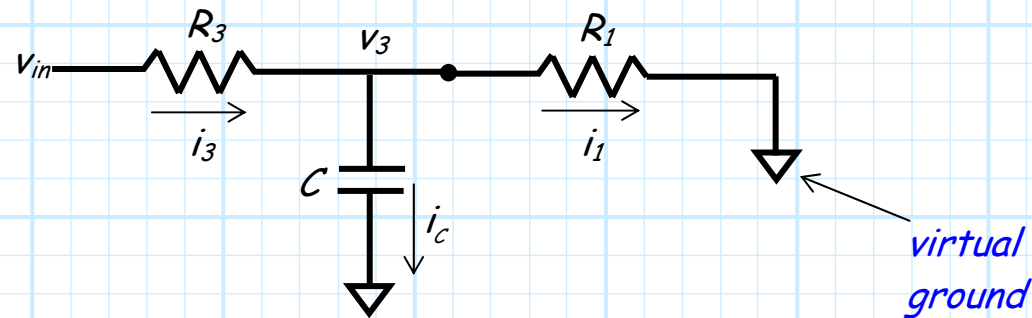
# Don't forget virtual ground!

We must therefore determine  $v_3$  in terms of  $v_i$ :



Note  $R_1$  and  $C$  are connected in **parallel!**

Thus, from **voltage division**, we find:

$$v_3 = \frac{R_1 \parallel \frac{1}{j\omega C}}{R_3 + \left( R_1 \parallel \frac{1}{j\omega C} \right)} v_{in}$$

where:

$$R_1 \parallel \frac{1}{j\omega C} = \frac{R_1 \left( \frac{1}{j\omega C} \right)}{R_1 + \frac{1}{j\omega C}} = \frac{R_1}{1 + j\omega R_1 C}$$



## The Eigen value at last!

Performing some algebra, we find:

$$v_3 = \left( \frac{R_1}{(R_1 + R_3) + j\omega R_1 R_3 C} \right) v_{in}$$

and since:

$$v_{out} = \frac{-R_2}{R_1} v_3$$

we finally discover that:

$$G(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = \left( \frac{-R_2}{(R_1 + R_3) + j\omega R_1 R_3 C} \right)$$

## This again is a low-pass filter

We can rearrange this transfer function to find that this circuit is likewise a **low-pass filter** with **pass-band gain**:

$$G(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = \frac{-R_2}{R_1 + R_3} \left( \frac{1}{1 + j(\omega/\omega_0)} \right)$$

where the **cutoff frequency**  $\omega_0$  is:

$$\omega_0 = \frac{1}{\left( \frac{R_1 R_3}{R_1 + R_3} \right) C} = \frac{1}{(R_1 \parallel R_3) C}$$

*I wish I had a  
nickel for every  
time my software  
has crashed—oh  
wait, I do!*

