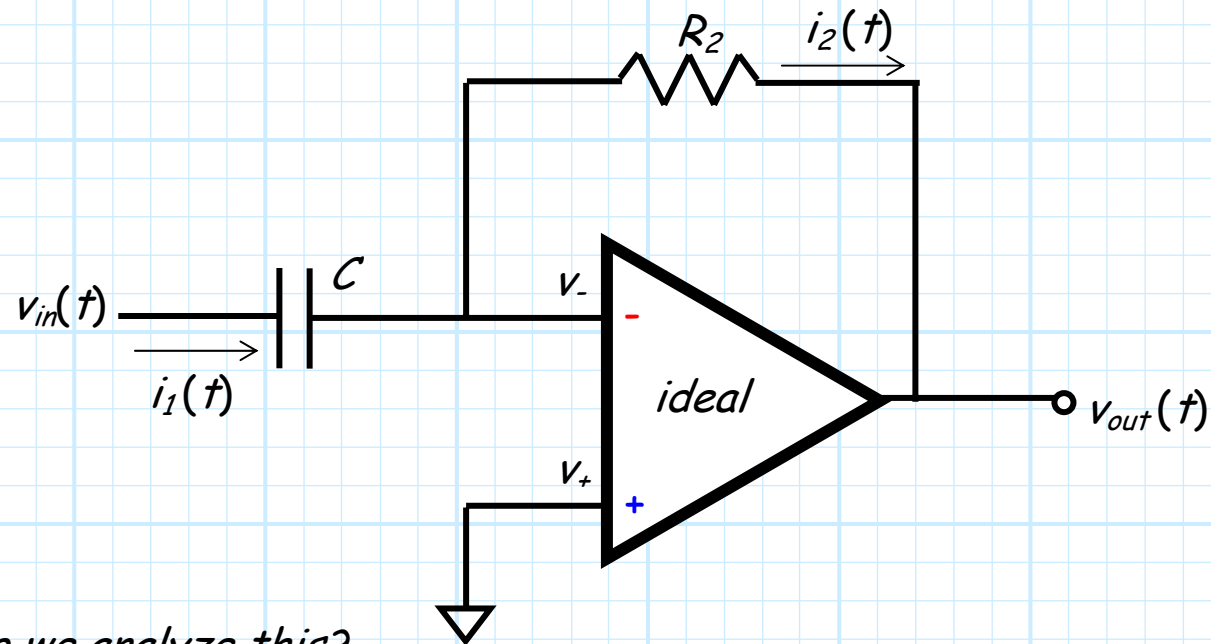


Op-Amp circuits with reactive elements

Now let's consider the case where the op-amp circuit includes **reactive elements**:



Q: *Yikes! How do we analyze this?*

A: Don't panic! Remember, the relationship between v_{out} and v_{in} is **linear**, so we can express the output as a **convolution**:

$$v_{out}(t) = \mathcal{L} [v_{in}(t)] = \int_{-\infty}^t g(t-t') v_{in}(t') dt'$$

Just find the Eigen value

Q: *I'm still panicking—how do we determine the impulse response $g(t)$ of this circuit?*

A: Say the input voltage $v_{in}(t)$ is an **Eigen function** of linear, time-invariant systems:

$$v_{in}(t) = e^{st} = e^{(\sigma + j\omega)t} = e^{\sigma t} e^{j\omega t}$$

Then, the **output** voltage is just a **scaled** version of this **input**:

$$v_{out}(t) = \mathcal{L}\left[e^{-st}\right] = \int_{-\infty}^t g(t-t') e^{-st'} dt' = G(s) e^{-st}$$

where the "scaling factor" $G(s)$ is the complex **Eigen value** of the linear operator \mathcal{L} .

Express the input as a superposition of eigen values (i.e., the Laplace transform)

Q: First of all, how could the input (and output) be this **complex** function e^{st} ? Voltages are **real-valued**!

A: True, but the **real-valued** input and output functions can be expressed as a weighted superposition of these **complex** Eigen functions!

$$v_{in}(s) = \int_0^{+\infty} v_{in}(t) e^{-st} dt$$

The Laplace transform \rightarrow

$$v_{out}(s) = \int_0^{+\infty} v_{out}(t) e^{-st} dt$$

Such that:


$$v_{out}(s) = G(s)v_{in}(s)$$

Find the eigen value from circuit theory and impedance

Q: *Still, I don't know how to find the eigen value $G(s)$!*


A: Remember, we can find $G(s)$ by analyzing the circuit using the Eigen value of each linear circuit element—a value we know as complex impedance!

$$\frac{v(s)}{i(s)} = Z(s)$$

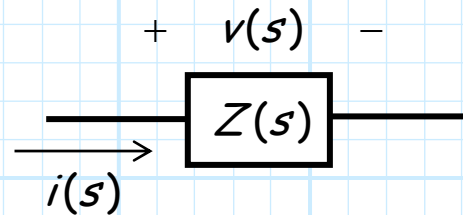

For example

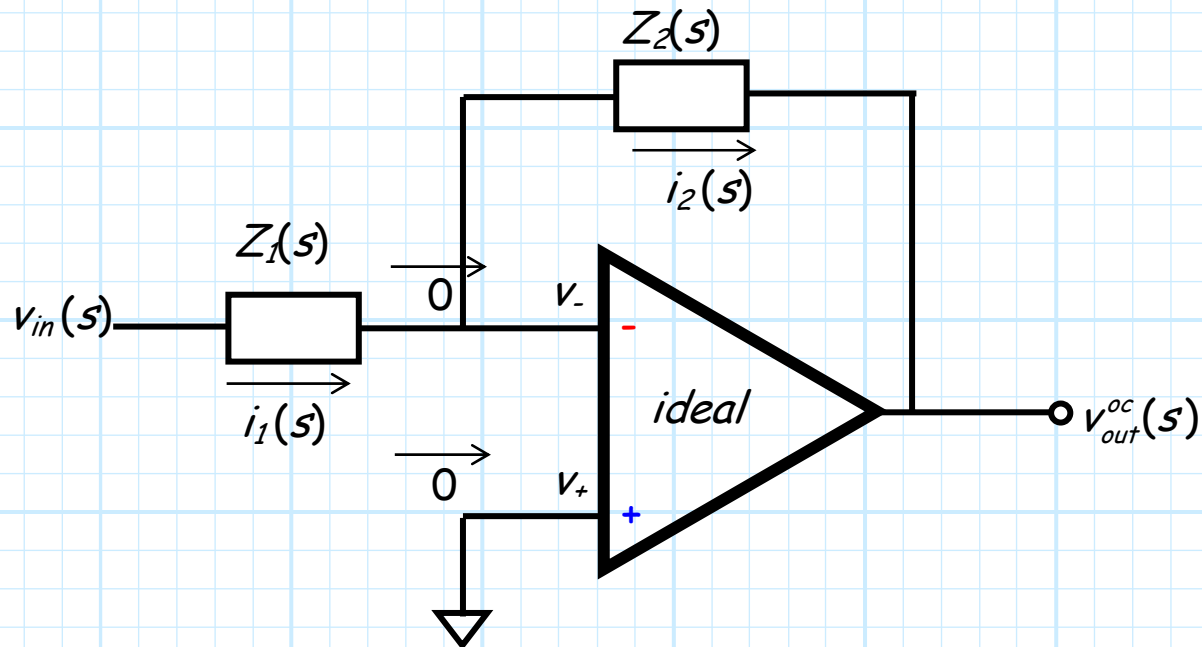For **example**, consider this amplifier in with the **inverting configuration**, where the resistors have been **replaced** with complex impedances:



What is the open-circuit voltage gain $A_{vo}(s) = \frac{v_{out}^{oc}(s)}{v_{in}(s)}$?

The eigen value of this linear operator

From KCL:


$$i_1(s) = i_2(s)$$

Since $v_-(s) = 0$, we find from Ohm's Law :

$$i_1(s) = \frac{v_{in}(s)}{Z_1(s)}$$

And also from Ohm's Law:
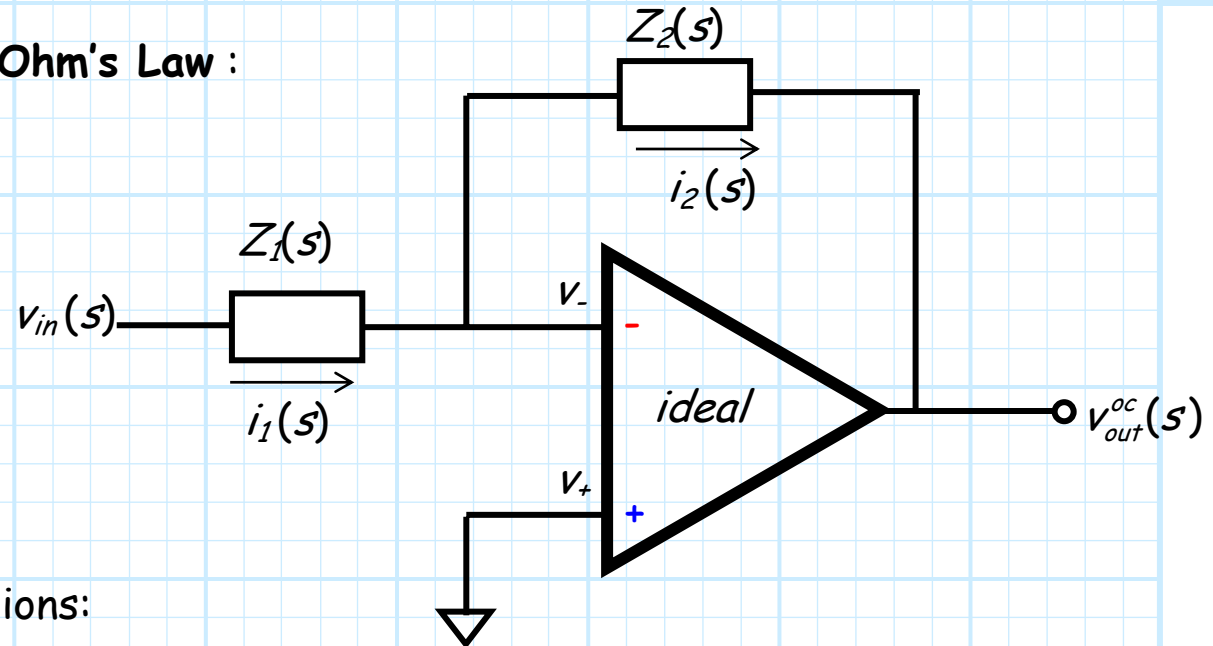
$$i_2(s) = \frac{-v_{out}^{oc}(s)}{Z_2(s)}$$



Equating the last two expressions:

$$\frac{v_{in}(s)}{Z_1(s)} = \frac{-v_{out}^{oc}(s)}{Z_2(s)}$$

Rearranging, we find the open-circuit voltage gain:

$$A_{vo}(s) = \frac{v_{out}^{oc}(s)}{v_{in}(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

The result passes the sanity check

Note that this complex voltage gain $A_{vo}(s)$ is the **Eigen value** $G(s)$ of the linear operator relating $v_{in}(t)$ and $v_{out}(t)$:

$$v_{out}(t) = \mathcal{L}[v_{in}(t)]$$

Note also that if the impedances $Z_1(s)$ and $Z_2(s)$ are real valued (i.e., they're resistors!):

$$Z_1(s) = R_1 + j0 \quad \text{and} \quad Z_2(s) = R_2 + j0$$

Then the voltage gain simplifies to the **familiar**:

$$A_{vo}(s) = \frac{v_{out}^{oc}(s)}{v_{in}(s)} = -\frac{R_2}{R_1}$$

Or, we can use the Fourier transform

Now, recall that the variable s is a **complex frequency**:


$$s = \sigma + j\omega.$$

If we set $\sigma = 0$, then $s = j\omega$, and the functions $Z(s)$ and $A_{vo}(s)$ in the Laplace domain can be written in the frequency (i.e., **Fourier**) domain!

$$A_{vo}(\omega) = A_{vo}(s)|_{\sigma=0}$$

And therefore, for the **inverting** configuration:
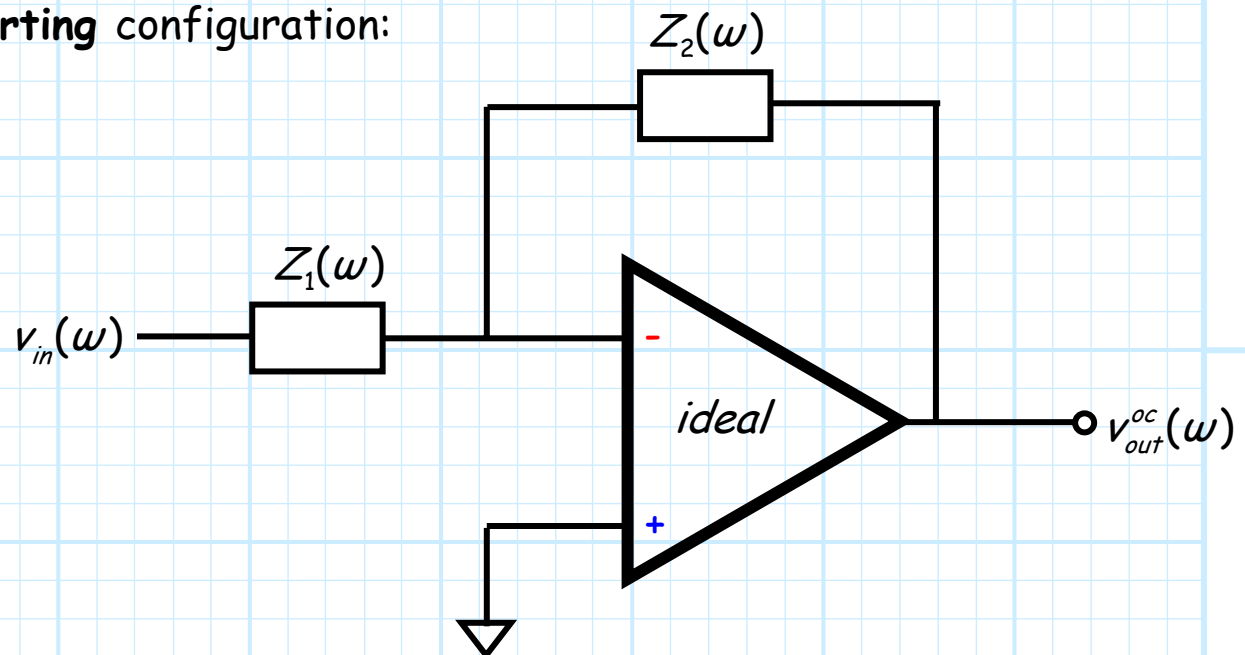
$$A_{vo}(\omega) = \frac{v_{out}^{oc}(\omega)}{v_{in}(\omega)} = -\frac{Z_2(\omega)}{Z_1(\omega)}$$



For the non-inverting

Likewise, for the non-inverting configuration, we find:

$$A_{vo}(\omega) = \frac{v_{out}^{oc}(\omega)}{v_{in}(\omega)} = 1 + \frac{Z_2(\omega)}{Z_1(\omega)}$$

$$A_{vo}(s) = \frac{v_{out}^{oc}(s)}{v_{in}(s)} = 1 + \frac{Z_2(s)}{Z_1(s)}$$

