

Special Problem 2.8-1

Determine the complex transfer function $G(\omega) = v_{out}(\omega)/v_{in}(\omega)$ for this circuit.

