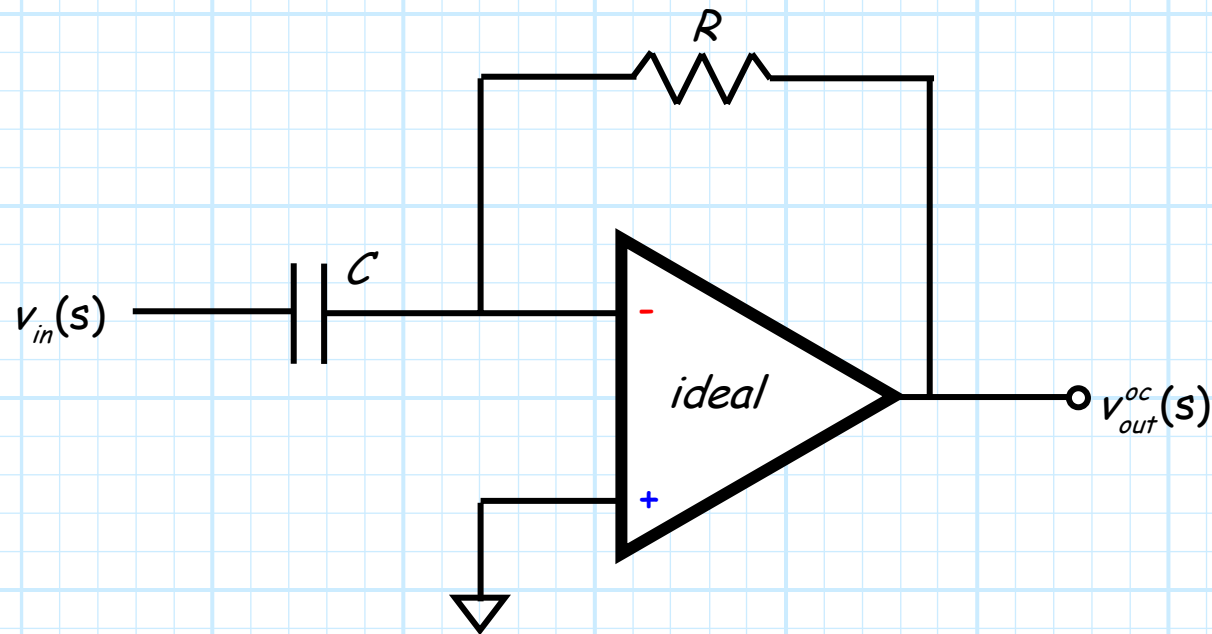


# The Inverting Differentiator

The circuit shown below is the inverting differentiator.



Since the circuit uses the **inverting** configuration, we can conclude that the circuit transfer function is:

$$G(s) = \frac{v_{out}^{oc}(s)}{v_{in}(s)} = -\frac{Z_2(s)}{Z_1(s)}$$

## Know the impedance; know the answer

For the **capacitor**, we know that its **complex impedance** is:

$$Z_1(s) = \frac{1}{sC}$$

And the complex impedance of the **resistor** is simply the real value:

$$Z_2(s) = R$$

Thus, the **eigen value** of the linear operator relating  $v_{in}(t)$  to  $v_{out}^{oc}(t)$  is:

$$G(s) = -\frac{Z_2(s)}{Z_1(s)} = -\frac{R}{\frac{1}{sC}} = -s RC$$

In other words, the (Laplace transformed) **output** signal is related to the (Laplace transformed) **input** signal as:

$$v_{out}^{oc}(s) = -s(RC) v_{in}(s)$$

From our knowledge of **Laplace Transforms**, we know this means that the output signal is proportional to the **derivative** of the input signal!

## Converting back to time domain

Taking the **inverse** Laplace Transform, we find:

$$v_{out}^{oc}(t) = -RC \frac{dv_{in}(t)}{dt}$$

For example, if the **input** is:

$$v_{in}(t) = \sin \omega t$$

then the **output** is:

$$\begin{aligned} v_{out}^{oc}(t) &= -RC \frac{dv_{in}(t)}{dt} \\ &= -RC \frac{d \sin \omega t}{dt} \\ &= -\omega RC \cos \omega t \end{aligned}$$

## Or, with Fourier analysis

We likewise could have determined this result using **Fourier analysis** (i.e., frequency domain):

$$G(\omega) = \frac{v_{out}^{oc}(\omega)}{v_{in}(\omega)} = -\frac{Z_2(\omega)}{Z_1(\omega)} = -\frac{R}{(1/j\omega C)} = -j\omega RC$$

Thus, the **magnitude** of the transfer function is:

$$\begin{aligned} |G(\omega)| &= |-j\omega RC| \\ &= \omega RC \end{aligned}$$

And since:

$$-j = e^{-j(\pi/2)} = \cos\left(-\frac{\pi}{2}\right) + j\sin\left(-\frac{\pi}{2}\right)$$

the **phase** of the transfer function is:

$$\begin{aligned} \angle G(\omega) &= -\frac{\pi}{2} \text{ radians} \\ &= -90^\circ \end{aligned}$$

## Look at the magnitude and phase

So given that:

$$|v_{out}^{oc}(\omega)| = |G(\omega)| |v_{in}(\omega)|$$

and:

$$\angle v_{out}^{oc}(\omega) = \angle G(\omega) + \angle v_{in}(\omega)$$

we find for the input:

$$v_{in}(t) = \sin \omega t$$

where:

$$|v_{in}(\omega)| = 1 \quad \text{and} \quad \angle v_{in}(\omega) = 0$$

that the **output** of the inverting differentiator is:

$$|v_{out}^{oc}(\omega)| = |G(\omega)| |v_{in}(\omega)| = \omega RC$$

and:

$$\angle v_{out}^{oc}(\omega) = \angle G(\omega) + \angle v_{in}(\omega) = -90^\circ + 0 = -90^\circ$$


## The result is the same!

Therefore, the output is:

$$\begin{aligned} v_{out}^{oc}(t) &= \omega RC \sin(\omega t - 90^\circ) \\ &= -\omega RC \cos \omega t \end{aligned}$$

Exactly the **same result** as before (using Laplace transforms)!

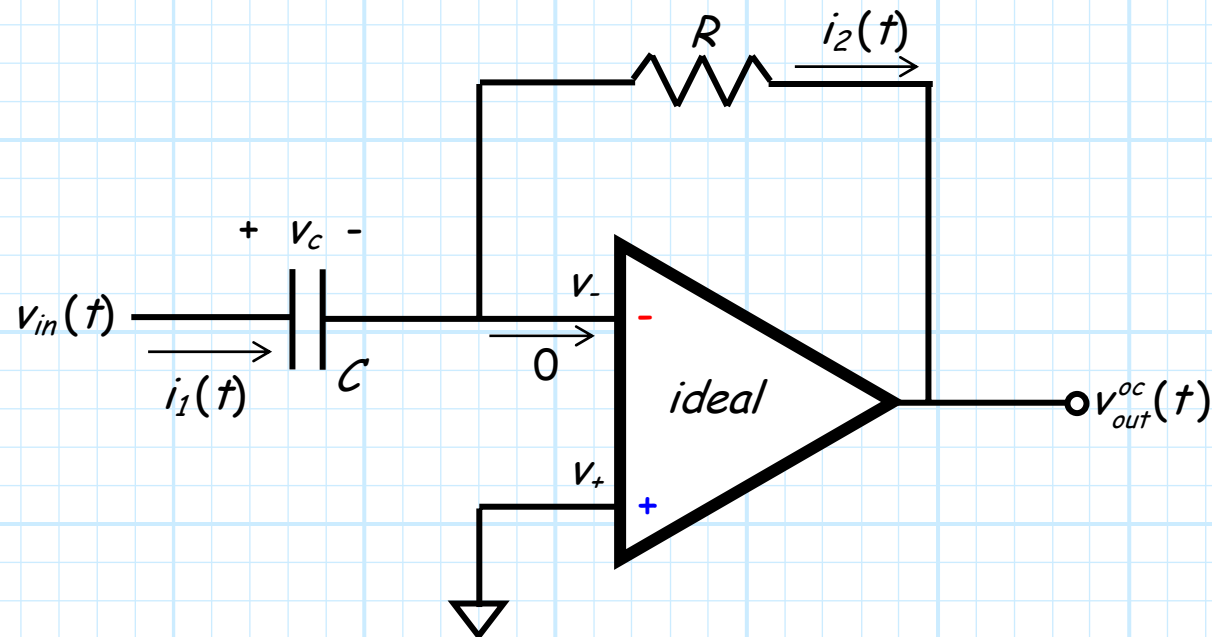
If you are still **unconvinced** that this circuit is a differentiator, consider this **time-domain analysis**.



## Let's do a time-domain analysis

From our elementary **circuits knowledge**, we know that the current through a capacitor ( $i_1(t)$ ) is:

$$i_1(t) = C \frac{dv_c(t)}{dt}$$

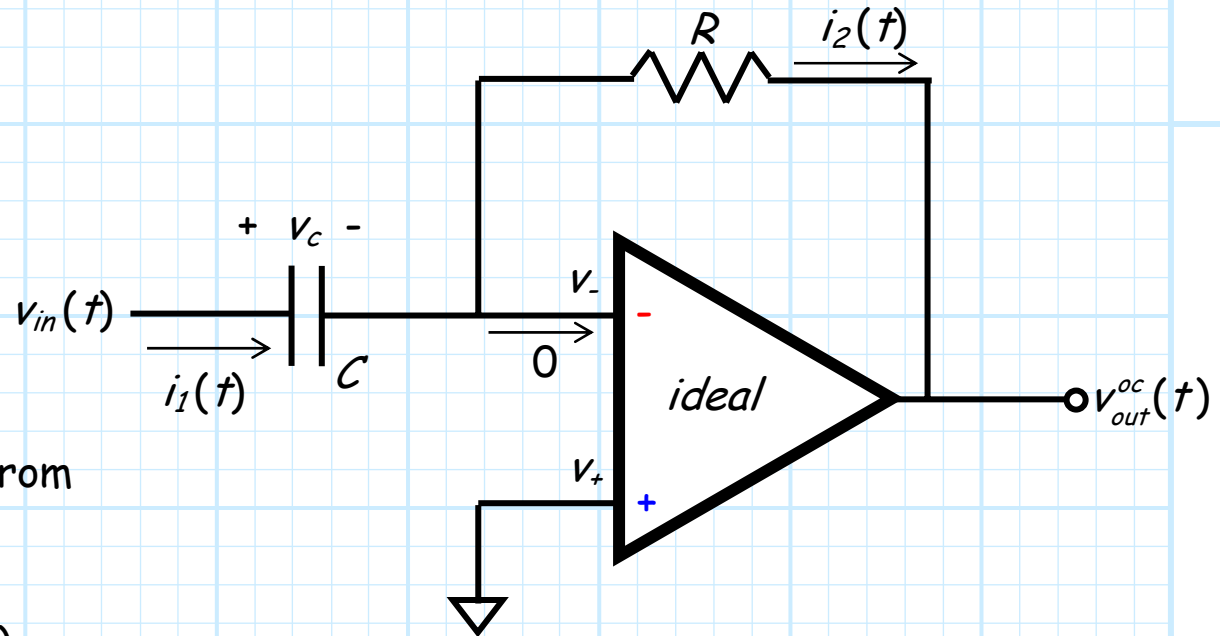

and from the circuit we see from KVL that:

$$v_c(t) = v_{in}(t) - v_-(t) = v_{in}(t)$$

therefore the **input current** is:

$$i_1(t) = C \frac{dv_{in}(t)}{dt}$$

# Laplace, Fourier, time-domain: the result is the same!

From KCL, we likewise know that:

$$i_1(t) = i_2(t)$$

and from Ohm's Law:


$$i_2(t) = \frac{v_1(t) - v_{out}^{oc}(t)}{R} = -\frac{v_{out}^{oc}(t)}{R}$$

Combining the two previous equations:

$$v_{out}^{oc}(t) = -i_1(t)R$$

and thus:
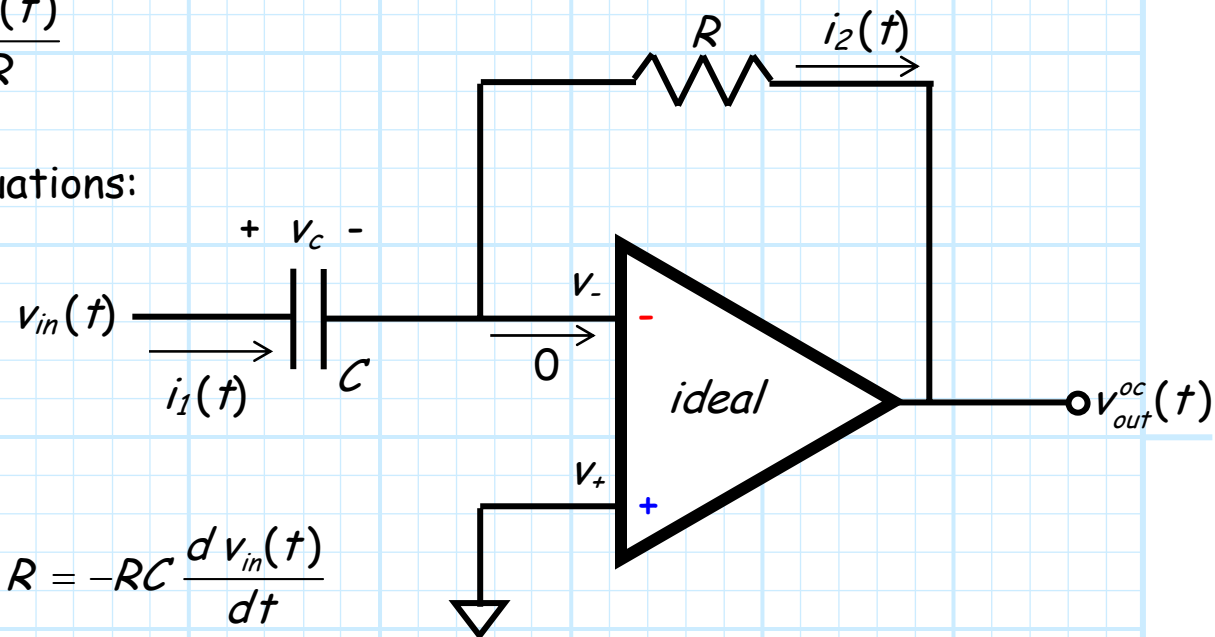
$$v_{out}^{oc}(t) = -i_1(t)R = -\left(C \frac{dv_{in}(t)}{dt}\right)R = -RC \frac{dv_{in}(t)}{dt}$$



The **same** result as before!