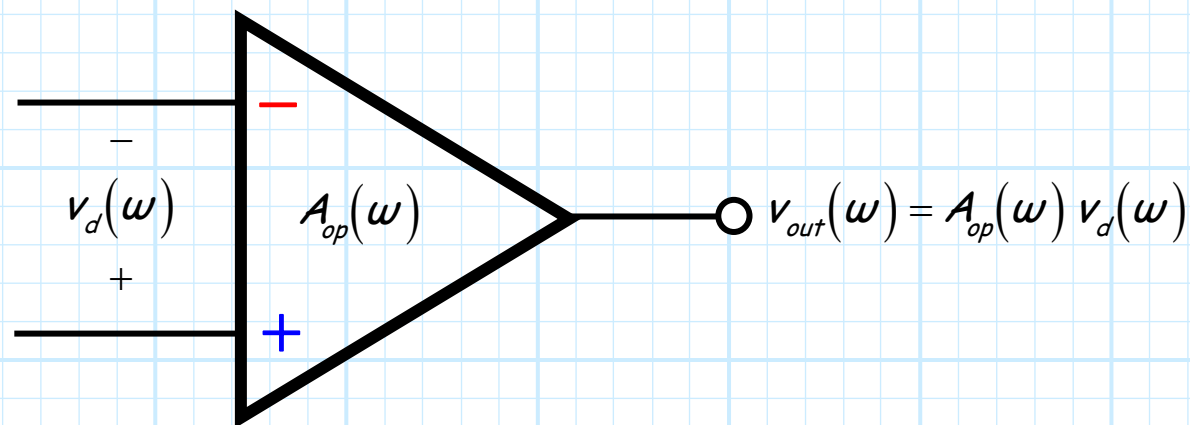


# The Gain of Real Op-Amps

The **open-circuit** voltage gain  $A_{op}$  (a **differential** gain!) of a **real** (i.e., **non-ideal**) operational amplifier is **very** large at D.C. (i.e.,  $\omega = 0$ ), but gets **smaller** as the signal frequency  $\omega$  **increases**!

In other words, the **differential** gain of an op-amp (i.e., the **open-loop** gain of a feedback amplifier) is a function of frequency  $\omega$ .

We will thus express this gain as a **complex** function in the **frequency domain** (i.e.,  $A_{op}(\omega)$ ).



## Gain is a complex function frequency

Typically, this op-amp behavior can be described mathematically with the **complex** function:

$$A_{op}(\omega) = \frac{A_0}{1 + j\left(\frac{\omega}{\omega_b}\right)}$$

or, using the frequency definition  $\omega = 2\pi f$ , we can write:

$$A_{op}(f) = \frac{A_0}{1 + j\left(\frac{f}{f_b}\right)}$$

where  $\omega$  is frequency expressed in units of **radians/sec**, and  $f$  is signal frequency expressed in units of **cycles/sec**.

## DC is when the signal frequency is zero

Note the squared **magnitude** of the op-amp gain is therefore the **real function**:

$$\begin{aligned} |A_{op}(\omega)|^2 &= \frac{A_0}{1 + j(\omega/\omega_b)} \frac{A_0}{1 - j(\omega/\omega_b)} \\ &= \frac{A_0^2}{1 + (\omega/\omega_b)^2} \end{aligned}$$

Therefore at **D.C.** ( $\omega = 0$ ) the op-amp gain is:

$$A_{op}(\omega = 0) = \frac{A_0}{1 + j(0/\omega_b)} = A_0$$

and thus:

$$|A_{op}(\omega = 0)|^2 = A_0^2$$

Where:

$$A_0 = \text{op-amp D.C. gain}$$

## The break frequency

Again, note that the D.C. gain  $A_0$  is:

- 1) an **open-circuit** voltage gain
- 2) a **differential** gain
- 3) also referred to as the **open-loop** D.C. gain

**Q:** *So just what **does** the value  $\omega_b$  indicate ?*

**A:** The value  $\omega_b$  is the op-amp's **break frequency**.

Typically, this value is very **small** (e.g.  $f_b = 10\text{Hz}$ ).

## The 3dB bandwidth

To see **why** this value is **important**, consider the op-amp gain at  $\omega = \omega_b$ :

$$A_{op}(\omega = \omega_b) = \frac{A_0}{1 + j(\omega/\omega_b)} = \frac{A_0}{1 + j} = \frac{A_0}{2} - j\frac{A_0}{2} = \frac{|A_0|}{\sqrt{2}} e^{-j\pi/4}$$


The **squared magnitude** of this gain is therefore:

$$|A_{op}(\omega = \omega_b)|^2 = \frac{A_0}{1 + j} \frac{A_0}{1 - j} = \frac{A_0^2}{1 - j^2} = \frac{A_0^2}{2}$$

As a result, the **break** frequency  $\omega_b$  is also referred to as the "**half-power**" frequency, or the "**3 dB**" frequency.

## This value is very important!

If we plot  $|A_{op}(\omega)|^2$  on a "log-log" scale, we get something like this:

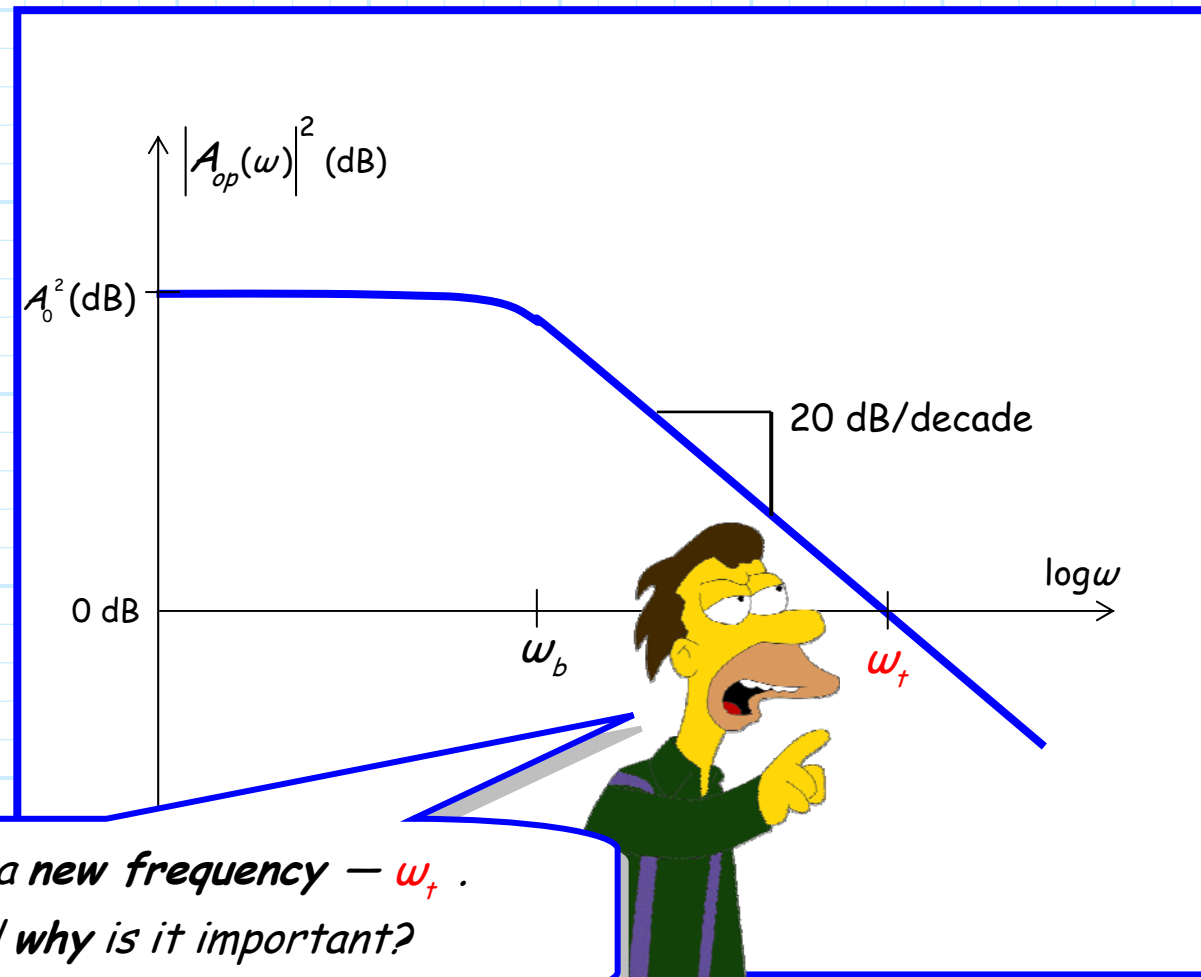

**Q:** Hey! You have defined a new frequency —  $\omega_t$ .  
What is this frequency and why is it important?

## The unity gain frequency

**A:** Note that  $\omega_t$  is the frequency where the magnitude of the gain is "unity" (i.e., where the gain is 1). I.E.,

$$|A_{op}(\omega = \omega_t)|^2 = 1$$

Note that when expressed in dB, **unity** gain is:

$$10 \log_{10} |A_{op}(\omega = \omega_t)|^2 = 10 \log_{10} (1) = 0 \text{ dB}$$

Therefore, on a "log-log" plot, the gain curve crosses the **horizontal axis** at frequency  $\omega_t$ .

We thus refer to the frequency  $\omega_t$  as the "**unity-gain frequency**" of the operational amplifier.

## It's the product of the gain and the bandwidth!

Note that we can **solve** for this frequency in terms of **break frequency**  $\omega_b$  and **D.C. gain**  $A_0$ :

$$1 = \left| A_{op}(\omega = \omega_t) \right|^2 = \frac{A_0^2}{1 + \left( \frac{\omega_t}{\omega_b} \right)^2}$$

meaning that:

$$\omega_t^2 = \omega_b^2 (A_0^2 - 1)$$

But recall that  $A_0 \gg 1$ , therefore  $A_0^2 - 1 \approx A_0^2$  and:

$$\omega_t = \omega_b |A_0|$$

Note since the frequency  $\omega_b$  defines the 3 dB **bandwidth** of the op-amp, the unity gain frequency  $\omega_t$  is simply the **product** of the op-amp's D.C. **gain**  $|A_0|$  and its **bandwidth**  $\omega_b$ .



## It's not rocket science!

As a result,  $\omega_f$  is alternatively referred to as the **gain-bandwidth product!**

$\omega_f \doteq$  **Unity Gain Frequency**

and

$\omega_f \doteq$  **Gain - Bandwidth Product**



*This is so **simple** perhaps even I can remember it:*

*The **gain-bandwidth-product** is the product of the gain and the bandwidth!*