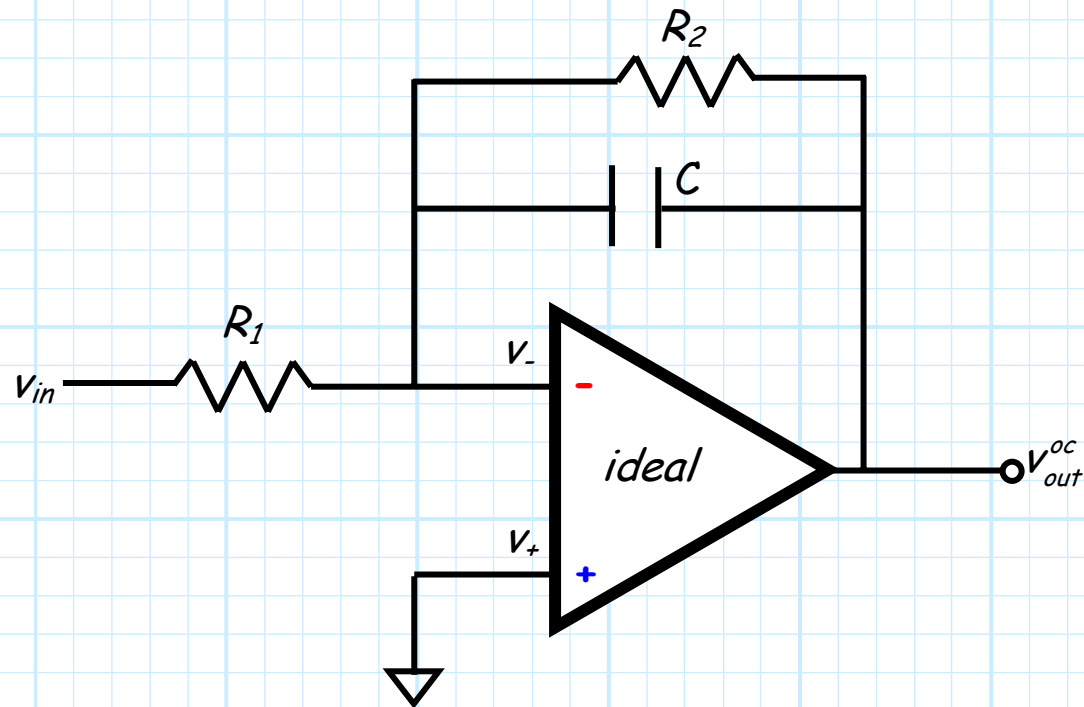


Example: An Inverting Network

Now let's determine the complex transfer function of this circuit:



It's the inverting configuration!

Note this circuit uses the **inverting** configuration, so that:

$$G(\omega) = -\frac{Z_2(\omega)}{Z_1(\omega)}$$

where $Z_1 = R_1$, and:

$$Z_2 = R_2 \parallel \frac{1}{j\omega C} = \frac{R_2}{1 + j\omega R_2 C}$$

Therefore, the **transfer function** of this circuit is:

$$G(\omega) = \frac{v_{out}^{oc}(\omega)}{v_{in}(\omega)} = -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_2 C}$$

Another low-pass filter

Thus, the transfer function **magnitude** is:

$$|G(\omega)|^2 = \left(-\frac{R_2}{R_1}\right)^2 \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$


where:

$$\omega_0 = \frac{1}{R_2 C}$$

Thus, just as with the previous example, this circuit is a **low-pass filter**, with **cutoff frequency** ω_0 and pass-band **gain** $(R_2/R_1)^2$.

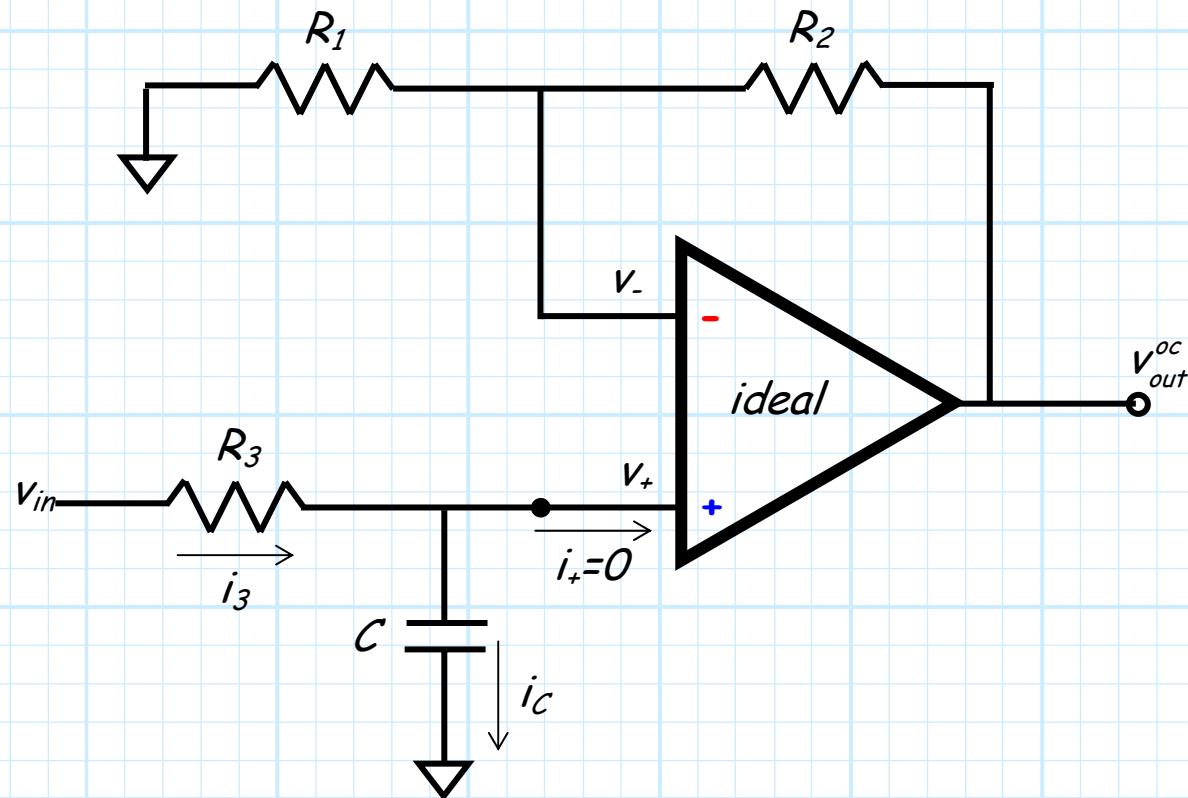Example: A Non-Inverting Network

Let's determine the transfer function $G(\omega) = v_{out}^{oc}(\omega)/v_{in}(\omega)$ for the following circuit:



Some enjoyable circuit analysis

From KCL, we know:

$$i_3(\omega) = i_c(\omega) + i_+(\omega) = i_c(\omega) + 0 = i_c(\omega)$$

where:


$$i_3(\omega) = \frac{v_{in}(\omega) - v_+(\omega)}{R_3} \quad \text{and} \quad i_c(\omega) = \frac{v_+(\omega) - 0}{\left(\frac{1}{j\omega C}\right)} = j\omega C v_+(\omega)$$

Equating, we find an expression involving $v_{in}(\omega)$ and $v_2(\omega)$ only:

$$\frac{v_{in}(\omega) - v_+(\omega)}{R_3} = j\omega C v_+(\omega)$$

and performing a little algebra, we find:
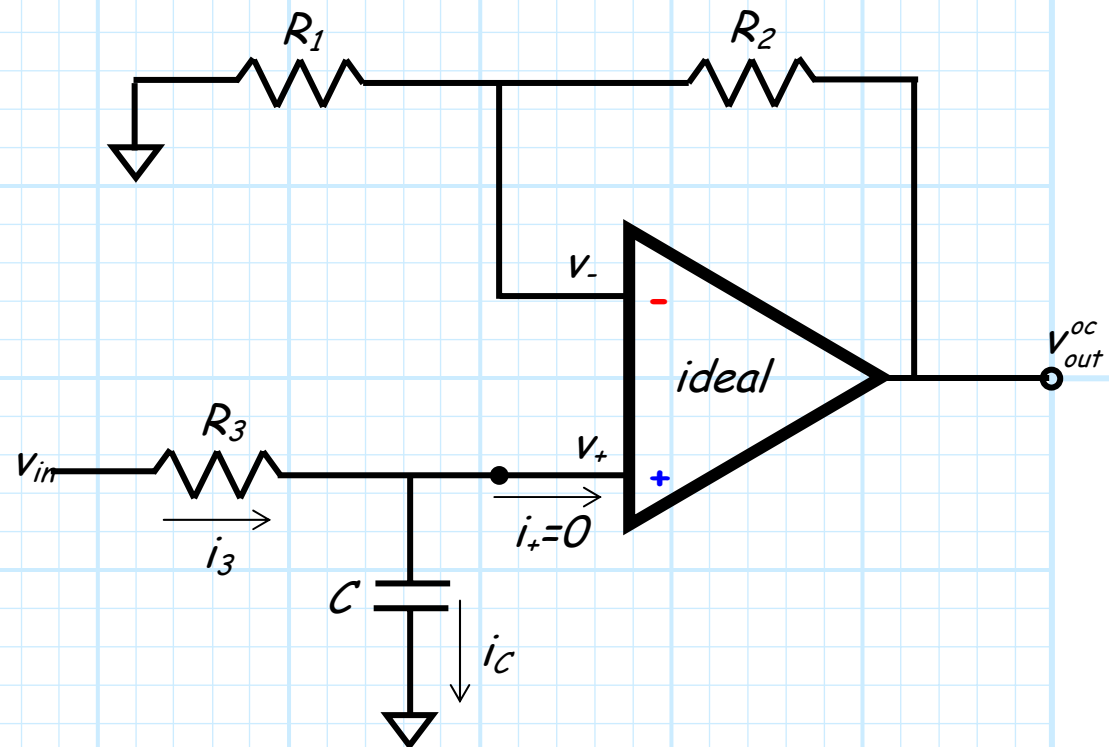
$$v_2(\omega) = \frac{v_{in}(\omega)}{1 + j\omega R_3 C}$$



No need to go further: we have a template!


The remainder of the circuit is simply the **non-inverting amplifier** that we studied earlier.

We know that:

$$v_{out}^{oc}(\omega) = \left(1 + \frac{R_2}{R_1}\right) v_+(\omega)$$

Combining these two relationships, we can determine the **complex transfer function** for this circuit:
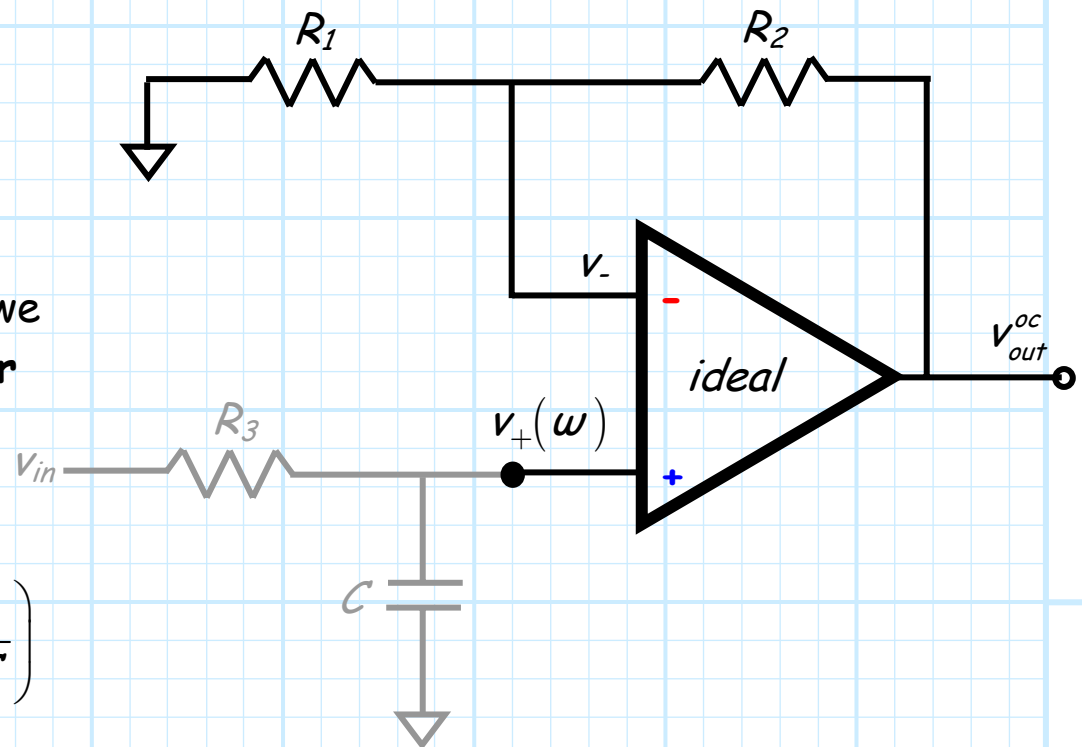
$$G(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = \left(1 + \frac{R_2}{R_1}\right) \left(\frac{1}{1 + j\omega R_3 C}\right)$$



It's a low-pass filter!!


The **magnitude** of this transfer function is therefore:

$$|G(\omega)|^2 = \left(1 + \frac{R_2}{R_1}\right)^2 \frac{1}{1 + \left(\frac{\omega}{\omega_0}\right)^2}$$

where:


$$\omega_0 = \frac{1}{R_3 C}$$

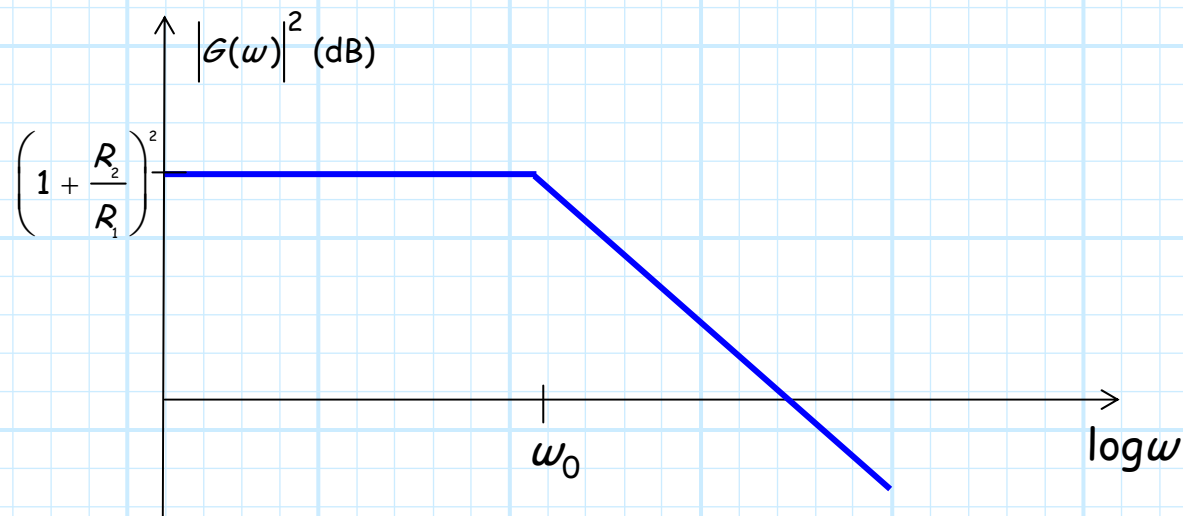This is a **low-pass filter**—one with **pass-band gain!**



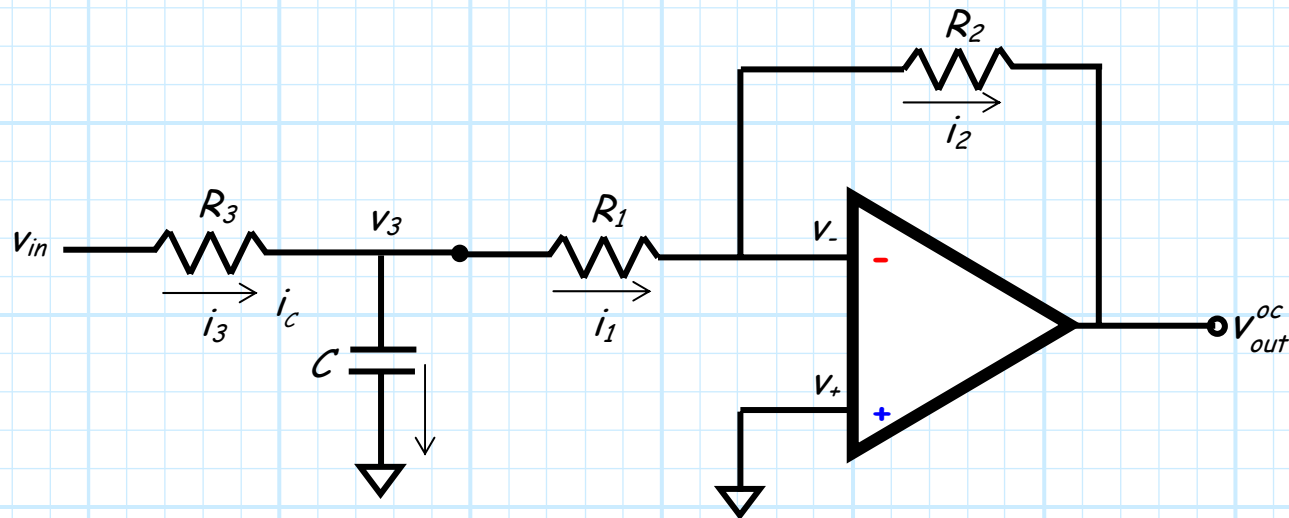Example: Another Inverting Network

Consider now the transfer function of this circuit:




Some more enjoyable circuit analysis

To accomplish this analysis, we must first...

Wait! You don't need to explain this to me.

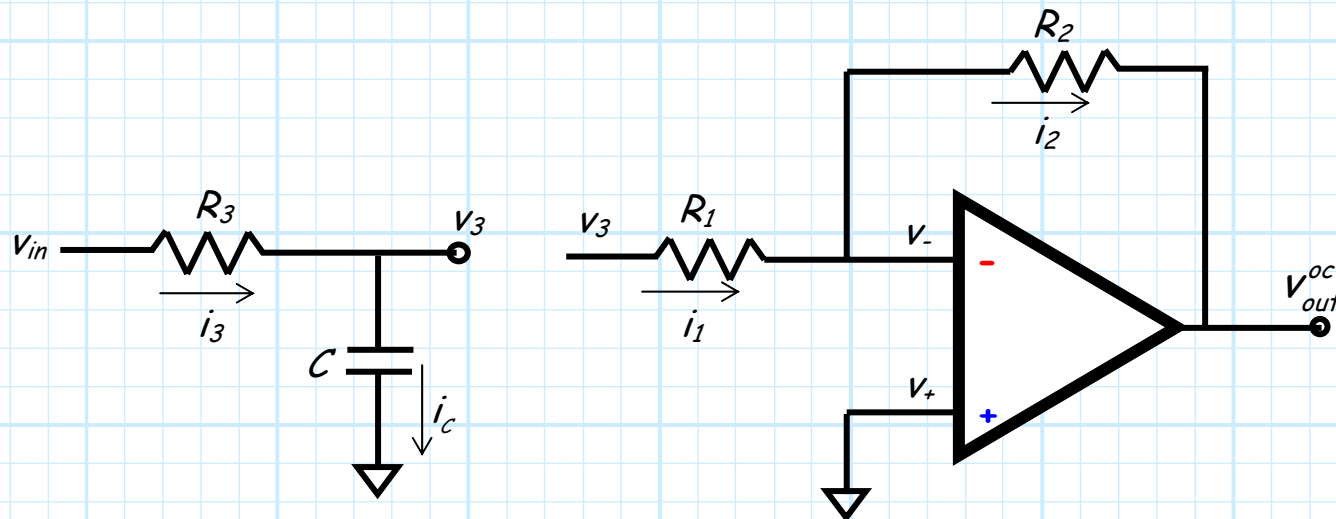*It is obvious that we can divide this is circuit into two pieces—the first being a complex **voltage divider** and the second a **non-inverting amplifier**.*



Can we analyze the circuit this way?

The transfer function of the complex voltage divider is:

$$\frac{v_3(\omega)}{v_{in}(\omega)} = \frac{1/j\omega C}{R_3 + 1/j\omega C} = \frac{1}{1 + j\omega R_3 C}$$

and that of the inverting amplifier:

$$\frac{v_{out}^{oc}(\omega)}{v_3(\omega)} = -\frac{R_2}{R_1}$$

And so of course **I** have correctly determined that the transfer function of this circuit is:



Joe Marquette / AP file

$$\frac{v_{out}^{oc}(\omega)}{v_{in}(\omega)} = \frac{v_{out}^{oc}(\omega)}{v_3(\omega)} \frac{v_3(\omega)}{v_{in}(\omega)} = -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_3 C}$$

No, we cannot

NO! This is **not** correct:

$$\frac{v_o(\omega)}{v_i(\omega)} \neq -\frac{R_2}{R_1} \frac{1}{1 + j\omega R_3 C}$$


The problem with the above "analysis" is that we **cannot** apply **this** complex voltage divider equation to determine $v_3(\omega)$:

$$v_3(\omega) \neq \frac{\frac{1}{j\omega C}}{R_3 + \frac{1}{j\omega C}} v_{in}(\omega)$$

The reason of course is that the output of this voltage divider is **not** open-circuited, and thus current $i_3(\omega) \neq i_C(\omega)$.

My computer suspiciously crashed while writing this (really, it did!)

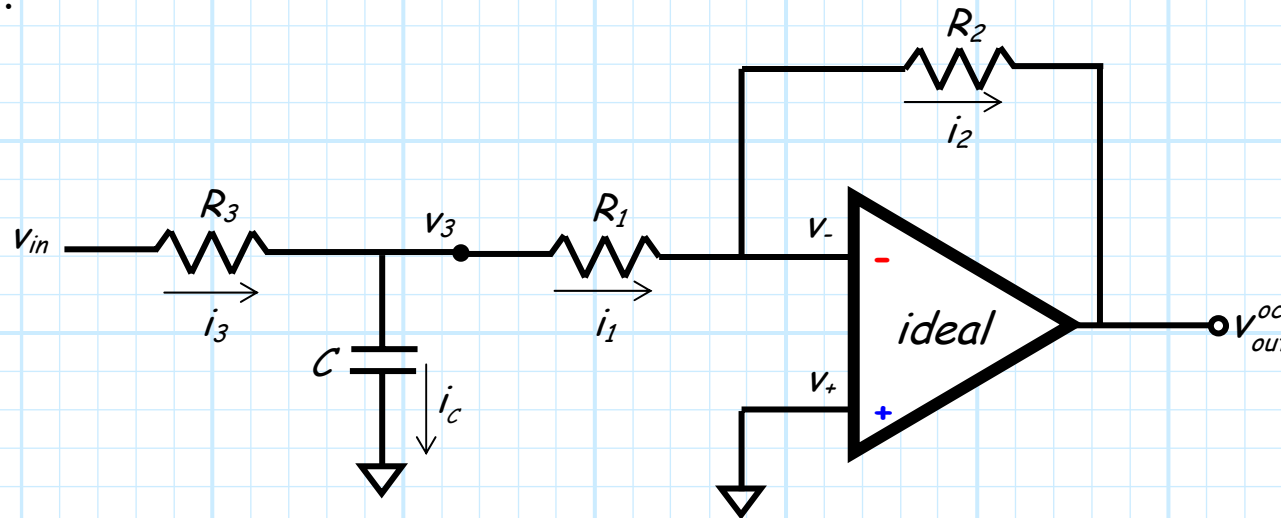We **cannot** divide this circuit into two independent pieces, we must analyze it as **one** circuit.




*Of course what I meant to say was that we should determine the **impedance** Z_1 of input network, and **then** use the inverting configuration equation $T(\omega) = -Z_2/Z_1$.*

An even worse idea than Vista

NO! This idea is as bad as the last one!

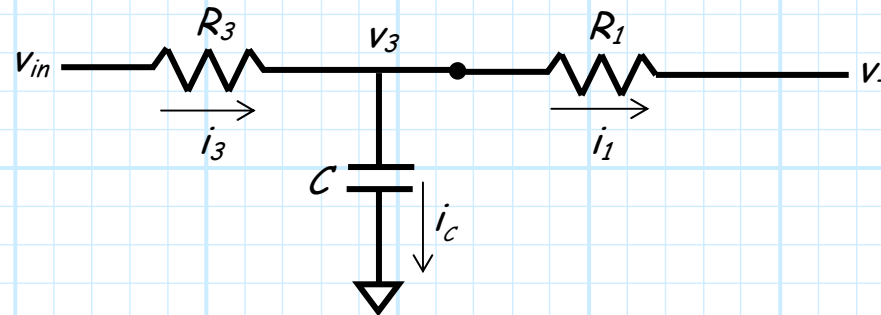We cannot specify an impedance for the input network:



After all, would we define this impedance as:

$$Z_1 = \frac{v_{in} - v_-}{i_3} \quad \text{or} \quad Z_1 = \frac{v_{in} - v_-}{i_1} \quad ???$$




Windows Vista™

Don't look for templates: trust what you know



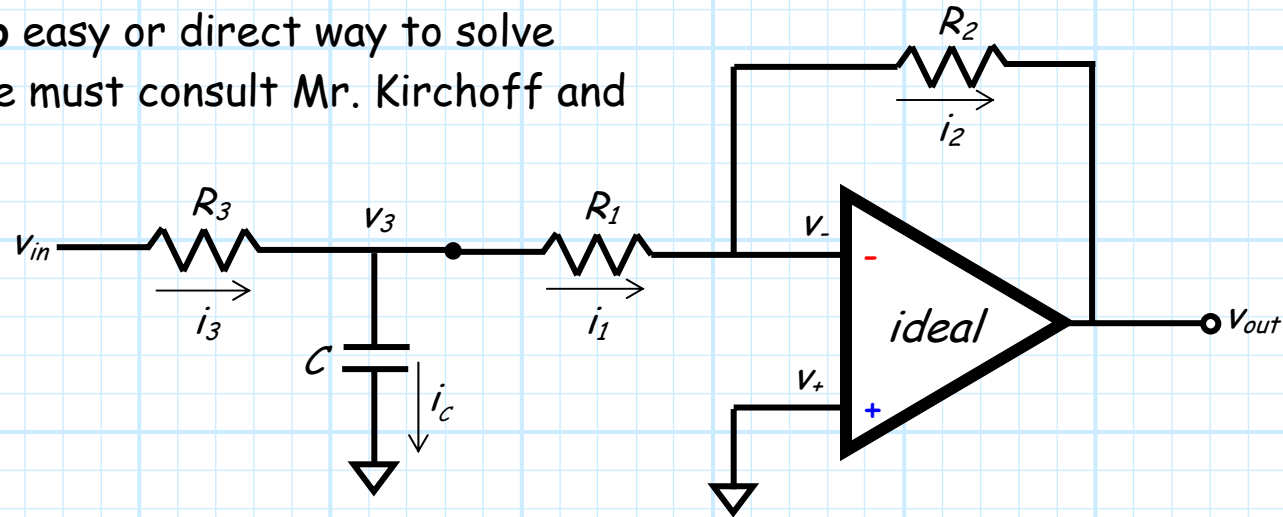So, there is **no** easy or direct way to solve this circuit, we must consult Mr. Kirchoff and his laws!



We know that $i_1 = i_2$, where:


$$i_1 = \frac{V_3 - V_-}{R_1} = \frac{V_3}{R_1} \quad \text{and} \quad i_2 = \frac{V_+ - V_{out}}{R_2} = \frac{-V_{out}}{R_2}$$

Combining these equations, we get the **expected** result:

$$V_{out} = -\frac{R_2}{R_1} V_3$$

Don't forget virtual ground!

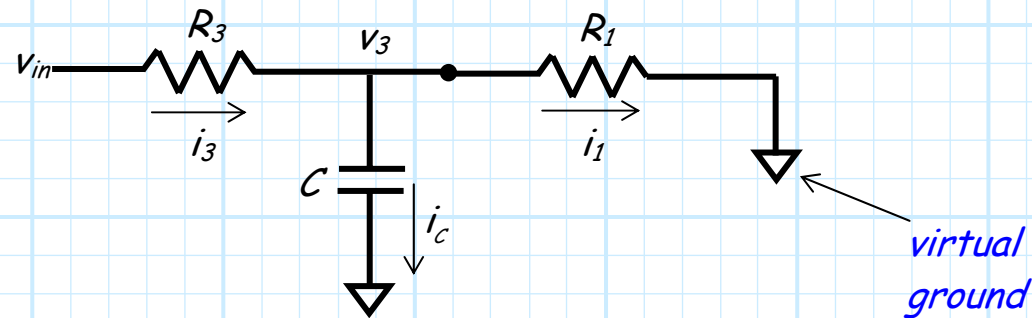We must therefore determine v_3 in terms of v_i :



Note R_1 and C are connected in **parallel!**

Thus, from **voltage division**, we find:

$$v_3 = \frac{R_1 \parallel \frac{1}{j\omega C}}{R_3 + \left(R_1 \parallel \frac{1}{j\omega C} \right)} v_{in}$$

where:

$$R_1 \parallel \frac{1}{j\omega C} = \frac{R_1 \left(\frac{1}{j\omega C} \right)}{R_1 + \frac{1}{j\omega C}} = \frac{R_1}{1 + j\omega R_1 C}$$

The Eigen value at last!

Performing some algebra, we find:

$$v_3 = \left(\frac{R_1}{(R_1 + R_3) + j\omega R_1 R_3 C} \right) v_{in}$$

and since:

$$v_{out} = \frac{-R_2}{R_1} v_3$$

we finally discover that:

$$G(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = \left(\frac{-R_2}{(R_1 + R_3) + j\omega R_1 R_3 C} \right)$$

This again is a low-pass filter

We can rearrange this transfer function to find that this circuit is likewise a **low-pass filter** with **pass-band gain**:

$$G(\omega) = \frac{v_{out}(\omega)}{v_{in}(\omega)} = \frac{-R_2}{R_1 + R_3} \left(\frac{1}{1 + j(\omega/\omega_0)} \right)$$

where the **cutoff frequency** ω_0 is:

$$\omega_0 = \frac{1}{\left(\frac{R_1 R_3}{R_1 + R_3} \right) C} = \frac{1}{(R_1 \parallel R_3) C}$$

I wish I had a nickel for every time my software has crashed—oh wait, I do!



Example: A Complex Processing Circuit using the Inverting Configuration


Note that we can combine inverting amplifiers to form a more **complex** processing system.

For **example**, say we wish to take **three** input signals $v_1(t)$, $v_2(t)$, and $v_3(t)$, and process them such that the open-circuit output voltage is:

$$v_{out}(t) = 5v_1(t) + \int_{-\infty}^t v_2(t') dt' + \frac{dv_3(t)}{dt}$$

Assuming that we use **ideal** (or near ideal) op-amps, with an **output resistance equal to zero** (or at least very small), we can realize the above signal processor with the following circuit:

This circuit performs this operation!

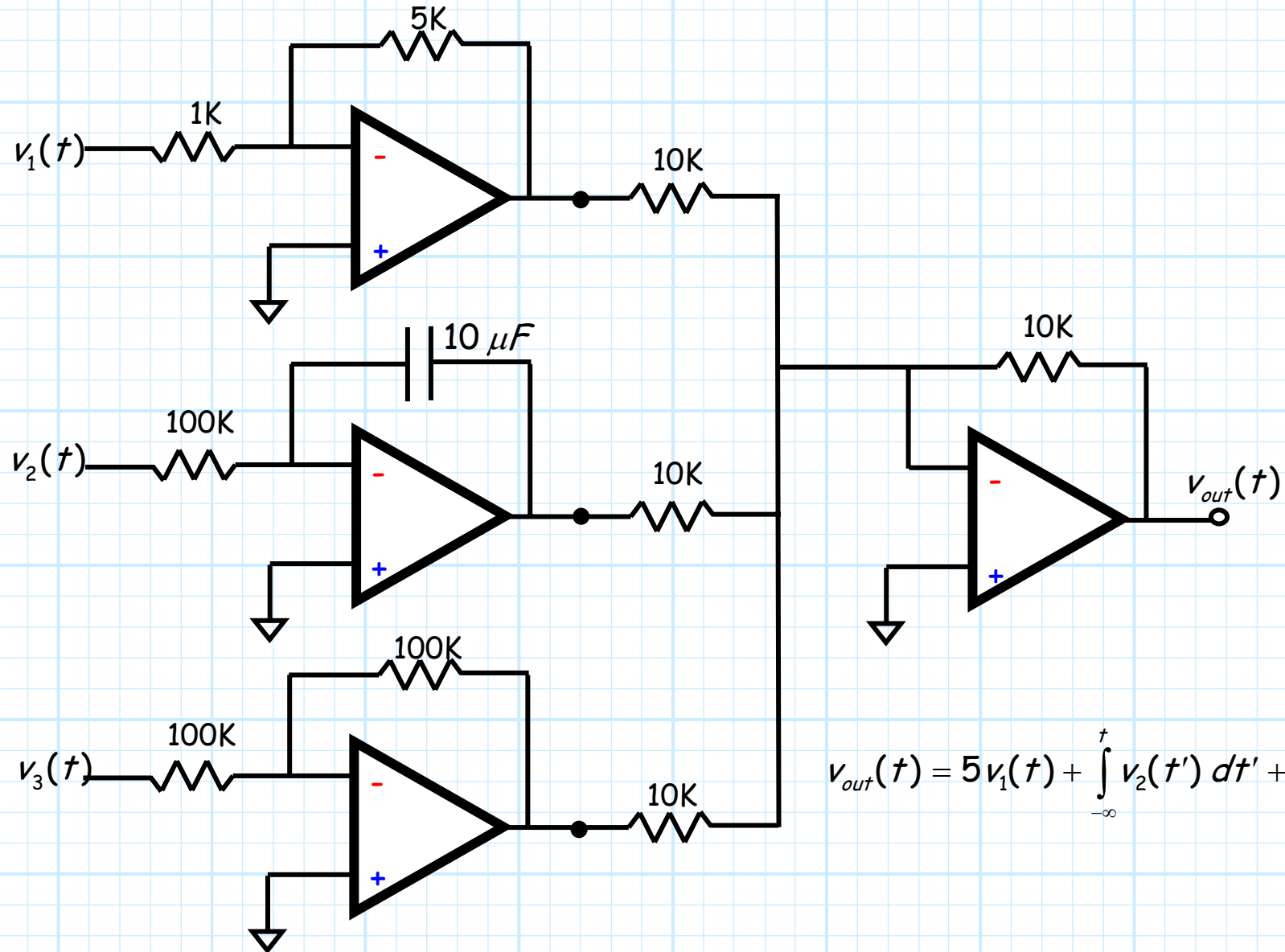

$$v_{out}(t) = 5v_1(t) + \int_{-\infty}^t v_2(t') dt' + \frac{dv_3(t)}{dt}$$