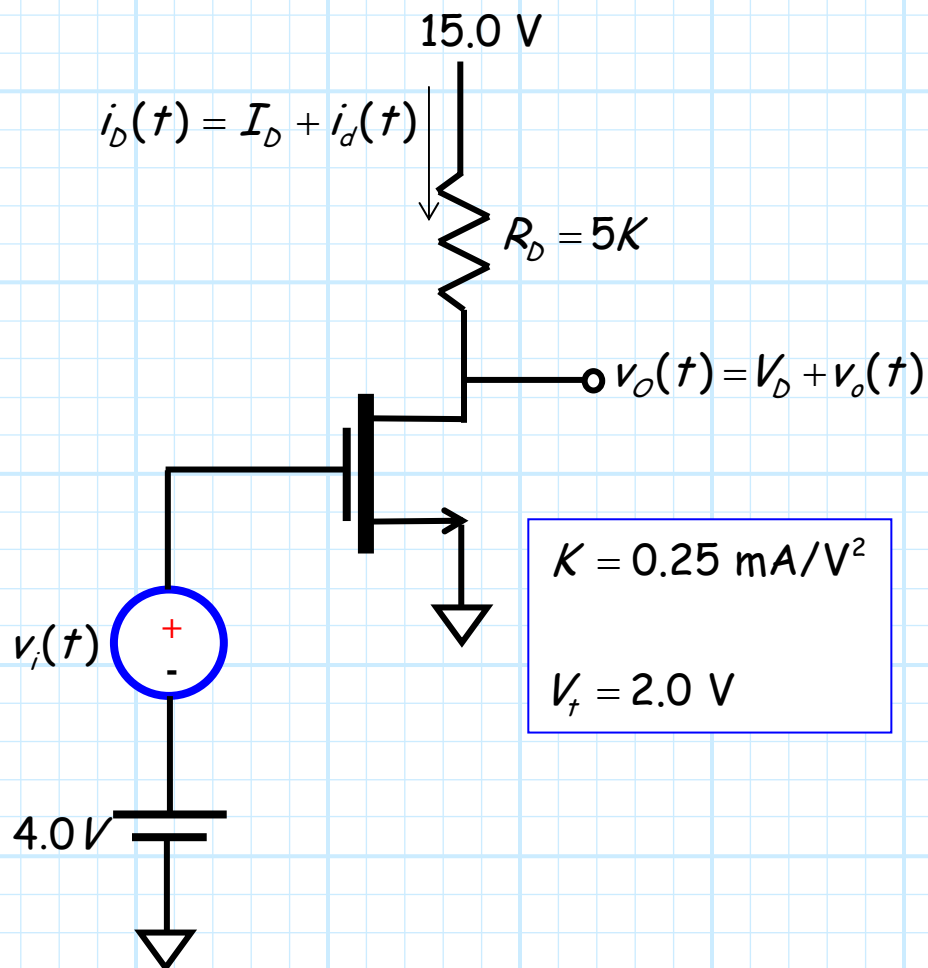


# Example: MOSFET Amplifier Distortion

Recall this circuit from a **previous** handout:



We found that the small-signal voltage gain is:

$$A_v = \frac{v_o(t)}{v_i(t)} = -5.0$$

Say the **input** voltage to this amplifier is:

$$v_i(t) = V_i \cos \omega t$$

**Q:** What is the **largest** value that  $V_i$  can take without producing a **distorted** output?

**A:** Well, we know that the **small-signal** output is:

$$\begin{aligned} v_o(t) &= A_{vo} v_i(t) \\ &= -5.0 V_i \cos \omega t \end{aligned}$$

**BUT**, this is **not** the output voltage!


The **total** output voltage is the **sum** of the **small-signal** output voltage and the **DC** output voltage!

Note for this example, the **DC** output voltage is the **DC** drain voltage, and we recall we determined in an earlier handout that its value is:

$$V_O = V_D = 10 \text{ V}$$


Thus, the **total output voltage** is :
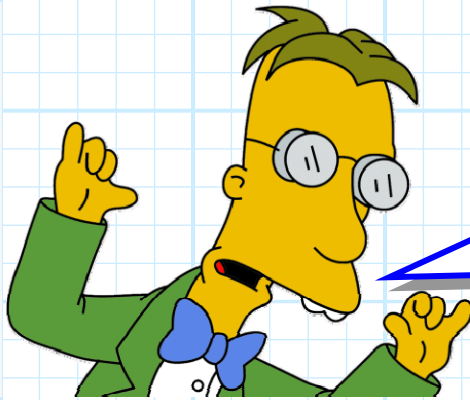
$$\begin{aligned} v_o(t) &= V_D + v_o(t) \\ &= 10.0 - 5.0 V_i \cos \omega t \end{aligned}$$



*It is very important that you realize there is a **limit** on both how high and how low the **total** output voltage  $v_o(t)$  can go!*

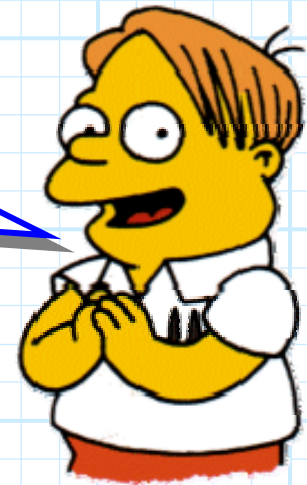*That's right! If the **total** output voltage  $v_o(t)$  tries to exceed these limits—even for a moment—the MOSFET will leave **saturation** mode.*



*And leaving saturation mode results in **signal distortion!***

Let's break the problem down into **two** separate problems:

- 1) If **total** output voltage  $v_o(t)$  becomes too **small**, the MOSFET will enter the **triode** mode.
- 2) If **total** output voltage  $v_o(t)$  becomes too **large**, the MOSFET will enter **cutoff**.

We'll first consider **problem 1**.

For a MOSFET to remain in saturation,  $v_{DS}(t)$  must remain **greater than** the excess gate voltage ( $V_{GS} - V_t$ ) for all time  $t$ .

$$v_{DS}(t) > V_{GS} - V_t$$

Since the source terminal of the MOSFET in **this** circuit is connected to ground, we know that  $V_S = 0$  V. Therefore:

$$v_{DS}(t) = v_D(t) = v_o(t) \quad \text{and} \quad V_{GS} = V_G$$

And so the MOSFET will remain in saturation **only** if the total output voltage remains **larger** than  $V_{GS} - V_t = V_G - V_t$ !

$$v_o(t) > V_G - V_t$$

Thus, we conclude for this amplifier that the output "floor" is:

$$L_- = V_G - V_t$$

And since  $V_G = 4.0\text{ V}$  and  $V_t = 2.0\text{ V}$ , we find:

$$L_- = V_G - V_t = 4 - 2 = 2.0\text{ V}$$

Thus, to remain in saturation, the **total** output voltage must remain larger than the "floor" voltage  $L_-$  for all time  $t$ :

$$v_o(t) > L_- = 2.0\text{ V}$$

Since this **total** voltage is:

$$v_o(t) = 10.0 - 5.0 V_i \cos \omega t$$

we can determine the **maximum** value of small-signal input magnitude  $V_i$ :

$$10.0 - 5.0 V_i \cos \omega t > 2.0$$

$$\Rightarrow 8.0 > 5.0 V_i \cos \omega t$$

$$\Rightarrow V_i \cos \omega t < 1.6$$

Since  $\cos\omega t$  can be as large as 1.0, we find that the **magnitude** of the **input** voltage can be **no larger** than 1.6 V, i.e.,

$$V_i < 1.6 \text{ V}$$

If the **input** magnitude exceeds this value, the MOSFET will (momentarily) leave the saturation region and enter the dreaded **triode** mode!

Now let's consider **problem 2**

For the MOSFET to remain in saturation, the **drain** current must be **greater** than zero (i.e.,  $i_D > 0$ ). Otherwise, the MOSFET will enter **cutoff** mode.

Applying **Ohm's Law** to the drain resistor, we find the **drain current** is:

$$i_D = \frac{V_{DD} - v_O}{R_C} = \frac{15 - v_O}{5}$$

it is evident that drain current is **positive** only if  $v_O < 15 \text{ V}$ .

In other words, the **upper** limit (i.e., the "ceiling") on the **total** output voltage is:

$$L_+ = V_{DD} = 15.0 \text{ V}$$

Since:

$$v_O(t) = 10.0 - 5.0 V_i \cos\omega t$$

we can conclude that in order for the MOSFET to remain in **saturation** mode:

$$10 - 5.0 V_i \cos \omega t > 15.0$$

Therefore, we find:

$$V_s \cos \omega t > \frac{-5.0}{5.0} = -1.0$$

Since  $\cos \omega t \geq -1$ , the above equation means that the **input signal magnitude**  $V_i$  can be **no larger** than:

$$V_i < 1.0 \text{ V}$$

If the input magnitude **exceeds** 1.0 V, the MOSFET will (momentarily) leave the saturation and enter the **cutoff** region!


**In summary:**

- 1)** If  $V_i > 1.6 \text{ V}$ , the MOSFET will at times enter **triode**, and **distortion** will occur!
- 2)** If  $V_i > 1.0 \text{ V}$ , the MOSFET will at times enter **cutoff**, and **even more** distortion will occur!

To demonstrate this, let's consider **three** examples:

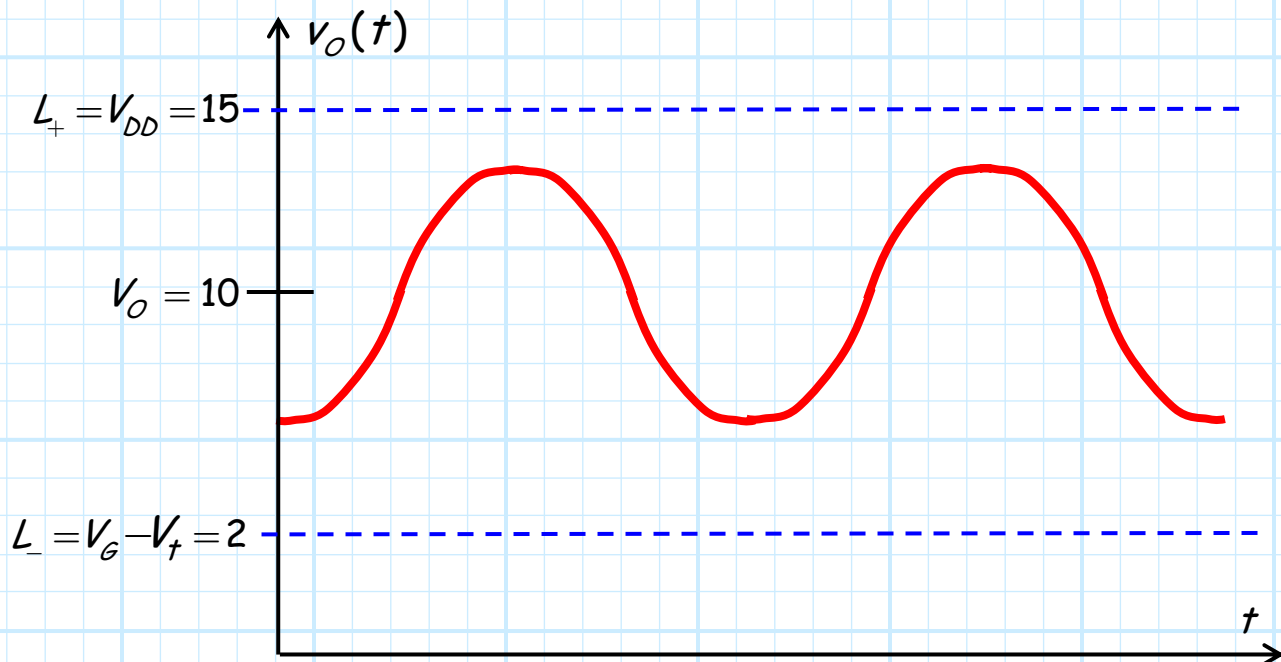**1.**  $V_i < 1.0 \text{ V}$


The output signal in this case remains between  $V_{DD} = 15.0$  and  $V_G - V_t = 2.0 \text{ V}$  for **all** time  $t$ . Therefore, the output signal is **not distorted**.



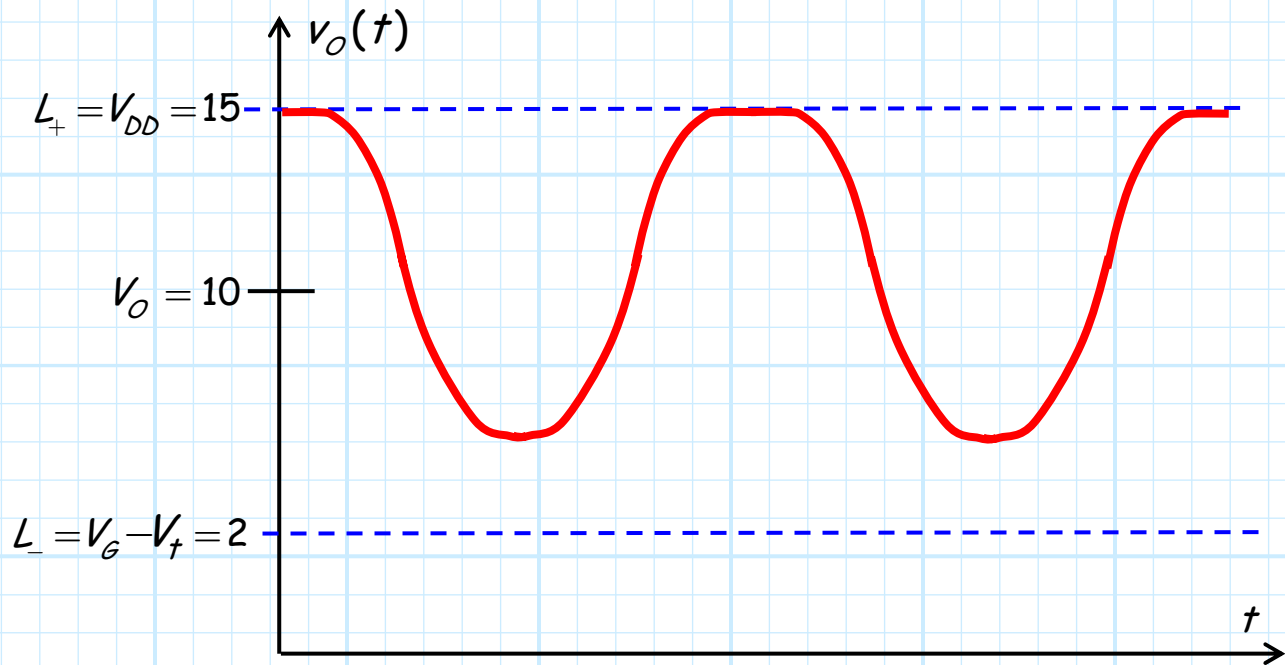**2.**  $1.6 \text{ V} > V_i > 1.0 \text{ V}$

The output signal in this case remains greater than  $L_- = V_G - V_t = 2$  for all time  $t$ . However, the small-signal output is now large enough so that the total output voltage at times tries to **exceed**  $L_+ = V_{DD} = 15$ . For these times, the MOSFET will enter **cutoff**, and the output signal will be **distorted**.





### 3. $V_i > 1.6\text{ V}$

In this case, the small-signal input signal is sufficiently **large** so that the total output will attempt to exceed **both** limits (i.e.,  $V_{DD} = 15.0\text{V}$  and  $V_G - V_t = 2.0\text{V}$ ). Therefore, there are periods of time when the MOSFET will be in **cutoff**, and periods when the MOSFET will be in **saturation**.

