

## 4.5 Biasing in BJT Amplifier Circuits

Reading Assignment: 280-286

Now let's examine how we DC bias MOSFETs amplifiers!

If we don't bias properly, distortion can result!

### EXAMPLE: MOSFET AMPLIFIER DISTORTION

There is a classic bias circuit for MOSFET amplifiers; let's see what it is!

### HO: MOSFET BIASING USING A SINGLE POWER SUPPLY

Let's do an example DC bias design.

### EXAMPLE: BIASING OF DISCRETE MOSFET AMPLIFIERS

We can also use a DC current source to bias the Amplifier.

**Q:** *Yes, but just how do we construct a current source?*

**A:** HO: THE MOSFET CURRENT MIRROR


HO: CURRENT STEERING CIRCUITS

## HO: MOSFET BIASING USING CURRENT MIRRORS

### EXAMPLE: MOSFET BIASING USING CURRENT MIRRORS
 
# Example: MOSFET Amplifier Distortion

Recall this circuit from a **previous** handout:



We found that the small-signal voltage gain is:

$$A_v = \frac{v_o(t)}{v_i(t)} = -5.0$$

Say the **input** voltage to this amplifier is:

$$v_i(t) = V_i \cos \omega t$$

**Q:** What is the **largest** value that  $V_i$  can take without producing a **distorted** output?

**A:** Well, we know that the **small-signal** output is:

$$\begin{aligned} v_o(t) &= A_{vo} v_i(t) \\ &= -5.0 V_i \cos \omega t \end{aligned}$$

**BUT**, this is **not** the output voltage!


The **total** output voltage is the **sum** of the **small-signal** output voltage and the **DC** output voltage!

Note for this example, the **DC** output voltage is the **DC** drain voltage, and we recall we determined in an earlier handout that its value is:

$$V_O = V_D = 10 \text{ V}$$

Thus, the **total** output voltage is :
 
$$\begin{aligned} v_o(t) &= V_D + v_o(t) \\ &= 10.0 - 5.0 V_i \cos \omega t \end{aligned}$$



*It is very important that you realize there is a **limit** on both how high and how low the **total** output voltage  $v_o(t)$  can go!*

*That's right! If the **total** output voltage  $v_o(t)$  tries to exceed these limits—even for a moment—the MOSFET will leave **saturation** mode.*



*And leaving saturation mode results in **signal distortion!***

Let's break the problem down into **two** separate problems:

- 1) If **total** output voltage  $v_o(t)$  becomes too **small**, the MOSFET will enter the **triode** mode.
- 2) If **total** output voltage  $v_o(t)$  becomes too **large**, the MOSFET will enter **cutoff**.

We'll first consider **problem 1**.

For a MOSFET to remain in saturation,  $v_{DS}(t)$  must remain **greater than** the excess gate voltage ( $V_{GS} - V_t$ ) for all time  $t$ .

$$v_{DS}(t) > V_{GS} - V_t$$

Since the source terminal of the MOSFET in **this** circuit is connected to ground, we know that  $V_S = 0$  V. Therefore:

$$v_{DS}(t) = v_D(t) = v_o(t) \quad \text{and} \quad V_{GS} = V_G$$

And so the MOSFET will remain in saturation **only** if the total output voltage remains **larger** than  $V_{GS} - V_t = V_G - V_t$ !

$$v_o(t) > V_G - V_t$$

Thus, we conclude for this amplifier that the output "floor" is:

$$L_- = V_G - V_t$$

And since  $V_G = 4.0\text{ V}$  and  $V_t = 2.0\text{ V}$ , we find:

$$L_- = V_G - V_t = 4 - 2 = 2.0\text{ V}$$

Thus, to remain in saturation, the **total** output voltage must remain larger than the "floor" voltage  $L_-$  for all time  $t$ :

$$v_o(t) > L_- = 2.0\text{ V}$$

Since this **total** voltage is:

$$v_o(t) = 10.0 - 5.0 V_i \cos \omega t$$

we can determine the **maximum** value of small-signal input magnitude  $V_i$ :

$$10.0 - 5.0 V_i \cos \omega t > 2.0$$

$$\Rightarrow 8.0 > 5.0 V_i \cos \omega t$$

$$\Rightarrow V_i \cos \omega t < 1.6$$

Since  $\cos\omega t$  can be as large as 1.0, we find that the **magnitude** of the **input** voltage can be **no larger** than 1.6 V, i.e.,

$$V_i < 1.6 \text{ V}$$

If the **input** magnitude exceeds this value, the MOSFET will (momentarily) leave the saturation region and enter the dreaded **triode** mode!

Now let's consider **problem 2**

For the MOSFET to remain in saturation, the **drain** current must be **greater** than zero (i.e.,  $i_D > 0$ ). Otherwise, the MOSFET will enter **cutoff** mode.

Applying **Ohm's Law** to the drain resistor, we find the **drain current** is:

$$i_D = \frac{V_{DD} - v_O}{R_C} = \frac{15 - v_O}{5}$$

it is evident that drain current is **positive** only if  $v_O < 15 \text{ V}$ .

In other words, the **upper** limit (i.e., the "ceiling") on the **total** output voltage is:

$$L_+ = V_{DD} = 15.0 \text{ V}$$

Since:

$$v_O(t) = 10.0 - 5.0 V_i \cos\omega t$$



we can conclude that in order for the MOSFET to remain in **saturation** mode:

$$10 - 5.0 V_i \cos \omega t > 15.0$$

Therefore, we find:

$$V_s \cos \omega t > \frac{-5.0}{5.0} = -1.0$$

Since  $\cos \omega t \geq -1$ , the above equation means that the **input signal magnitude**  $V_i$  can be **no larger** than:

$$V_i < 1.0 \text{ V}$$

If the input magnitude **exceeds** 1.0 V, the MOSFET will (momentarily) leave the saturation and enter the **cutoff** region!


**In summary:**

- 1) If  $V_i > 1.6 \text{ V}$ , the MOSFET will at times enter **triode**, and **distortion** will occur!
- 2) If  $V_i > 1.0 \text{ V}$ , the MOSFET will at times enter **cutoff**, and **even more** distortion will occur!

To demonstrate this, let's consider **three** examples:

 
**1.**  $V_i < 1.0 \text{ V}$

The output signal in this case remains between  $V_{DD} = 15.0$  and  $V_G - V_t = 2.0 \text{ V}$  for **all** time  $t$ . Therefore, the output signal is **not distorted**.



 
**2.**  $1.6 \text{ V} > V_i > 1.0 \text{ V}$

The output signal in this case remains greater than  $L_- = V_G - V_t = 2$  for all time  $t$ . However, the small-signal output is now large enough so that the total output voltage at times tries to **exceed**  $L_+ = V_{DD} = 15$ . For these times, the MOSFET will enter **cutoff**, and the output signal will be **distorted**.



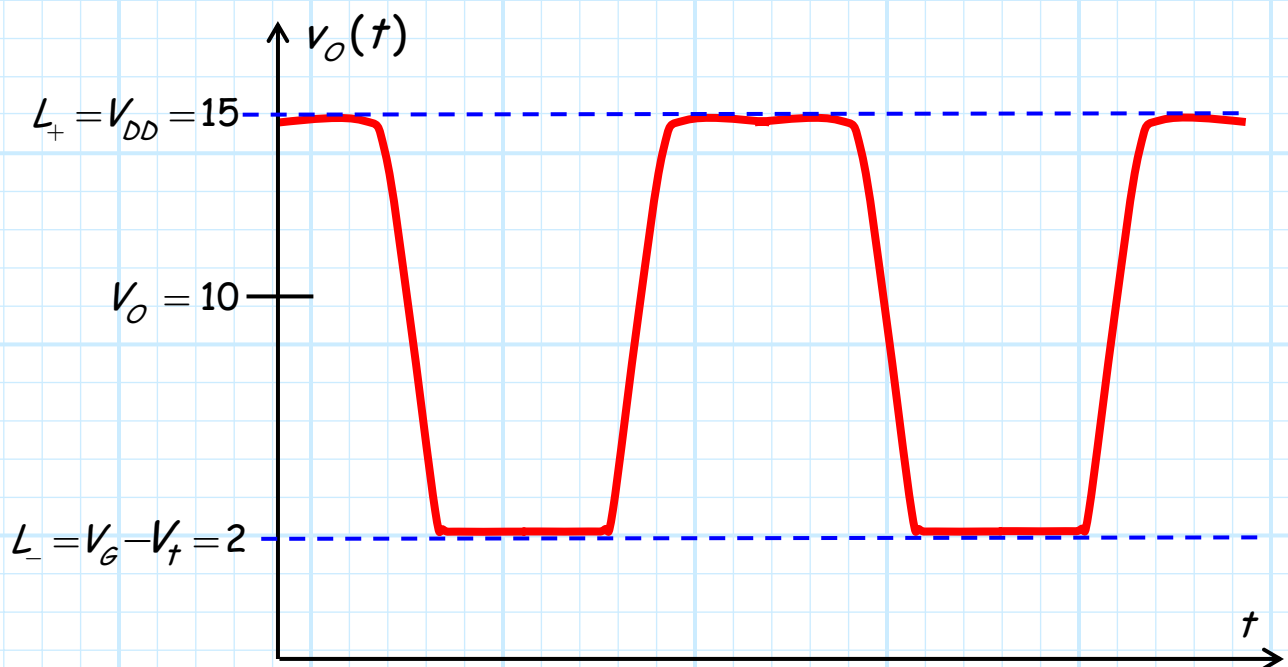
### 3. $V_i > 1.6\text{ V}$

In this case, the small-signal input signal is sufficiently **large** so that the total output will attempt to exceed **both** limits (i.e.,  $V_{DD} = 15.0\text{ V}$  and  $V_G - V_t = 2.0\text{ V}$ ). Therefore, there are periods of time when the MOSFET will be in **cutoff**, and periods when the MOSFET will be in **saturation**.


 
# MOSFET Biasing using a Single Power Supply

The general form of a single-supply MOSFET amplifier biasing circuit is:



Just like BJT biasing, we typically attempt to satisfy three main bias design goals:

## 1) Maximize Gain

Typically, the small-signal **voltage gain** of a MOSFET amplifier will be proportional to transconductance  $g_m$ :

$$A_{vo} \propto g_m$$

Thus, to maximize the amplifier voltage gain, we must **maximize** the MOSFET transconductance.

**Q:** *What does this have to do with D.C. biasing?*

**A:** Recall that the transconductance depends on the **DC excess gate voltage**:

$$g_m = 2K(V_{GS} - V_t)$$

Another way to consider transconductance is to express it in terms of DC drain current  $I_D$ . Recall this DC current is related to the DC excess gate voltage (in saturation!) as:

$$I_D = K(V_{GS} - V_t)^2 \quad \Rightarrow \quad (V_{GS} - V_t) = \sqrt{\frac{I_D}{K}}$$

And so transconductance can be alternatively expressed as:

$$g_m = 2K(V_{GS} - V_t) = 2K\sqrt{\frac{I_D}{K}} = 2\sqrt{KI_D}$$

Therefore, the amplifier voltage gain is typically **proportional** to the square-root of the DC drain current:

$$A_{vo} \propto \sqrt{I_D}$$

To maximize  $A_{vo}$ , maximize  $I_D$

## 2) Maximize Voltage Swing

Recall that if the DC drain voltage  $V_D$  is biased too close to  $V_{DD}$ , then even a small small-signal drain voltage  $v_d(t)$  can result in a **total** drain voltage that is too **large**, i.e.:

$$v_D(t) = V_D + v_d(t) \geq V_{DD}$$

In other words, the MOSFET enters **cutoff**, and the result is a **distorted** signal!

To avoid this (to allow  $v_d(t)$  to be as large as possible without MOSFET entering cutoff), we need to bias our MOSFET such that the DC drain voltage  $V_D$  is as **small** as possible.

Note that the drain voltage is:

$$V_D = V_{DD} - R_D I_D$$

Therefore  $V_D$  is minimized by designing the bias circuit such that the DC drain current  $I_D$  is as **large** as possible.

However, we must **also** consider the signal distortion that occurs when the MOSFET enters **triode**. This of course is avoided if the total voltage drain-to-source remains greater than the excess gate voltage, i.e.:

$$v_{DS}(t) = V_{DS} + v_{ds}(t) > (V_{GS} - V_t)$$

Thus, to avoid the MOSFET triode mode—and the resulting signal distortion—we need to bias our MOSFET such that the DC voltage  $V_{DS}$  is as **large** as possible.

To minimize signal distortion, maximize  $V_{DS}$

### 3) Minimize Sensitivity to changes in $K, V_t$

We find that MOSFETs are **sensitive** to temperature—specifically, the value of  $K$  is a function of temperature.

Likewise, the values of  $K$  and threshold voltage  $V_t$  are not particularly constant with regard to the manufacturing process.

Both of these facts lead to the requirement that our bias design be **insensitive** to the values of  $K$  and  $V_t$ . Specifically, we want to design the bias network such that the DC bias current does **not** change values when  $K$  and/or  $V_t$  does.

**Mathematically**, we can express this requirement as minimizing the value:

$$\frac{d I_D}{dK} \quad \text{and} \quad \frac{d I_D}{dV_f}$$

Similar to the BJT, we find that these derivatives are minimized by maximizing the value of **source resistor**  $R_S$ .


To minimize  $d I_D / dK$ , maximize  $R_S$

So, let's **recap** what we have learned about designing our bias network:

 1. Make  $I_D$  as large as possible.
2. Make  $V_{DS}$  as large as possible.
3. Make  $R_S$  as large as possible.

Again analogous to BJT biasing, we find that these three goals are conflicting, as they are constrained by the KVL equation of the bias circuit:





$$V_{DD} - I_D R_D - V_{DS} - I_D R_S = 0$$

or

$$I_D R_D + V_{DS} + I_D R_S = V_{DD}$$

Maximize  $A_{vo}$  by maximizing this term.

Minimize distortion by maximizing this term.

Minimize sensitivity by maximizing this term.

But the **total** of the three terms must equal this!

Resolving this conflict is a subject choice of the amplifier designer. However, here is a "rule-of-thumb" procedure.

However, verify that these results satisfy your design requirements (or the requirements assigned to you by your boss and/or professor!).

**1.** Given the desired value of  $I_D$ , make source voltage  $V_S = V_{DD}/4$ , i.e. set the source resistor  $R_S$  to:

$$R_S = \frac{V_S}{I_D} = \frac{V_{DD}}{4I_D} \quad (1)$$

This value reduces the sensitivity  $dI_D/dK$  !

**2.** Now determine the required value of  $V_{GS}$ . Since  $I_D = K(V_{GS} - V_t)^2$ , we find that  $V_{GS}$  should be:

$$V_{GS} = \sqrt{\frac{I_D}{K}} + V_t$$

**3.** Set the required value of gate voltage  $V_G$ .

Note that:

$$V_G = V_{GS} + V_S$$

Thus, we can **add** the results of the previous **two** steps to find the required value of the gate voltage  $V_G$ .

To set the gate voltage to this value, we must select the proper values of **resistors**  $R_1$  and  $R_2$ .

Since the gate current is **zero** ( $i_G = 0$ ), we find from voltage division that:

$$V_G = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right) = \frac{V_{DD}}{\left( \frac{R_1}{R_2} \right) + 1} \quad (2)$$

Note this equation determines the **ratio** of resistors  $R_1$  and  $R_2$ , but not the resistors themselves.

We need a **second** equation to explicitly determine the resistors values—the **sum** of the two resistances, for example.

We find that making the resistances  $R_1$  and  $R_2$  as **large** as possible is **very desirable!** This will typically maximize the amplifier input resistance, as well as result in minimum power dissipation.

As a result, we make the resistors as **large a practicable**. For **example**:

$$R_1 + R_2 = 250 \text{ K} \quad (3)$$

**4.** Set the required value of DC drain voltage  $V_D$ .

Recall that:

**a)** we require  $V_D \ll V_{DD} = V_+$  to avoid **cutoff** mode.

b) and, we require that  $V_D \gg V_G - V_t = V_{GS}$  to avoid **triode** mode.

**Solution:** set the drain voltage  $V_D$  to a value **half-way** between  $V_{DD}$  and  $V_G - V_t$ !

In other words, set the DC **drain voltage** to be:

$$V_D = \frac{V_{DD} + (V_G - V_t)}{2}$$

To achieve this, we must select the drain **resistor**  $R_D$  so that:

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{V_{DD} - (V_G - V_t)}{2I_D} \quad (4)$$


Thus, use equations (1), (2), (3), and (4) to determine the **standard** DC bias design (i.e.,  $R_1$ ,  $R_2$ ,  $R_S$ , and  $R_D$ ) for MOSFET amplifiers.

*If I were you, I'd make sure I understood this material well enough that I could also bias a **non-standard** MOSFET amplifier problem.*

*It's not enough to simply know how, you must also know **why!***


 
# Example: Biasing of Discrete MOSFET Amplifiers



If the MOSFET has device values  $K = 1.0 \text{ mA/V}^2$  and  $V_f = 1.0 \text{ V}$ , determine the resistor values to bias this MOSFET with a DC drain current of:

$$I_D = 4 \text{ mA}$$

- Given the desired value of  $I_D$ , make **source voltage**  $V_s = V_{DD}/4 = 4.0 \text{ V}$ , i.e. set the source resistor  $R_S$  to:

$$R_S = \frac{V_s}{I_D} = \frac{4.0}{4.0} = 1 \text{ K}\Omega$$

2. Now determine the required value of  $V_{GS}$ . Since  $I_D = K(V_{GS} - V_t)^2$ , we find that  $V_{GS}$  should be:

$$\begin{aligned} V_{GS} &= \sqrt{\frac{I_D}{K}} + V_t \\ &= \sqrt{\frac{4.0}{1.0}} + 1.0 \\ &= 3.0 \text{ V} \end{aligned}$$

3. Set the required value of **gate voltage**  $V_G$ .

$$\begin{aligned} V_G &= V_{GS} + V_S \\ &= 3.0 + 4.0 \\ &= 7.0 \text{ V} \end{aligned}$$

Since the gate current is **zero** ( $i_G = 0$ ), we find from voltage division that:

$$V_G = \frac{V_{DD}}{\left(\frac{R_1}{R_2}\right) + 1}$$

Therefore:

$$\begin{aligned} \frac{R_1}{R_2} &= \frac{V_{DD}}{V_G} - 1 \\ &= \frac{16.0}{7.0} - 1 \\ &= \frac{9}{7} \end{aligned}$$

We need a **second** equation to explicitly determine the resistors values—the **sum** of the two resistances, for example.

We make the resistors as large a practicable. For **example**:

$$R_1 + R_2 = 240 \text{ K}$$

Therefore:

$$\frac{9}{7}R_2 + R_2 = 240$$

$$\frac{16}{7}R_2 = 240$$

and thus:

$$R_1 = 135 \text{ K}\Omega \quad \text{and} \quad R_2 = 105 \text{ K}\Omega$$

**4.** Set the required value of DC drain voltage  $V_D$ .


Set the drain voltage  $V_D$  to a value **half-way** between  $V_{DD}$  and  $V_G - V_t$ !

In other words, set the DC **drain voltage** to be:

$$\begin{aligned} V_D &= \frac{V_{DD} + (V_G - V_t)}{2} \\ &= \frac{16 + (7.0 - 1.0)}{2} \\ &= 11.0 \text{ V} \end{aligned}$$

To achieve this, we must select the drain resistor  $R_D$  so that:
 
$$\begin{aligned} R_D &= \frac{V_{DD} - V_D}{I_D} \\ &= \frac{16.0 - 11.0}{4.0} \\ &= 1.25 \text{ K}\Omega \end{aligned}$$





# The MOSFET Current Mirror

Consider the following MOSFET circuit:


Note  $V_D = V_G$ , therefore:

$$V_{DS} = V_{GS}$$

and thus:

$$V_{DS} > V_{GS} - V_t$$

 So, if  $V_{GS} > V_t$ , then the MOSFET is in **saturation**!



We know that for a MOSFET in saturation, the drain current is equal to:

$$I_D = K (V_{GS} - V_t)^2$$

Say we want this current  $I_D$  to be a **specific** value—call it  $I_{ref}$ .

Since  $V_s = 0$ , we find that from the above equation, the drain voltage must be:

$$V_D = \sqrt{\frac{I_{ref}}{K}} + V_t$$

Likewise, from KVL we find that:

$$I_{ref} = \frac{V_{DD} - V_D}{R}$$

And thus the **resistor** value to achieve the desired drain current  $I_{ref}$  is:


$$R = \frac{V_{DD} - V_D}{I_{ref}}$$

where:

$$V_D = \sqrt{\frac{I_{ref}}{K}} + V_t$$

**Q:** *Why are we doing this?*

 **A:** Say we now add another component to the circuit, with a second MOSFET that is **identical** to the first :



**Q:** *So what is current  $I_L$  ?*

**A:** Note that the gate voltage of each MOSFET is the **same** (i.e.,  $V_{GS1} = V_{GS2}$ ), and if the MOSFETS are the **same** (i.e.,  $K_1 = K_2$ ,  $V_{t1} = V_{t2}$ ), and if the second MOSFET is likewise in **saturation**, its drain current  $I_L$  is:

$$\begin{aligned} I_L &= K_2 (V_{GS2} - V_{t2})^2 \\ &= K_1 (V_{GS1} - V_{t1})^2 = I_{ref} \end{aligned}$$


Therefore, the drain current of the **second** MOSFET is **equal** to the current of the **first**!

$$I_{ref} = I_L$$

**Q:** *Wait a minute! You mean to say that the current through the resistor  $R_L$  is **independent** of the value of resistor  $R_L$  ?*

**A:** Absolutely! As long as the second MOSFET is in **saturation**, the current through  $R_L$  is equal to  $I_{ref}$ —**period**.

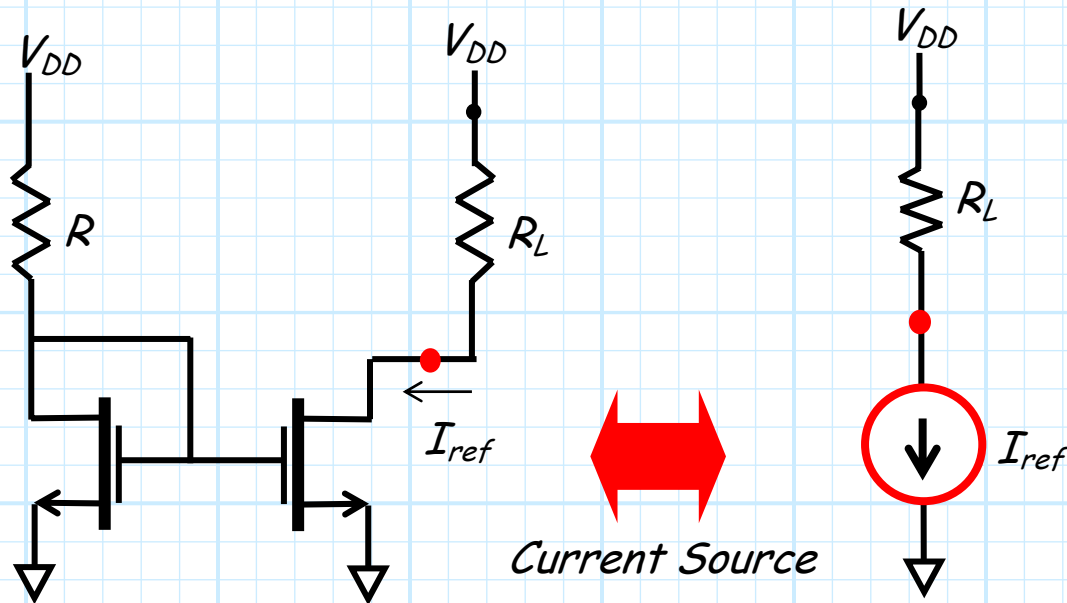The current through  $R_L$  is independent on the value of  $R_L$  (provided that the MOSFET remains in saturation). Think about what this means—this device is a **current source** !



Remember, the second MOSFET **must** be in saturation for the current through  $R_L$  to be a constant value  $I_{ref}$ . As a result, we find that:

$$V_{D_{S2}} > V_{G_{S2}} - V_{t2}$$

or for this example, since  $V_s = 0$ :

$$V_{D_2} > V_{G_2} - V_{t2}$$

Since  $V_{D_2} = V_{DD} - R_L I_{ref}$ , we find that in order for the MOSFET to be in saturation:

$$V_{DD} - R_L I_{ref} > V_{G_2} - V_{t2} = V_{G_1} - V_{t1}$$

Or, stated another way, we find that the load resistor  $R_L$  can be **no larger** than:

$$R_L < \frac{V_{DD} - V_{G1} + V_{t1}}{I_{ref}}$$

Where we know that:

$$V_{G1} = V_{DD} - R I_{ref}$$

and thus we can alternatively write the above equation as:


$$R_L < R + \frac{V_{t1}}{I_{ref}}$$

If the **load** resistor becomes **larger** than  $R + V_{t1}/I_{ref}$ , the voltage  $V_{DS2}$  will drop **below** the excess gate voltage  $V_{GS2} - V_{t2}$ , and thus the second MOSFET will enter the **triode** region. As a result, the drain current will **not** equal  $I_{ref}$  — the current source will **stop working!**




Although the circuit presented here is sometimes referred to as a **current sink**, understand that the circuit is clearly a way of designing a **current source**.

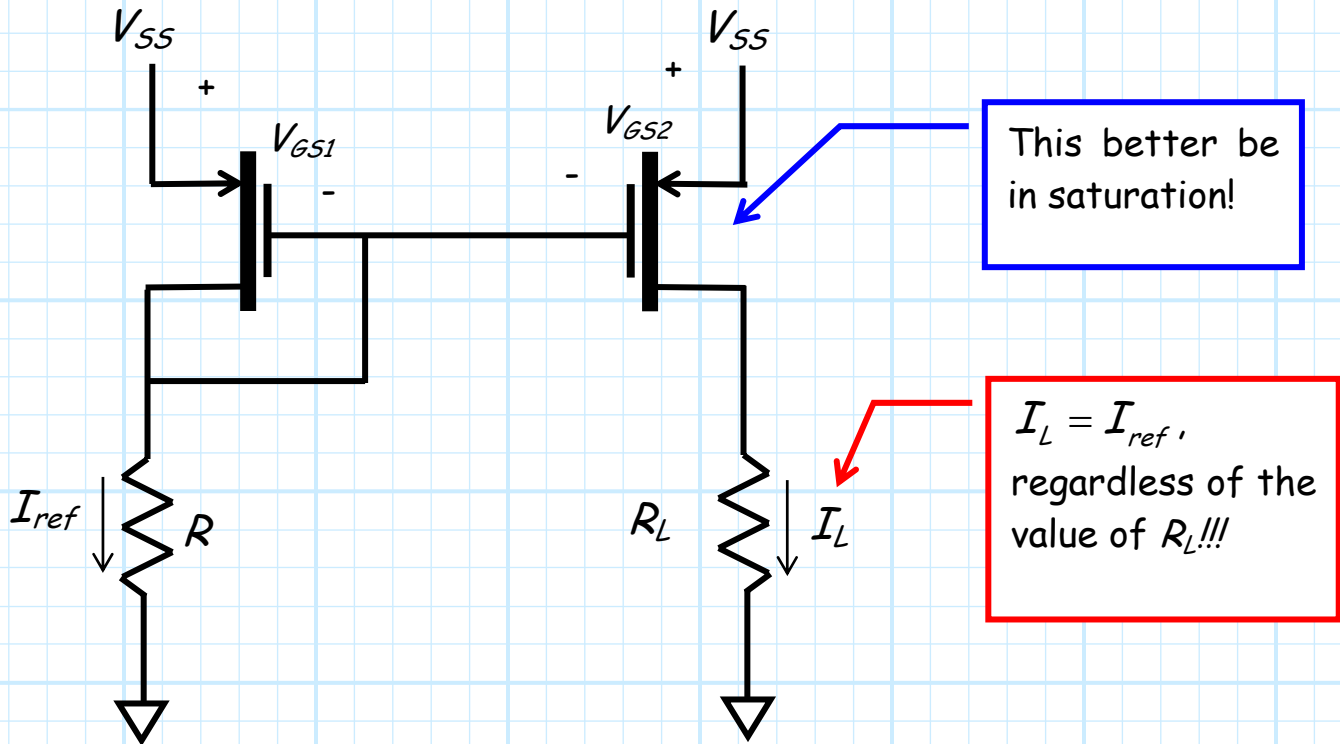We can also use **PMOS** devices to construct a current mirror!


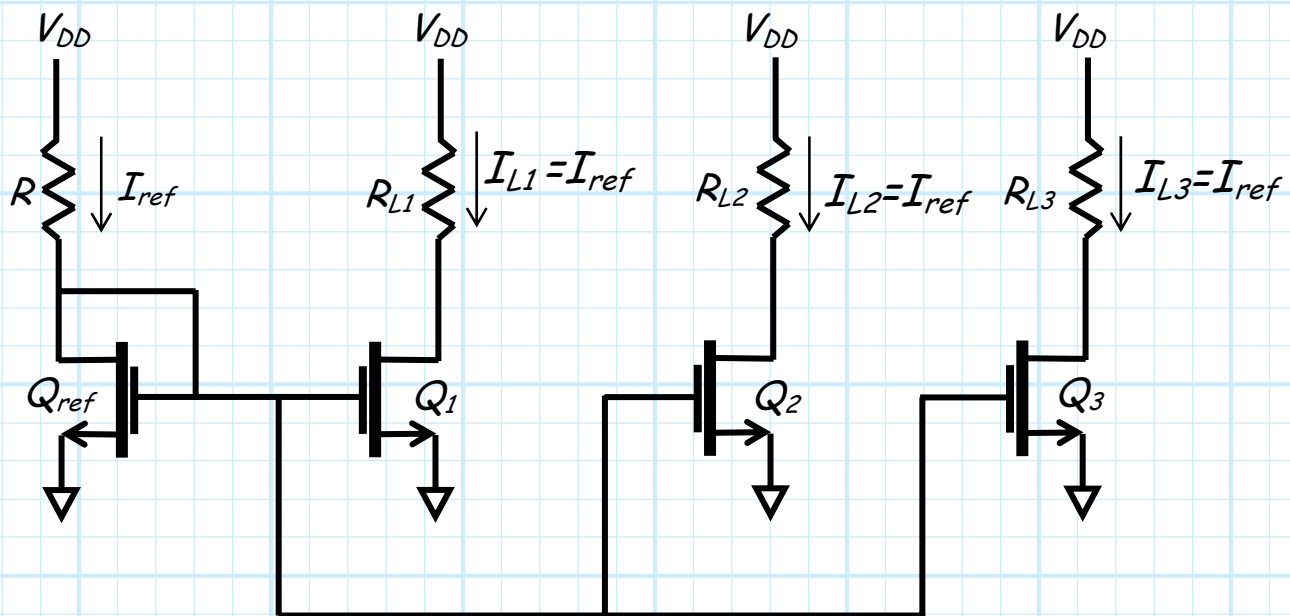
# Current Steering Circuits

A current mirror may consist of **many** MOSFET current sources!



This circuit is particularly useful in integrated circuit design, where **one** resistor  $R$  is used to make **multiple** current sources.

**Q:** What if we want to make the sources have **different** current values? Do we need to make **additional** current mirrors?

**A:** NO!!

Recall that the current mirror simply ensures that the gate to source voltages of **each** transistor is **equal** to the gate to source voltage of the **reference**:

$$V_{GS}^{ref} = V_{GS1} = V_{GS2} = V_{GS3} = \dots$$

Therefore, if each transistor is identical (i.e.,  $K_{ref} = K_1 = \dots$ , and  $V_t^{ref} = V_{t1} = V_{t2} = \dots$ ) then:

$$\begin{aligned} I_{ref} &= K_{ref} (V_{GS}^{ref} - V_t^{ref})^2 \\ &= K_n (V_{GSn} - V_{tn})^2 = I_{Dn} \end{aligned}$$

In other words, if each transistor  $Q_n$  is **identical** to  $Q_{ref}$ , then each current  $I_{Dn}$  will **equal** reference current  $I_{ref}$ .

**But**, consider what happens if the MOSFETS are not identical. Specifically, consider the case where  $K_n \neq K_{ref}$  (but  $V_{tn} = V_t^{ref}$ ).

Remember, we know that  $V_{GSn} = V_{GS}^{ref}$  still, even when  $K_n \neq K_{ref}$ . Thus, the drain current  $I_{Dn}$  will now be:

$$\begin{aligned} I_{Dn} &= K_n (V_{GSn} - V_{tn})^2 \\ &= K_n (V_{GS}^{ref} - V_t^{ref})^2 \\ &= K_n \left( \frac{I_{ref}}{K_{ref}} \right) \\ &= \left( \frac{K_n}{K_{ref}} \right) I_{ref} \end{aligned}$$


The drain current is a scaled value of  $I_{ref}$ !



For example, if  $K_1$  is twice that of  $K_{ref}$  (i.e.,  $K_1 = 2K_{ref}$ ), then  $I_{D1}$  will be twice as large as  $I_{ref}$  (i.e.,  $I_1 = 2I_{ref}$ ).


From the standpoint of integrated circuit design, we can change the value of  $K$  by modifying the MOSFET channel **width-to-length ratio** ( $W/L$ ) for each transistor.
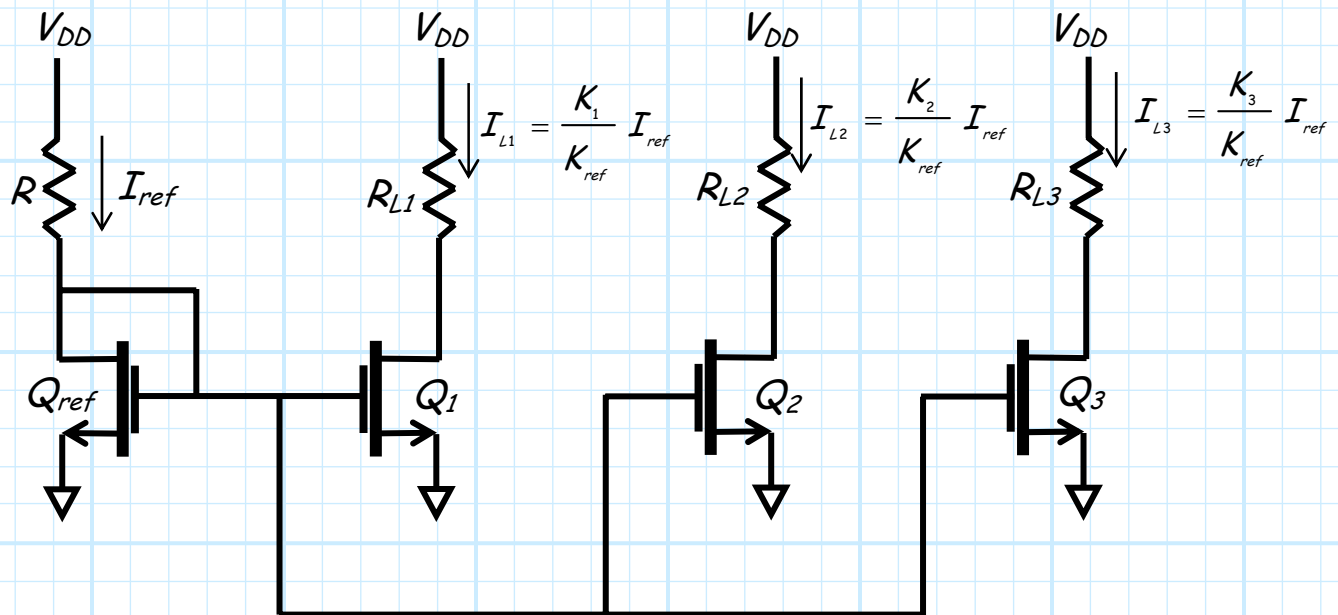
$$\frac{K_n}{K_{ref}} = \frac{\frac{1}{2}k'(W/L)_n}{\frac{1}{2}k'(W/L)_{ref}} = \frac{(W/L)_n}{(W/L)_{ref}}$$


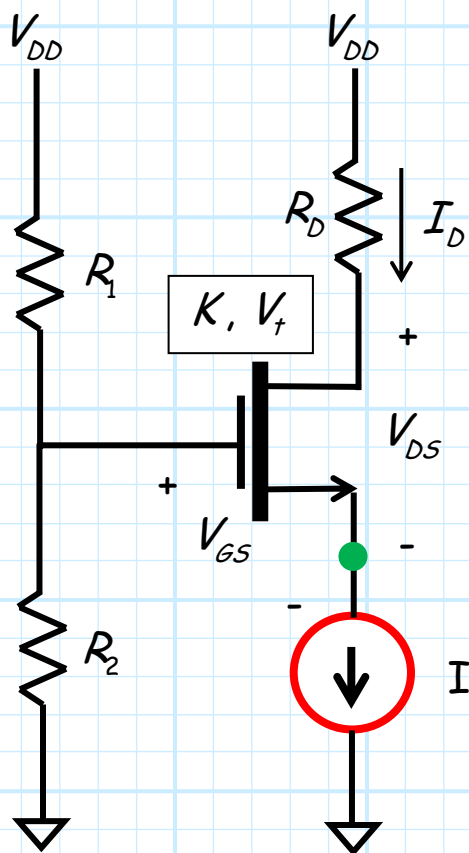
# MOSFET Biasing using a Current Mirror


Just as with BJT amplifiers, we can likewise bias a MOSFET amplifier using a **current source**:



It is evident that the DC drain current  $I_D$ , is equal to the current source  $I$ , **regardless** of the MOSFET values  $K$  or  $V_t$ !

Thus, this bias design maximizes drain current **stability**!

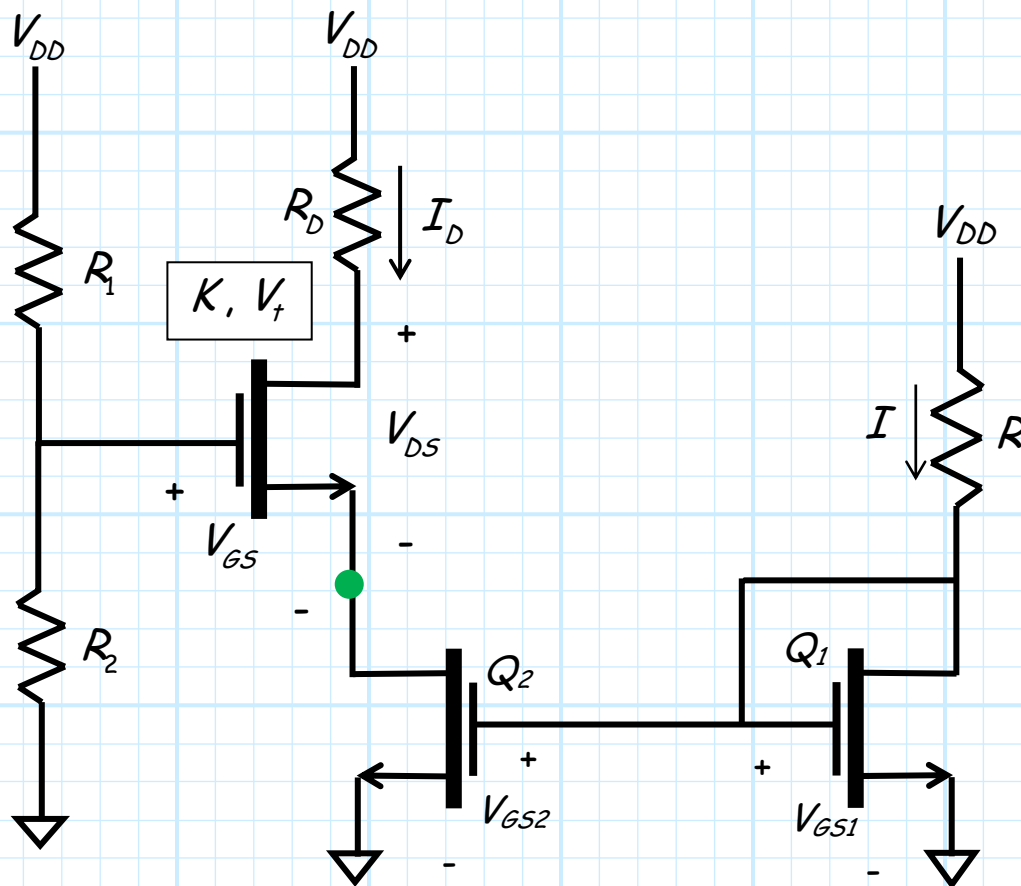We now know how to implement this bias design with MOSFETs—we use the **current mirror** to construct the current source!



Since  $I_D = I$ , it is evident that  $V_{GS}$  must be equal to:

$$V_{GS} = \sqrt{\frac{I}{K}} + V_t$$

and since the DC gate voltage is:

$$V_G = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right)$$

It is evident that the DC source voltage  $V_S$  is thus:

$$\begin{aligned}
 V_S &= V_G - V_{GS} \\
 &= V_{DD} \left( \frac{R_2}{R_1 + R_2} \right) - \left( \sqrt{\frac{I}{K}} + V_t \right)
 \end{aligned}$$

Since we are biasing with a current source, we do **not** need to worry about drain current **stability**—the current source will determine the DC drain current for **all** conditions (i.e.,  $I_D = I$ ).

We might conclude therefore, that we should make DC source voltage  $V_S$  as **small** as possible. After all, this would allow us to **maximize** the output voltage swing (i.e., maximize  $I_D R_D$  and  $V_{DS}$ ).

Note however, that the **source** voltage  $V_S$  of the MOSFET is numerically equal to the **drain** voltage  $V_{D2}$  (and thus  $V_{DS2}$ ) of the second MOSFET of the **current mirror**.


**Q:** *So what?!*

**A:** The voltage  $V_{DS2} = V_S$  must be **greater** than:

$$\begin{aligned}
 V_{GS2} - V_{t2} &= V_{GS1} - V_{t1} \\
 &= (V_{DD} - I_{ref} R) - V_{t1}
 \end{aligned}$$

in order for the **second MOSFET** to remain in **saturation**.

 There is a **minimum voltage** across the current source in order for the current source to properly operate!



Thus, to maximize output swing, we **might** wish to set:

$$V_S = V_{GS1} - V_{t1}$$

(although to be practical, we should make  $V_S$  **slightly greater** than this to allow for some design **margin**).

**Q:** How do we "set" the DC source voltage  $V_S$ ??

**A:** By setting the DC gate voltage  $V_G$ !!

Recall that the DC voltage  $V_{GS}$  is determined by the DC current source value  $I$ :

$$V_{GS} = \sqrt{\frac{I}{K}} + V_t$$

and the DC gate voltage is determined by the **two** resistors  $R_1$  and  $R_2$ :

$$V_G = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right)$$

Thus, we should **select** these resistors such that:

$$\begin{aligned} V_G &= V_{GS} + V_S \\ &= \left( \sqrt{\frac{I}{K}} + V_t \right) + (V_{GS1} - V_{t1}) \end{aligned}$$

**Q:** *So what should the value of resistor  $R_D$  be?*

**A:** Recall that we should set the DC drain voltage  $V_D$ :

a) much **less** than  $V_{DD}$  to avoid **cutoff**.

b) much **greater** than  $V_G - V_t$  to avoid **triode**.

Thus, we **compromise** by setting the DC drain voltage to a point **halfway** in between!


$$V_D = \frac{V_{DD} + (V_G - V_t)}{2}$$

To achieve this, we must select the drain **resistor**  $R_D$  so that:

$$R_D = \frac{V_{DD} - V_D}{I_D} = \frac{V_{DD} - (V_G - V_t)}{I_D}$$
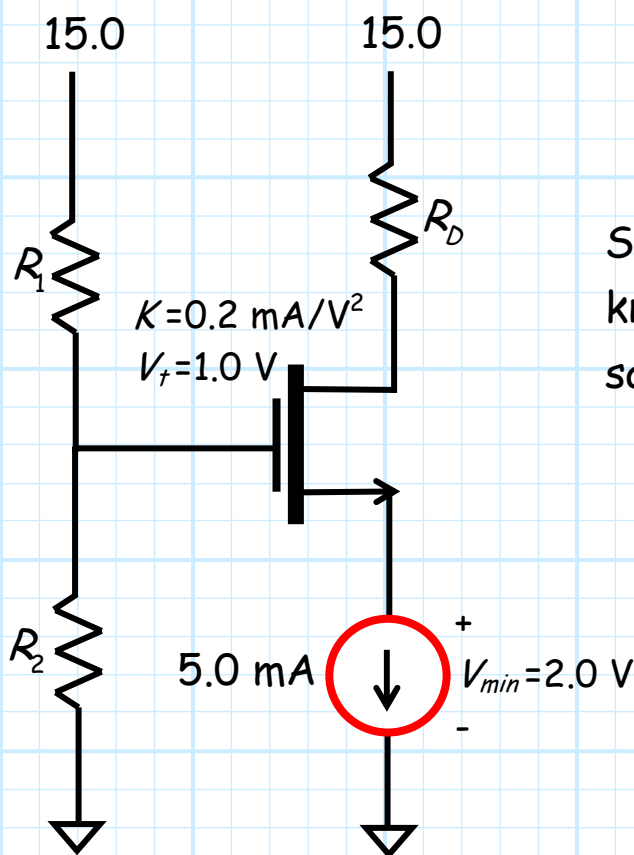
# Example: MOSFET Biasing using a Current Mirror

Let's determine the proper resistor values to DC bias this MOSFET. The current source is 5.0 mA and has a minimum voltage of 2.0 Volts in order to operate properly



Since  $I = I_D = 5.0\text{ mA}$ , we know that  $V_{GS}$  will be (if in saturation):

$$\begin{aligned} V_{GS} &= \sqrt{\frac{I}{K}} + V_t \\ &= \sqrt{\frac{5.0}{0.2}} + 1.0 \\ &= 6.0\text{ V} \end{aligned}$$

Assuming that we want the DC source voltage to be the minimum value of  $V_S = 2.0$ , we need for the DC gate voltage to be:

$$\begin{aligned} V_G &= V_{GS} + V_S \\ &= 6.0 + 2.0 \\ &= 8.0\text{ V} \end{aligned}$$

Thus, we need to select resistors  $R_1$  and  $R_2$  so that:

$$V_G = 8.0 = V_{DD} \left( \frac{R_2}{R_1 + R_2} \right)$$

or in other words, we want:

$$\left( \frac{R_2}{R_1 + R_2} \right) = \frac{8.0}{15.0}$$

Since we can make  $R_1$  and  $R_2$  large, let's assume that we want:

$$R_1 + R_2 = 300\text{K}$$

So that  $R_1 = 140\text{ K}\Omega$  and  $R_2 = 160\text{ K}\Omega$ .

Finally, we want the DC drain voltage to be:

$$\begin{aligned} V_D &= \frac{V_{DD} + (V_G - V_t)}{2} \\ &= \frac{15.0 + (8.0 - 1.0)}{2} \\ &= 11.0\text{ V} \end{aligned}$$

So that the resistor  $R_D$  is:

$$\begin{aligned} R_D &= \frac{V_{DD} - V_D}{I_D} \\ &= \frac{15.0 - 11.0}{5.0} \\ &= 0.8\text{ K}\Omega \end{aligned}$$



