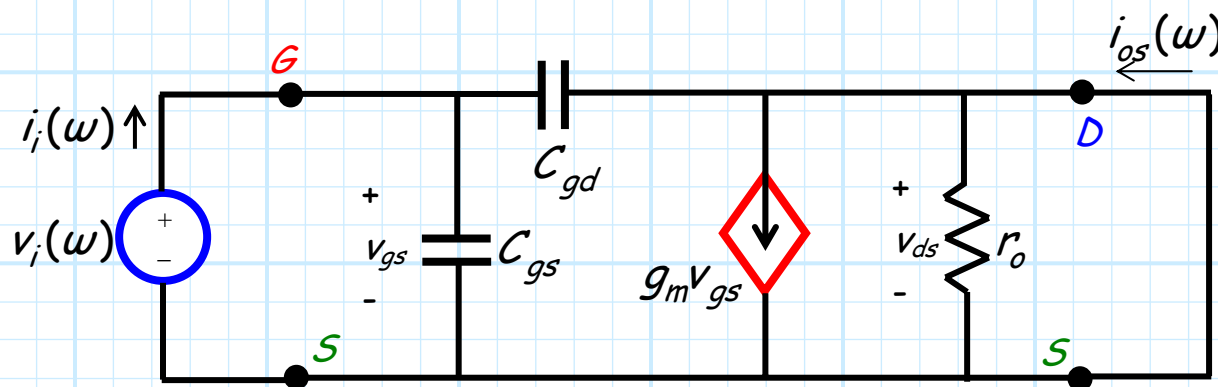


The MOSFET Unity Gain Frequency

Consider the short-circuit current gain of the high-frequency MOSFET small-signal model:



Note that because of the output short, $v_d = v_s$, so that $v_i = v_{gs} = v_{gd}$.

Therefore:

$$\begin{aligned} i_{os}(\omega) &= g_m v_{gs}(\omega) - j\omega C_{gd} v_{gd}(\omega) \\ &= g_m v_{gs}(\omega) - j\omega C_{gd} v_{gs}(\omega) \\ &= (g_m - j\omega C_{gd}) v_i(\omega) \end{aligned}$$

and

$$\begin{aligned} i_i(\omega) &= j\omega C_{gs} v_{gs}(\omega) + j\omega C_{gd} v_{gd}(\omega) \\ &= j\omega C_{gs} v_{gs}(\omega) + j\omega C_{gd} v_{gs}(\omega) \\ &= j\omega (C_{gs} + C_{gd}) v_i(\omega) \end{aligned}$$

The **short-circuit current gain** of the MOSFET is thus:

$$\begin{aligned} \frac{i_{os}}{i_i} &= \frac{(g_m - j\omega C_{gd})v_i(\omega)}{j\omega(C_{gs} + C_{gd})v_i(\omega)} \\ &= \frac{(g_m - j\omega C_{gd})}{j\omega(C_{gs} + C_{gd})} \\ &\approx \frac{g_m}{j\omega(C_{gs} + C_{gd})} \end{aligned}$$

Note that this is **not** a **low-pass function**! Therefore, there is no "break" frequency associated with this frequency response.

However, there is a "**unity gain**" frequency ω_T —it's the frequency where the short-circuit current gain is equal to **one**:

$$\left| \frac{i_{os}(\omega = \omega_T)}{i_i(\omega = \omega_T)} \right| = 1 = \frac{g_m}{\omega_T(C_{gs} + C_{gd})}$$

Therefore we find that the **unity-gain frequency** of a MOSFET is:

$$\omega_T = \frac{g_m}{C_{gs} + C_{gd}}$$

Note as the capacitances get **smaller**, the unity gain frequency gets **larger**. The unity gain frequency is a MOSFET **device parameter**—the larger the value, the better the MOSFET high frequency performance.