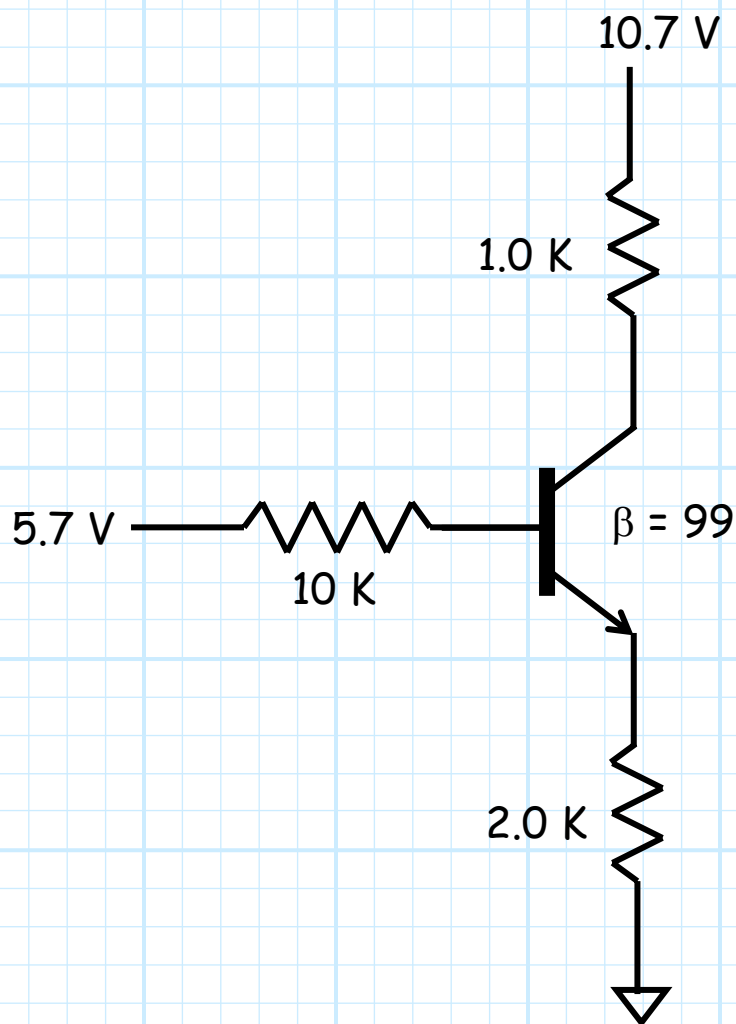


# Example: D.C. Analysis of a BJT Circuit

Consider **again** this circuit from lecture:




**Q:** What is  $I_B$ ,  $I_C$ ,  $I_E$  and also  $V_{CE}$ ,  $V_{CB}$ ,  $V_{BE}$ ??

**A:** I don't know! But, we can find out—IF we complete **each** of the five steps **required** for BJT DC analysis.

Step 1 - **ASSUME** an operating mode.

Let's **ASSUME** the BJT is in the **ACTIVE** region !

 Remember, this is just a **guess**; we have no way of knowing for sure what mode the BJT is in at this point.

Step 2 - **ENFORCE** the conditions of the assumed mode.

For **active** region, these are:

$$V_{BE} = 0.7 \text{ V} \quad \text{and} \quad I_C = \beta I_B = 99 I_B$$


Step 3 - **ANALYZE** the circuit.

This is the **BIG** step !

**Q:** *Where do we even start ?*

**A:** Recall what the hint sheet says:

**"Write KVL equations for the base-emitter "leg"**

 I think we should try that !

The **base-emitter KVL** equation is:


$$5.7 - 10 I_B - V_{BE} - 2 I_E = 0$$

This is the **circuit** equation; note that it contains 3 unknowns ( $i_B$ ,  $i_C$ , and  $V_{BE}$ ).

Now let's add the relevant **device** equations:

$$V_{BE} = 0.7 \text{ V}$$
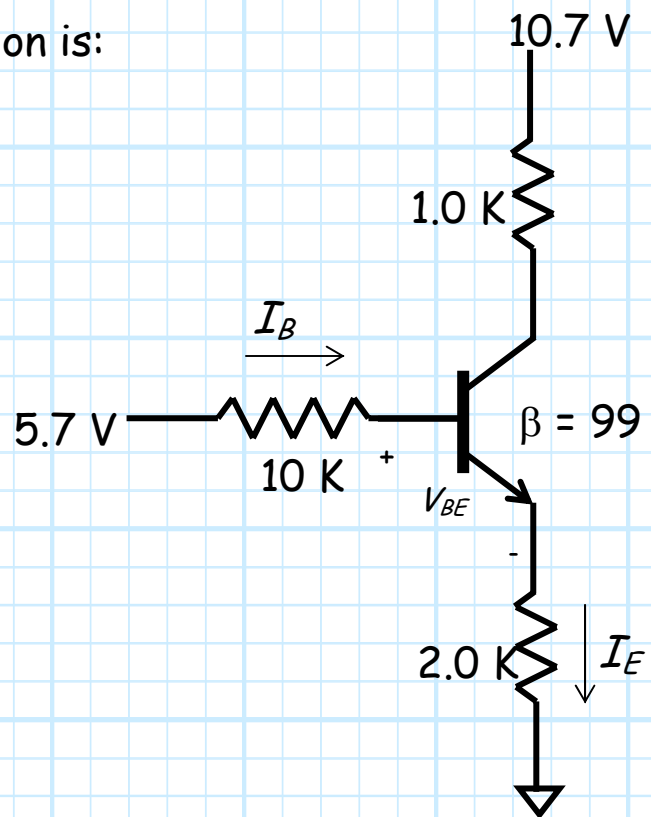
$$\begin{aligned} I_E &= (\beta + 1) I_B \\ &= 100 I_B \end{aligned}$$



Look what we now have ! **3** equations and **3** unknowns (this is a **good** thing).

Inserting the device equations into the B-E KVL:

$$5.7 - 10 I_B - 0.7 - 2(99 + 1)I_B = 0$$

Therefore:

$$5.0 - 210 I_B = 0 \quad \rightarrow \quad 1 \text{ equations and 1 unknown !}$$

Solving, we get:

$$I_B = \frac{5.0}{210} = \underline{23.8 \mu A}$$

**Q:** Whew ! That was an **awful** lot of work for just one current, and we still have **two more** currents to find.

**A:** No we don't ! Since we determined **one** current for a BJT in **active** mode, we've determined them **all** !

I.E.,

$$I_C = \beta I_B = \underline{2.356 \text{ mA}}$$

$$I_E = (\beta + 1) I_B = \underline{2.380 \text{ mA}}$$

(Note that  $I_C + I_B = I_E$ )

Now for the **voltages** !

Since we know the **currents**, we can find the voltages **using KVL**.

For example, let's **determine**  $V_{CE}$ . We can do this **either** by finding the voltage at the **collector**  $V_C$  (wrt ground) and voltage at the **emitter**  $V_E$  (wrt ground) and then subtracting ( $V_{CE} = V_C - V_E$ ).

OR, we can determine  $V_{CE}$  **directly** from the **C-E KVL equation**.


$$\begin{aligned} V_C &= 10.7 - I_C (1) \\ &= 10.7 - 2.36 \\ &= 8.34 \text{ V} \end{aligned}$$

and:

$$\begin{aligned} V_E &= 0 + I_E (2) \\ &= 0 + 4.76 \\ &= 4.76 \text{ V} \end{aligned}$$

Therefore,
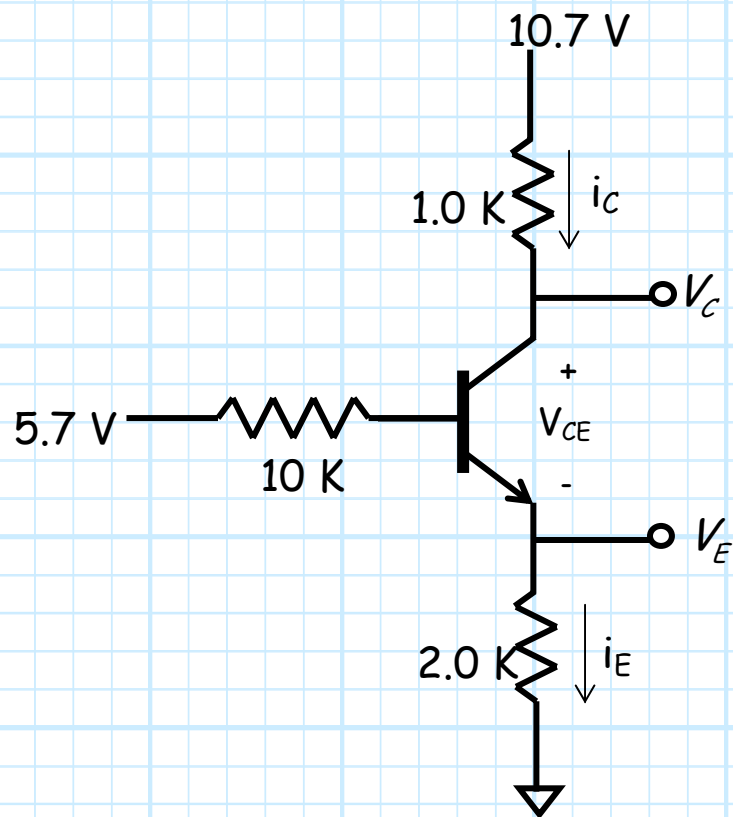
$$V_{CE} = V_C - V_E = \underline{3.58 \text{ V}}$$



Note we could have **likewise** written the C-E KVL:

$$10.7 - I_C (1) - V_{CE} - I_E (2) = 0$$

Therefore,

$$V_{CE} = 10.7 - I_C (1) - I_E (2) = 3.58 \text{ V}$$

**Q:** So, I guess we write the collector-base KVL to find  $V_{CB}$ ?

**A:** You can, but a **wiser** choice would be to simply apply KVL to the **transistor**!

$$\text{I.E., } V_{CE} = V_{CB} + V_{BE} !!$$

$$\text{Therefore } V_{CB} = V_{CE} - V_{BE} = \underline{2.88 \text{ V}}$$

**Q:** *This has been hard. I'm glad we're finished!*

**A:** Finished! We still have **2 more** steps to go!

**Step 4** - CHECK to see if your results are **consistent** with your assumption.

For **active** mode:

$$V_{CE} = 3.58 \text{ V} > 0.7 \text{ V} \quad \checkmark$$

$$I_B = 23.8 \mu\text{A} > 0.0 \quad \checkmark$$

Are assumption was **correct**, and therefore so are our **answers!**

**No need** to go on to Step 5 .