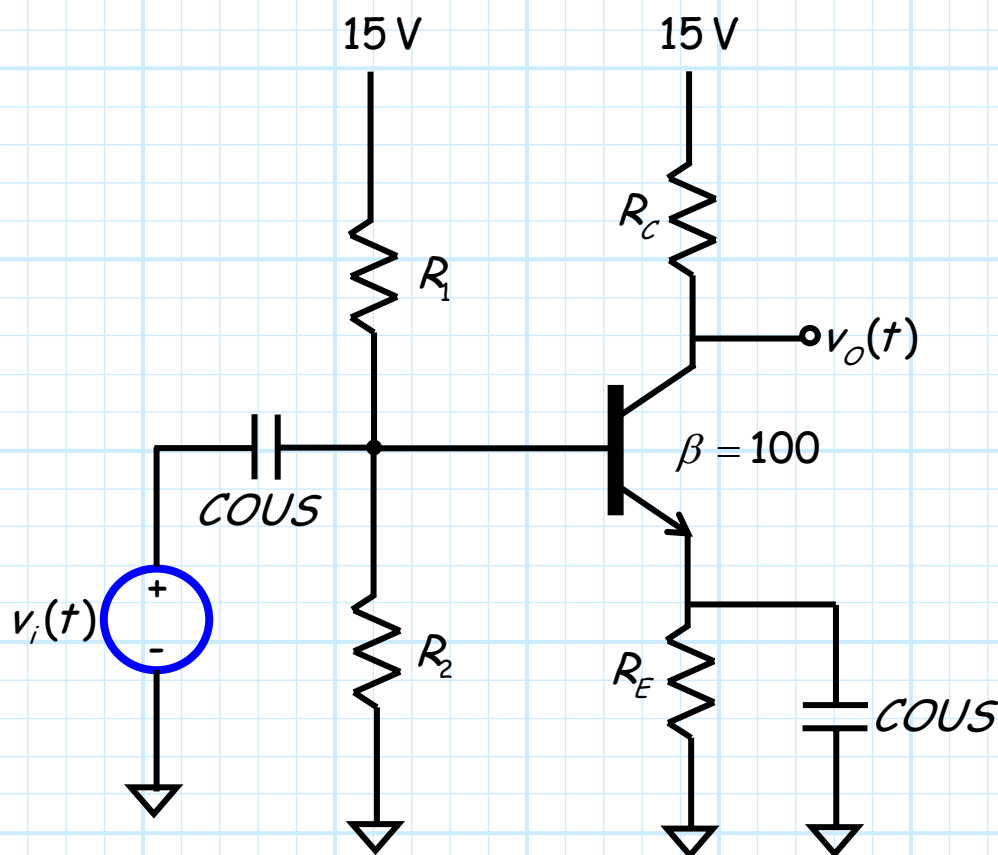


# Example: Single-Supply DC Bias

Consider this small-signal amplifier:




Say we decide that the DC collector current should be  $I_C = 5\text{mA}$ .

Let's find the **resistor** values for  $R_1$ ,  $R_2$ ,  $R_C$  and  $R_E$  that properly **bias** this amplifier!
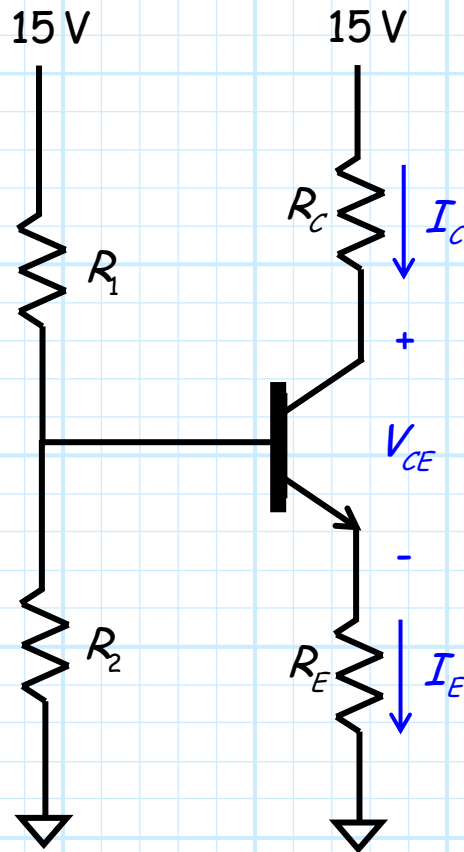
### Step 1: Write the DC Circuit Schematic

➔ After all, we are designing the DC bias!



### Step 2: Enforce the design goals for $V_E$ and $V_C$

Recall that our DC bias "rule-of-thumb" was to divide the  $V_{CC}$  voltage into "thirds" so that:

$$V_E = V_{CC}/3 = 5.0 \text{ V}$$

and

$$V_C = 2V_{CC}/3 = 10.0 \text{ V}$$

Since we want  $I_C = 5\text{mA}$ , we find that the **collector resistor** must be:

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{15 - 10}{5} = 1\text{K}$$

Likewise, the **emitter resistor** is:

$$R_E = \frac{V_E}{I_E} = \frac{\alpha}{I_C} V_E = \frac{5.0}{5.05} = 0.99\text{K} \cong 1\text{K}$$

### Step 3: Choose $I_1$ and find $R_1$ and $R_2$

Recall our "rule-of-thumb" for the current  $I_1$  is:

$$0.1 I_C < I_1 < I_C$$

Let's pick a value in the middle, i.e.:

$$I_1 = 0.5 I_C = 2.5\text{mA}$$

Since we know that that the **base voltage** is approximately:


$$V_B \approx 0.7 + V_E = 5.7\text{V}$$

and we know that the **base current** is:

$$I_B = \frac{I_C}{\beta} = \frac{5.0}{100} = 0.05\text{mA}$$

we can thus determine resistor  $R_1$ :
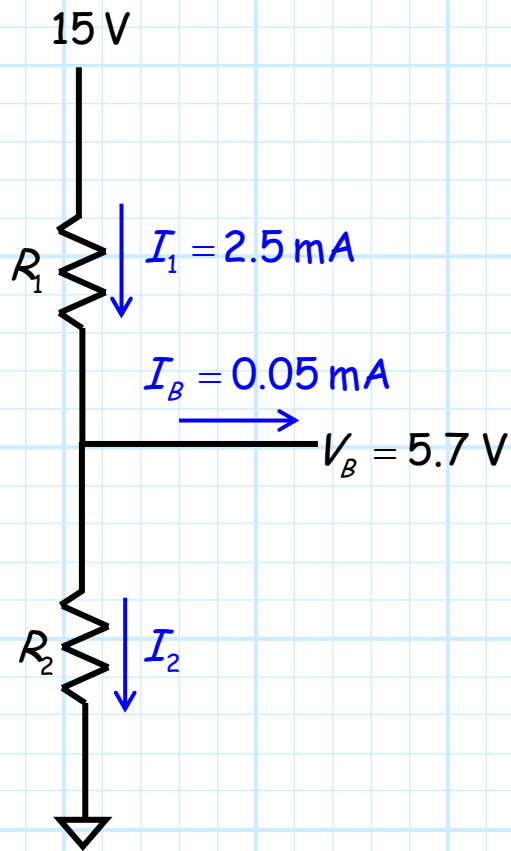
$$\begin{aligned} R_1 &= \frac{15.0 - V_B}{I_1} \\ &= \frac{15.0 - 5.7}{2.5} \\ &= 3.72 \text{ K} \end{aligned}$$



Likewise, since we know that the current  $I_2$  is:

$$\begin{aligned} I_2 &= I_1 - I_B \\ &= 2.5 - 0.05 \\ &\approx 2.5 \text{ mA} \end{aligned}$$

we can find the second resistor  $R_2$ :

$$R_2 = \frac{V_B}{I_2} = \frac{5.7}{2.5} = 2.28 \text{ K}$$

Therefore, our completed **amplifier design** is:

