

5.5 Biasing in BJT Amplifier Circuits

Reading Assignment: 436-442

Now let's examine how we DC bias BJT amplifiers!

HO: A GRAPHICAL ANALYSIS OF BJT AMPLIFIERS

If we don't bias properly, distortion can result!

EXAMPLE: AMPLIFIER DISTORTION

There is a classic bias circuit for BJT amplifiers; let's see what it is!

HO: DC BIASING USING A SINGLE POWER SUPPLY

We can also use a DC current source to bias the BJT.

HO: BJT BIASING USING A CURRENT SOURCE


Let's do an example DC bias design.

EXAMPLE: SINGLE-SUPPLY DC BIAS

Graphical Analysis of a BJT Amplifier

Consider again this simple BJT amplifier:

 We note that for this amplifier, the **output** voltage is equal to the **collector-to-emitter** voltage ($v_o(t) = v_{CE}(t)$).



$$\underline{y = m x + b}$$


If we apply **KVL** to the collector-emitter leg, we find:

$$V_{CC} - i_C R_C - v_{CE} = 0$$

We can rearrange this to get an expression for the **collector current** i_C in terms of voltage v_{CE} (i.e., $i_C = f(v_{CE})$):


$$i_C = \frac{1}{R_C} v_{CE} + \frac{V_{CC}}{R_C}$$

Note this is an equation of a **line**!

 

The load line

 This equation is referred to as the amplifier's **load line**, which we can graphically represent as:




The load line provides the **circuit** relationship (via KVL) between i_c and v_{CE} .

→ The value of i_c and v_{CE} **must** lie somewhere along the load line!

i_C vs V_{CE} for a BJT

Exactly where on the load line depends on the **device** (BJT) relationship between i_C and v_{CE} .

Recall that this relationship is:

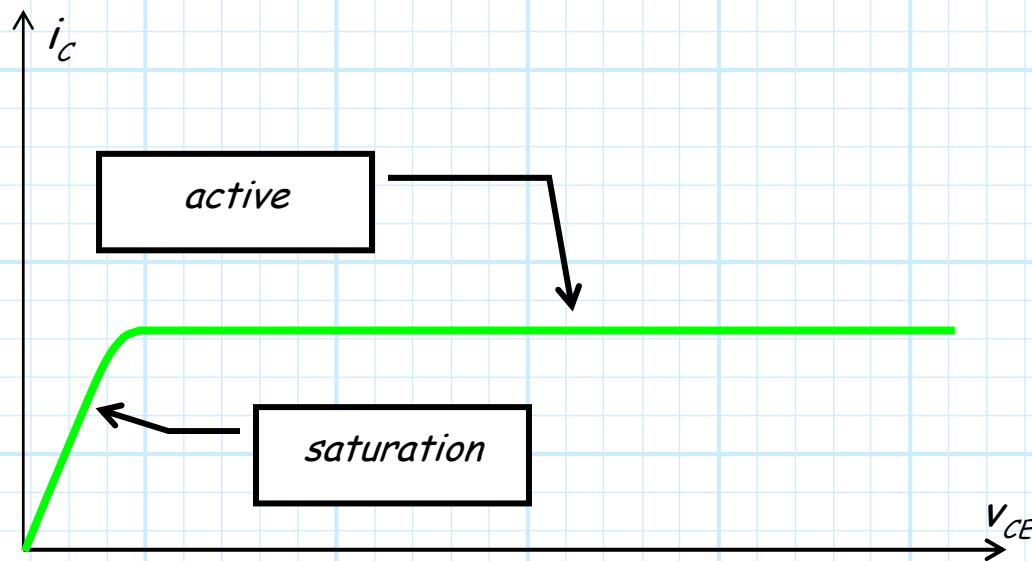


→ The value of i_C and v_{CE} **must** also lie somewhere along this device curve!

Sort of like the Grandview triangle

Q: How can the values for i_C and v_{CE} *simultaneously* be a point on the load line, and a point on the device (BJT) curve?

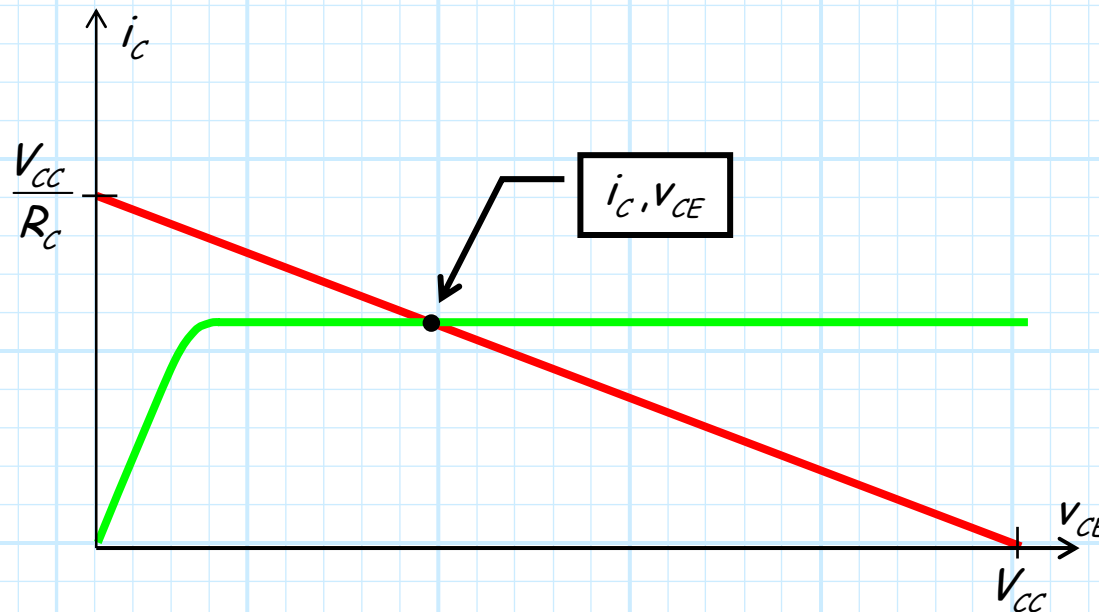A: Easy! the values for i_C and v_{CE} lie at the point where the two curves intersect!



But it all depends on the input!

Of course, the values of i_C and v_{CE} depend on the **input** to the amplifier:

$$v_I(t) = V_{BB} + v_i(t)$$

As the voltage $v_I(t)$ changes, so will the values i_C and v_{CE} .

Note, however, that the load line will **not** change—the slope $-1/R_C$ and y -intercept V_{CC}/R_C are **independent** of voltage $v_I(t)$.

What **does** change is the **BJT** relationship between i_C and v_{CE} .


For example, in active mode, the collector current i_C is **independent** of v_{CE} (we're ignoring the Early effect)!

However, the collector current i_C of a BJT is dependent on the voltage base-to-emitter v_{BE} .

Thus, as $v_I(t)$ changes, so does v_{BE} , resulting in a **new** BJT relationship (curve) between i_C and v_{CE} .

i_c changes as the input changes

Graphically, we can represent this as:

 

where V_{I1} , V_{I2} , V_{I3} are three different **input** voltages such that $V_{I1} < V_{I2} < V_{I3}$.

Thus, as the **input** voltage $v_I(t)$ changes with time, the BJT i_c versus v_{CE} **curve** will change, and its **intersection** with the amplifier load line will change— i_c and v_{CE} will likewise be a function of **time**!


The operating point

Say that the **small-signal** input voltage is **zero** ($v_o(t) = 0$).

In this case, the input voltage is simply a **constant** bias voltage ($v_I(t) = V_{BB}$).

The collector current and voltage collector-to-emitter are likewise **DC bias** values (I_C and V_{CE}).

 The intersection of the two curves in this case define the **operating point** (bias point, Q point) of the amplifier.




What happens if you make I_B too large

Q: *I see! We know that a large DC collector current results in a large transconductance g_m —a result that is typically required for large voltage gain. It appears that we should make V_{BB} (and thus I_C) as large as possible, right?*

A: **NO!** There is a **big problem** with making the bias voltage V_{BB} too large—BJT **saturation** will result !

 
We can **graphically** show this unfortunate occurrence:



There's still a problem

A BJT in **saturation** makes a **poor** amplifier!

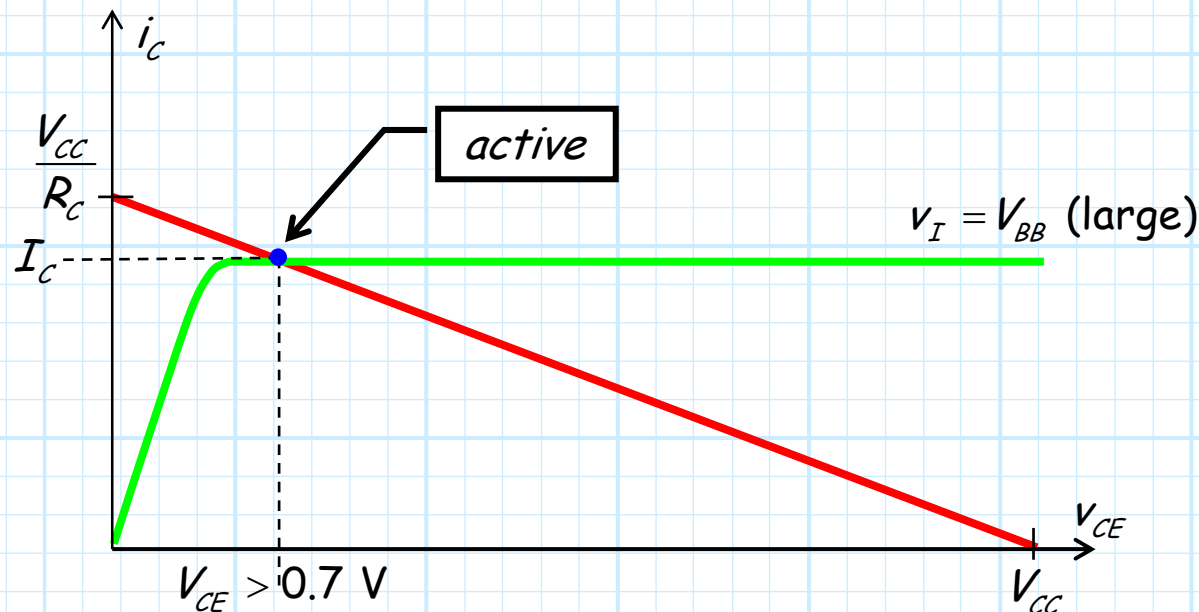Q: *Oh I see! We need to set bias voltage V_{BB} to be large, but **not** so large that we push the BJT into saturation, right?*



A: **NO!!** There is a **big problem** with this strategy as well!

Remember, it is the **total** input voltage that will determine the BJT curve. If we DC bias the amplifier so that it is **nearly** in saturation, then even a small voltage v_i can "push" the BJT into saturation mode.

A little more than bias; then a little less than bias

For **example**, recall that the small signal input $v_i(t)$ is an **AC** signal. In other words its time averaged (i.e., DC) value is **zero**, meaning that the value of $v_i(t)$ will effectively be **negative** half of the time and positive the other half.

Say then that the **magnitude** of the small signal input is limited to a value Δv_i :

$$|v_i(t)| \leq \Delta v_i$$

So that:

$$-\Delta v_i \leq v_i(t) \leq \Delta v_i \quad \text{for all time } t$$

and thus:

$$V_{BB} - \Delta v_i \leq v_I(t) \leq V_{BB} + \Delta v_i \quad \text{for all time } t$$

Let's now look at **three** scenarios for the small-signal input voltage v_i :


1) $v_i = -\Delta v_i$

2) $v_i = 0$

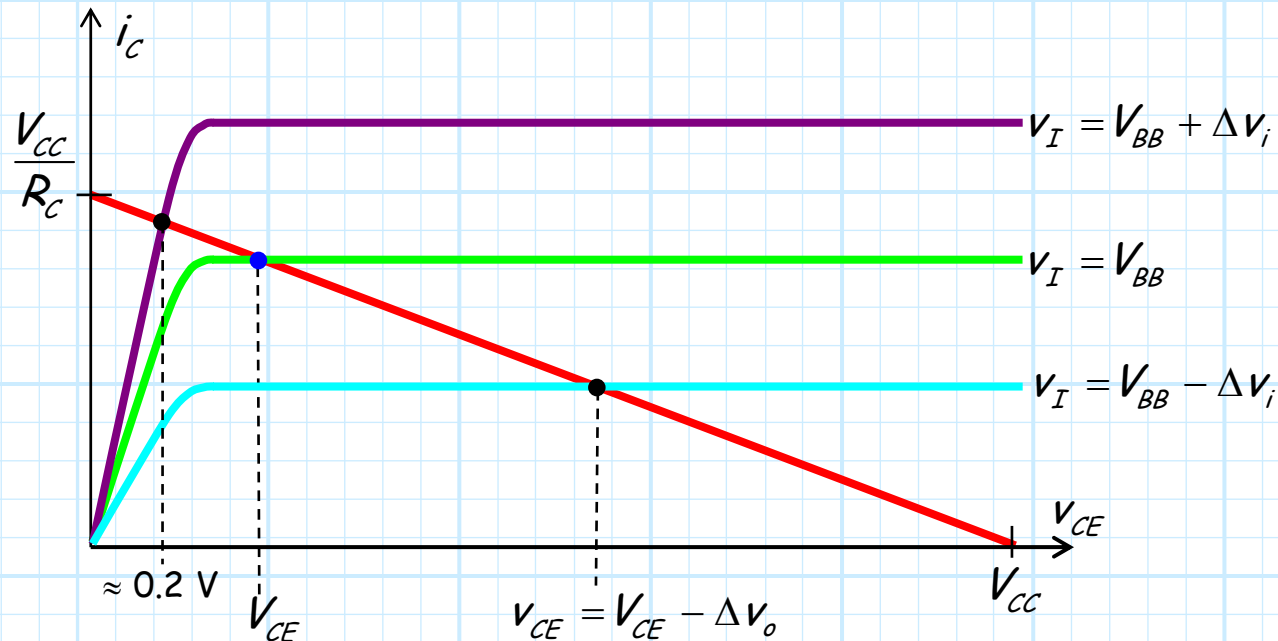3) $v_i = +\Delta v_i$

We're hitting the floor

The resulting output voltage will of course be different for each case:



Look what happened here!

If the input small-signal is "large" and **positive**, the **total** input voltage (and thus total V_{BE}) will be **too large**, and thus push the BJT into **saturation**.

Distortion!!!!!!!

The **output** voltage in this case (when $v_I = V_{BB} + \Delta v_i$) will simply be equal to:

$$v_o(t) \approx 0.2 \text{ (BJT saturated)}$$

as opposed to the **ideal** value:

$$v_o(t) = V_{CE} + \Delta v_o \text{ (BJT active)}$$

where $\Delta v_o = A_{v_o} \Delta v_i$. Note for this amplifier, the small-signal voltage gain A_{v_o} is **negative**, so that the value Δv_o is **also** negative:

$$\Delta v_o = A_{v_o} \Delta v_i < 0$$


Since the BJT is in saturation during some portion of $v_i(t)$, the amplifier output signal will **not** look like the input signal—**distortion** will result!

I never said this was easy

Q: Now I get it! We need to make V_{BB} **small**, so that the BJT does **not** enter saturation, and the output signal is **not** distorted!

A: NO!! There is a **problem** with this too!

 We can again **graphically** examine what happens if we make the bias voltage V_{BB} too **small**.



Look what happened here!

Now we're hitting the ceiling

If the **input** small-signal is "large" and **negative**, the **total** input voltage (and thus total v_{BE}) will be too **small**, and thus push the BJT into **cutoff**.

Note the collector current will be **zero** ($i_c = 0$) when the BJT is in cutoff!

The **output** voltage in this case (i.e., when $v_I = V_{CE} - \Delta v_i$) will simply be equal to:

$$v_o(t) = V_{CC} \quad (\text{BJT cutoff})$$

as opposed to the **ideal** value:

$$v_o(t) = V_{CE} - \Delta v_o \quad (\text{BJT active})$$

where $\Delta v_o = A_v \Delta v_i$. Note for this amplifier, the small-signal voltage gain is **negative**, so that the value $-\Delta v_o$ is **positive**.

Since the BJT is in **cutoff** during some portion of $v_i(t)$, the amplifier output signal will **not** look like the input signal—**distortion** will result!

What do we do?

Q: *Yikes! Is there **nothing** we can do to avoid signal distortion?*

A: To get allow for the **largest** possible (distortion-free) output signal $v_o(t)$, we typically need to bias our BJT such that we are about "**half way**" between biasing the BJT in **saturation** and biasing the BJT in **cutoff**.

Note if the BJT is in **saturation**:

$$i_c \approx \frac{V_{CC}}{R_C}$$

(BJT saturation)

$$V_{CE} \approx 0.2 \text{ V}$$

Bias in the middle

Whereas, if it is in **cutoff**:

$$i_C = 0$$

(BJT cutoff)

$$V_{CE} = V_{CC}$$

It is evident that for this particular amplifier, biasing **"half-way"** between saturation and cutoff means biasing such that:


$$V_{CE} \approx \frac{V_{CC}}{2}$$

or equivalently:

$$I_C \approx \frac{V_{CC}}{2R_C}$$



The output is maximized

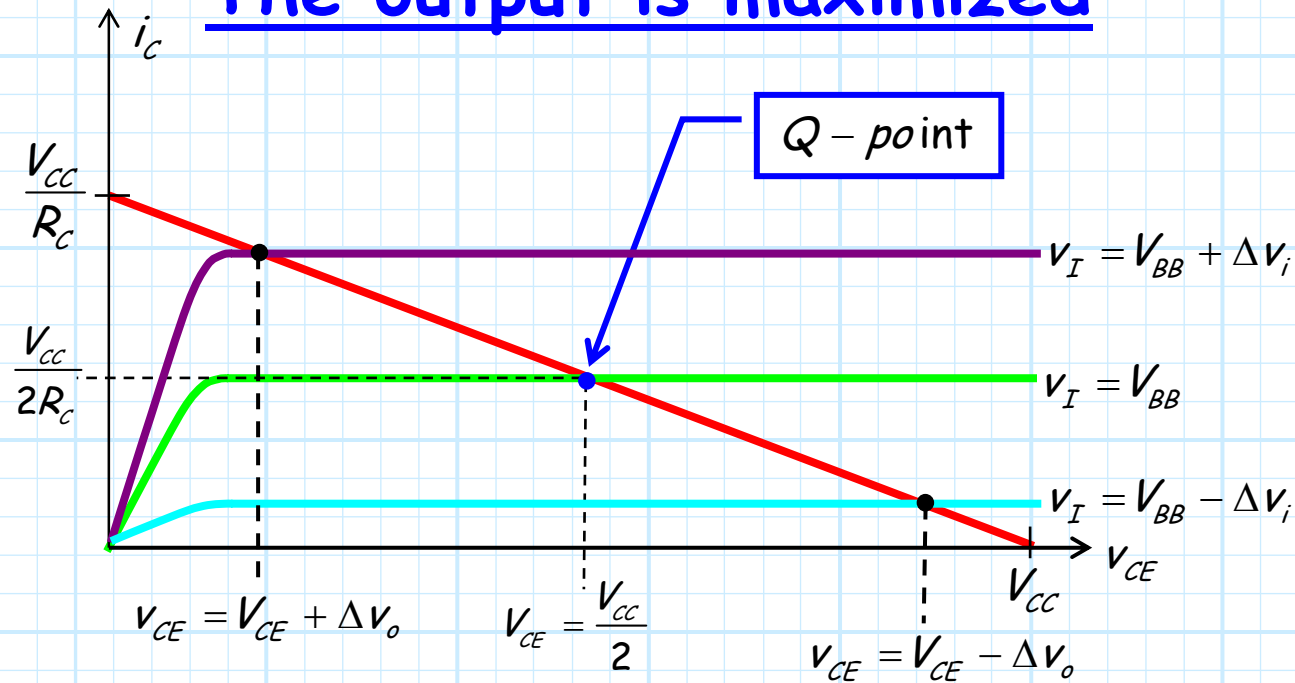


The bias solution above is optimal for **this** particular amplifier design. **Other** amplifier designs will result in **other** optimal bias designs—it is up to **you** determine what they are.

Remember, the **total** voltage $v_{CE}(t)$ must be larger than 0.7 V for all time; otherwise **saturation** (and thus signal distortion) will result).

Likewise, the **total** collector current $i_c(t)$ must be greater than zero for all time; other wise **cutoff** (and thus signal distortion) will result.

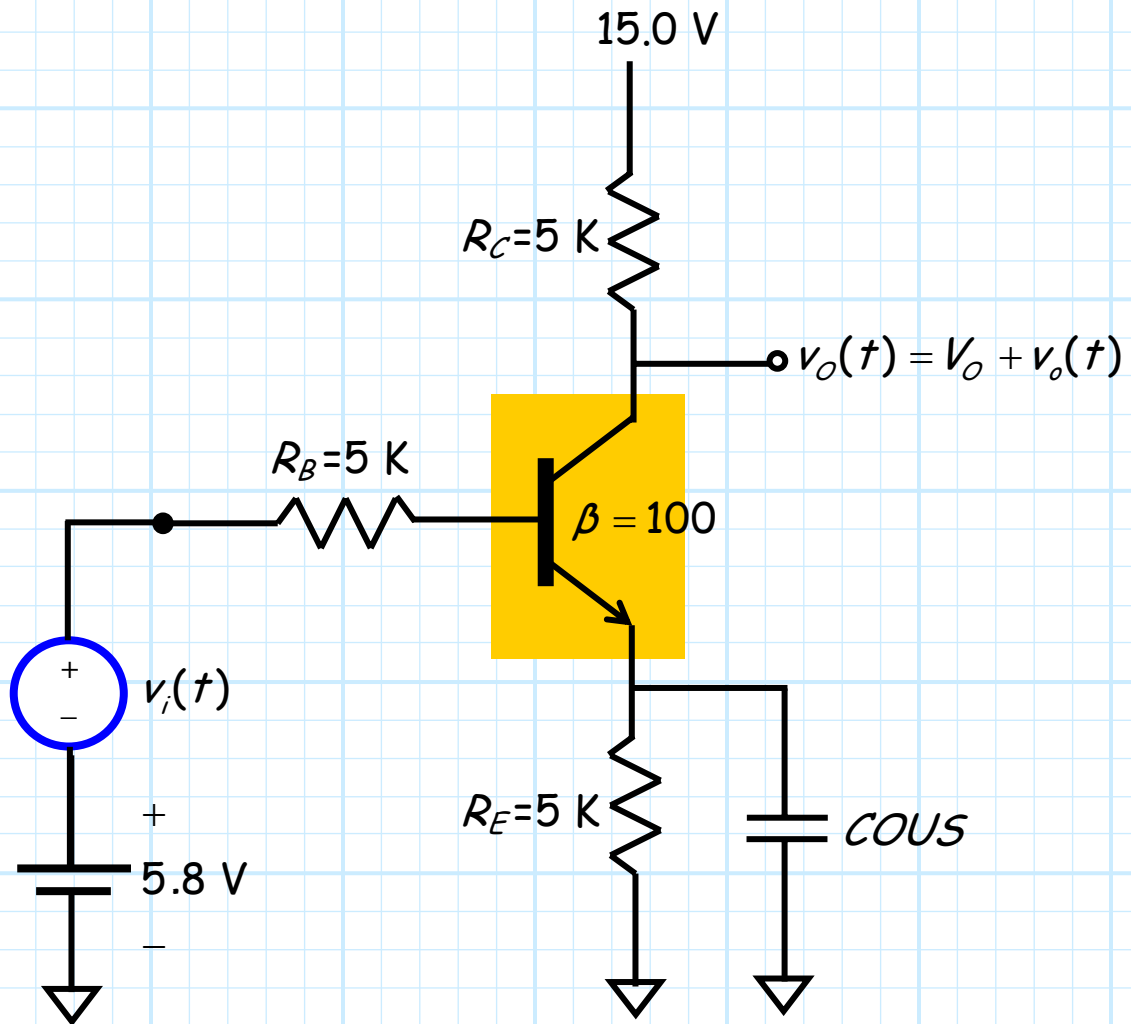Example: Amplifier Distortion

Recall this circuit from a previous handout:



We found that the small-signal voltage gain is:

$$A_{vo} = \frac{v_o(t)}{v_i(t)} = -66.7$$

Say the **input** voltage to this amplifier is:

$$v_i(t) = V_s \cos \omega t$$

Q: What is the **largest** value that V_s can take without producing a **distorted** output?

A: Well, we know that the **small-signal** output is:

$$\begin{aligned} v_o(t) &= A_{vo} v_i(t) \\ &= -66.7 V_s \cos \omega t \end{aligned}$$

BUT, this is **not** the output voltage!


The **total** output voltage is the **sum** of the **small-signal** output voltage and the **DC** output voltage!

Note for this example, the **DC** output voltage is the **DC collector** voltage, and we recall we determined in an earlier handout that its value is:

$$V_o = V_c = 10 \text{ V}$$



Thus, the **total output voltage** is :
 
$$\begin{aligned} v_o(t) &= V_o + v_o(t) \\ &= 10.0 - 66.7 V_s \cos \omega t \end{aligned}$$



*It is very important that you realize there is a **limit** on both how high and how low the **total** output voltage $v_o(t)$ can go!*

  *That's right! If the **total** output voltage $v_o(t)$ tries to exceed these limits—even for a moment—the BJT will leave the **active** mode.*



*And leaving the active mode results in **signal distortion!***

Let's break the problem down into **two** separate problems:

- 1) If **total** output voltage $v_o(t)$ becomes too **small**, the BJT will enter saturation.
- 2) If **total** output voltage $v_o(t)$ becomes too **large**, the BJT will enter cutoff.

We'll first consider **problem 1**.

For the BJT to remain in active mode, $v_{CE}(t)$ must remain **greater than 0.7 V** for all time t (or equivalently $v_{CB}(t) > 0.0$).

From an earlier handout, we know that $V_E = 5.05 \text{ V}$. The large **capacitor** on the emitter keeps this voltage **constant** with respect to time.

Therefore, the voltage $v_{CE}(t)$ will remain greater than 0.7 V **only** if the collector voltage $v_C(t)$ remains **greater** than $5.05 + 0.7 = 5.75 \text{ V}$. Note 5.75 is the **base voltage** V_B .

Of course, the collector voltage is also the output voltage ($v_o(t) = v_C(t)$), so that we can conclude that the **output** voltage must remain **larger** than $V_B = 5.75 \text{ V}$ to remain in **active** mode:

$$5.75 < v_o(t) = 10 - 66.7V_s \cos\omega t$$

In other words, the **lower** limit on the **total** output voltage is:

$$L_- = 5.75 \text{ V}$$

Note that we can solve this equation to determine the **maximum** value of small-signal **input** magnitude V_s :

$$\begin{aligned} 5.75 &< 10 - 66.7V_s \cos\omega t \\ 66.7V_s \cos\omega t &< 4.25 \\ V_s \cos\omega t &< 0.064 \end{aligned}$$

Since $\cos\omega t$ can be as large as 1.0, we find that the magnitude of the **input** voltage can be **no larger** than 64 mV, i.e.,

$$V_s < 0.064 \text{ V}$$

If the **input** magnitude exceeds this value, the BJT will (momentarily) leave the active region and enter the **saturation** mode!

Now let's consider **problem 2**

For the BJT to remain in **active** mode, the **collector** current must be **greater** than zero (i.e., $i_c > 0$). Otherwise, the BJT will enter **cutoff** mode.

Applying **Ohm's Law** to the collector resistor, we find the **collector current** is:

$$i_c = \frac{V_{CC} - v_o}{R_C} = \frac{15 - v_o}{5}$$

it is evident that collector current is **positive** only if $v_o < 15$ V.

In other words, the **upper** limit on the **total** output voltage is:

$$L_+ = 15.0 \text{ V}$$

Since:

$$v_o(t) = 10 - 66.7V_s \cos\omega t$$

we can conclude that in order for the BJT to remain in **active** mode:

$$10 - 66.7V_s \cos\omega t > 15.0$$

Therefore, we find:

$$V_s \cos\omega t > \frac{-5.0}{66.7} = -0.0075$$

Since $\cos\omega t \geq -1$, the above equation means that the **input** signal magnitude V_s can be **no larger** than:

$$V_s < 75 \text{ mV}$$

If the input magnitude **exceeds** 75 mV, the BJT will (momentarily) leave the active region and enter the **cutoff** region!


In summary:

- 1) If $V_s > 64 \text{ mV}$, the BJT will at times enter **saturation**, and **distortion** will occur!
- 2) If $V_s > 75 \text{ mV}$, the BJT will at times enter **cutoff**, and **even more** distortion will occur!

To demonstrate this, let's consider **three** examples:

 
1. $V_s < 64 \text{ mV}$

The output signal in this case remains between $V_{CC}=15.0 \text{ V}$ and $V_B=5.75 \text{ V}$ for **all** time t . Therefore, the output signal is **not distorted**.



 
2. $64 \text{ mV} < V_s < 75 \text{ mV}$

The output signal in this case remains less than $V_{CC}=15.0$ V for all time t . However, the small-signal output is now large enough so that the total output voltage at times tries to drop **below** $V_B = 5.75$ V (i.e., V_{CE} drops below 0.7 V). For these times, the BJT will enter **saturation**, and the output signal will be **distorted**.



 
3. $V_s > 75$ mV

In this case, the small-signal input signal is sufficiently **large** so that the total output will attempt to exceed **both** limits (i.e., $V_{CC} = 15.0$ V and $V_B = 5.75$ V). Therefore, there are periods of time when the BJT will be in **cutoff**, and periods when the BJT will be in **saturation**.




For a given amplifier voltage gain, you must determine the **largest possible** input $v_i(t)$ that will produce a **distortion-free** output signal.

 To do this, you must determine the **limits** of the **total** output voltage. There will be **two** limits—one for **saturation** (L_-) and one for **cutoff** (L_+).



D.C Biasing using a Single Power Supply

 The general form of a **single-supply** BJT amplifier biasing circuit is:



Just three goals

Generally, we have **three goals** in designing a biasing network:

1) Maximize Gain

Typically, we seek to set the operating point of the BJT amplifier such that the resulting small signal voltage gain is **maximized**.

However, we sometimes seek to set the bias point such that the **output resistance** is minimized, or the **input resistance** is maximized.

2) Maximize Voltage Swing

We seek to set the operating point of the BJT amplifier such that the maximum small signal output can be as **large** as possible.

If we make V_{CE} too small, then the BJT will easily **saturate**, whereas if V_{CE} is too large, the BJT will easily **cutoff**.

This suddenly seems like a lot of goals

3) Minimize Sensitivity to changes in β

Manufacturing and temperature variances will result in significant changes in the value β .

We seek to design the bias network such that the amplifier parameters will be **insensitive** to these changes.



Q: *You're kidding me right?*

*We're supposed to achieve **all** these goals with just **four** resistors?*

A: Actually, the three design goals listed above are often in **conflict**.

We typically have to settle for a **compromise** DC bias design.

How we maximize gain

Let's take a closer look at each of the **three** design goals:

1) Maximize Gain

Typically, the small-signal **voltage gain** of a BJT amplifier will be proportional to transconductance g_m :

$$A_{vo} \propto g_m$$

Thus, to maximize the amplifier voltage gain, we must **maximize** the BJT transconductance.

Q: *What does this have to do with D.C. biasing?*

A: Recall that the transconductance depends on the DC **collector current** I_C :

$$g_m = \frac{I_C}{V_T}$$

Maximize that darn bias current!

Therefore the amplifier voltage gain is typically **proportional** to the DC collector current:

$$A_{vo} \propto \frac{I_C}{V_T}$$

We of course can't decrease the thermal voltage V_T , but we can design the bias circuit such that I_C is **maximized**.

To maximize A_{vo} , maximize I_C

We don't want distortion!

2) Maximize Voltage Swing

Recall that if the DC collector voltage V_C is biased too close to V_{CC} , then even a small small-signal collector voltage $v_c(t)$ can result in a **total** collector voltage that is too **large**, i.e.:

$$v_c(t) = V_C + v_c(t) \geq V_{CC}$$

In other words, the BJT enters **cutoff**, and the result is a **distorted** signal!

To avoid this (to allow $v_c(t)$ to be as large as possible without BJT entering cutoff), we need to bias our BJT such that the DC collector voltage V_C is as **small** as possible.

How to avoid cutoff

Note that the collector voltage is:

$$V_C = V_{CC} - R_C I_C$$

Therefore V_C is minimized by designing the bias circuit such that the DC collector current I_C is as **large** as possible.



Q: *Hey hey! It looks like amplifier bias design is going to be **easy**. We can **both** maximize transconductance g_m **and** minimize the DC collector voltage V_C by maximizing the DC collector current I_C !*

A: Just a second! We must **also** consider the signal distortion that occurs when the BJT enters **saturation**.

But also avoid saturation

Saturation of course is avoided if the total voltage collector to emitter remains greater than 0.7 V, i.e.:

$$v_{CE}(t) = V_{CE} + v_{ce}(t) > 0.7 \text{ V}$$

Thus, to avoid BJT saturation—and the resulting signal distortion—we need to bias our BJT such that the DC voltage V_{CE} is as **large** as possible.

To minimize signal distortion, maximize V_{CE}

BJTs are pretty sensitive

3) Minimize Sensitivity to changes in β

We find that BJTs are very **sensitive** to temperature—specifically, the value of β is a function of temperature.

Likewise, the value of β is not particularly constant with regard to the manufacturing process.

We find that 100 otherwise “identical” BJTs will result have 100 **different** values of β !

Both of these facts lead to the requirement that our bias design be **insensitive** to the value of β .


Specifically, we want to design the bias network such that the DC bias currents (e.g., I_c) do **not** change values when β does.

Mathematically, we can express this requirement as minimizing the value:

$$\frac{d I_c}{d \beta}$$

How do we determine this derivative?

 
Let's determine this derivative value for our **standard** bias network:



Q: *Yuck! This looks like a disturbingly difficult circuit to analyze.*


A: One way to **simplify** the analysis it to use a **Thevenin's** equivalent circuit.

 Specifically, replace this portion of the bias circuit with its **Thevenin's** equivalent:




Good ol' Thevenin's!

 We find that this **equivalent** circuit is:



 The **bias network** can therefore be equivalently represented as:



You're always having fun if you're doing calculus

If we **ASSUME** that the BJT is in active mode, then we **ENFORCE** the proper equalities and **ANALYZE** this circuit to find collector current I_C :

$$I_C = \frac{\beta(V_{BB} - 0.7)}{(\beta + 1)R_E + R_B}$$

We find therefore that:

$$\frac{dI_C}{d\beta} = \frac{-(V_{BB} - 0.7)}{\left(\beta \frac{R_E}{R_B} + 1\right)^2}$$

Note then that:

$$\lim_{R_E/R_B \rightarrow \infty} \frac{dI_C}{d\beta} = 0$$

Maximize that darn resistor!

In other words, if we wish to make the DC collector current **insensitive** to changes in β , we need to make:

$$R_E \gg R_B$$

We of course could accomplish this by making the **base resistance** $R_B = R_1 \parallel R_2$ small, but we will find out later that there are problems with doing this.

Instead, we can minimize the circuit sensitivity to changes in β by maximizing the **emitter resistor** R_E .

To minimize $dI_C/d\beta$, maximize R_E

This seems so simple...

So, let's **recap** what we have learned about designing our bias network:

1. Make I_C as large as possible.
2. Make V_{CE} as large as possible.
3. Make R_E as large as possible.




Q: *Seems easy enough! Let's get started biasing BJT amplifiers!*

A: Not so fast! We still have a **serious problem**.

...NOT!

 To see what this problem is, write the KVL equation for the **Collector-Emitter Leg** of the Bias Network:



$$V_{CC} - I_C R_C - V_{CE} - I_E R_E = 0$$

or

$$I_C R_C + V_{CE} + I_E R_E = V_{CC}$$

Maximize A_{vo} by **maximizing** this term.

Minimize distortion by **maximizing** this term.

Minimize β sensitivity by **maximizing** this term.

But the **total** of the three terms must equal this!

A logical compromise



Q: *Yikes! It's like owing 3 really big guys \$15 each, but having only \$15 in your pocket.*

What do we do?

A: Split the total voltage 3 ways (give each guy \$5).

$$I_C R_C = \frac{V_{CC}}{3}$$

$$V_{CE} = \frac{V_{CC}}{3}$$


$$+ \quad I_E R_E = \frac{V_{CC}}{3}$$

$$I_C R_C + V_{CE} + I_E R_E = V_{CC}$$

The result of this compromise

In other words, for an *n*p*n* BJT, set:

 
$$V_C = \frac{2}{3} V_{CC} \quad \text{and} \quad V_E = \frac{1}{3} V_{CC}$$



Don't forget *pn*p

Likewise, for a *pn*p BJT, set:
 
$$V_E = \frac{2}{3} V_{EE} \quad \text{and} \quad V_C = \frac{1}{3} V_{EE}$$



What should I_C be?

Q: We have determined that the **product** $I_C R_C$ should be equal to $V_{CC}/3$.

We can of course accomplish this with a larger resistor R_C and a smaller current I_C , or a larger current I_C and a smaller resistor R_C . What **should** the value of I_C be?

A: Generally speaking, the value of the **DC collector current** I_C affects:

- 1) Voltage Gain ($g_m \rightarrow \infty$ as $I_C \rightarrow \infty$).
- 2) Input Resistance ($r_\pi \rightarrow 0$ as $I_C \rightarrow \infty$).
- 3) BJT Output Resistance ($r_o \rightarrow 0$ as $I_C \rightarrow \infty$).
- 4) Power Consumption ($P \rightarrow \infty$ as $I_C \rightarrow \infty$).
- 5) Amplifier Bandwidth ($BW \rightarrow \infty$ as $I_C \rightarrow \infty$).

The "best" value of collector current I_C is a **trade** between these parameters.

There are two resistors left

Q: *OK, we now have enough information to set I_C , V_C , and V_E , and thus resistors R_C and R_E .*


*But we still have **two** bias resistors left— R_1 and R_2 . How do we determine their values?*

A: Well, we have found that **reducing** $R_B = R_1 \parallel R_2$ decreases the circuit sensitivity to $\beta \Rightarrow$ This is **good!**

But, we **will** find that **reducing** $R_B = R_1 \parallel R_2$ will often decrease the amplifier input resistance $R_i \Rightarrow$ This is **bad!**

Also, we find that **reducing** $R_B = R_1 \parallel R_2$ will increase the power dissipation \Rightarrow This is also **bad!**

A "rule of thumb"

 

$$I_1 \approx \frac{V_{CC}}{R_1 + R_2} \quad \text{if } I_1 \gg I_B$$

$$\therefore P = V_{CC} I_1 \approx \frac{V_{CC}^2}{R_1 + R_2}$$

A general "rule of thumb" is to select the values of R_1 and R_2 so that I_C is:


$$0.1 I_C < I_1 < I_C$$

Remember, the resistors R_1 and R_2 also determine the **base voltage** V_B , which should approximately be:

$$\begin{aligned} V_B &= V_{BE} + V_E \\ &= 0.7 + \frac{V_{CC}}{3} \end{aligned}$$

Example: Single-Supply DC Bias

Consider this small-signal amplifier:

 


Say we decide that the DC collector current should be $I_C = 5\text{mA}$.

Let's find the **resistor** values for R_1 , R_2 , R_C and R_E that properly **bias** this amplifier!

Step 1: Write the DC Circuit Schematic

 ➔ After all, we are designing the DC bias!



Step 2: Enforce the design goals for V_E and V_C

Recall that our DC bias "rule-of-thumb" was to divide the V_{CC} voltage into "thirds" so that:

$$V_E = V_{CC}/3 = 5.0 \text{ V}$$

and

$$V_C = 2V_{CC}/3 = 10.0 \text{ V}$$

Since we want $I_C = 5\text{mA}$, we find that the **collector resistor** must be:

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{15 - 10}{5} = 1\text{K}$$

Likewise, the **emitter resistor** is:

$$R_E = \frac{V_E}{I_E} = \frac{\alpha}{I_C} V_E = \frac{5.0}{5.05} = 0.99\text{K} \cong 1\text{K}$$

Step 3: Choose I_1 and find R_1 and R_2

Recall our "rule-of-thumb" for the current I_1 is:

$$0.1 I_C < I_1 < I_C$$

Let's pick a value in the middle, i.e.:

$$I_1 = 0.5 I_C = 2.5\text{mA}$$

Since we know that that the **base voltage** is approximately:


$$V_B \approx 0.7 + V_E = 5.7\text{V}$$

and we know that the **base current** is:

$$I_B = \frac{I_C}{\beta} = \frac{5.0}{100} = 0.05\text{mA}$$

we can thus determine resistor R_1 :
 
$$\begin{aligned} R_1 &= \frac{15.0 - V_B}{I_1} \\ &= \frac{15.0 - 5.7}{2.5} \\ &= 3.72 \text{ K} \end{aligned}$$




Likewise, since we know that the current I_2 is:

$$\begin{aligned} I_2 &= I_1 - I_B \\ &= 2.5 - 0.05 \\ &\approx 2.5 \text{ mA} \end{aligned}$$

we can find the second resistor R_2 :


$$R_2 = \frac{V_B}{I_2} = \frac{5.7}{2.5} = 2.28 \text{ K}$$

 Therefore, our completed **amplifier design** is:



BJT Biasing using a Current Source

 Another way to bias a BJT small signal amplifier is to use one voltage source and one **current source**. This biasing scheme has a number of **important advantages**:



1. The DC emitter current is **independent** of β or BJT temperature!

Therefore, the DC collector current $I_C = \alpha I_E \approx I_E$ is nearly independent of these parameters as well.


2. This means that the **emitter voltage** can be set at an arbitrarily low value!

Therefore, the output voltage swing can be much **larger** than an equivalent single-supply amplifier!

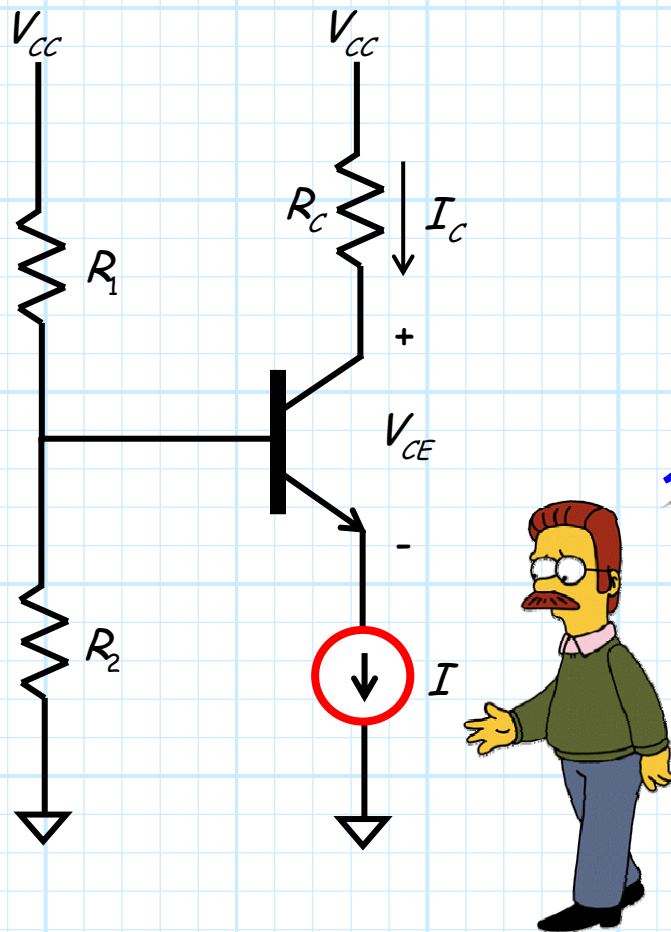3. We can make resistors R_1 and R_2 **large** without making design sensitive to temperature and β .

The current source: not as easy as it appears

Note that **ideally**, we would set the emitter voltage to **zero** ($V_E = 0$), and thus the collector voltage to $V_C = V_{CC}/2$ to **maximize** the output swing (i.e., maximize the largest possible **undistorted** output signal).



Q: *But, isn't it diddly darn difficult to actually build an ideal current source!?*

A: True! For reasons we shall study later, most current sources require a **minimum voltage** across them in order to operate properly.

Put collector voltage half way between floor and ceiling

Thus, our **bias rule** should be:

*Make the DC emitter voltage V_E as **small** as possible (and still have the current source work!).*

Then set the **current source** to a value equal to the desired DC collector current (i.e., $I_C \approx I_E$):

$$I = I_E \approx I_C$$

To maximize the output voltage swing, we still want to place the DC collector voltage V_C **half way** between V_{CC} and V_E .

$$V_C = \frac{V_{CC} + V_E}{2}$$

The **collector resistor** therefore should be:

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{V_{CC} - V_C}{I} = \frac{V_{CC} - V_E}{2I}$$

R_1 and R_2 : same as before

The remaining resistors R_1 and R_2 are determined in the **same** manner as with the single-supply bias design, i.e.:

$$R_1 = \frac{V_{CC} - V_B}{I_1}$$

and

$$R_2 = \frac{V_B}{I_2} \approx \frac{V_B}{I_1}$$

where the base voltage is approximately:

$$V_B = 0.7 + V_E$$

and the current I_1 is any value in the range:


$$0.1I_C < I_1 < I_C$$

Just the kind of subtle topic I might put on an exam

For **example**, say we wish to design a biasing network where:

$$I_C = 2 \text{ mA} \quad V_E \geq 2.0 \text{ V} \quad V_{CC} = 15.0 \text{ V} \quad I_1 = 0.5 I_C$$

The result would be:

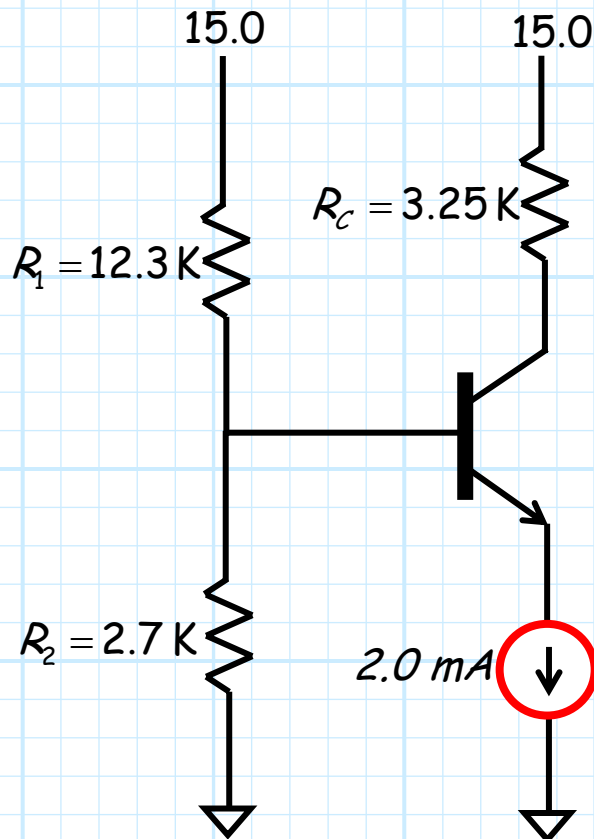


*It is obvious to me that this bias design **satisfies** the parameters described above.*

*But, don't take my word for it—verify for **yourself** that these resistor values are correct.*



Example: Single-Supply DC Bias

Consider this small-signal amplifier:

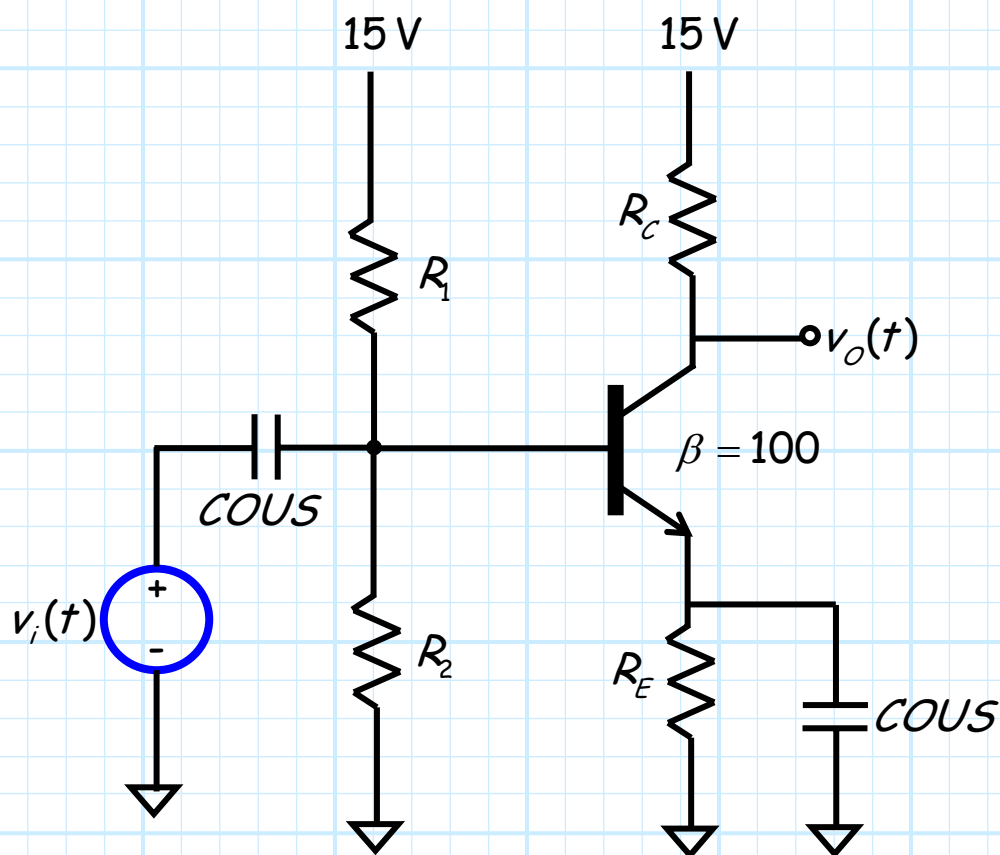


Say we decide that the DC collector current should be $I_C = 5\text{mA}$.

Let's find the **resistor** values for R_1 , R_2 , R_C and R_E that properly **bias** this amplifier!

Step 1: Write the DC Circuit Schematic

 ➔ After all, we are designing the DC bias!



Step 2: Enforce the design goals for V_E and V_C

Recall that our DC bias "rule-of-thumb" was to divide the V_{CC} voltage into "thirds" so that:

$$V_E = V_{CC}/3 = 5.0 \text{ V}$$

and

$$V_C = 2V_{CC}/3 = 10.0 \text{ V}$$

Since we want $I_C = 5\text{mA}$, we find that the **collector resistor** must be:

$$R_C = \frac{V_{CC} - V_C}{I_C} = \frac{15 - 10}{5} = 1\text{K}$$

Likewise, the **emitter resistor** is:

$$R_E = \frac{V_E}{I_E} = \frac{\alpha}{I_C} V_E = \frac{5.0}{5.05} = 0.99\text{K} \cong 1\text{K}$$

Step 3: Choose I_1 and find R_1 and R_2

Recall our "rule-of-thumb" for the current I_1 is:

$$0.1 I_C < I_1 < I_C$$

Let's pick a value in the middle, i.e.:

$$I_1 = 0.5 I_C = 2.5\text{mA}$$

Since we know that that the **base voltage** is approximately:


$$V_B \approx 0.7 + V_E = 5.7\text{V}$$

and we know that the **base current** is:

$$I_B = \frac{I_C}{\beta} = \frac{5.0}{100} = 0.05\text{mA}$$

we can thus determine resistor R_1 :
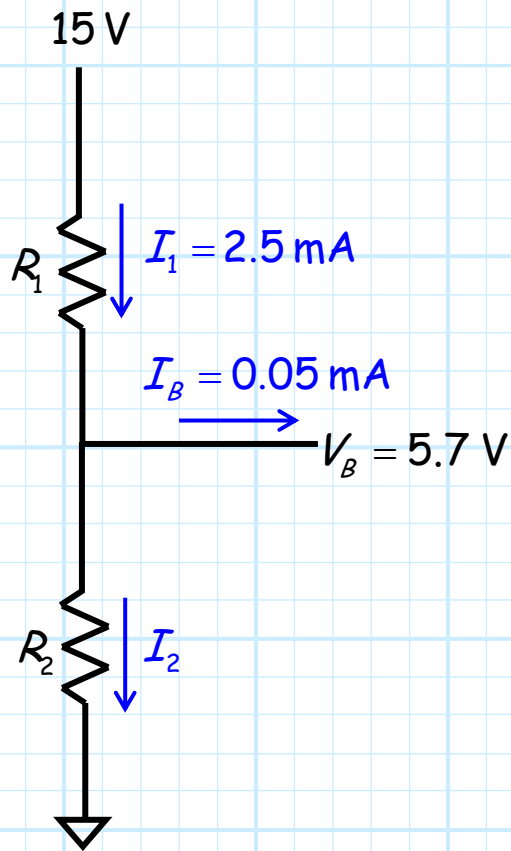
$$\begin{aligned} R_1 &= \frac{15.0 - V_B}{I_1} \\ &= \frac{15.0 - 5.7}{2.5} \\ &= 3.72 \text{ K} \end{aligned}$$



Likewise, since we know that the current I_2 is:

$$\begin{aligned} I_2 &= I_1 - I_B \\ &= 2.5 - 0.05 \\ &\approx 2.5 \text{ mA} \end{aligned}$$

we can find the second resistor R_2 :

$$R_2 = \frac{V_B}{I_2} = \frac{5.7}{2.5} = 2.28 \text{ K}$$

Therefore, our completed **amplifier design** is:

