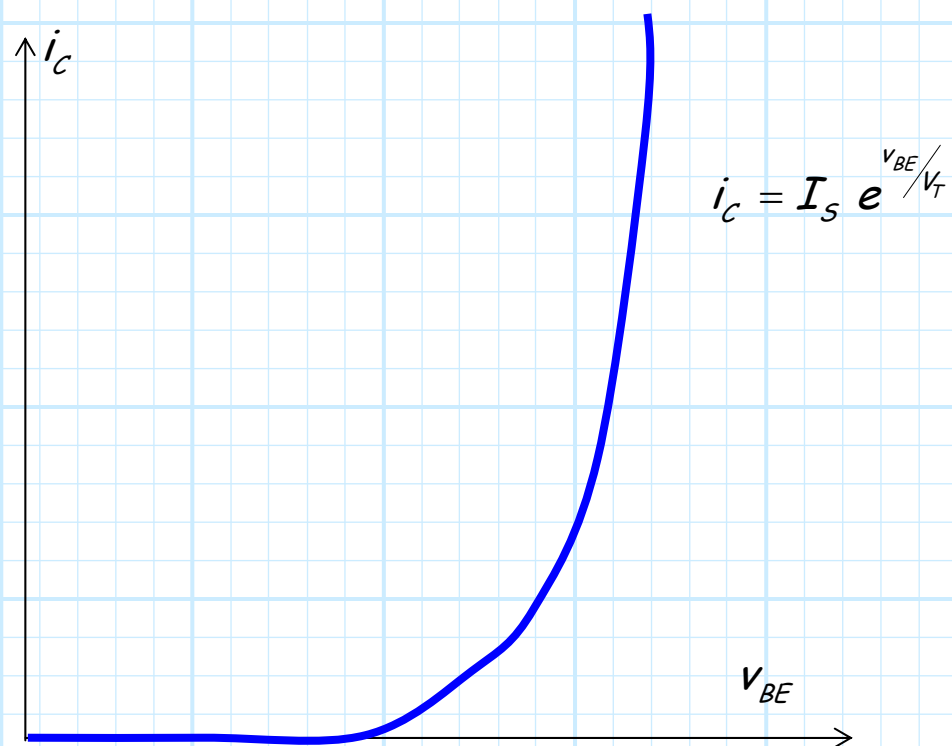


# A Small-Signal Analysis of a BJT

The collector current  $i_c$  of a BJT is related to its base-emitter voltage  $v_{BE}$  as:



## One messy result

Say the current and voltage have both **D.C.** ( $I_C$ ,  $V_{BE}$ ) and **small-signal** ( $i_c$ ,  $v_{be}$ ) components:

$$i_c(t) = I_C + i_c(t)$$

and

$$v_{BE}(t) = V_{BE} + v_{be}(t)$$

Therefore, the **total** collector current is:

$$i_c(t) = I_S e^{\frac{v_{BE}(t)}{V_T}}$$

$$I_C + i_c(t) = I_S e^{\frac{V_{BE} + v_{be}(t)}{V_T}}$$

## Apply the Small-Signal Approximation

**Q:** *Yikes! The exponential term is very messy. Is there some way to approximate it?*

**A:** Yes! The collector current  $i_c$  is a **function** of base emitter voltage  $v_{BE}$ .

Let's perform a **small-signal analysis** to determine an **approximate** relationship between  $i_c$  and  $v_{BE}$ .

Note that the value of  $v_{BE}(t) = V_{BE} + v_{be}(t)$  is **always** very close to the D.C. voltage for all time  $t$  (since  $v_{be}(t)$  is very **small**).

We therefore will use this D.C. voltage as the **evaluation point** (i.e., bias point) for our small-signal analysis.

## How fast it grows!

We first determine the value of the collector current  $i_C$  when the base emitter voltage  $v_{BE}$  is equal to the **DC value**  $V_{BE}$  :

$$i_C \Big|_{v_{BE}=V_{BE}} = I_S e^{\frac{v_{BE}}{V_T}} \Big|_{v_{BE}=V_{BE}} = I_S e^{\frac{V_{BE}}{V_T}} = I_C$$

Of course, the result is the **D.C. collector current**  $I_C$ .

We now determine the **change** in collector current due to a **change** in base-emitter voltage (i.e., a first **derivative**), **evaluated** at the D.C. voltage  $V_{BE}$  :

$$\begin{aligned} \frac{d i_C}{d v_{BE}} \Big|_{v_{BE}=V_{BE}} &= \frac{d (I_S \exp[v_{BE}/V_T])}{d v_{BE}} \Big|_{v_{BE}=V_{BE}} \\ &= \frac{I_S}{V_T} e^{v_{BE}/V_T} \Big|_{v_{BE}=V_{BE}} \\ &= \frac{I_S}{V_T} e^{V_{BE}/V_T} \quad [A/V] \end{aligned}$$

## A simple approximation

Thus, when the base-emitter voltage is equal to the D.C. "bias" voltage  $V_{BE}$ , the collector current  $i_c$  will equal the D.C. "bias" current  $I_C$ .

Likewise, this collector current will increase (decrease) by an amount of  $(I_S/V_T)e^{V_{BE}/V_T}$  mA for every 1mV increase (decrease) in  $v_{BE}$ .

Thus, we can easily **approximate** the collector current when the base-emitter voltage is equal to values such as:

$$v_{BE} = V_{BE} + 1 \text{ mV}$$

$$v_{BE} = V_{BE} + 3 \text{ mV}$$

$$v_{BE} = V_{BE} - 2 \text{ mV}$$

$$v_{BE} = V_{BE} - 0.5 \text{ mV}$$

Respectively, the answers are:

$$i_c = I_C + (I_S/V_T) e^{V_{BE}/V_T} \quad (1) \quad \text{mA}$$

$$i_c = I_C + (I_S/V_T) e^{V_{BE}/V_T} \quad (3) \quad \text{mA}$$

$$i_c = I_C + (I_S/V_T) e^{V_{BE}/V_T} \quad (-2) \quad \text{mA}$$

$$i_c = I_C + (I_S/V_T) e^{V_{BE}/V_T} \quad (-0.5) \quad \text{mA}$$

where we have assumed that scale current  $I_S$  is expressed in mA, and thermal voltage  $V_T$  is expressed in mV.

## The small signal approximation

Recall that the **small-signal voltage**  $v_{be}(t)$  represents a small **change** in  $v_{BE}(t)$  from its nominal (i.e., bias) voltage  $V_{BE}$ .

For example, we might find that the value of  $v_{be}(t)$  at four different times  $t$  are:

$$v_{be}(t_1) = 1 \text{ mV}$$

$$v_{be}(t_2) = 3 \text{ mV}$$

$$v_{be}(t_3) = -2 \text{ mV}$$

$$v_{be}(t_4) = -0.5 \text{ mV}$$

Thus, we can approximate the collector current using the **small-signal approximation** as:

$$i_c(t) = I_C + (I_S/V_T) e^{V_{BE}/V_T} v_{be}(t)$$

where of course  $I_C = I_S e^{V_{BE}/V_T}$ .

This is a very useful result, as we can now **explicitly** determine an expression for the **small-signal current**  $i_c(t)$ !

# The small-signal collector current

Recall  $i_C(t) = I_C + i_c(t)$ , therefore:

$$i_C(t) = I_C + i_c(t) = I_C + (I_S/V_T) e^{V_{BE}/V_T} v_{be}(t)$$

Subtracting the D.C. current from each side, we are left with an expression for the **small-signal current**  $i_c(t)$ , in terms of the **small-signal voltage**  $v_{be}(t)$  :

$$i_c(t) = (I_S/V_T) e^{V_{BE}/V_T} v_{be}(t)$$

We can **simplify** this expression by noting that  $I_C = I_S e^{V_{BE}/V_T}$ , resulting in:

$$\begin{aligned} (I_S/V_T) e^{V_{BE}/V_T} &= \frac{I_S e^{V_{BE}/V_T}}{V_T} \\ &= \frac{I_C}{V_T} \end{aligned}$$

and thus:

$$i_c(t) = \frac{I_C}{V_T} v_{be}(t)$$

# Transconductance: A small signal parameter

We define the value  $I_C/V_T$  as the **transconductance**  $g_m$ :

$$g_m = \frac{I_C}{V_T} \quad \left[ \frac{A}{V} \right]$$

and thus the **small-signal equation** simply becomes:

$$i_c(t) = g_m v_{be}(t)$$



## How transistors got their name

Let's now consider for a moment the transconductance  $g_m$ .

The term is short for transfer conductance: conductance because its units are amps/volt, and transfer because it relates the **collector** current to the voltage from **base to emitter**—the collector voltage is **not relevant** (if in **active mode**)!

Note we can rewrite the small-signal equation as:

$$\frac{v_{be}(t)}{i_c(t)} = \frac{1}{g_m}$$

The value  $(1/g_m)$  can thus be considered as transfer resistance, the value describing a **transfer resistor**.

**Transfer Resistor**—we can shorten this term to **Transistor** (this is how these devices were named)!

## Summarizing

We can **summarize** our results as:

$$I_C = I_S e^{V_{BE}/V_T}$$

D.C. Equation

$$i_c(t) = g_m v_{be}(t)$$

Small-Signal Equation

$$i_c(t) = I_C + g_m v_{be}(t)$$

Small-Signal Approximation

Note that we know have **two** expressions for the **total** (D.C. plus small-signal) collector current. The **exact** expression:


$$i_c(t) = I_S e^{\frac{V_{BE} + v_{be}(t)}{V_T}}$$

and the **small-signal approximation**:

$$i_c(t) = I_C + g_m v_{be}(t)$$
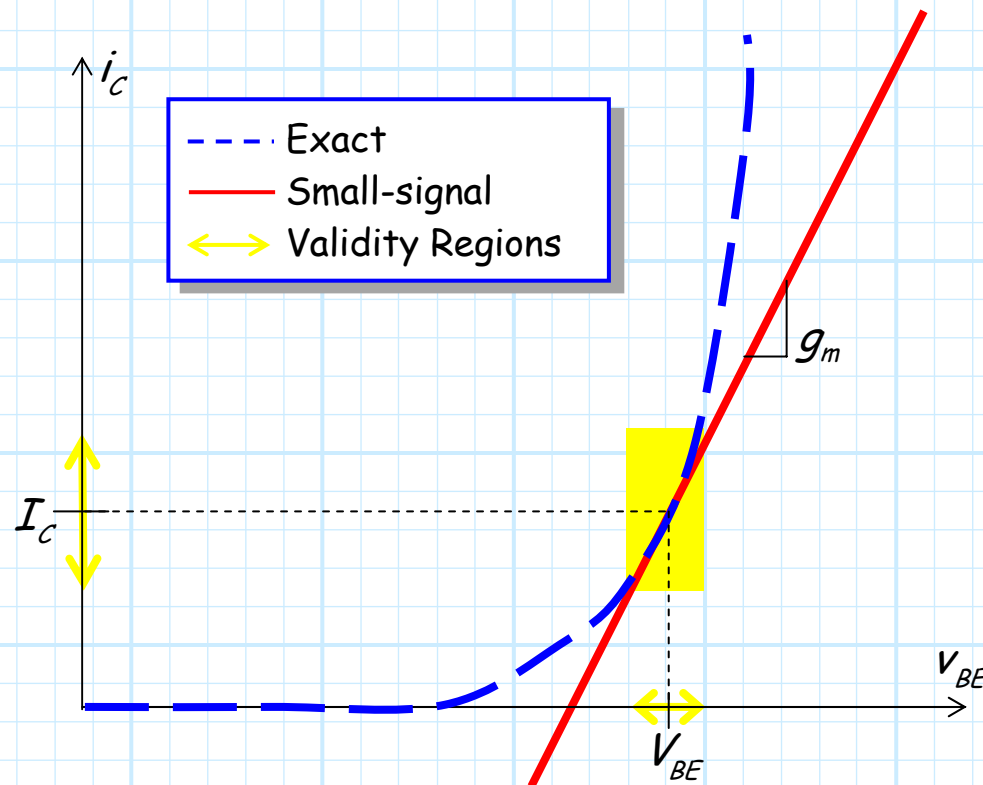
## Accurate over a small region

Let's plot these two expressions and see how they compare:



It is evident that the small-signal approximation is accurate (it provides **nearly** the exact values) **only** for values of  $i_C$  **near** the D.C. bias value  $I_C$ , and **only** for values of  $v_C$  **near** the D.C. bias value  $V_C$ .

The point  $(V_{BE}, I_C)$  is alternately known as the **D.C. bias point**, the **transistor operating point**, or the **Q-point**.

## Change the DC bias, change the transconductance

Note if we **change the D.C. bias** of a transistor circuit, the transistor operating point will change.

The small-signal model will **likewise** change, so that it provides accurate results in the region of this new operating point:

