

# Example: Small-Signal BJT

## Approximations

Say that we wish to find the collector current  $i_c$  of a BJT biased in the active mode, with  $I_S = 10^{-12} \text{ A}$  and a **base-emitter voltage** of:

$$V_{BE} = 0.6 + 0.001 \cos \omega t \quad \text{V}$$

**Q:** Easy! Since:

$$i_c = I_S e^{V_{BE}/V_T}$$

we find:

$$i_c(t) = \left( I_S e^{0.6/V_T} \right) e^{(0.001 \cos \omega t / V_T)}$$

right?

**A:** Although this answer is definitely **correct**, it is **not very useful** to us as engineers. Clearly, the base-emitter voltage consists of a **D.C.** bias term (0.6 V) and a **small-signal** term ( $0.001 \cos \omega t$ ).

Accordingly, we are interested in the **D.C.** collector current  $I_C$  and the **small-signal** collector current  $i_c$ . The D.C. collector current is obviously:

$$\begin{aligned}
 I_C &= I_S e^{0.6/V_T} \\
 &= 10^{-12} e^{0.6/0.025} \\
 &= 26 \text{ mA}
 \end{aligned}$$

But **how** do we determine the **small-signal** collector current  $i_c(t)$  from:

$$i_c(t) = \left( I_S e^{0.6/V_T} \right) e^{(0.001 \cos \omega t / V_T)} \quad ???$$

The answer, of course, is to use the **small-signal approximation**.

We know that:

$$i_c(t) = g_m v_{be}(t)$$

where:

$$g_m = \frac{I_C}{V_T} = \frac{26 \text{ mA}}{25 \text{ mV}} = 1.06 \Omega^{-1}$$

Therefore, the **small-signal collector current** is approximately:

$$\begin{aligned}
 i_c(t) &= g_m v_{be}(t) \\
 &= 1.06 (0.001 \cos \omega t) \\
 &= 1.06 \cos \omega t \quad \text{mA}
 \end{aligned}$$

and therefore the **total** collector current is:

**Q:** Say the D.C. bias voltage *increases* from  $V_{BE} = 0.6 \text{ V}$  to  $V_{BE} = 0.7 \text{ V}$ . What happens to the BJT collector current?

**A:** The D.C. bias current becomes:

$$I_C = I_S e^{0.7/V_T} = 10^{-12} e^{0.7/0.025} = 1446 \text{ mA} \quad !!!$$

since the **transconductance** is now:

$$g_m = \frac{I_C}{V_T} = \frac{1446 \text{ mA}}{25 \text{ mV}} = 57.84 \text{ } \Omega^{-1}$$

the **small-signal collector current** is:

$$\begin{aligned} i_c(t) &= g_m v_{be}(t) \\ &= 57.84 (0.001 \cos \omega t) \\ &= 57.8 \cos \omega t \quad \text{mA} \end{aligned}$$

Quite an **increase!**

Changing the transistor operating point (i.e., the DC bias point) will typically make a **big** difference in the small-signal result!