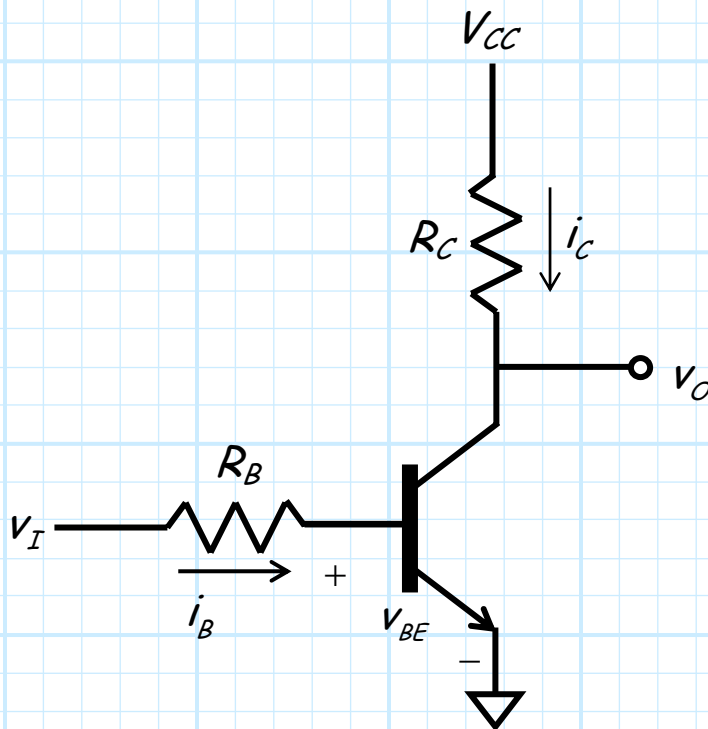


Example: Calculating the Small-Signal Gain

For this circuit, we have now determined (if BJT is in active mode), the **small-signal equations** are:



$$1) \quad v_i = i_b R_B + v_{be}$$

$$2) \quad i_c = \beta i_b$$

$$3) \quad v_o = -R_C i_c$$

$$4) \quad i_c \cong g_m v_{be}$$

Q: So, can we now determine the **small-signal open-circuit voltage gain** of this amplifier? I.E.:

$$A_{v_o} = \frac{v_o(t)}{v_i(t)}$$

A: Look at the **four** small-signal equations—there are **four** unknowns (i.e., i_b , v_{be} , i_c , v_o)!

Combining equations 2) and 4), we get:

$$v_{be} = \frac{\beta}{g_m} i_b = r_{\pi} i_b$$

Inserting this result in equation 1), we find:

$$v_i = (R_B + r_{\pi}) i_b$$

Therefore:

$$i_b = \frac{v_i}{R_B + r_{\pi}}$$

and since $i_c = \beta i_b$:

$$i_c = \frac{\beta}{R_B + r_{\pi}} v_i$$

which we insert into equation 3):

$$v_o = -i_c R_C = \frac{-\beta R_C}{R_B + r_{\pi}} v_i$$

Therefore, the **small-signal gain** of this amplifier is:

$$A_{vo} = \frac{v_o(t)}{v_i(t)} = \frac{-\beta R_C}{R_B + r_{\pi}}$$

Note this is the small signal gain of **this** amplifier—and this amplifier **only**!