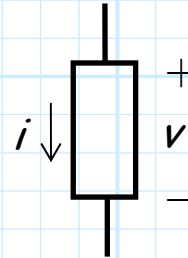


### Special Problem 5.6-1

A **strange**, two-terminal device has the following relationship between the current through it ( $i$ ) and the voltage across it ( $v$ ):

$$i = 4v + v^2$$

where  $v$  is in **volts** and  $i$  in **mA**.



We can define the **small-signal resistance**  $r_{ss}$  of this device as:

$$r_{ss} = \frac{v_{ss}}{i_{ss}}$$

where  $v_{ss}$  is the **small-signal voltage** across the device and  $i_{ss}$  is the **small-signal current** through it.

- a) Determine the **value** of this small-signal resistance  $r_{ss}$  if the **DC voltage** across the device is  $V = 3.0 \text{ V}$
- b) Determine the **small-signal voltage**  $v_{ss}(t)$  across this device if the **DC voltage** across it is  $3.0 \text{ V}$ , and the **small-signal current**  $i_{ss}$  through it is:

$$i_{ss}(t) = 0.2 \cos \omega t \text{ mA}$$