

# Small-Signal Output Resistance

Recall that due to the **Early effect**, the collector current  $i_c$  is slightly dependent on  $v_{CE}$ :

$$i_c = \beta i_B \left( 1 + \frac{v_{CE}}{V_A} \right)$$

where we recall that  $V_A$  is a BJT device parameter, called the **Early Voltage**.

**Q:** How does this affect the *small-signal response* of the BJT?

**A:** Well, if  $i_c(t) = I_C + i_c(t)$  and  $v_{CE}(t) = V_{CE} + v_{ce}(t)$ , then with the small-signal approximation:

$$\begin{aligned} I_C + i_c &= \beta i_B \left( 1 + \frac{v_{CE}}{V_A} \right) \bigg|_{v_{CE}=V_{CE}} + \left( \frac{\partial i_c}{\partial v_{CE}} \bigg|_{v_{CE}=V_{CE}} \right) v_{ce} \\ &= \beta I_B \left( 1 + \frac{V_{CE}}{V_A} \right) + \beta I_B \left( 1 + \frac{V_{CE}}{V_A} \right) \left( \frac{1}{V_A} \right) v_{ce} \end{aligned}$$

## Small-signal base resistance

Equating the **DC** components:

$$I_C = \beta I_B \left( 1 + \frac{V_{CE}}{V_A} \right)$$

And equating the **small-signal** components:

$$i_c = \beta I_B \left( 1 + \frac{V_{CE}}{V_A} \right) \left( \frac{1}{V_A} \right) v_{ce}$$

Note that by inserting the DC result, this expression can be simplified to:

$$i_c = I_C \left( \frac{1}{V_A} \right) v_{ce} = \left( \frac{I_C}{V_A} \right) v_{ce}$$

Therefore, another **small-signal** equation is found, one that expresses the small-signal response of the **Early effect**:

$$i_c = \left( \frac{I_C}{V_A} \right) v_{ce}$$

## Small-signal base resistance

Recall that we defined (in EECS 312) the BJT **output resistance**  $r_o$ :

$$\frac{I_C}{V_A} \doteq \frac{1}{r_o}$$



Be careful! Although the Early Voltage  $V_A$  is a **device parameter**, the **output resistance**  $r_o$ —since it depends on DC collector current  $I_C$ —is **not a device parameter!**

Therefore, the **small-signal collector current** resulting from the **Early effect** can likewise be expressed as:


$$i_c = \frac{v_{ce}}{r_o}$$

## Small-signal base resistance

Combining this result with an earlier result (i.e.,  $i_c = g_m v_{be}$ ), we find that the **total** small-signal collector current is:

$$i_c = g_m v_{be} + \frac{v_{ce}}{r_o} = \beta i_b + \frac{v_{ce}}{r_o}$$

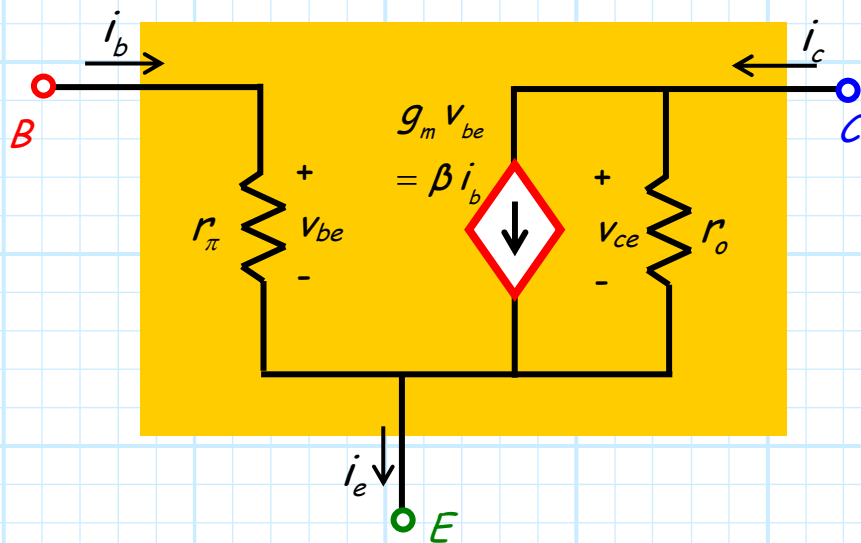We can account for this effect in our small-signal **circuit models**. For example, the Hybrid-II becomes:




$$i_b = \frac{v_{be}}{r_\pi}$$

$$i_c = g_m v_{be} + \frac{v_{ce}}{r_o}$$

$$i_e = i_b + i_c$$

# Small-signal base resistance

And for the T-model:

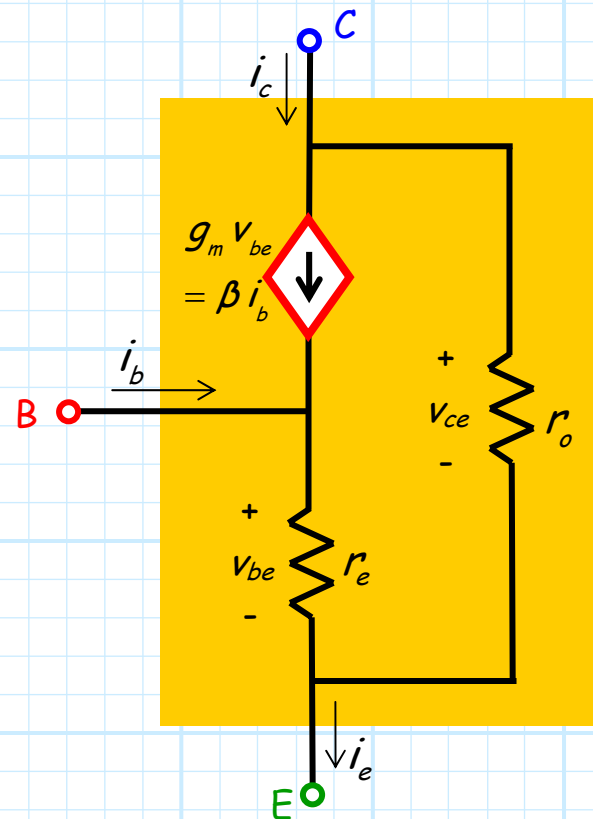

Often,  $r_o$  is so **large** that it can be ignored (**caution**: ignoring the output resistance means approximating it as an **open** circuit, i.e.,  $r_o = \infty$ ).

