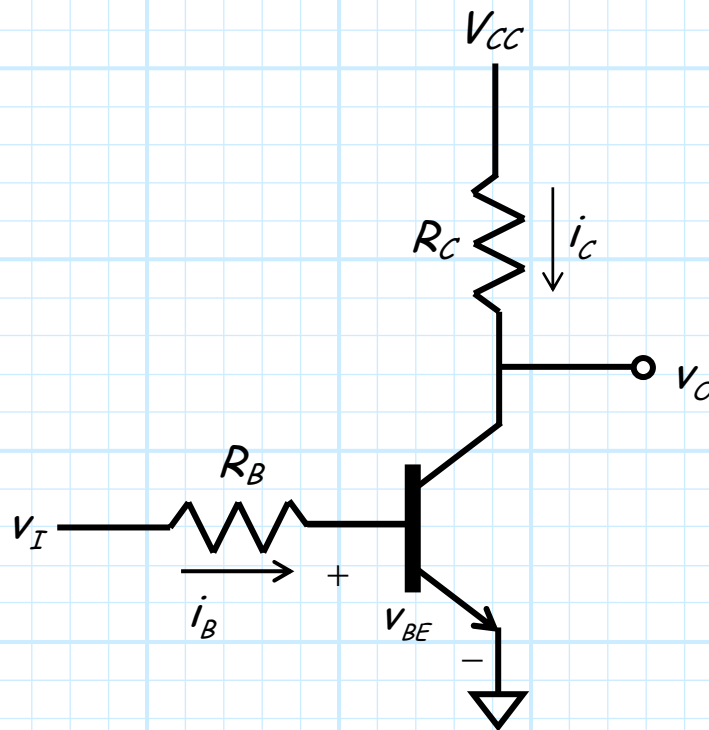


The Small-Signal Circuit Equations

Now let's again consider this circuit, where we assume the BJT is in the **active** mode:



The **four** equations describing this circuit are:

$$1) \quad v_I - R_B i_B - v_{BE} = 0 \quad (\text{KVL})$$

$$2) \quad i_C = \beta i_B \quad (\text{BJT})$$

$$3) \quad v_O = V_{CC} - R_C i_C \quad (\text{KVL})$$

$$4) \quad i_C = I_s e^{v_{BE}/V_T} \quad (\text{BJT})$$

Now, we assume that each current and voltage has **both** a small-signal and DC component. Writing each equation **explicitly** in terms of these components, we find that the four circuit equations become:

$$(1) \quad (V_I + v_i) - R_B (I_B + i_b) - (V_{BE} + v_{be}) = 0$$

$$(V_I - R_B I_B - V_{BE}) + (v_i - R_B i_b - v_{be}) = 0$$

$$(2) \quad I_C + i_c = \beta (I_B + i_b)$$

$$I_C + i_c = \beta I_B + \beta i_b$$

$$(3) \quad V_O + v_o = V_{CC} - R_C (I_C + i_c)$$

$$V_O + v_o = (V_{CC} - R_C I_C) - R_C i_c$$

$$(4) \quad I_C + i_c = I_S e^{(V_{BE} + v_{be})/V_T}$$

$$I_C + i_c = I_S e^{V_{BE}/V_T} e^{v_{be}/V_T}$$

Note that each equation is really **two** equations!

1. The sum of the **DC** components on **one** side of the equal sign must equal the sum of the **DC** components on the **other**.

2. The sum of the **small-signal** components on **one** side of the equal sign must equal the sum of the **small-signal** components on the **other**.

This result can greatly **simplify** our quest to determine the **small-signal** amplifier parameters!



*You see, all we need to do is determine four **small-signal** equations, and we can then solve for the four **small-signal** values $i_b, i_c, v_{be}, v_o!$*

From (1) we find that the **DC** equation is:

$$V_I - R_B I_B - V_{BE} = 0$$

while the **small-signal** equation from 1) is:

$$v_i - R_B i_b - v_{be} = 0$$

Similarly, from equation (2) we get these equations:

$$I_C = \beta I_B \quad (\text{DC})$$

$$i_c = \beta i_b \quad (\text{small signal})$$

And from equation (3):

$$V_O = V_{CC} - R_C I_C \quad (\text{DC})$$

$$v_o = -R_C i_c \quad (\text{small-signal})$$

Finally, from equation (4) we, um, get, er—just what the heck do we get?

$$(4) \quad I_C + i_c = I_s e^{(V_{BE} + v_{be})/V_T} \quad ????$$

$$I_C + i_c = I_s e^{V_{BE}/V_T} e^{v_{be}/V_T}$$

Q: *Jeepers! Just what are the DC and small-signal components of:*

$$I_s e^{V_{BE}/V_T} e^{v_{be}/V_T} \quad ???$$



A: Precisely speaking, we **cannot** express the above expression as the sum of a DC and **small-signal** component. Yet, we **must** determine a **fourth** small-signal equation in order to determine the **four** small signal values $i_b, i_c, v_{be}, v_o!$

However, we can **approximate** the above expression as the sum of DC and small-signal components. To accomplish this, we must apply the **small-signal approximation** (essentially a Taylor series approx.).

We will find that the **small-signal approximation** provides an accurate small-signal equation for expressions such (4). We will likewise find that this approximate equation is accurate **if** the small-signal voltage v_{be} is, well, **small!**