

The Small-Signal Equation Matrix

We can **summarize** our small-signal equations with the small-signal equation matrix. Note this matrix relates the **small-signal BJT parameters** v_{be} , i_b , i_c , and i_e .

		Column Parameters			
		v_{be}	i_b	i_c	i_e
Row Parameters	v_{be}	1	$r_\pi = \frac{\beta}{g_m}$	$\frac{1}{g_m}$	$r_e = \frac{\alpha}{g_m}$
	i_b	$\frac{1}{r_\pi} = \frac{g_m}{\beta}$	1	$\frac{1}{\beta}$	$\frac{1}{(\beta+1)}$
	i_c	g_m	β	1	$\alpha = \frac{\beta}{\beta+1}$
	i_e	$\frac{1}{r_e} = \frac{g_m}{\alpha}$	$\beta+1$	$\frac{1}{\alpha} = \frac{\beta+1}{\beta}$	1

Here's how you use this

To use this matrix, note that the **row parameter** is equal to the product of the **column parameter** and the **matrix element**. For example:

$$i_b = \frac{1}{r_\pi} v_{be}$$

	v_{be}	i_b	i_c	i_e
v_{be}	1	$r_\pi = \frac{\beta}{g_m}$	$\frac{1}{g_m}$	$r_e = \frac{\alpha}{g_m}$
i_b	$\frac{1}{r_\pi} = \frac{g_m}{\beta}$	1	$\frac{1}{\beta}$	$\frac{1}{(\beta + 1)}$
i_c	g_m	β	1	$\alpha = \frac{\beta}{\beta + 1}$
i_e	$\frac{1}{r_e} = \frac{g_m}{\alpha}$	$\beta + 1$	$\frac{1}{\alpha} = \frac{\beta + 1}{\beta}$	1