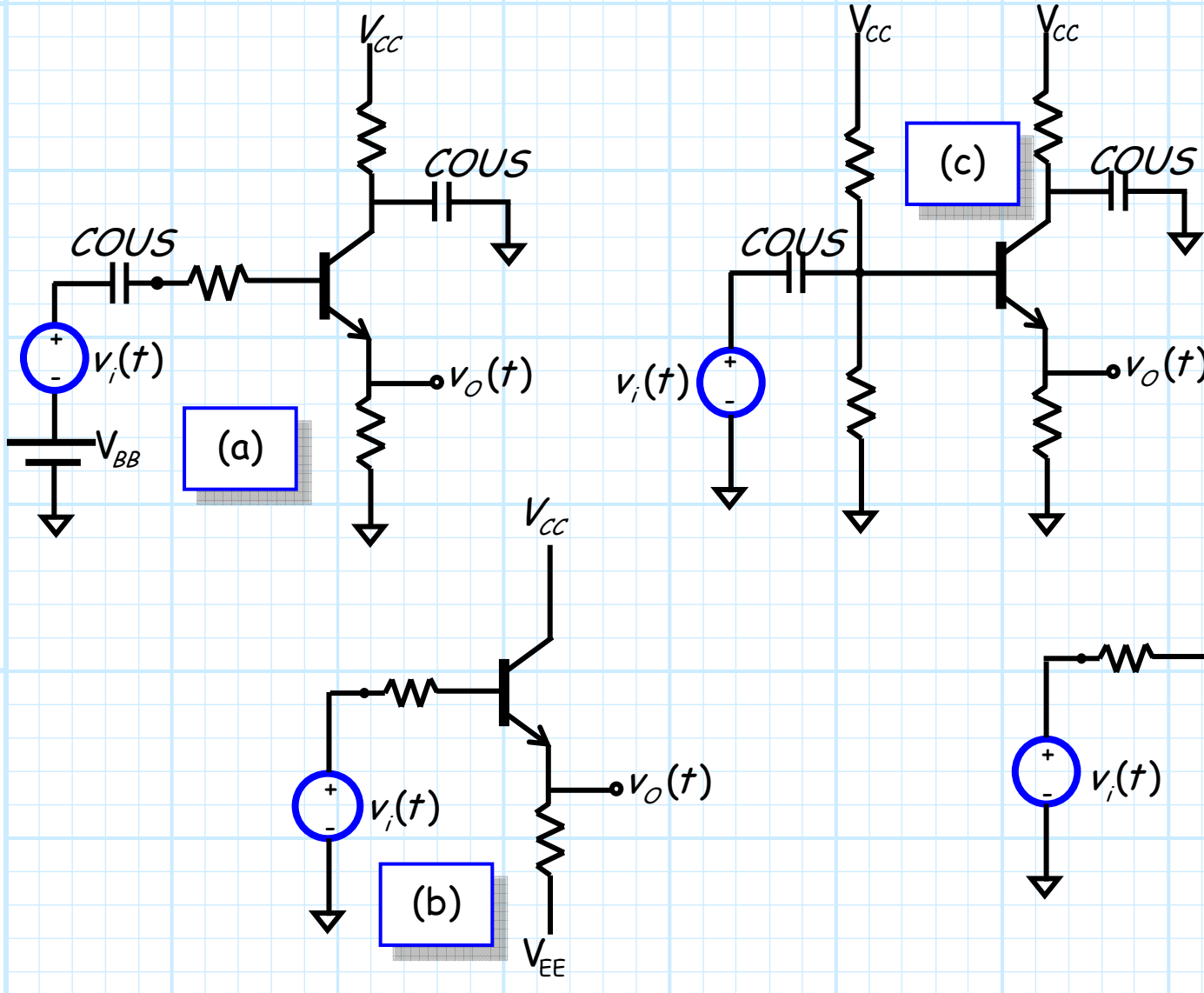


The Common-Collector Amplifier

The **common-collector** amplifier: the BJT collector is at small-signal ground!
Examples of this type of amplifier include:



Do you see why each of these four circuits is a gul-durn common-collector amplifier?

Make dang sure that you do!




We'll use the T-model



Let's consider **circuit (a)**.

It turns out that for **common-collector** amplifiers, the **T-model** (as opposed to the hybrid- π) typically provides the **easiest** small-signal analysis.

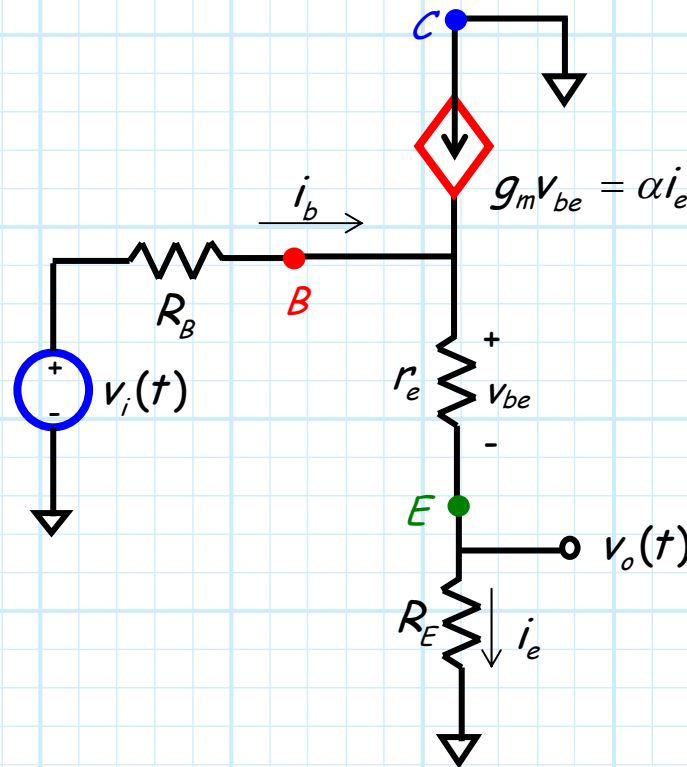Using the **T-model**, we find that the **small-signal circuit** for amplifier (a) is:



Let's analyze this amplifier!


Let's determine the open-circuit voltage gain of this small-signal amplifier:

$$A_{v_o} = \frac{v_o^{oc}}{v_i}$$

We therefore must determine the output voltage v_o in terms of input voltage v_i .

From **KVL**, we find that:

$$0 + v_i - R_B i_b - v_{be} = v_o$$

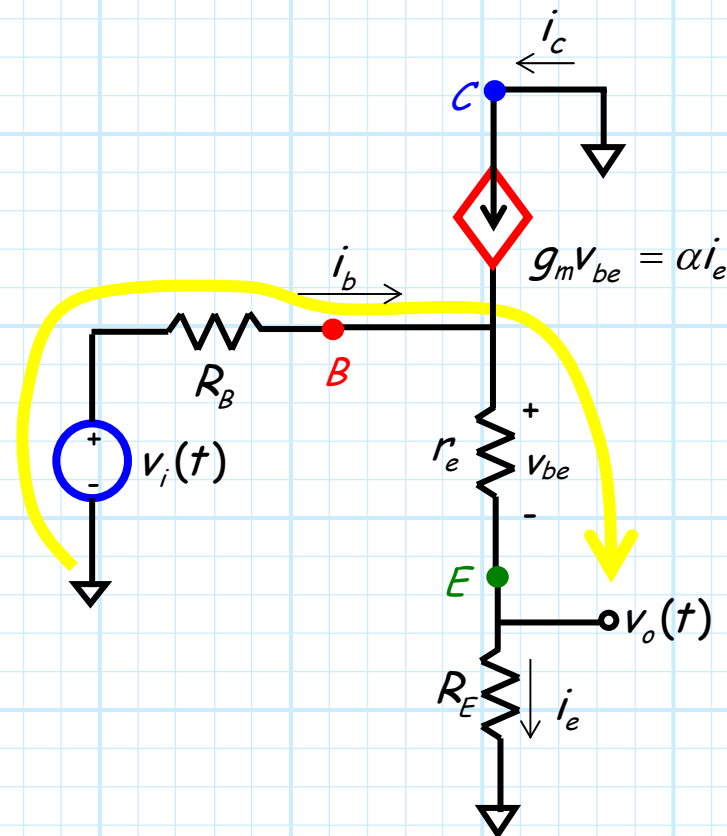

Let's apply KCL!

And from **KCL**, we find:

$$\begin{aligned} i_b &= i_e - i_c \\ &= i_e - g_m v_{be} \end{aligned}$$

Where from Ohm's Law:


$$i_e = \frac{v_o - 0}{R_E} = \frac{v_o}{R_E}$$

So:

$$i_b = i_e - g_m v_{be} = \frac{v_o}{R_E} - g_m v_{be}$$

Inserting this into the **KVL** equation above:
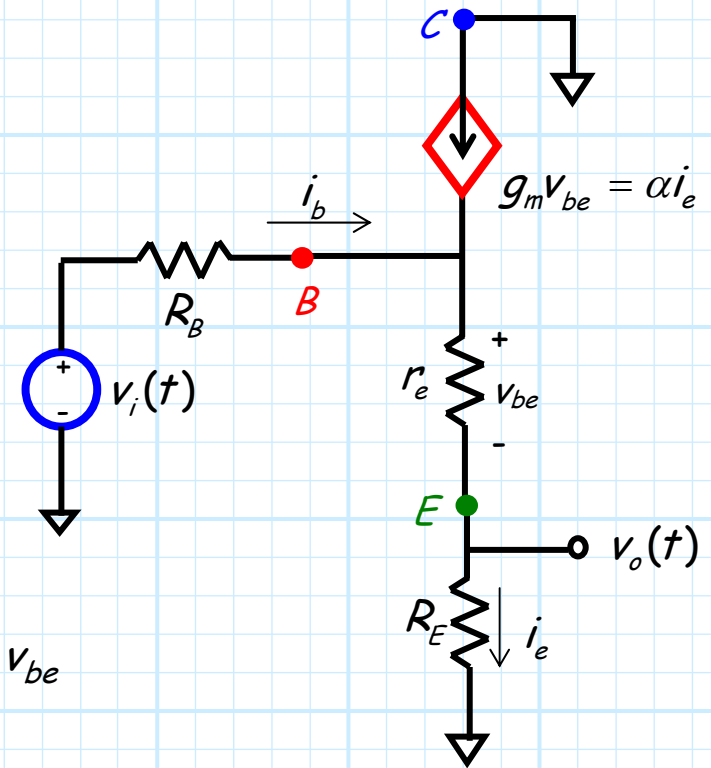
$$\begin{aligned} v_o &= v_i - R_B i_b - v_{be} \\ &= v_i - R_B \left(\frac{v_o}{R_E} - g_m v_{be} \right) - v_{be} \\ &= v_i - \frac{R_B}{R_E} v_o + g_m R_B v_{be} \end{aligned}$$



Let's apply Ohm's Law!

Likewise using KCL and Ohm's Law:


$$i_e = \frac{v_{be}}{r_e} = \frac{v_o}{R_E}$$

Or rearranging:

$$v_{be} = \frac{r_e}{R_E} v_o$$

Inserting this result in the solution above:
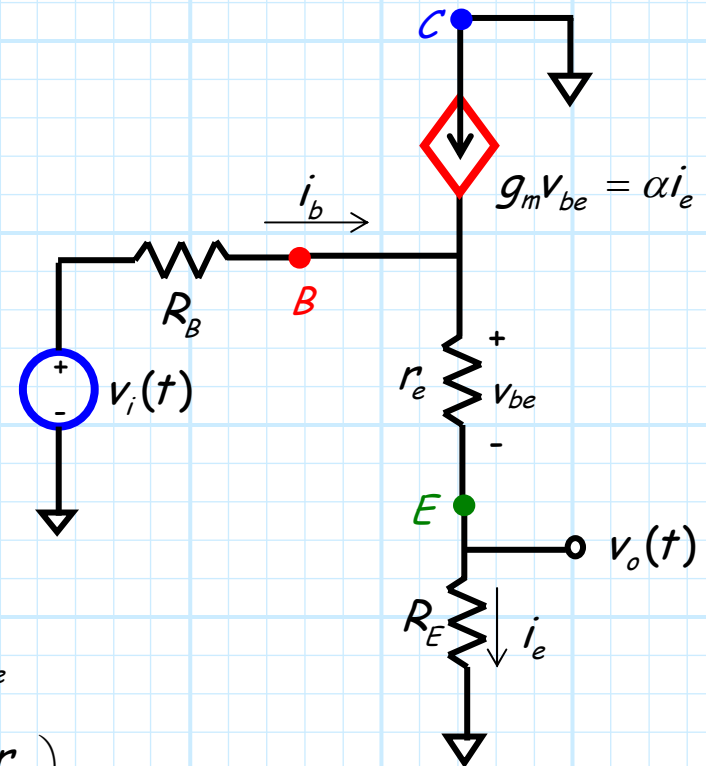
$$\begin{aligned} v_o &= v_i - \left(\frac{R_B}{R_E} \right) v_o + g_m R_B v_{be} \\ &= v_i - \left(\frac{R_B}{R_E} \right) v_o + g_m R_B \left(\frac{r_e}{R_E} \right) v_o \\ &= v_i - \left(\frac{R_B}{R_E} \right) v_o + g_m r_e \left(\frac{R_B}{R_E} \right) v_o \\ &= v_i + (g_m r_e - 1) \left(\frac{R_B}{R_E} \right) v_o \end{aligned}$$



It's the gain—but look closer!

From this result we can determine the small-signal output voltage:

$$v_o = \left(1 + (1 - g_m r_e) \frac{R_B}{R_E} \right)^{-1} v_i$$

And so the open-circuit voltage gain is:

$$A_{v_o} = \frac{v_o}{v_i} = \left(1 + (1 - g_m r_e) \frac{R_B}{R_E} \right)^{-1}$$

We now note that:

$$g_m r_e = \frac{V_T}{I_E} \frac{I_C}{V_T} = \frac{I_C}{I_E} = \alpha$$

Therefore:

$$1 - g_m r_e = 1 - \alpha = 1 - \frac{\beta}{\beta + 1} = \frac{1}{\beta + 1}$$

The output is no bigger than the input!

And so the gain becomes:

$$A_{vo} = \frac{v_o}{v_i} = \left(1 + \frac{1}{\beta + 1} \frac{R_B}{R_E} \right)^{-1}$$

We note here that:

$$\frac{1}{\beta + 1} \ll 1$$

We find therefore, that the **small-signal gain** of this common-collector amplifier is approximately:

$$\begin{aligned} A_{vo} &= \left(1 + \frac{1}{\beta + 1} \frac{R_B}{R_E} \right)^{-1} \\ &\cong (1 + 0)^{-1} \\ &= 1.0 \end{aligned}$$

The gain is approximately **one!**

This doesn't seem to be useful

Q: *What!? The gain is equal to one? That's just dog-gone silly!*

What good is an amplifier with a gain of one?



A: Remember, the open-circuit voltage gain is just **one** of **three** fundamental amplifier parameters.

The other two are **input resistance** R_{in} and **output resistance** R_{out} .

First, let's examine the **input** resistance.

Let's determine the input resistance

Using the small-signal circuit, we find that:


$$R_{in} = \frac{v_i}{i_i} = \frac{v_i}{i_b}$$

Using **KVL**,

$$0 + v_i - R_B i_b - (r_e + R_E) i_e = 0$$

and adding the fact that $i_e = (\beta + 1) i_b$, we find that the small-signal **base** current is:
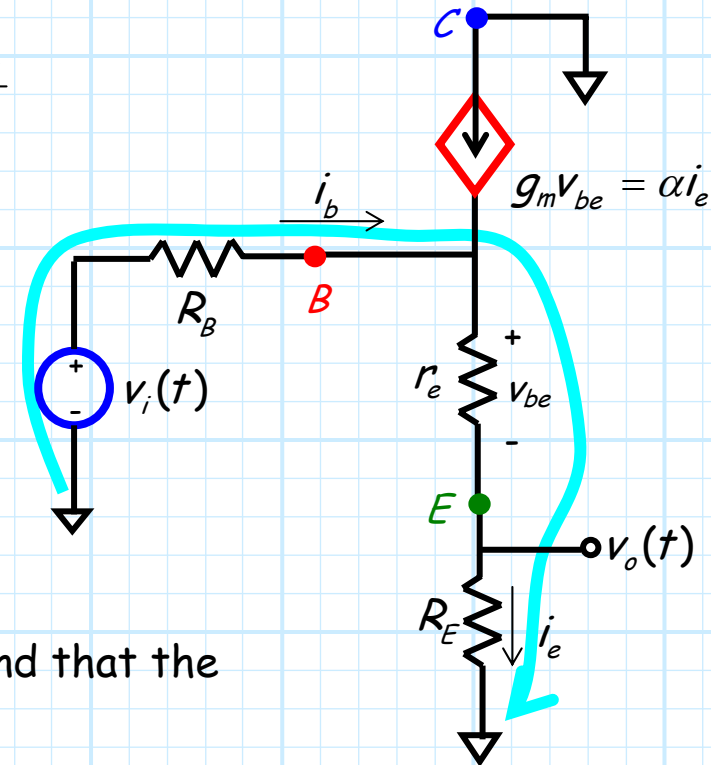
$$i_b = \frac{v_i}{R_B + (\beta + 1)(r_e + R_E)}$$



A large input resistance; it's a very good thing

Combining these equations, we find that the input resistance for **this** common-collector amplifier is:

$$R_{in} = \frac{v_i}{i_b} = R_B + (\beta + 1)(r_e + R_E)$$

Since beta is large, the input resistance is **typically large**—this is **good!**

Now, let's consider the **output** resistance R_{out} of this particular common-collector amplifier.

Recall that the output resistance is defined as:

$$R_{out} = \frac{v_o^{oc}}{i_o^{sc}}$$

where v_o^{oc} is the **open-circuit output voltage** and i_o^{sc} is the **short-circuit output current**.

We must find the short circuit output current

Using **KVL**,

$$0 + v_i - R_B i_b - r_e i_e = 0$$


and adding the fact that

$i_b = (\beta + 1)^{-1} i_e$, we find that the small-signal **emitter** current is:

$$i_e = \frac{v_i}{R_B (\beta + 1)^{-1} + r_e}$$

And from KCL, this emitter current is likewise the short circuit output current:
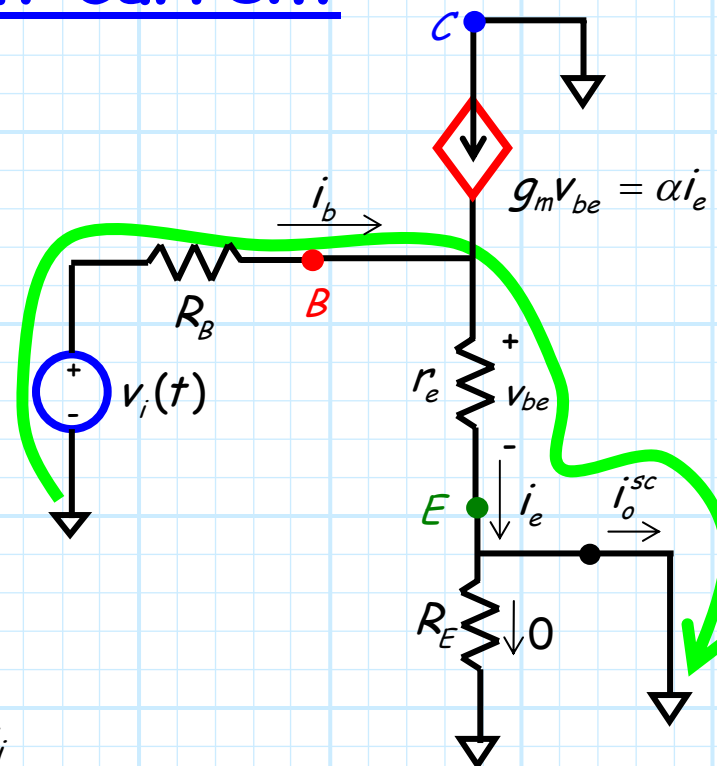
$$i_o^{sc} = i_e = \frac{v_i}{R_B (\beta + 1)^{-1} + r_e}$$



A small output resistance; it's a very good thing as well

Of course, we already have determined that the open-circuit **output** voltage is approximately **equal** to the **input** voltage:

$$v_o^{oc} = v_i \quad (\text{i.e., } A_{vo} \cong 1)$$

Therefore, we find that the **output** resistance will be:

$$R_{out} = \frac{v_o^{oc}}{i_o^{sc}} = R_B (\beta + 1)^{-1} + r_e$$

Since the emitter resistance r_e is typically **small** (e.g., $r_e = 2.5\Omega$ if $I_E = 10.0mA$), and β is typically large, we find that the **output** resistance of this common-collector amplifier will typically be **small**!

The emitter follower is like a voltage follower—it's a buffer!

Let's **summarize** what we have learned about this **common-collector amplifier**:

1. The small-signal voltage **gain** is approximately equal to **one**.
2. The **input** resistance is typically very **large**.
3. The **output** resistance is typically very **small**.

This is just like the op-amp voltage follower !

The common-collector amplifier is alternatively referred to as an **emitter follower** (i.e., the output voltage follows the input voltage).

The emitter follower is a great output stage

The common-collector amplifier is typically used as an **output stage**, where it **isolates** a high gain **amplifier** with large output resistance (e.g. a **common emitter**) from an output **load** of small resistance (e.g. an audio speaker).

