


BJT Internal Capacitances

There are **very small capacitances** in a BJT between the collector and the base, and the base and the emitter.

Since the capacitor values are very small, their impedance at **low** and moderate frequencies is large.

I.E.:
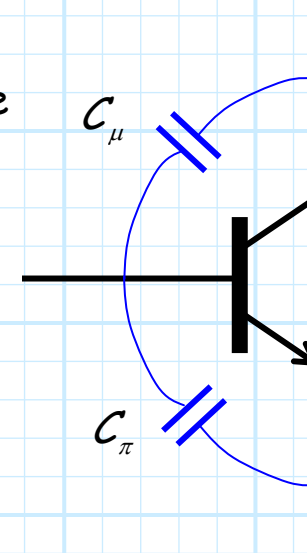
$$Z_c = \frac{1}{j\omega C} \text{ is large if } \omega C \ll 1$$



In other words, at low and moderate frequencies, these capacitor impedances are approximately **open** circuits, and thus they can be **ignored**.

However, at **high** frequencies, the capacitor impedance can drop to **moderate** values (e.g., $K\Omega$ s).

In this case, we can **no longer** ignore these capacitances, but instead must incorporate them into our **small-signal model!**

The capacitance between base and collector

Q: What are C_{μ} and C_{π} ?


A: See below!

C_{μ}

C_{μ} is a parasitic capacitance between the **collector** and the **base**.

This capacitance is due to the *pn junction* (between collector and base).

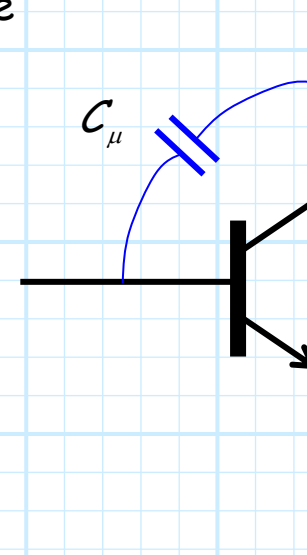Typical values of C_{μ} are a few picofarads or **less**.



The capacitance between base and emitter

C_{π}

C_{π} is a parasitic (i.e., small) capacitance between the base and the emitter.

This capacitance actually consists of **two** parts:

$$C_{\pi} = C_{je} + C_{de}$$

where:

$$\left. \begin{array}{l} C_{de} = \text{diffusion capacitance} \\ C_{je} = \text{junction capacitance} \end{array} \right\} \text{pn junction capacitance}$$

Typically, C_{π} is a few picofarads.

