

5.8 BJT Internal Capacitances

Reading Assignment: 485-490

BJT's exhibit **capacitance** between each of its terminals (i.e., base, emitter, collector). These capacitances ultimately limit amplifier **bandwidth**.

Q: *Yikes! Who put these capacitors in the BJT? Why did they put them there? Why don't we just **remove** them?*

A: These capacitances are **parasitic** capacitances. Since the terminals are made of conducting materials (e.g., metal), there will **always** be some capacitance associated with any two terminals.

BJT designers and manufacturers work hard to **minimize** these capacitances—and indeed they are **very small**—but we **cannot** eliminate them entirely.

If the **signal frequency** gets **high** enough, these capacitances can affect amplifier performance.

HO: BJT INTERNAL CAPACITANCES

Now that we are aware of these internal capacitances, we must **modify** our small-signal circuit **models**.

HO: THE HIGH-FREQUENCY HYBRID PI MODEL

The significance of the internal capacitances are typically specified in terms of a frequency-dependent BJT parameter called $h_{fe}(\omega)$. This parameter is often referred to as the "short-circuit current gain" of the BJT.

From this function $h_{fe}(\omega)$ we can extract a BJT parameter called the **unity-gain bandwidth**—a result very analogous to op-amps!

HO: THE SHORT-CIRCUIT CURRENT GAIN


BJT Internal Capacitances

There are **very small capacitances** in a BJT between the collector and the base, and the base and the emitter.

Since the capacitor values are very small, their impedance at **low** and moderate frequencies is large.

I.E.:
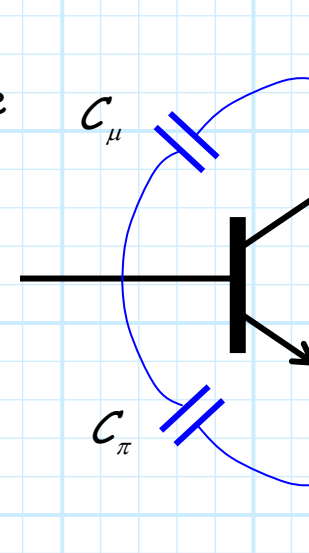
$$Z_c = \frac{1}{j\omega C} \text{ is large if } \omega C \ll 1$$



In other words, at low and moderate frequencies, these capacitor impedances are approximately **open** circuits, and thus they can be **ignored**.

However, at **high** frequencies, the capacitor impedance can drop to **moderate** values (e.g., $K\Omega$ s).

In this case, we can **no longer** ignore these capacitances, but instead must incorporate them into our **small-signal model!**

The capacitance between base and collector

Q: What are C_{μ} and C_{π} ?


A: See below!

C_{μ}

C_{μ} is a parasitic capacitance between the **collector** and the **base**.

This capacitance is due to the *pn junction* (between collector and base).

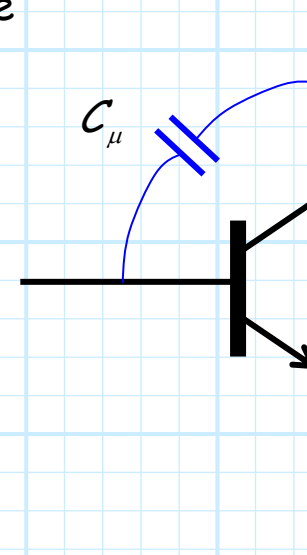Typical values of C_{μ} are a few picofarads or **less**.



The capacitance between base and emitter

C_π

C_π is a parasitic (i.e., small) capacitance between the base and the emitter.


This capacitance actually consists of **two** parts:

$$C_\pi = C_{je} + C_{de}$$

where:


$$\left. \begin{array}{l} C_{de} = \text{diffusion capacitance} \\ C_{je} = \text{junction capacitance} \end{array} \right\} \text{pn junction capacitance}$$

Typically, C_π is a few picofarads.

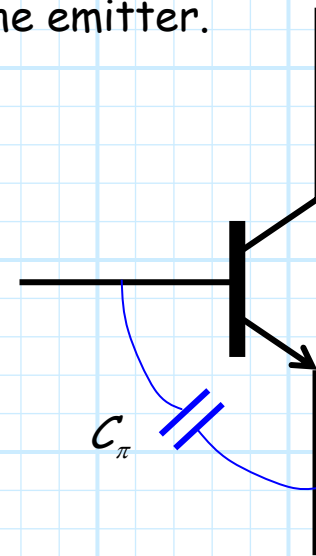

The High-Frequency Hybrid- π Model

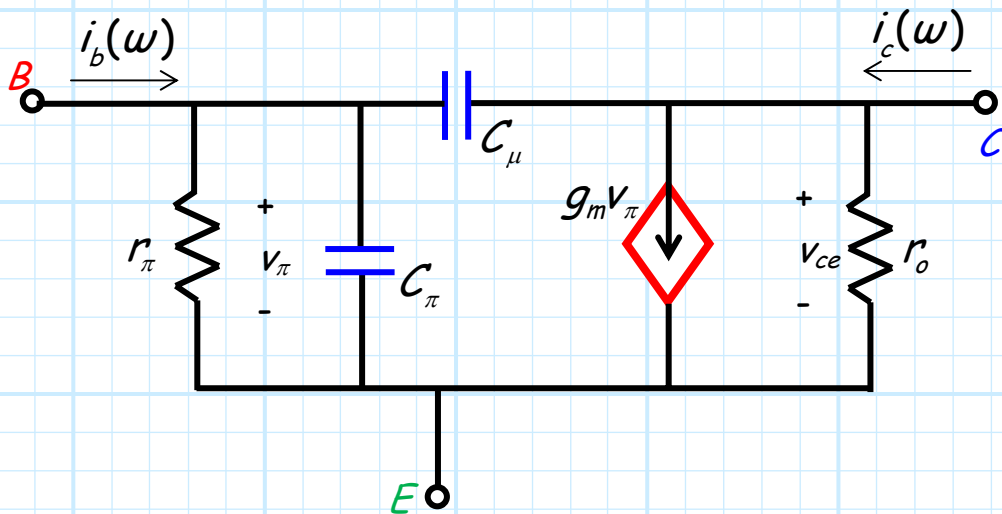
Combine the internal capacitances and lead resistance in a **modified** Hybrid- π model.



- * Therefore use this model to construct small-signal circuit when v_i is operating at **high** frequency.
- * Note since $Z_c = 1/j\omega C$, all currents and voltages will be **dependent on operating frequency** ω .
- * Note the voltage across r_π is v_π , but $v_\pi \neq v_{be}$!!!
- * Note at low-frequencies, the model reverts to the **original** Hybrid- π model.

The Short-Circuit Current Gain h_{fe}

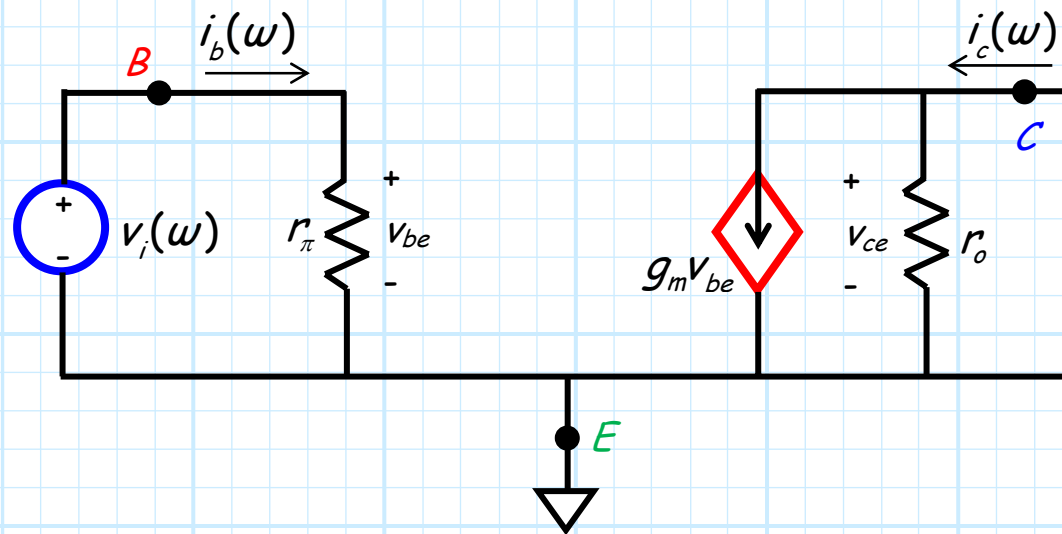Consider the common emitter "low-frequency" small-signal model with its output short-circuited.



Boring! Tell me something
I don't already know

In this case we find:

$$\begin{aligned}i_c(\omega) &= g_m v_{be}(\omega) \\ &= g_m r_\pi i_b(\omega)\end{aligned}$$

But we know that:

$$g_m r_\pi = \frac{I_C}{V_T} \frac{V_T}{I_B} = \frac{I_C}{I_B} = \beta$$


Therefore:

$$\frac{i_c(\omega)}{i_b(\omega)} = \beta$$

Just as we **expected!**

When the input signal is changing rapidly

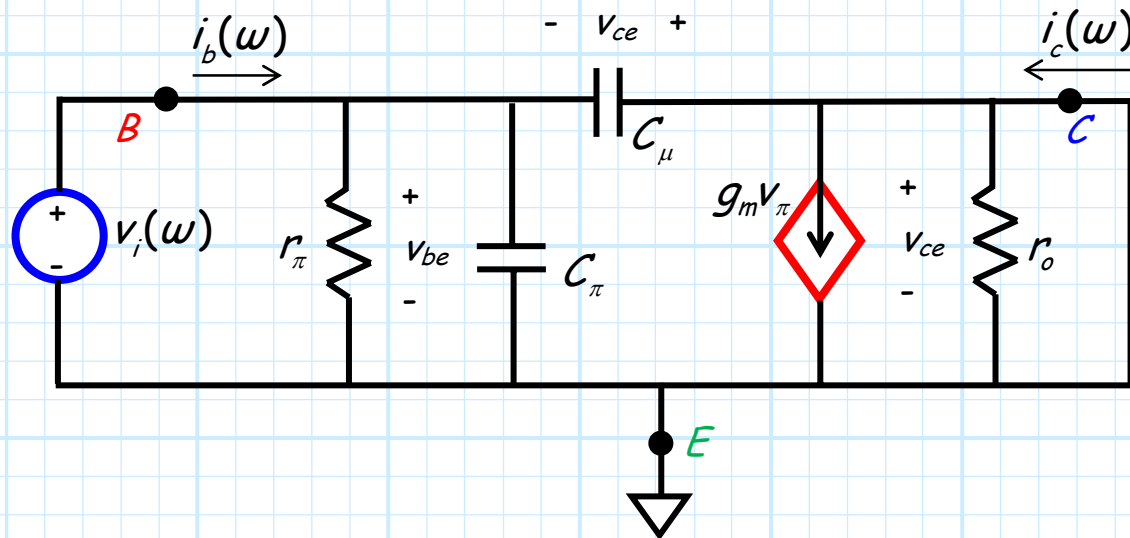Now, contrast this with the results using the **high frequency** model:



Evaluating this circuit, it is evident that the small-signal **base** current is:

$$i_b(\omega) = v_\pi(\omega) \left(\frac{1}{r_\pi} + j\omega(C_\pi + C_\mu) \right)$$

While the small-signal **collector** current is:

$$i_c(\omega) = v_\pi(\omega) (g_m - j\omega C_\mu)$$

Here's something you did not know

Therefore, the **ratio** of small-signal collector current to small-signal base current is:

$$\frac{i_c(\omega)}{i_b(\omega)} = \frac{r_\pi g_m - j\omega r_\pi C_\mu}{1 + j\omega r_\pi (C_\mu + C_\pi)}$$

Typically, we find that $g_m \gg \omega C_\mu$, so that we find:

$$\frac{i_c(\omega)}{i_b(\omega)} \approx \frac{r_\pi g_m}{1 + j\omega r_\pi (C_\mu + C_\pi)}$$

and again we know:

$$r_\pi g_m = \frac{I_C}{V_T} \frac{V_T}{I_B} = \frac{I_C}{I_B} = \beta$$

Therefore:

$$\frac{i_c(\omega)}{i_b(\omega)} \approx \frac{\beta}{1 + j\omega r_\pi (C_\mu + C_\pi)}$$

Your BJT is frequency dependent!

We define this ratio as the **small-signal BJT (short-circuit) current gain**, $h_{fe}(\omega)$:

$$h_{fe}(\omega) \doteq \frac{i_c(\omega)}{i_b(\omega)} \approx \frac{\beta}{1 + j\omega r_\pi (C_\mu + C_\pi)}$$

Note this function is a **low-pass** function, where we can define a **3dB break frequency** as:


$$\omega_\beta = \frac{1}{r_\pi (C_\pi + C_\mu)}$$

Therefore:

$$h_{fe}(\omega) \doteq \frac{i_c(\omega)}{i_b(\omega)} \approx \frac{\beta}{1 + j\omega/\omega_\beta}$$

This is how we define BJT bandwidth

Plotting the magnitude of $h_{fe}(\omega)$ (i.e., $|h_{fe}(\omega)|^2$) we find that:

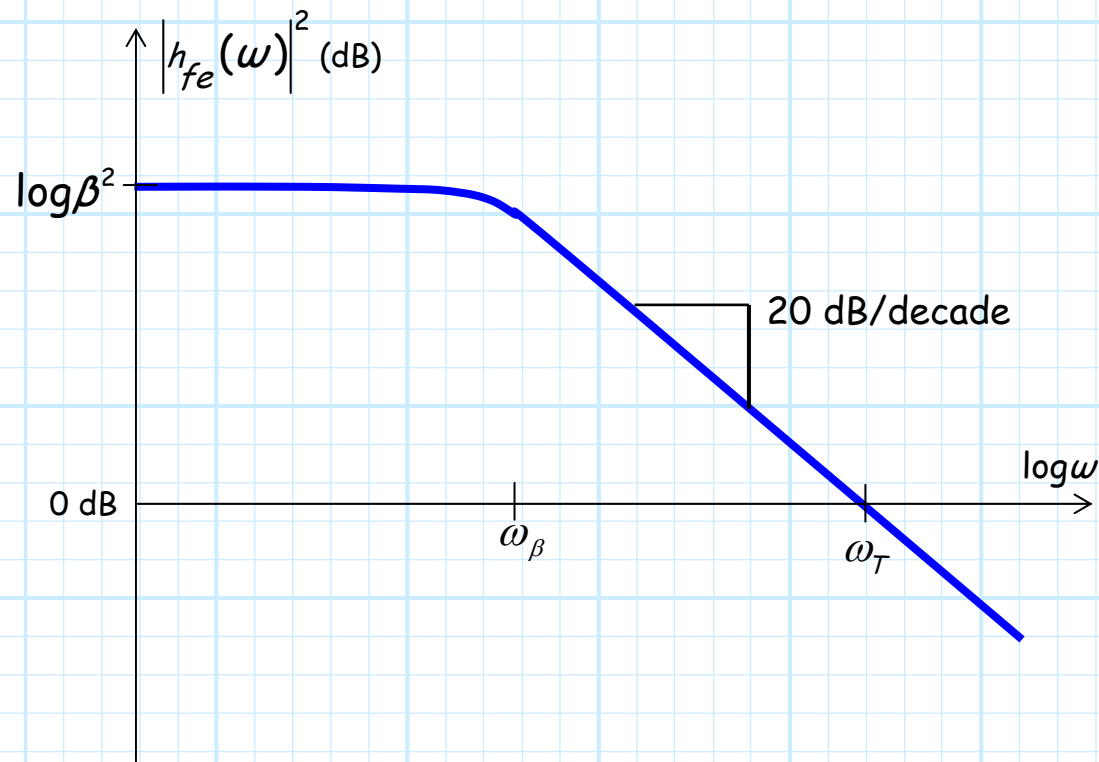

We see that for frequencies **less** than the 3 dB break frequency, the value of $h_{fe}(\omega)$ is approximately equal to **beta**:

$$h_{fe}(\omega) \approx \beta \quad \omega < \omega_\beta$$

This should SO remind you of op-amps

Note then for frequencies greater than this break frequency:

$$h_{fe}(\omega) = \frac{\beta}{1 + j\omega/\omega_\beta}$$
$$\approx j\frac{\beta\omega_\beta}{\omega} \quad \omega > \omega_\beta$$

Note then that $|h_{fe}(\omega)| = 1$ when $\omega = \beta\omega_\beta$.

We can thus define this frequency as ω_T , the **unity-gain** frequency:

$$\omega_T \doteq \beta\omega_\beta$$

so that:

$$|h_{fe}(\omega = \omega_T)| = 1.0$$

Déjà vu; all over again

We can therefore state that:

$$|h_{fe}(\omega)| \approx \frac{\beta \omega_{\beta}}{\omega} = \frac{\omega_T}{\omega} \quad \omega > \omega_{\beta}$$

and also that:

$$|h_{fe}(\omega)| \approx \beta \quad \omega < \omega_{\beta}$$