

5.9 Frequency Response of the Common-Emitter Amp

Reading Assignment: 491-503

Amplifiers made with BJTs are similar to amplifiers made with op-amps—the both exhibit **finite bandwidth**.

HO: AMPLIFIER BANDWIDTH

The gain within the bandwidth is usually constant with respect to frequency—we call this value the **mid-band gain**.

HO: MID-BAND GAIN

Large capacitors (e.g., C_{OUS}) determine the low-frequency limit of amplifier bandwidth. We can explicitly determine this value by analyzing the **low-frequency** small-signal circuit.

HO: THE LOW-FREQUENCY RESPONSE

Parasitic capacitors (e.g., C_{π}) determine the high-frequency limit of amplifier bandwidth. We can explicitly determine this value by analyzing the **high-frequency** small-signal circuit.

HO: THE HIGH-FREQUENCY RESPONSE

Amplifier Bandwidth


BJT amplifiers are band-limited devices—in other words, they exhibit a **finite bandwidth**.

Q: ???

A: Say the input to a BJT small-signal amplifier is **the** eigen function of **linear**, time-invariant system:

$$V_{in} \cos \omega t = V_{in} \operatorname{Re} \{ e^{-j\omega t} \}$$

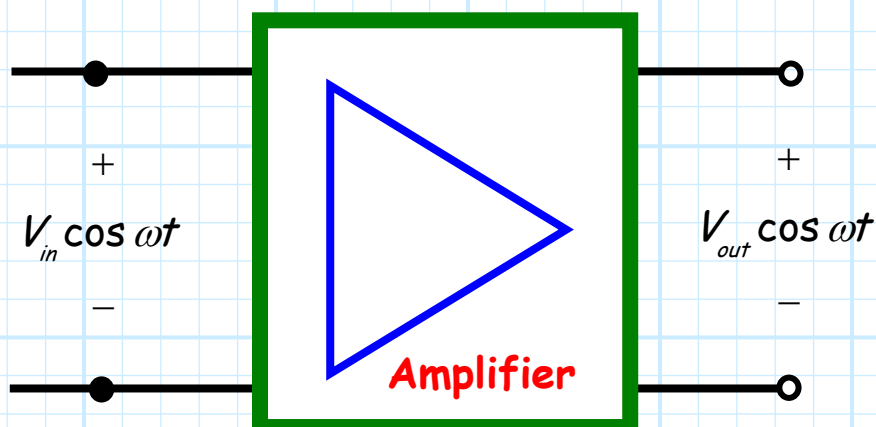Since the small-signal BJT amp is (approximately) a **linear** system, the output will likewise be **the** eigen function—an **undistorted** sinusoidal function of precisely the same frequency ω as the input!



Q: *Of course that's true! We know that:*

$$v_{out}(t) = A_{vo} v_{in}(t)$$

Therefore the magnitudes of the input and output sinusoids are related as:


$$V_{out} = A_{vo} V_{in}$$

Right?

A: Not necessarily!

The small-signal, open-circuit voltage gain of a BJT amplifier depends on the frequency ω of the input signal!

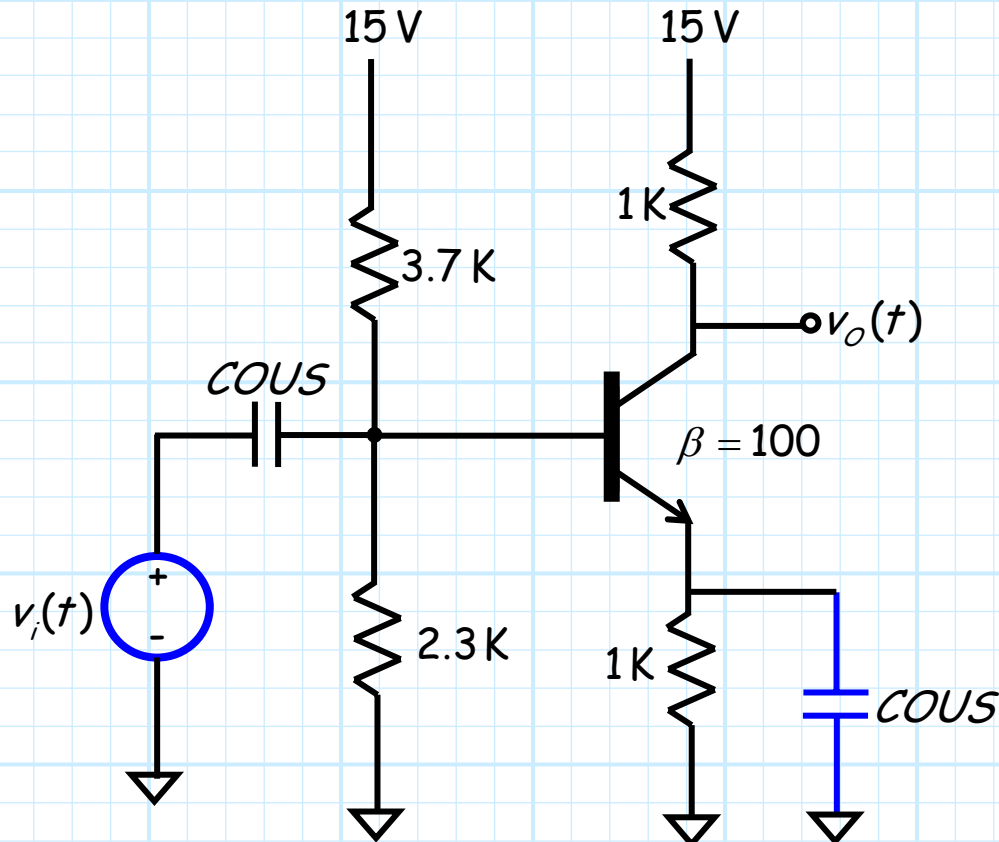Q: Huh!?! We determined earlier that the small-signal voltage gain of this amplifier:



was:

$$A_{vo} = \frac{V_o}{V_i} = -200$$

So then if the small-signal input is:

$$v_i(t) = V_{in} \cos \omega t$$

isn't the small-signal output simply:

$$v_o(t) = -200 V_{in} \cos \omega t \quad ??????????$$

A: Maybe—or maybe not!

Again, the gain of the amplifier is **frequency dependent**. We find that if ω is **too high** (i.e., large) or **too low** (i.e., small), then the output might be much less than the 200 times larger than the input (e.g., only 127.63 times larger than the input—Doh!).

Now, the signal frequencies ω for which

$$v_o(t) = -200 V_{in} \cos \omega t$$

is an **accurate** statement, are frequencies that are said to lie **within the bandwidth** of this amplifier (ω is just right!).


Conversely, frequencies ω for which:

$$v_o(t) \neq -200 V_{in} \cos \omega t$$

are frequencies ω that lie **outside** this amplifier's bandwidth.

Fortunately, the frequencies that compose an amplifier's bandwidth typically form a **continuum**, such that the frequencies outside this bandwidth are either **higher** or **lower** than all frequencies within the bandwidth.

Perhaps a **plot** would help.

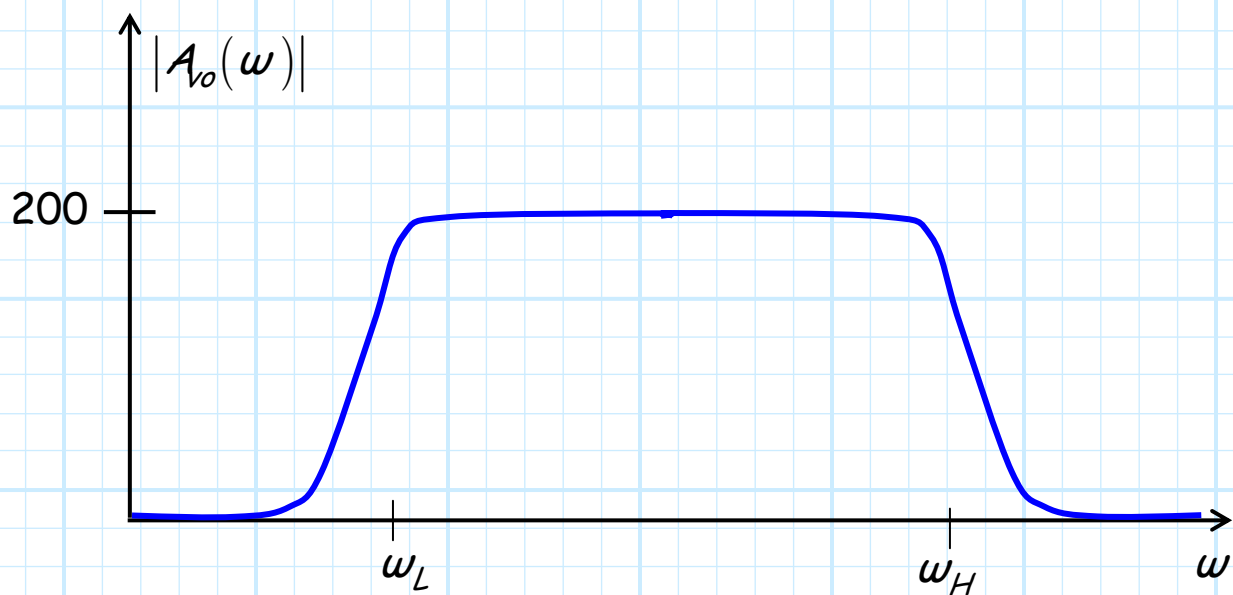

The frequencies **between** ω_L and ω_H thus lie within the **bandwidth** of the amplifier. The gain within the bandwidth is sometimes referred to as the **midband gain**.


For signals with frequencies less than ω_L (f_L), the amplifier gain will be **less** than the midband gain—likewise for frequencies greater than ω_H (f_H).

Q: So what then is the value:

$$A_{vo} = \frac{v_o}{v_i} = -200$$

determined for the example amplifier? It doesn't seem to be a function of frequency!

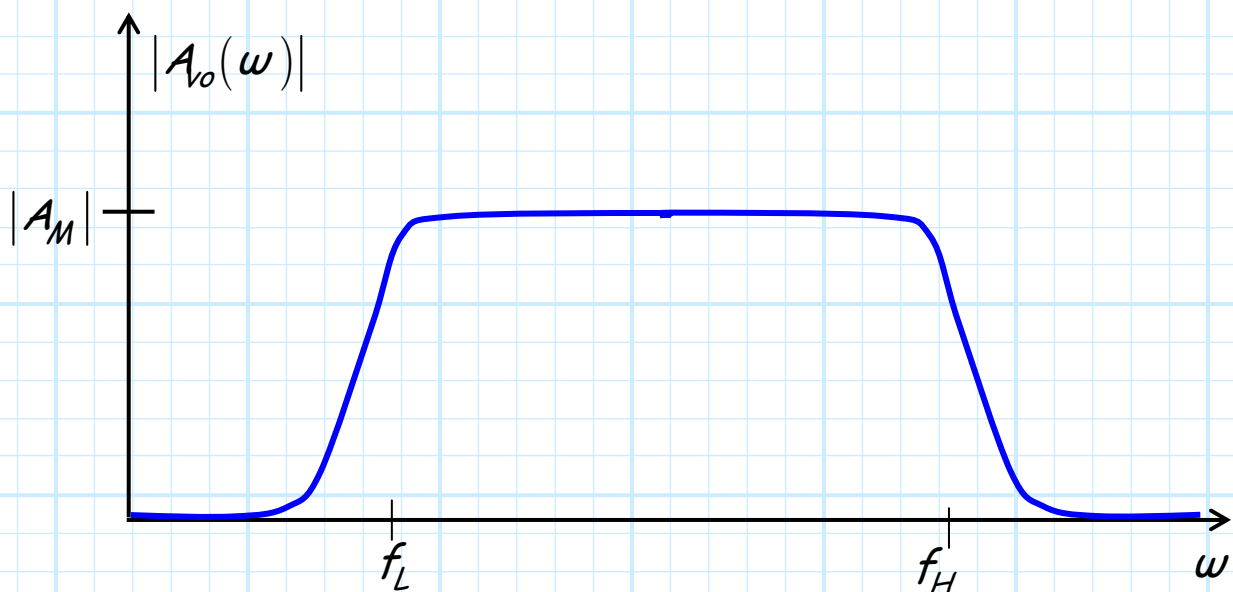A: The value -200 calculated for this amplifier is the **midband gain**—it's the gain exhibited for all signals that lie within the amplifier bandwidth. Your **book** at times uses the variable A_M to denote this value:



Q: So it's actually the **midband gain** that we've been determining from our small-signal circuit analysis (e.g. $A_M = -200$)?

A: That's **exactly** correct!

Q: *So how do we determine the frequency dependent gain $A_{vo}(\omega)$? More specifically, how do we determine midband gain A_M , along with f_L and f_H ?*

A: The function $A_{vo}(\omega)$ is simply the **eigen value** of the **linear operator** relating the small-signal input and the small signal output:


$$v_o(t) = \mathcal{L}\{v_i(t)\} \quad \Rightarrow \quad V_o(\omega) = A_{vo}(\omega) V_i(\omega)$$

Q: *Yikes! How do we determine the eigen value of this linear operator?*

A: We simply **analyze** the small-signal circuit, determining $V_o(\omega)$ in terms of $V_i(\omega)$.


Specifically, we must **explicitly** consider the capacitance in the small-signal amplifier—**no longer** can we make **approximations!**

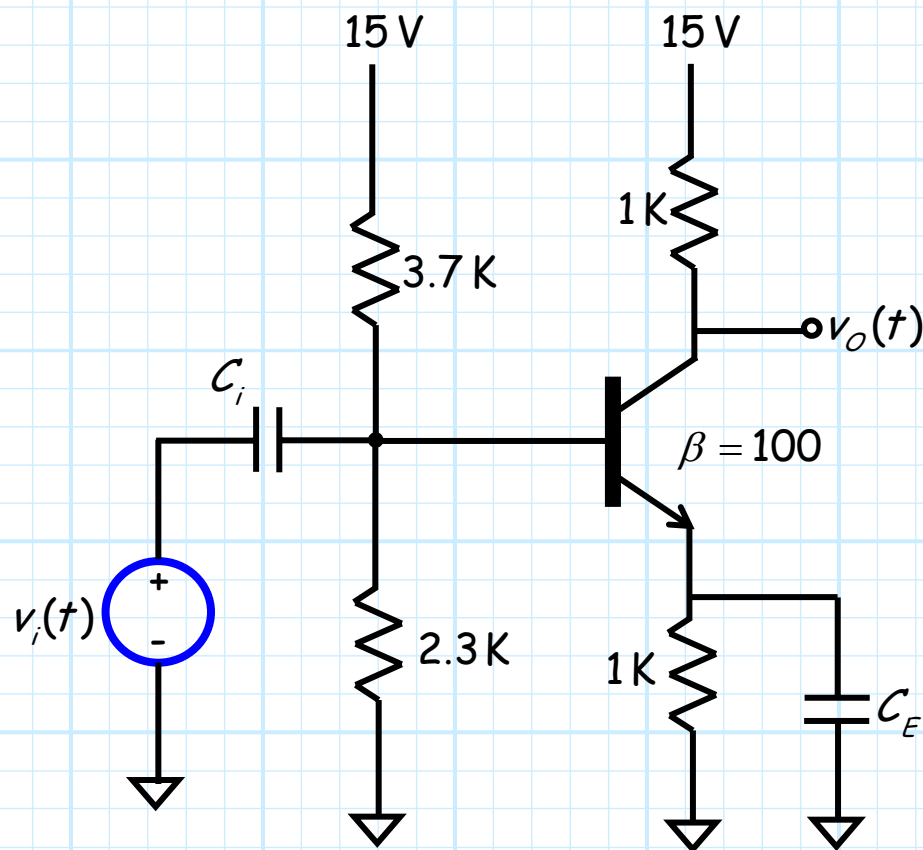So, instead of **vaguely** labeling large capacitors as **Capacitors Of Unusual Size**, let's explicitly consider the **exact values** of these large capacitors:



Likewise, we must consider the **parasitic capacitances** of the BJT—specifically C_μ and C_π .

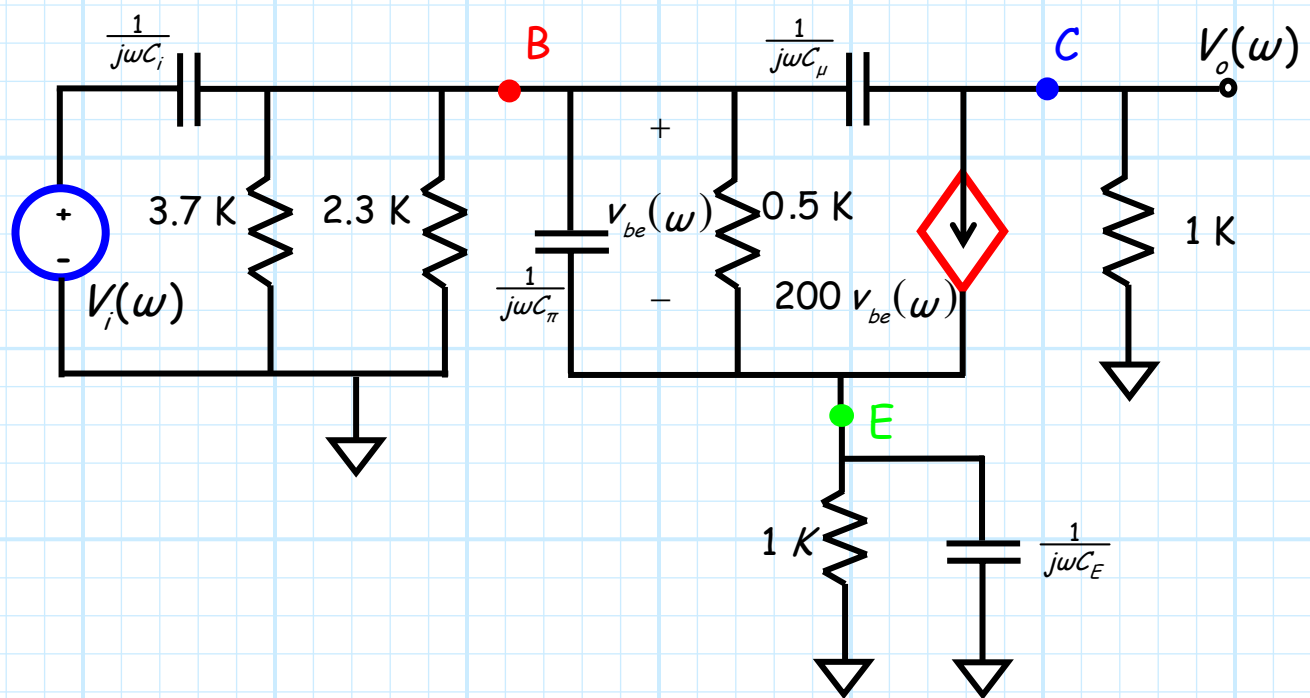The **small-signal circuit**—when we explicitly consider these capacitances—is thus:



We **analyze** this circuit to determine $V_o(\omega)$, and then the eigen value—the small-signal gain—is determined as:

$$A_{v_o}(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

Q: So what again is the meaning of $V_i(\omega)$ and $V_o(\omega)$?

A: It's the **Fourier transform** of $v_i(t)$ and $v_o(t)$!

$$V_i(\omega) = \int_{-\infty}^{\infty} v_i(t) e^{j\omega t} dt \quad \text{and} \quad V_o(\omega) = \int_{-\infty}^{\infty} v_o(t) e^{j\omega t} dt$$

Q: So—I can't recall—what's the **relationship** between $v_i(t)$ and $v_o(t)$?

A: If:

$$V_o(\omega) = A_{v_o}(\omega) V_i(\omega)$$

Then in the time domain, we find that the input and output are related by the **always enjoyable convolution** integral!!!

$$v_o(t) = \int_{-\infty}^{\infty} g(t-t') v_i(t') dt'$$

where the **impulse response** of the amplifier is of course:

$$g(t) = \int_{-\infty}^{\infty} A_{v_o}(\omega) e^{-j\omega t} d\omega$$

Q: *What the heck? What happened to solutions like:*

$$v_o(t) = -200 v_i(t) \quad ??$$

A: This result implies that the **impulse response** of the amplifier is:

$$g(t) = -200 \delta(t)$$

Such that:

$$\begin{aligned} v_o(t) &= \int_{-\infty}^{\infty} g(t-t') v_i(t') dt' \\ &= -200 \int_{-\infty}^{\infty} \delta(t-t') v_i(t') dt' \\ &= -200 v_i(t) \end{aligned}$$

Q: You say that the result:

$$v_o(t) = -200 v_i(t)$$

"implies" that the impulse response of the amplifier is:

$$g(t) = -200 \delta(t)$$

Are you saying the impulse response of the common-emitter example is **not** this function?

A: It is definitely **not** that function. The impulse response

$$g(t) = -200 \delta(t)$$

is **ideal**—the impulse response of an amplifier with an **infinite bandwidth!**

Q: So *all* our small-signal analysis up to this point has been incorrect and **useless**???

A: Not at all! The small-signal gain we have been evaluating up to this point (e.g., -200) is the amplifier **midband gain** A_M .

As long as the small-signal input $v_i(t)$ **resides completely** within the amplifier **bandwidth**, then the output will be:

$$v_o(t) = -200 v_i(t)$$

The **problem** occurs when the input signal lies—at least partially—**outside** the amplifiers bandwidth.

In that case, we find that:

$$v_o(t) \neq -200 v_i(t)$$


And instead:

$$v_o(t) = \int_{-\infty}^{\infty} g(t-t') v_i(t') dt'$$

where:

$$g(t) = \int_{-\infty}^{\infty} A_v(\omega) e^{-j\omega t} d\omega$$

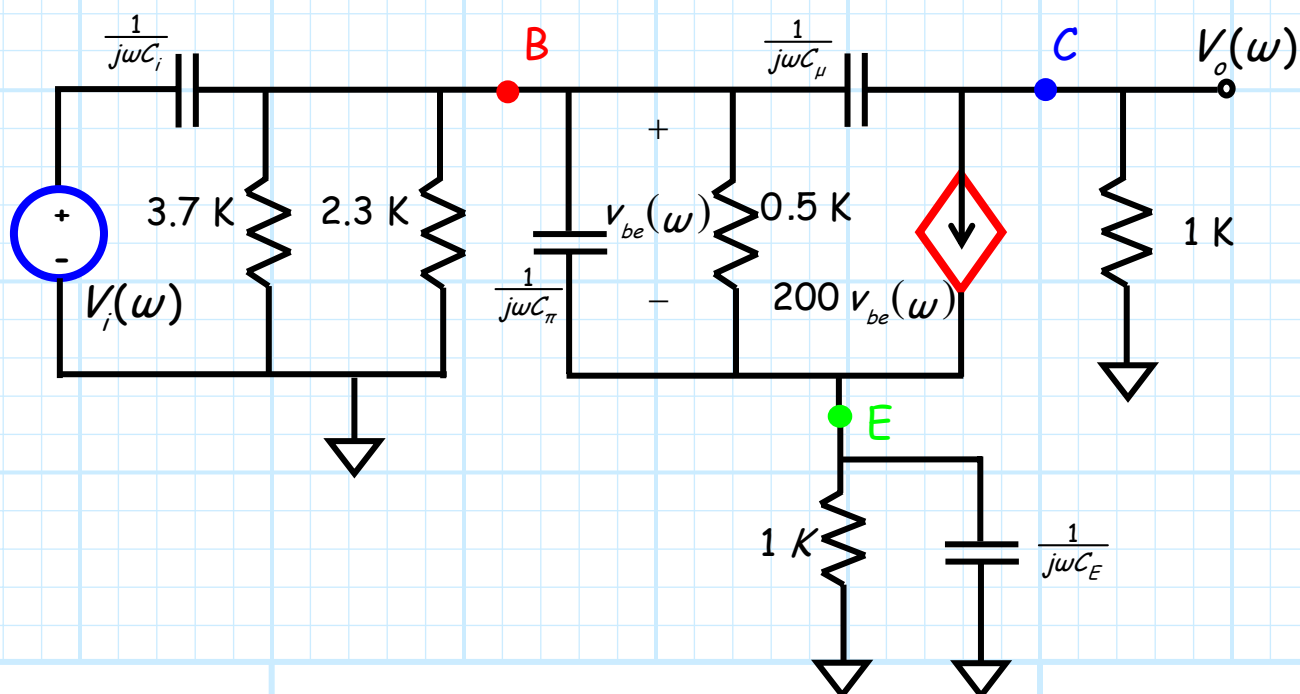
and the eigen value $A_v(\omega) = V_o(\omega)/V_i(\omega)$ is determined by evaluating this small-signal circuit:



Q: What do you mean when you say that a signal lies "**within** the amplifier bandwidth" or "**outside** the amplifier bandwidth? How can we tell?


A: Use the Fourier Transform!

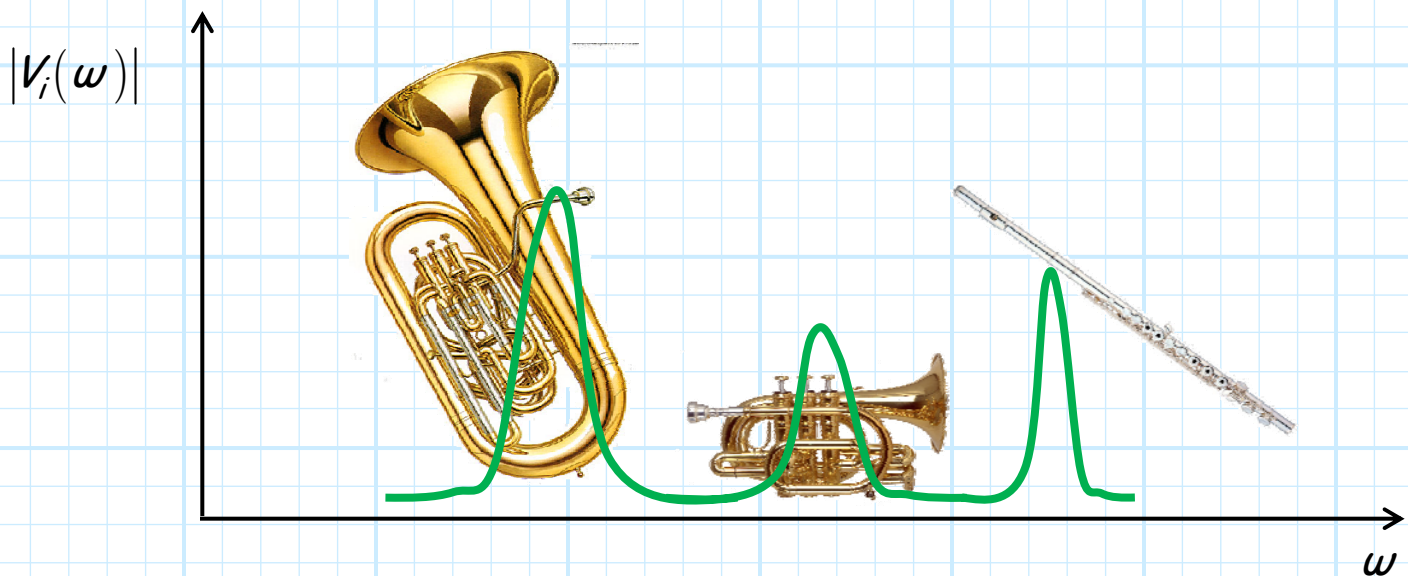If we plot the magnitude of the Fourier Transform $V_i(\omega)$ of the input signal $v_i(t)$, we can see the **spectrum** of the input signal:



For example, if you are attempting to amplify a signal representing the audio of **symphonic music**, the spectrum $|V_i(\omega)|$ will include **low-frequency** signals (e.g., from the tubas), **mid-range** frequency signals (e.g., from the trumpets), and **high-frequency** signals (e.g., from the flutes).

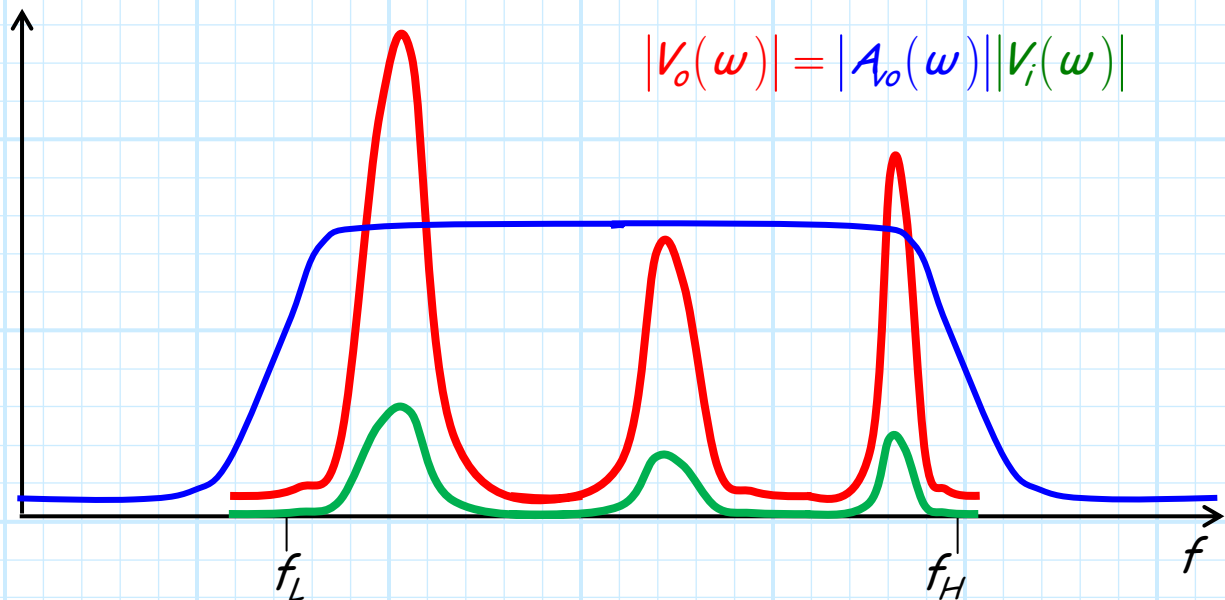Now, if it is your desire to reproduce **exactly** this music at the output of your amplifier, then the amplifier bandwidth must be **wide enough** to include **all** these spectral components !




For the case above, the input signal resides **completely** within the bandwidth of the amplifier (i.e., between f_L and f_H), and so we find (for $A_M = -200$) that:

$$|V_o(\omega)| = (200) |V_i(\omega)|$$

and:

$$v_o(t) = -200 v_i(t)$$

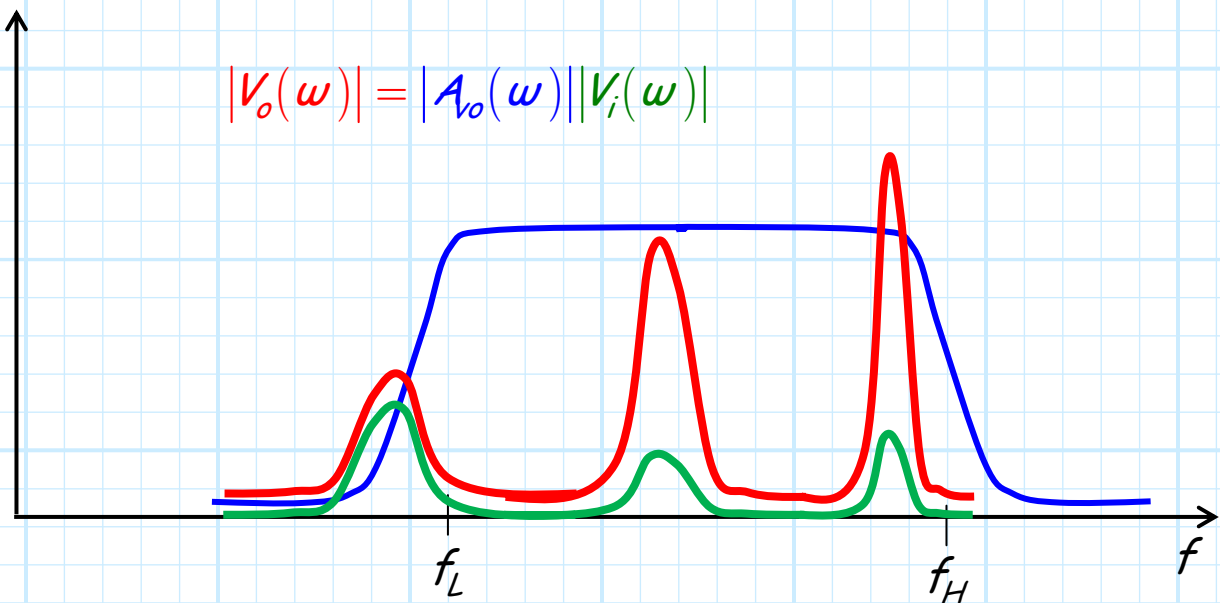However, if the input spectrum resides (at least partially) **outside** the amplifier bandwidth, e.g.:



then we find that:

$$|V_o(\omega)| \neq (200) |V_i(\omega)|$$

and:

$$v_o(t) \neq -200 v_i(t) !!!!$$

Instead, we find the more general (and more **difficult!**) expressions:

$$V_o(\omega) = A_{v_o}(\omega) V_i(\omega)$$

and:

$$v_o(t) = \int_{-\infty}^{\infty} g(t-t') v_i(t') dt'$$

where the **impulse response** of the amplifier is:

$$g(t) = \int_{-\infty}^{\infty} A_{vo}(\omega) e^{-j\omega t} d\omega$$

Q: *So just what **causes** this amplifier to have a finite bandwidth?*

A: For mid-band frequencies f_m (i.e., between $f_L < f_m < f_H$), we will find that the Capacitors Of Unusual Size exhibit an impedance that is pretty small—approximately an **AC short** circuit:

$$|Z_{COUS}(\omega_m)| = \frac{1}{\omega_m C_{ous}} \cong 0$$

Likewise, the **tiny parasitic capacitances** C_μ and C_π exhibit an impedance that is very large for mid-band frequencies—approximately an **open** circuit:

$$|Z_{C_\pi}(\omega_m)| = \frac{1}{\omega_m C_\pi} \cong \infty$$

However, when the signal frequency ω drops too low, the COUS will **no longer** be a small-signal short.


The result is that the amplifier **gain is reduced**—the values of the COUS determine the **low-end amplifier bandwidth** f_L .

Likewise, when the signal frequency ω is **too high**, the parasitic caps will **no longer** be a small-signal open.


The result is that the amplifier **gain is reduced**—the values of the **parasitic capacitors** determine the **high-end amplifier bandwidth** f_H .

Mid-band Gain

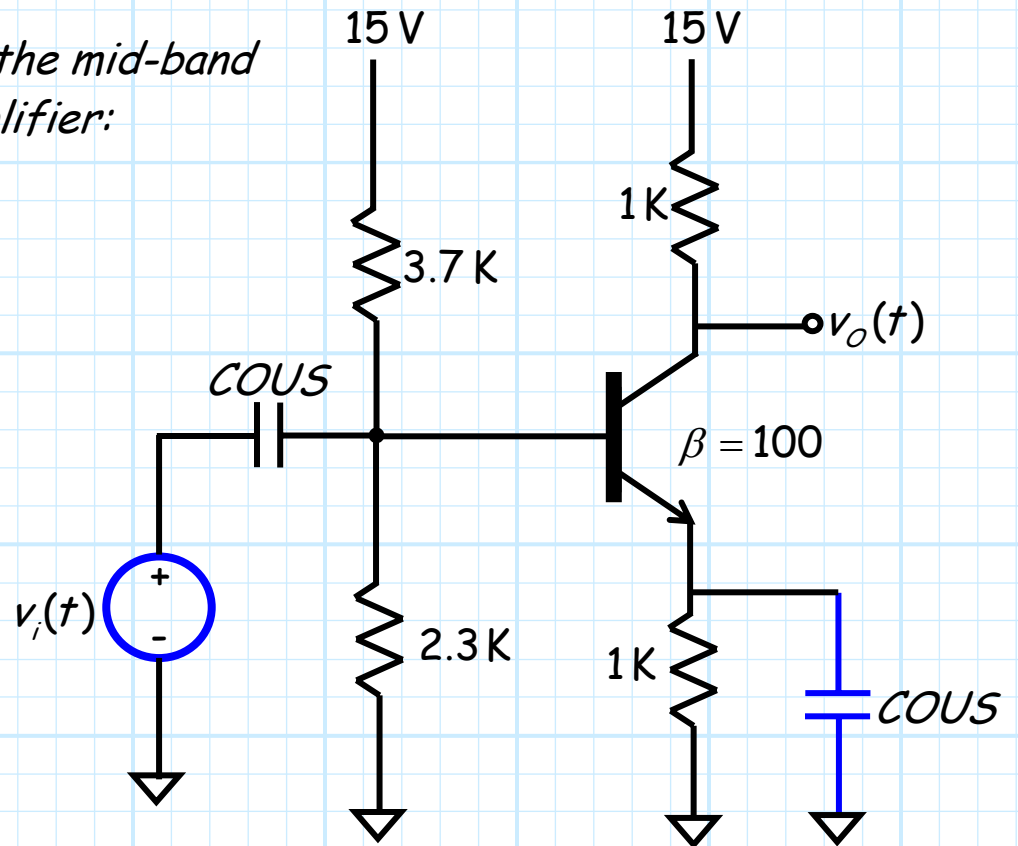Q: So, to find the mid-band gain of **this** amplifier:



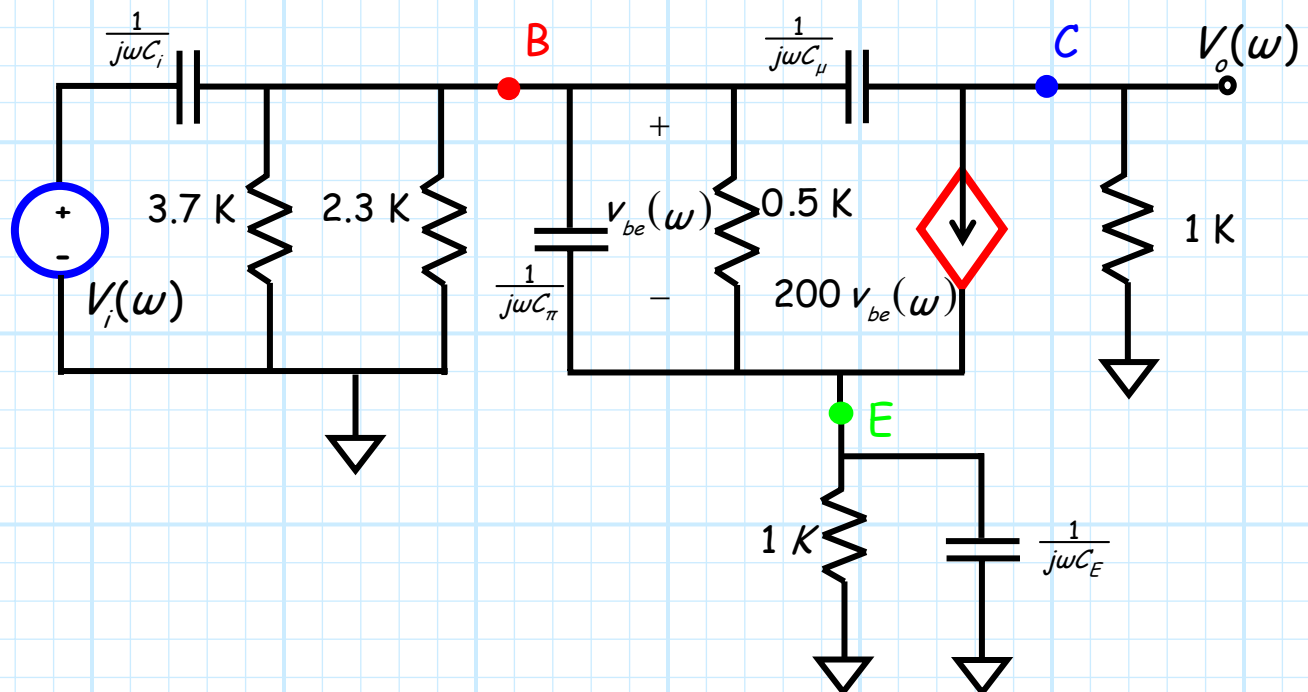
we must find the analyze this small signal circuit:



to determine:

$$A_{vo}(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

and then plotting the magnitude:

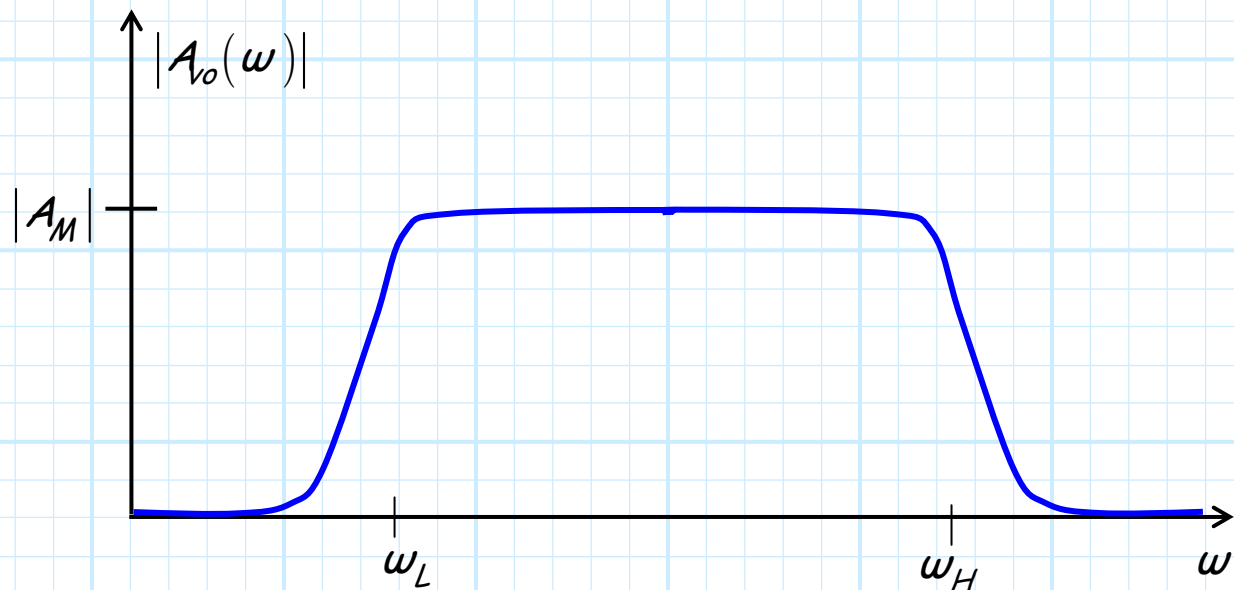


we determine mid-band gain A_M , right?

A: You could do all that, but there is an easier way.


Recall the midband gain is the value of $|A_{vo}(\omega)|$ for frequencies within the amplifier bandwidth. For those frequencies, the AC coupling capacitors (i.e., COUS) are approximate AC short-circuits (i.e., very low impedance).

Likewise, for the signal frequencies within the amplifier bandwidth, the parasitic BJT capacitances are approximate AC open-circuits (i.e., very high impedance).

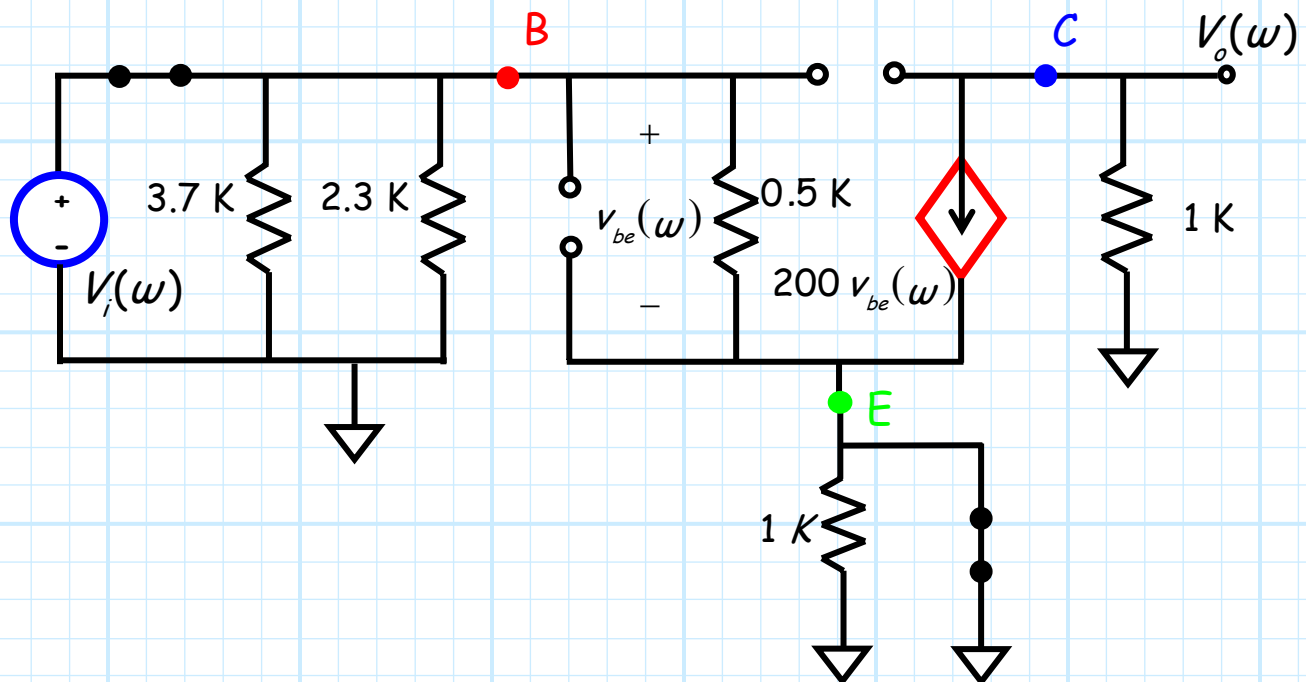Thus, we can apply these approximations to the capacitors in our small-signal circuit:



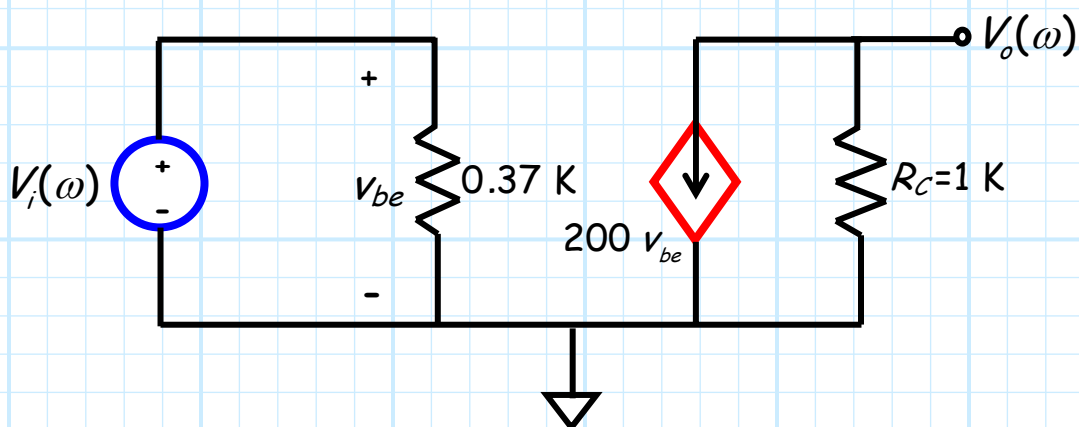Now simplifying this circuit (look, no capacitors!):



Q: *Hey wait! Isn't this the same small-signal circuit that we analyzed earlier, where we found that:*

$$v_o(t) = -200 v_i(t) \quad ??$$

A: It is exactly!

All of the small-signal analysis that we performed **previously** (i.e., the circuits with **no capacitors!**) actually provided us with the **mid-band** amplifier gain.

Taking the Fourier transform of the equation above:

$$\begin{aligned} V_o(\omega) &= -200 V_i(\omega) \\ &= e^{j\pi} 200 V_i(\omega) \end{aligned}$$


Thus, the midband gain of this amplifier is:

$$A_M = -200 = e^{j\pi} 200$$

Low-Frequency Response

Q: OK, I see how to determine mid-band gain, but what about determining amplifier **bandwidth**?

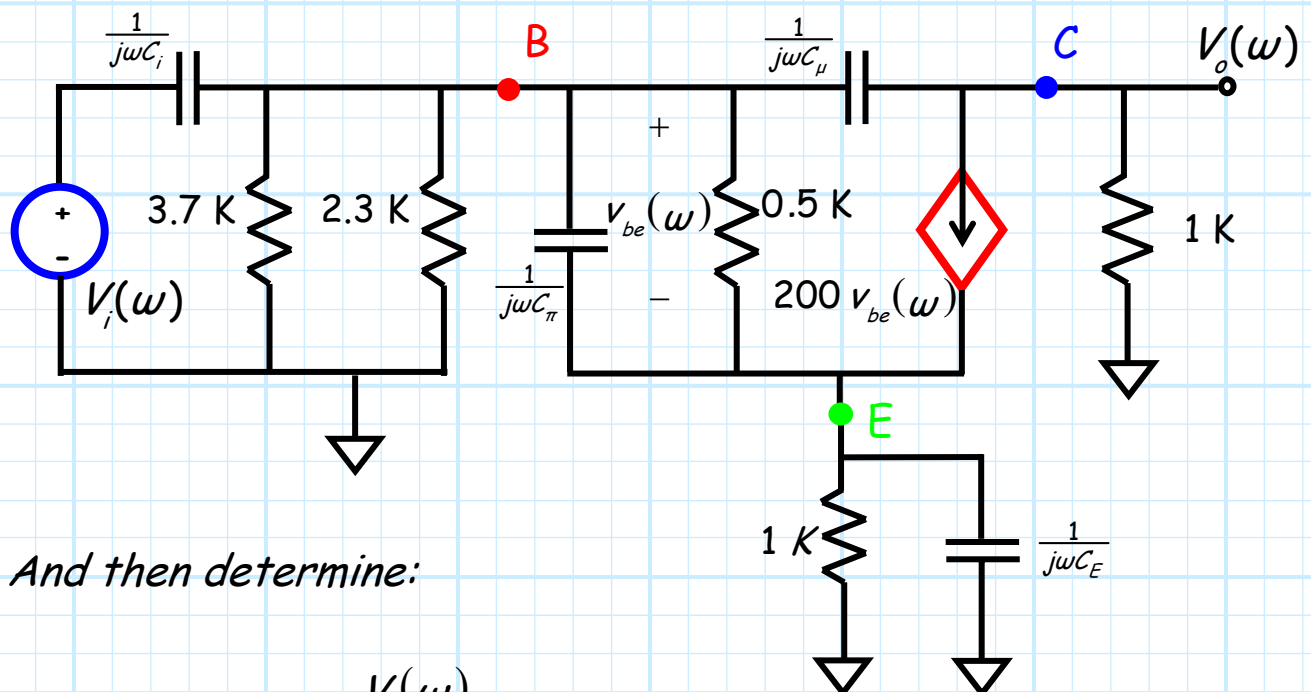
It seems like I have no alternative but to analyze the exact small-signal circuit (explicitly considering all capacitances):



And then determine:

$$A_{vo}(\omega) = \frac{V_o(\omega)}{V_i(\omega)}$$

and then **plot** the magnitude:

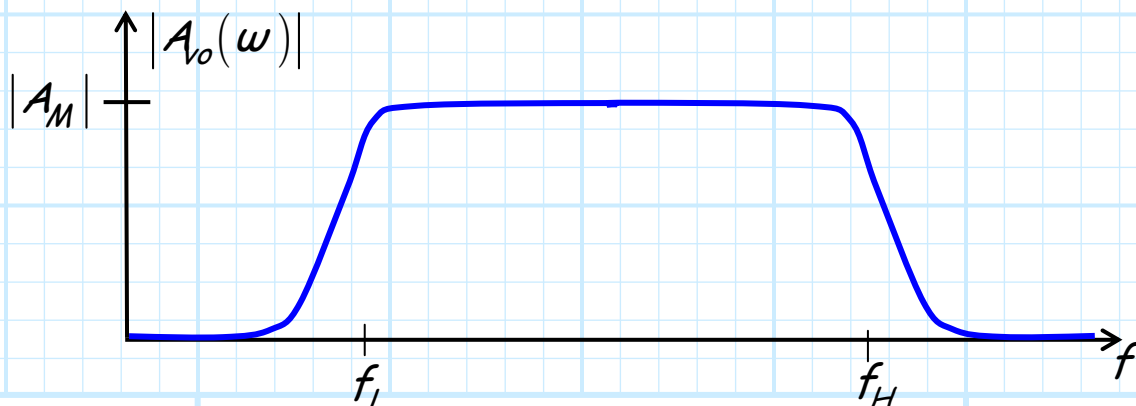

And then from the plot determine the amplifier bandwidth (i.e., determine f_L and f_H)?

A: You could do all that, but there is an easier way.

An amplifier frequency response $A_o(\omega)$ (i.e., its eigen value!) can generally be expressed as the product of **three** distinct terms:

$$A_o(\omega) = F_L(\omega) A_M F_H(\omega)$$

The middle term is of course the **mid-band gain**—a number that is not frequency dependent.

The function $F_L(\omega)$ describes the **low-frequency response** of the amplifier—from it we can determine the lower cutoff frequency f_L .

Conversely, the function $F_H(\omega)$ describes the **high-frequency response** of the amplifier—from it we can determine the upper cutoff frequency f_H .


Q: *So just how do we determine these functions $F_L(\omega)$ and $F_H(\omega)$??*

A: The low-frequency response $F_L(\omega)$ is dependent **only** on the large capacitors (COUS) in the amplifier circuit. In other

words the parasitic capacitances have **no affect** on the low-frequency response.


Thus, we simply "ignore" the **parasitic** capacitances when determining $F_L(\omega)$!

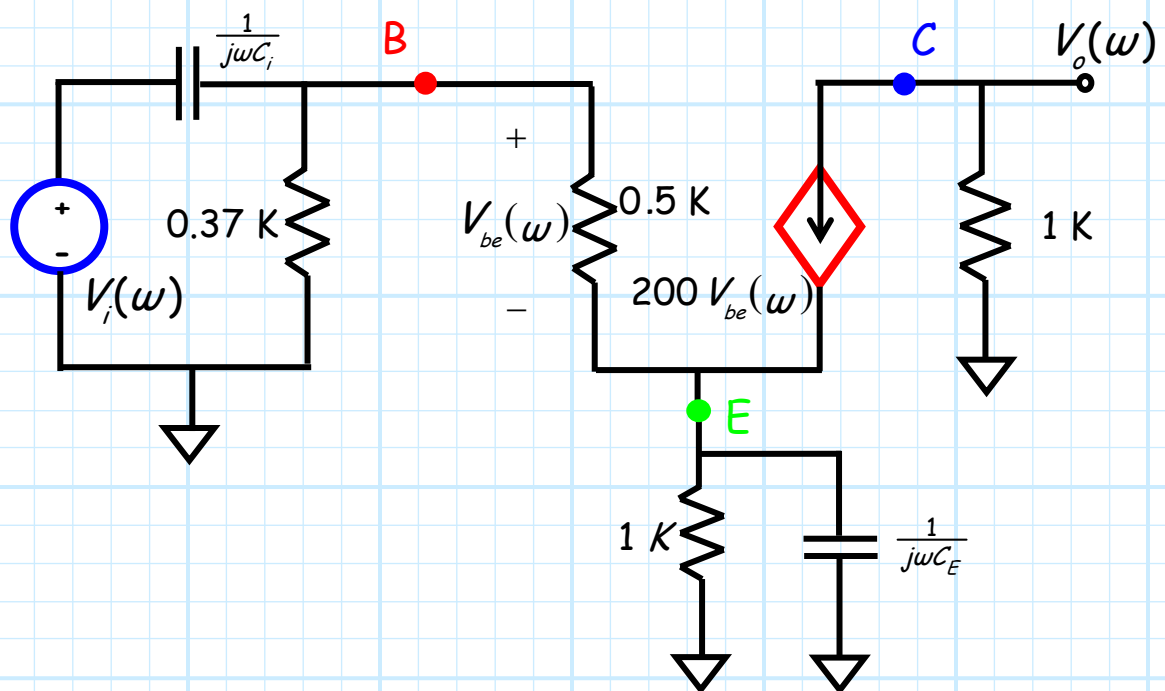For example, say we include the COUS in our common-emitter example, but **ignore** C_μ and C_π . The resulting small-signal circuit is:



To simplify this analysis, we first determine the **Thevenin's** equivalent circuit of the portion of the circuit connected to the base.

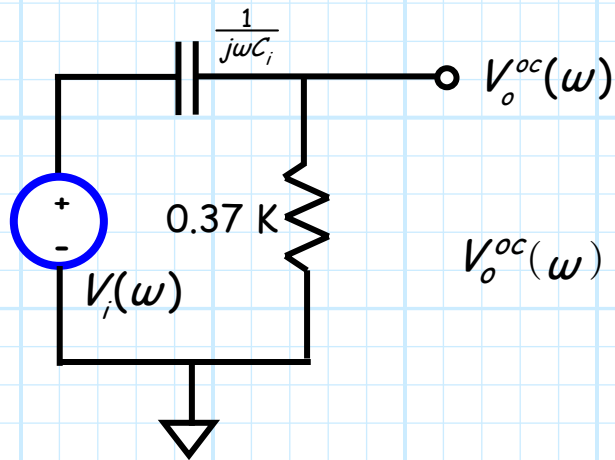
We start by finding the **open-circuit voltage**:



$$V_o^{oc}(\omega) = V_i(\omega) \left(\frac{0.37}{0.37 + \frac{1}{j\omega C_i}} \right)$$


$$= V_i(\omega) \left(\frac{j\omega(0.37)C_i}{1 + j\omega(0.37)C_i} \right)$$

And the short-circuit output current is:

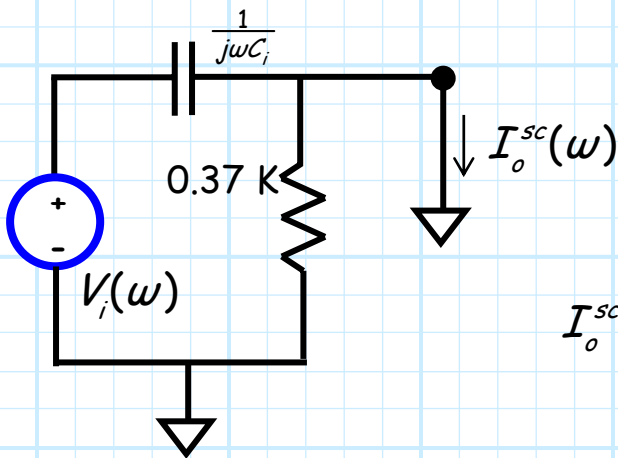

$$I_o^{sc}(\omega) = \frac{V_i(\omega)}{\frac{1}{j\omega C_i}} = V_i(\omega) (j\omega C_i)$$

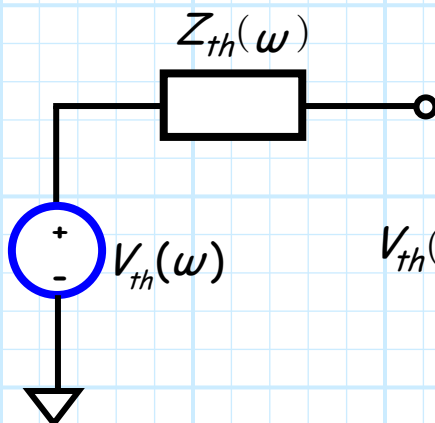And thus the Thevenin's equivalent source is:



$$V_{th}(\omega) = V_o^{oc}(\omega)$$


$$= V_i(\omega) \left(\frac{j\omega(0.37)C_i}{1 + j\omega(0.37)C_i} \right)$$

$$\begin{aligned}
 Z_{th}(\omega) &= \frac{V_o^{oc}(\omega)}{I_o^{sc}(\omega)} \\
 &= \left(\frac{j\omega(0.37)C_i}{1 + j\omega(0.37)C_i} \right) \left(\frac{1}{j\omega C_i} \right) \\
 &= \frac{(0.37)}{1 + j\omega(0.37)C_i}
 \end{aligned}$$

Likewise, the two parallel elements on the emitter terminal can be combined:

$$Z_E(\omega) = \frac{\frac{1}{j\omega C_E}}{1 + \frac{1}{j\omega C_E}} = \frac{1}{1 + j\omega C_E}$$

Thus, the small-signal circuit is now:

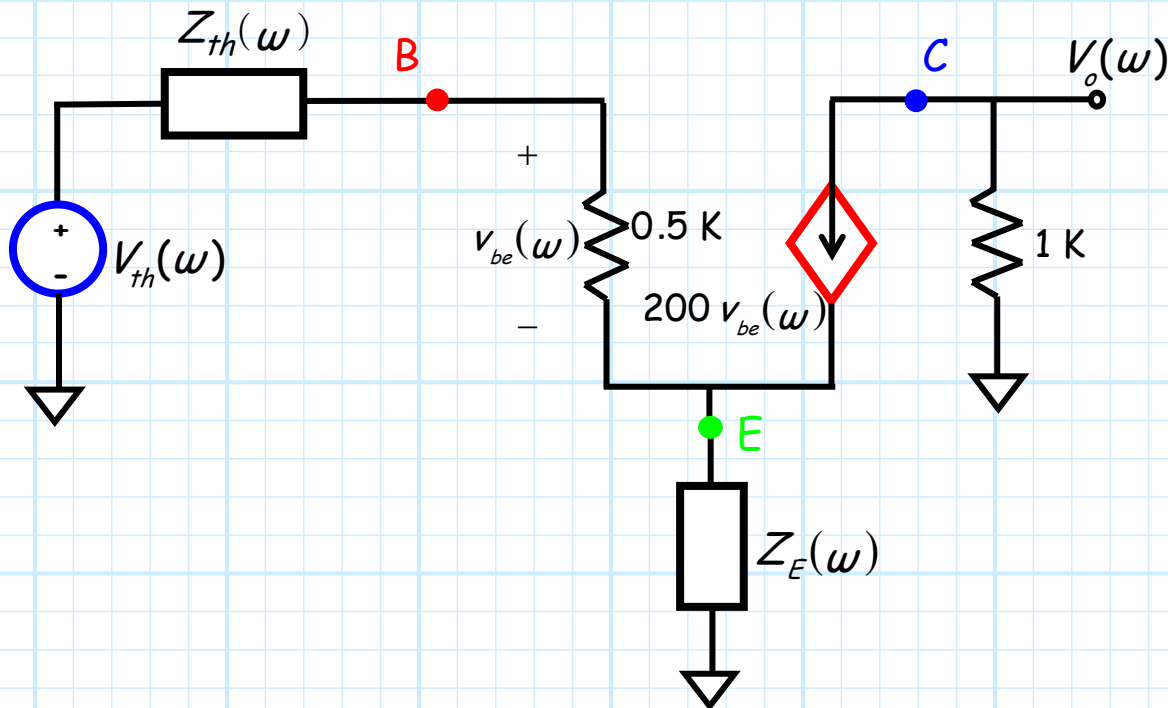

From KVL:

$$0 + V_{th} - I_b (Z_{th} + 0.5) - (\beta + 1) I_b Z_E = 0$$

$$\Rightarrow I_b = \frac{V_{th}}{Z_{th} + 0.5 + 101Z_E}$$

From Ohm's Law:

$$V_{be} = 0.5I_b$$

Therefore:

$$\begin{aligned} V_o(\omega) &= -200 V_{be}(1) \\ &= -200(0.5) \frac{V_{th}(\omega)}{Z_{th} + 0.5 + 101Z_E} \\ &= V_{th}(\omega) \left(\frac{-100}{Z_{th} + 0.5 + 101Z_E} \right) \end{aligned}$$

Inserting the expressions for the Thevenin's equivalent source, as well as Z_E .

$$\begin{aligned} V_o(\omega) &= V_{th}(\omega) \left(\frac{-100}{Z_{th} + 0.5 + 101Z_E} \right) \\ &= V_i(\omega) \left(\frac{j\omega(0.37)C_i}{1 + j\omega(0.37)C_i} \right) \left(\frac{-200}{\frac{2(0.37)}{1 + j\omega(0.37)C_i} + 1 + \frac{202}{1 + j\omega C_E}} \right) \end{aligned}$$

Now, it can be shown that:



$$\frac{1}{\frac{2(0.37)}{1 + j\omega(0.37)C_i} + 1 + \frac{202}{1 + j\omega C_E}} \approx \frac{j\omega(C_E/203)}{1 + j\omega(C_E/203)}$$

Therefore:

$$V_o(\omega) = V_i(\omega) \left(\frac{j\omega(0.37)C_i}{1 + j\omega(0.37)C_i} \right) \left(\frac{j\omega(C_E/203)}{1 + j\omega(C_E/203)} \right) (-200)$$

And so:

$$A_{v_o}(\omega) = \left(\frac{j\omega(0.37)C_i}{1 + j\omega(0.37)C_i} \right) \left(\frac{j\omega(C_E/203)}{1 + j\omega(C_E/203)} \right) (-200)$$

Now, since we are **ignoring** the parasitic capacitances, the function $F_H(\omega)$ that describes the high frequency response is:

$$F_H(\omega) = 1$$

And so:

$$A_{v_o}(\omega) = F_L(\omega) A_M F_H(\omega) = F_L(\omega) A_M$$

By inspection, we see for this example:

$$A_M = -200 \quad \leftarrow \text{We knew this already!}$$

And:

$$F_L(\omega) = \left(\frac{j\omega(0.37)C_i}{1 + j\omega(0.37)C_i} \right) \left(\frac{j\omega(C_E/203)}{1 + j\omega(C_E/203)} \right)$$

Now, let's define:

$$\omega_{P1} = \frac{1}{0.37C_i} = \frac{2.7}{C_i} \quad \text{and} \quad \omega_{P2} = \frac{203}{C_E}$$

Thus,

$$F_L(\omega) = \left(\frac{j(\omega/\omega_{P1})}{1 + j(\omega/\omega_{P1})} \right) \left(\frac{j(\omega/\omega_{P2})}{1 + j(\omega/\omega_{P2})} \right)$$


Now, functions of the type:

$$\left(\frac{j(\omega/\omega_p)}{1 + j(\omega/\omega_p)} \right)$$

are **high-pass** functions:

$$\left| \frac{j(\omega/\omega_p)}{1 + j(\omega/\omega_p)} \right|^2 = \frac{(\omega/\omega_p)^2}{1 + (\omega/\omega_p)^2}$$

with a **3dB break frequency** of ω_p .

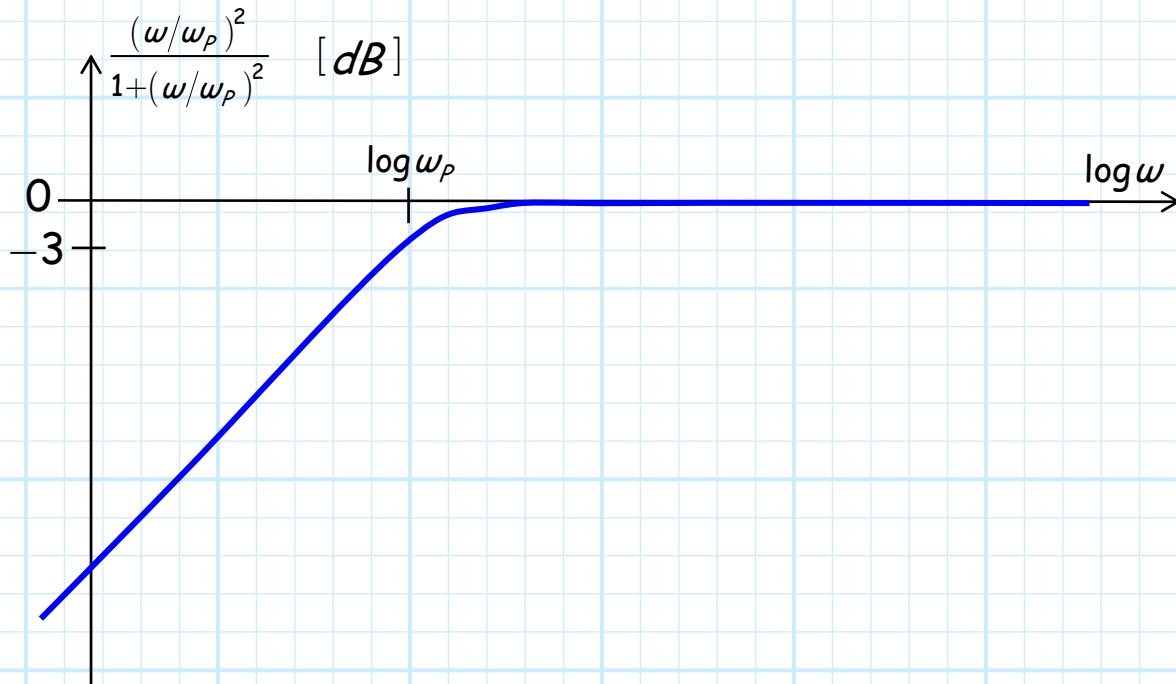

Thus:

$$\frac{(\omega/\omega_p)^2}{1 + (\omega/\omega_p)^2} = \begin{cases} \approx 1.0 & \text{for } \omega > \omega_p \\ 0.5 & \text{for } \omega = \omega_p \\ 0 & \text{for } \omega = 0 \end{cases}$$

As a result, we find that the transfer function:

$$\begin{aligned} A_v(\omega) &= F_L(\omega) A_M \\ &= \left(\frac{j(\omega/\omega_{p1})}{1 + j(\omega/\omega_{p1})} \right) \left(\frac{j(\omega/\omega_{p2})}{1 + j(\omega/\omega_{p2})} \right) (-200) \end{aligned}$$

will be **approximately** equal to the midband gain $A_M = -200$ for all frequencies ω that are greater than **both** ω_{p1} and ω_{p2} .

I.E.,:

$$A_{vo}(\omega) \cong A_M = -200 \quad \text{if } \omega > \omega_{p1} \text{ and } \omega > \omega_{p2}$$

Hopefully, it is **now** apparent (please tell me it is!) that the lower end of the amplifier bandwidth—specified by frequency ω_L —is determined by the **larger** of the two frequencies ω_{p1} and ω_{p2} !

The **larger** of the two frequencies is called the **dominant pole** of the transfer function $F_L(\omega)$.

For our example—comparing the two frequencies ω_{p1} and ω_{p2} :

$$\omega_{p1} = \frac{1}{0.37C_i} = \frac{2.7}{C_i} \quad \text{and} \quad \omega_{p2} = \frac{203}{C_E}$$

it is apparent that the **larger** of the two (the dominant pole!) is likely ω_{p2} —that darn **emitter capacitor** is the key!


Say we want the common-emitter amplifier in this circuit to have a bandwidth that extends down to $f_L = 100 \text{ Hz}$

The emitter capacitor **must** therefore be:

$$2\pi f_L > \omega_{p2} = \frac{203}{C_E}$$


$$\Rightarrow C_E > \frac{203}{2\pi f_L} = \frac{203}{2\pi(1000)} = 32,300\mu F \quad !!!$$

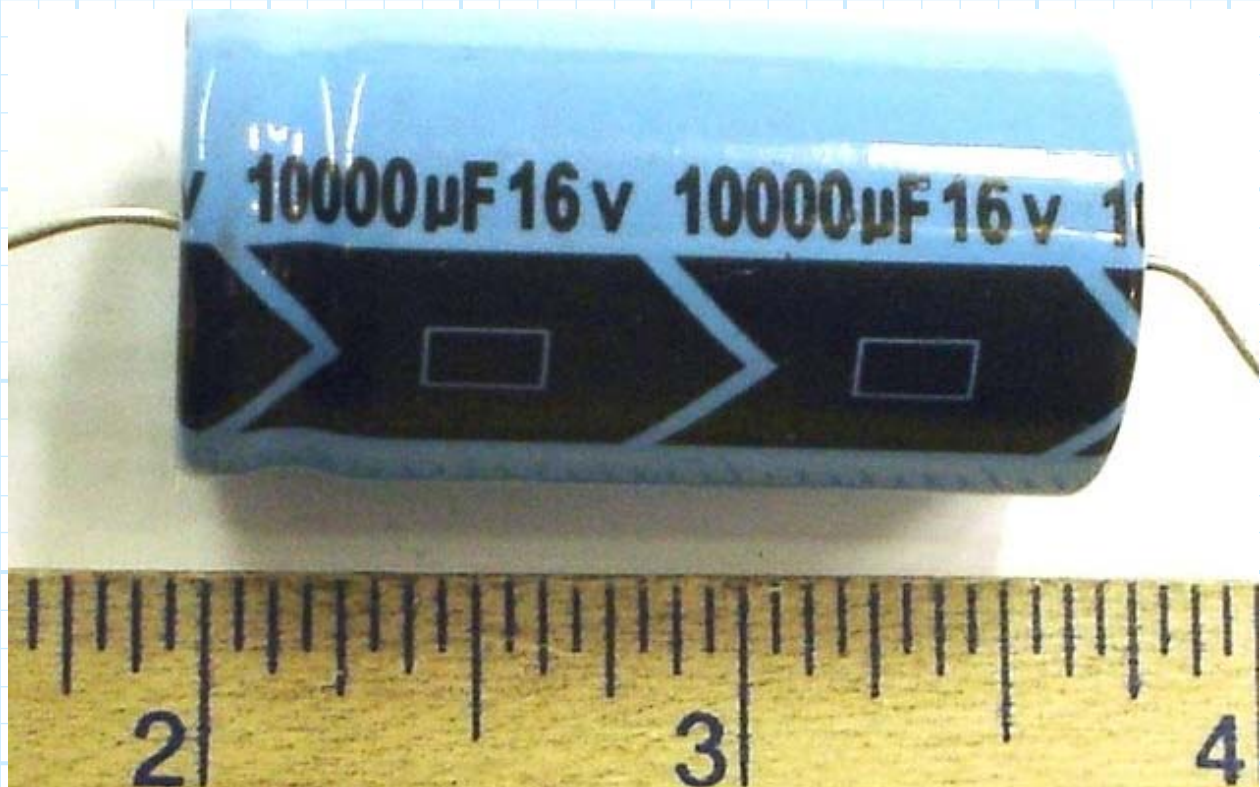This certainly is a **Capacitor Of Unusual Size** !



High-Frequency Response

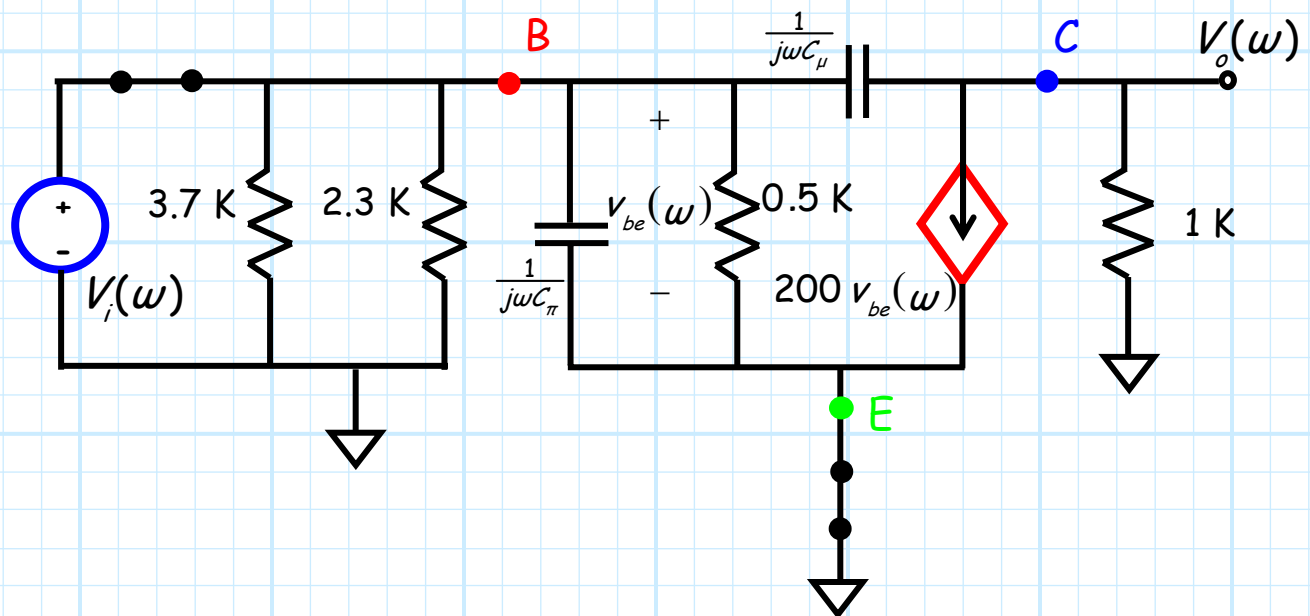To determine the high-frequency response of our example common-emitter amp, we simply consider explicitly the parasitic capacitances in the small-signal model, while approximating the COUS as small-signal short-circuits:



Now, since we are **ignoring** the COUS, the function $F_L(\omega)$ that describes the low-frequency response is:

$$F_L(\omega) = 1$$

And so:

$$A_{vo}(\omega) = F_L(\omega) A_M F_H(\omega) = A_M F_H(\omega)$$

We will find that the high-frequency response will (approximately) have the form.

$$F_H(\omega) = \left(\frac{1}{1 + j(\omega/\omega_{p3})} \right) \left(\frac{1}{1 + j(\omega/\omega_{p4})} \right)$$


Now, functions of the type:

$$\left(\frac{1}{1 + j(\omega/\omega_p)} \right)$$

are **low-pass** functions:

$$\left| \frac{1}{1 + j(\omega/\omega_p)} \right|^2 = \frac{1}{1 + (\omega/\omega_p)^2}$$

with a **3dB break frequency** of ω_p .

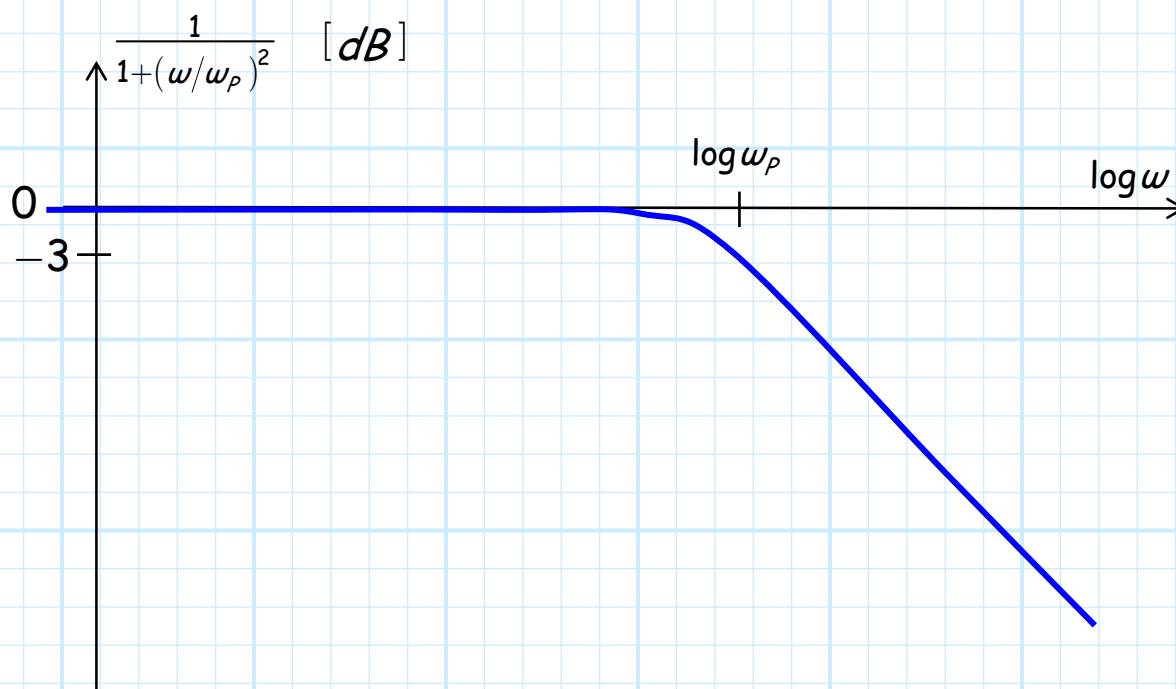

Thus:

$$\frac{1}{1 + (\omega/\omega_p)^2} = \begin{cases} \cong 1.0 & \text{for } \omega < \omega_p \\ 0.5 & \text{for } \omega = \omega_p \\ 0 & \text{for } \omega \rightarrow \infty \end{cases}$$

As a result, we find that the transfer function:

$$\begin{aligned} A_{vo}(\omega) &= A_M F_H(\omega) \\ &= (-200) \left(\frac{1}{1 + j(\omega/\omega_{p3})} \right) \left(\frac{1}{1 + j(\omega/\omega_{p4})} \right) \end{aligned}$$

will be **approximately** equal to the midband gain $A_M = -200$ for all frequencies ω that are less than **both** ω_{p3} **and** ω_{p4} .

I.E.:

$$A_{vo}(\omega) \cong A_M = -200 \quad \text{if } \omega < \omega_{p3} \text{ and } \omega > \omega_{p4}$$

Hopefully, it is **now** apparent (please tell me it is!) that the higher end of the amplifier bandwidth—specified by frequency ω_H —is determined by the **smaller** of the two frequencies ω_{p3} and ω_{p4} !

The **smaller** of the two frequencies is called the **dominant pole** of the transfer function $F_H(\omega)$.

Generally speaking, to **increase** the value ω_H , we must increase the **DC bias currents** of our amplifier design!