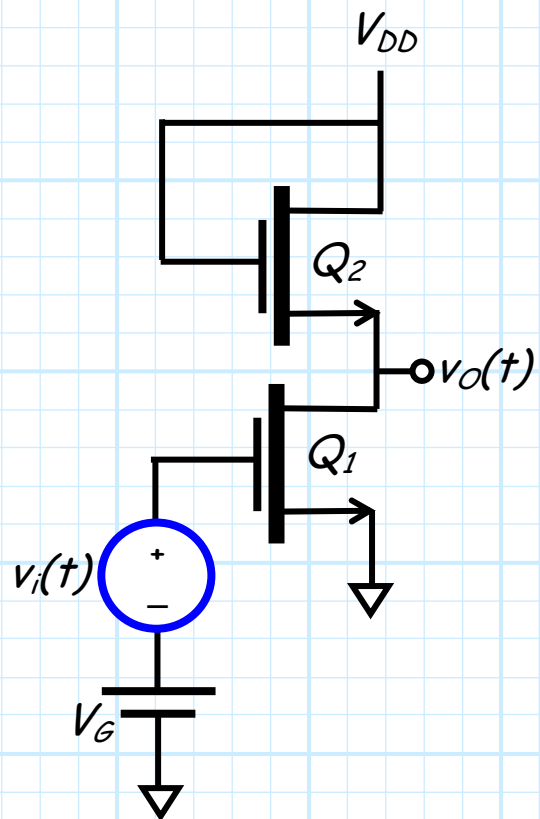


The Common Source Amp with Enhancement Load

Consider this NMOS amplifier using an enhancement load.

- * Note no resistors or capacitors are present!
- * This is a common source amplifier.
- * I_D stability could be a problem




Q: What is the small-signal open-circuit voltage gain, input resistance, and output resistance of this amplifier?

A: The values that we will determine when we follow precisely the same steps as before!!

Step 1 - DC Analysis

The DC circuit of this amplifier is:

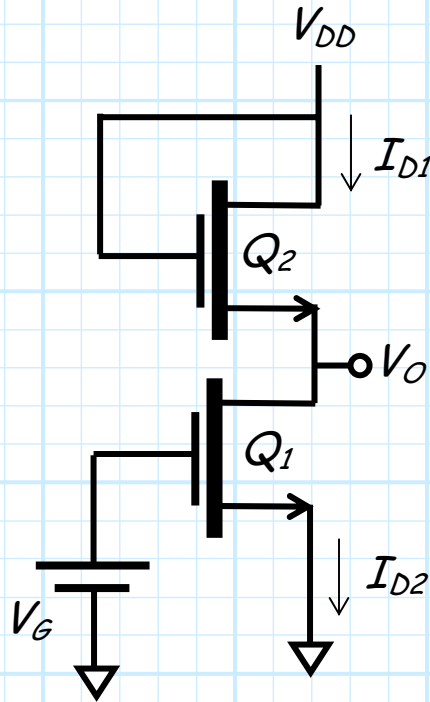

Note that:

$$I_{D1} = I_{D2} \doteq I_D$$

and that:

$$V_{GS1} = V_G - 0 = V_G$$

and also that:

$$V_{DS2} = V_{GS2}$$

and finally that:

$$V_{DS1} = V_{DD} - V_{DS2}$$

Let's of course **ASSUME** that both Q_1 and Q_2 are in saturation. Therefore we **ENFORCE**:

$$\begin{aligned} I_{D1} &= K_1 (V_{GS1} - V_{t1})^2 \\ &= K_1 (V_G - V_{t1})^2 \end{aligned}$$

Note that there are no unknowns in the previous equation. The drain current is explicitly determined from K_1 , V_G , and V_{t1} !

Continuing with the **ANALYSIS**, we can find the drain current through the enhancement load (I_{D2}), since it is equal to the current through Q_1 :

$$I_{D2} = I_{D1} = K_1 (V_G - V_{t1})^2$$

Yet we also know that V_{GS2} must be related to this drain current as:

$$I_{D2} = K_2 (V_{GS2} - V_{t2})^2$$

and therefore combining the above equations:

$$\begin{aligned} I_{D1} &= I_{D2} \\ K_1 (V_G - V_{t1})^2 &= K_2 (V_{GS2} - V_{t2})^2 \end{aligned}$$

Note this last equation has only one unknown (V_{GS2})!

Rearranging, we find that:

$$V_{GS2} = \sqrt{\frac{K_1}{K_2}} (V_G - V_{t1}) + V_{t2}$$

Since $V_{DS2} = V_{GS2}$ and $V_{DS1} = V_{DD} - V_{DS2}$, we can likewise state that:

$$V_{DS2} = \sqrt{\frac{K_1}{K_2}} (V_G - V_{t1}) + V_{t2}$$

and:

$$V_{DS1} = V_{DD} - V_{t2} - \sqrt{\frac{K_1}{K_2}} (V_G - V_{t1})$$

Now, we must **CHECK** to see if our assumption is correct.

The saturation assumption will be correct if:

$$\begin{aligned}V_{DS1} &> V_{GS1} - V_{t1} \\ &> V_G - V_{t1}\end{aligned}$$

and:

$$V_{GS1} > V_{t1} \quad \therefore \quad \text{if } V_G > V_{t1}$$

Step 2 - Calculate small-signal parameters

We require the small-signal parameters for each of the transistors Q_1 and Q_2 . Therefore:


$$g_{m1} = 2K_1(V_G - V_{t1}) \quad \text{and} \quad g_{m2} = 2K_1(V_{GS2} - V_{t2})$$

and:


$$r_{o1} = \frac{1}{\lambda_1 I_D} \quad \text{and} \quad r_{o2} = \frac{1}{\lambda_2 I_D}$$

Step 3 - Determine the small-signal circuit

First, let's turn off the DC sources:

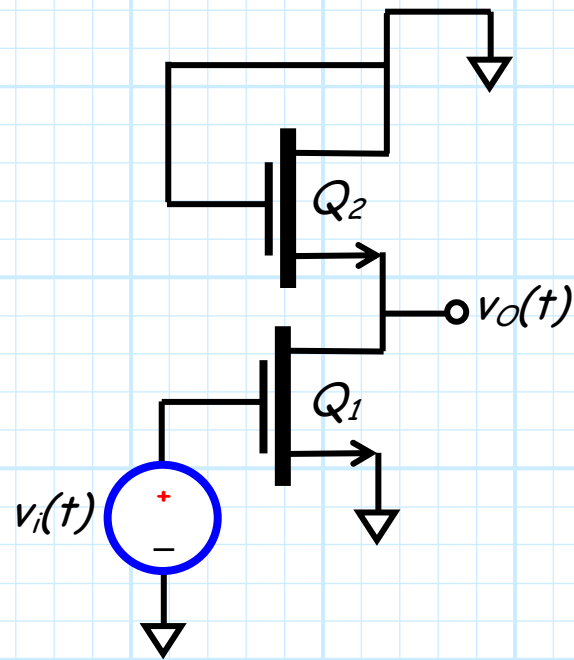


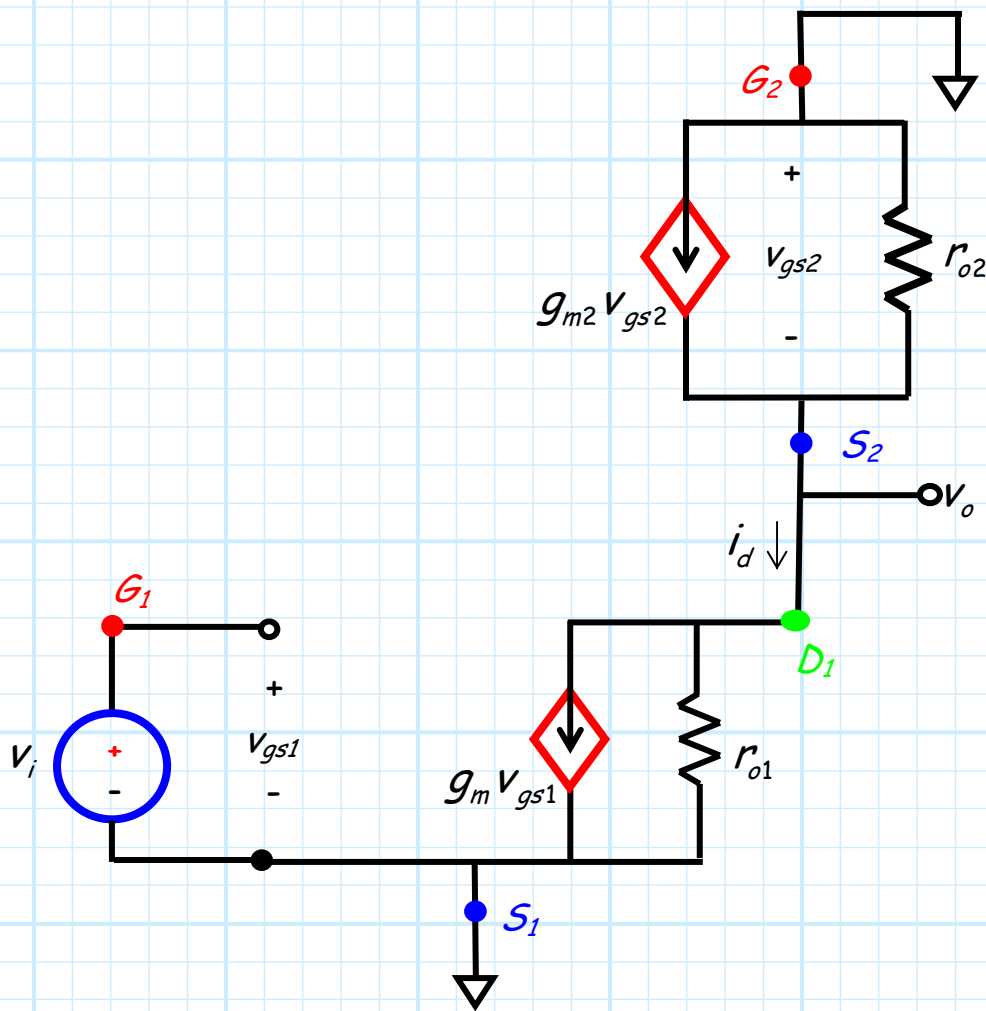We now replace **MOSFET Q_1** with its equivalent small-signal model, **and** replace the **enhancement load** with its equivalent small-signal model.




Note S_1 and G_2 are at **small-signal ground!**

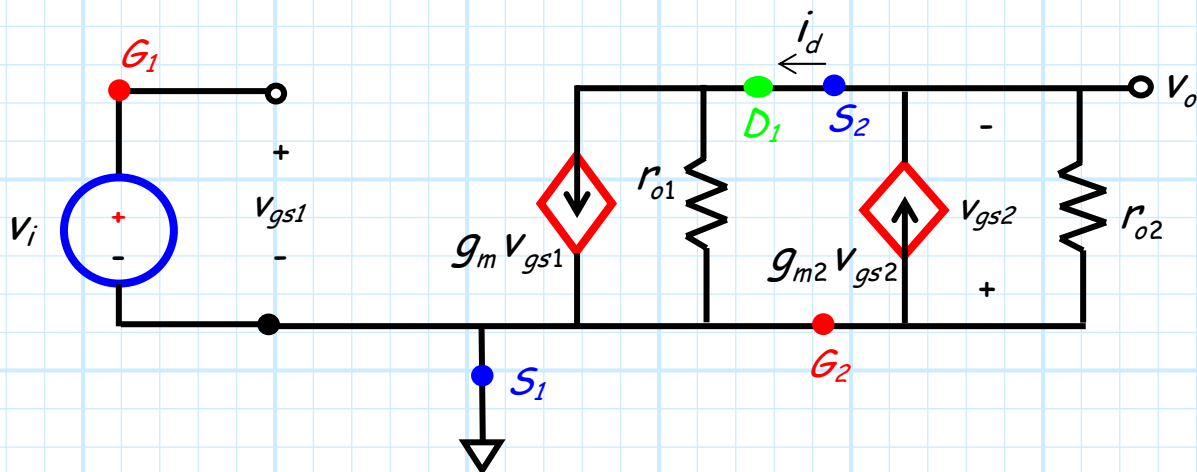Therefore, we can rewrite this circuit as:



Simplifying further, we find:

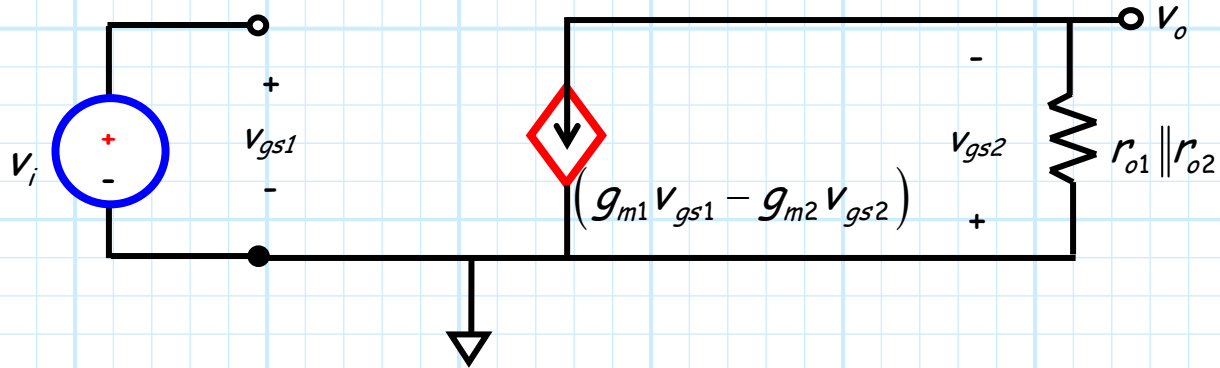

Therefore, we find that:

$$v_{gs1} = v_i$$

and that:

$$v_{gs2} = -v_o$$

as well as that:

$$\begin{aligned} v_o &= -(g_{m1} v_{gs1} - g_{m2} v_{gs2}) (r_{o1} \parallel r_{o2}) \\ &= -(g_{m1} v_i + g_{m2} v_o) (r_{o1} \parallel r_{o2}) \end{aligned}$$

Rearranging, we find:

$$A_{v_o} = \frac{v_o}{v_i} = \frac{-(r_{o1} \parallel r_{o2}) g_{m1}}{1 + (r_{o1} \parallel r_{o2}) g_{m2}} \approx \frac{-g_{m1}}{g_{m2}}$$

But recall that:

$$\begin{aligned} g_m &= 2K(V_{GS} - V_t) \\ &= 2\sqrt{K} \sqrt{I_D} \end{aligned}$$


where we have used the fact that $I_D = K(V_{GS} - V_t)^2$ to determine that $(V_{GS} - V_t) = \sqrt{I_D/K}$.

Therefore:

$$A_{vo} = \frac{-g_{m1}}{g_{m2}} = \frac{2\sqrt{K_1}\sqrt{I_D}}{2\sqrt{K_2}\sqrt{I_D}} = \sqrt{\frac{K_1}{K_2}} = \frac{\sqrt{(W/L)_1}}{\sqrt{(W/L)_2}}$$

In other words, we adjust the MOSFET channel geometry to set the small-signal gain of this amplifier!

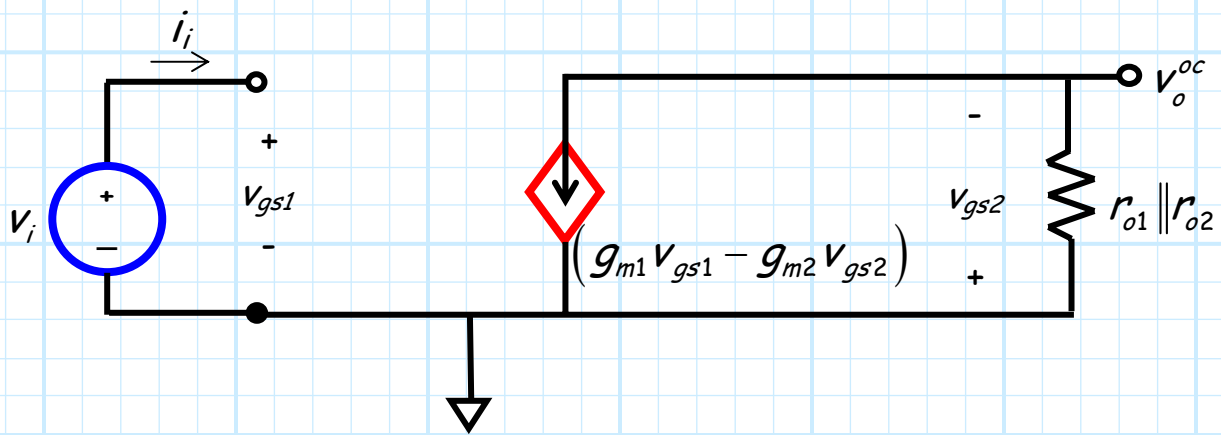Now let's determine the small-signal input and output resistances of this amplifier!




It is evident that since $i_i = i_g = 0$:

$$R_i = \frac{v_i}{i_i} = \infty \quad (\text{Great!!!})$$

Now for the output resistance, we know that the open-circuit output voltage is:
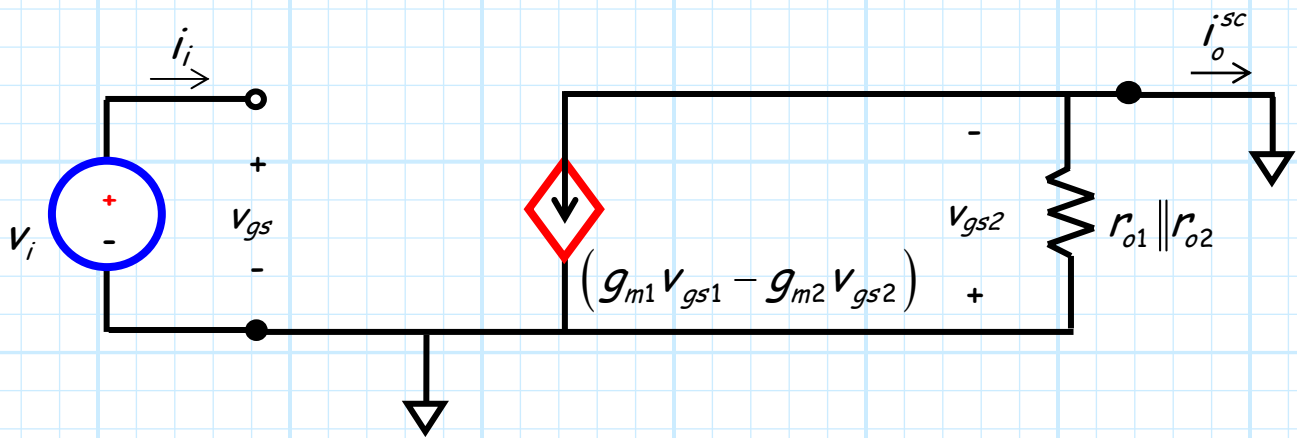
$$v_o^{oc} = -(g_{m1} v_{gs1} - g_{m2} v_{gs2}) (r_{o1} \parallel r_{o2})$$



Likewise, the short-circuit output current i_o^{sc} is:

$$i_{os} = -(g_{m1} v_{gs1} - g_{m2} v_{gs2})$$

Thus, the small-signal output resistance of this amplifier is equal to:

$$R_o = \frac{v_o^{oc}}{i_o^{sc}} = \frac{-(g_{m1} v_{gs1} - g_{m2} v_{gs2})(r_{o1} || r_{o2})}{-(g_{m1} v_{gs1} - g_{m2} v_{gs2})} = (r_{o1} || r_{o2}) \quad (\text{Doh!!!})$$

The input resistance and open-circuit voltage gain of this common source amplifier are good, but the output resistance stinks!!

Smells like a common emitter amplifier!

