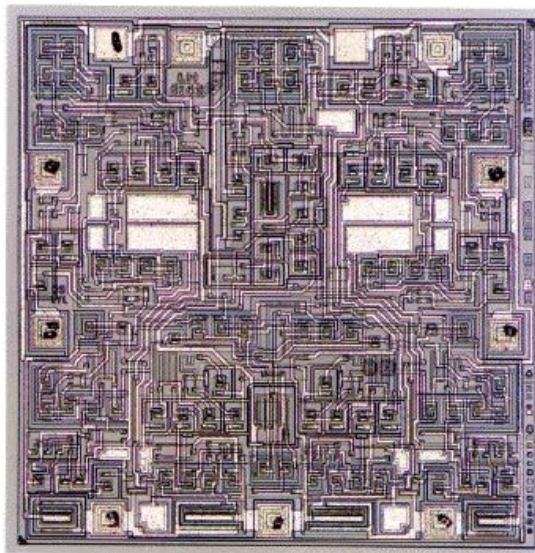


## 6.5 The Common Source Amp with Active Loads

*Reading Assignment: pp. 582-587*

Amplifiers are frequently made as **integrated circuits** (e.g., op-amps).



Although both BJTs and MOSFET integrated circuit amplifiers are implemented as ICs, we find that MOSFETs amplifiers are almost **exclusively** implemented as integrated circuits (i.e., **rarely** are MOSFET amps made of "discrete" components).

Making integrated circuit amplifiers has many positives, but a few negatives:

**Positives:**

The amplifier circuit can be quite **complex**, yet still **small and inexpensive**. Thus, **current sources** are “no big deal”.

### **Negatives:**

We **cannot** make large capacitors (i.e., **COUS**), so that DC blocking capacitors are not possible—this makes **bias solutions more complex**, particularly for multi-stage amplifiers.

Additionally, it is difficult to make **resistors** in integrated circuits. Instead, we use “resistors” constructed from transistors—so-called “**active loads**”.

### **HO: Enhancement loads**

### **HO: The Common Source Amp with an Active Load**

The **sensitivity** problem of the previous circuit can be solved using a **current source** as a “load”

### **HO: The Common Source Amp with a Current Source**


# Enhancement Loads

**Resistors** take up far too much **space** on integrated circuit substrates.

Therefore, we need to make a **resistor** out of a **transistor**!

**Q:** *How can we do that!? After all, a resistor is a **two** terminal device, whereas a transistor is a **three** terminal device.*

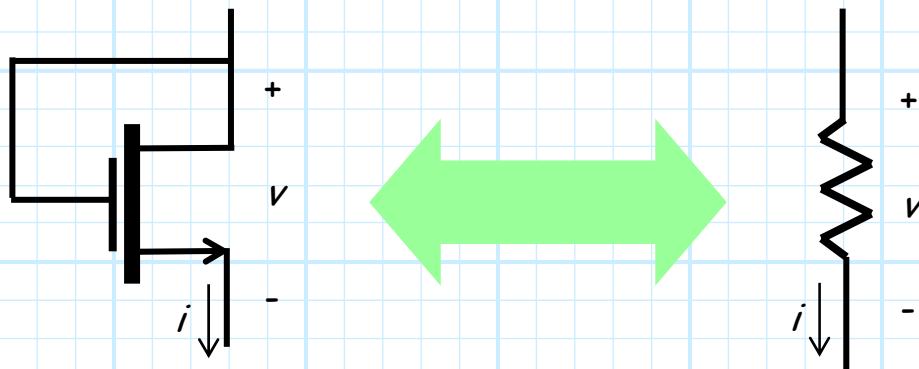**A:** We can make a two terminal device from a MOSFET by **connecting** the gate and the drain!




*Enhancement Load*

*Resistor Load*

**Q:** *How does this "enhancement load" resemble a resistor?*

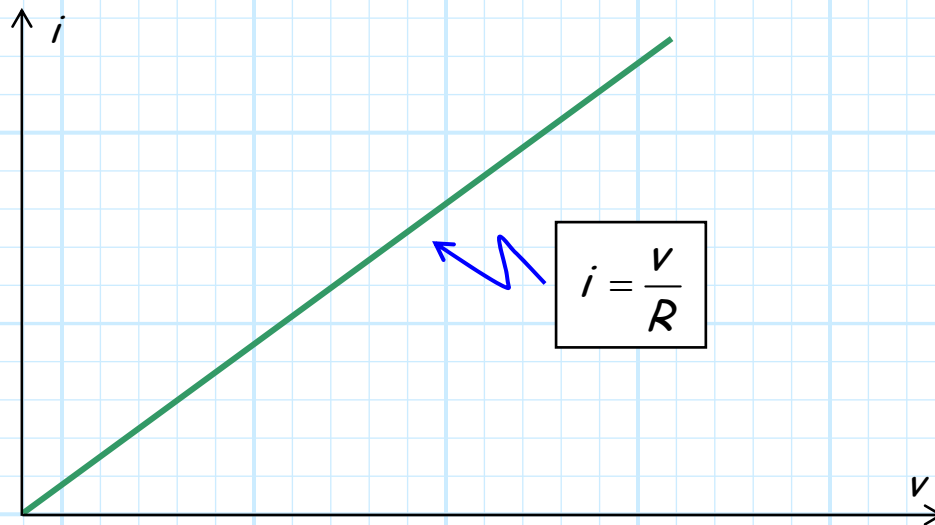**A:** Consider the  $i$ - $v$  curve for a **resistor**:



Now consider the same curve for an **enhancement load**.


Since the gate is tied to the drain, we find  $v_G = v_D$ , and thus  $v_{GS} = v_{DS}$ . As a result, we find that  $v_{DS} > v_{GS} - V_t$  **always**.

Therefore, we find that if  $v_{GS} > V_t$ , the MOSFET will be in **saturation** ( $i_D = K(v_{GS} - V_t)^2$ ), whereas if  $v_{GS} < V_t$ , the MOSFET is in **cutoff** ( $i_D = 0$ ).

Since for enhancement load  $i = i_D$  and  $v = v_{GS}$ , we can describe the enhancement load as:


$$i = \begin{cases} 0 & \text{for } v < V_t \\ K(v - V_t)^2 & \text{for } v > V_t \end{cases}$$

Plotting this equation:

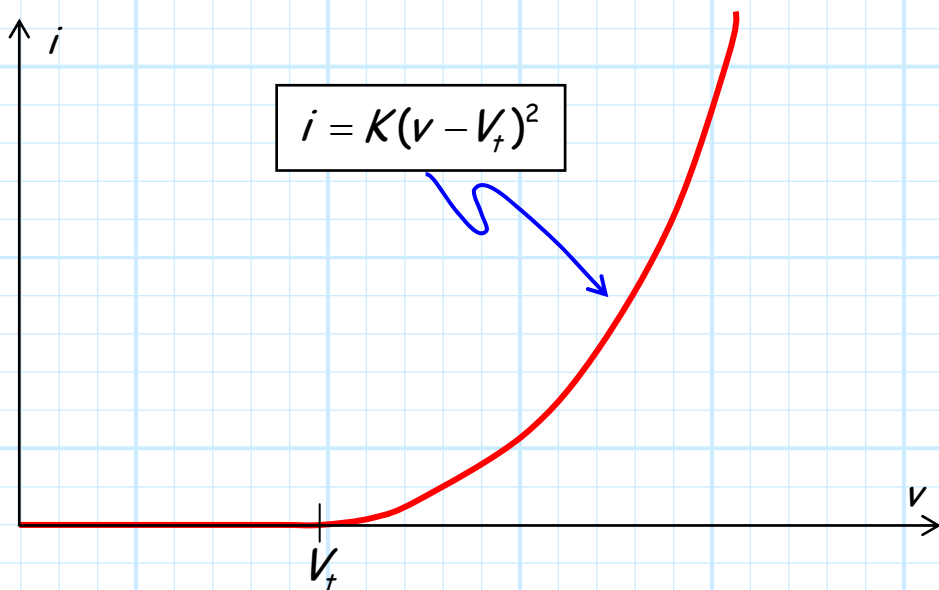


So, resistors and enhancement loads are far from **exactly** the same, but:

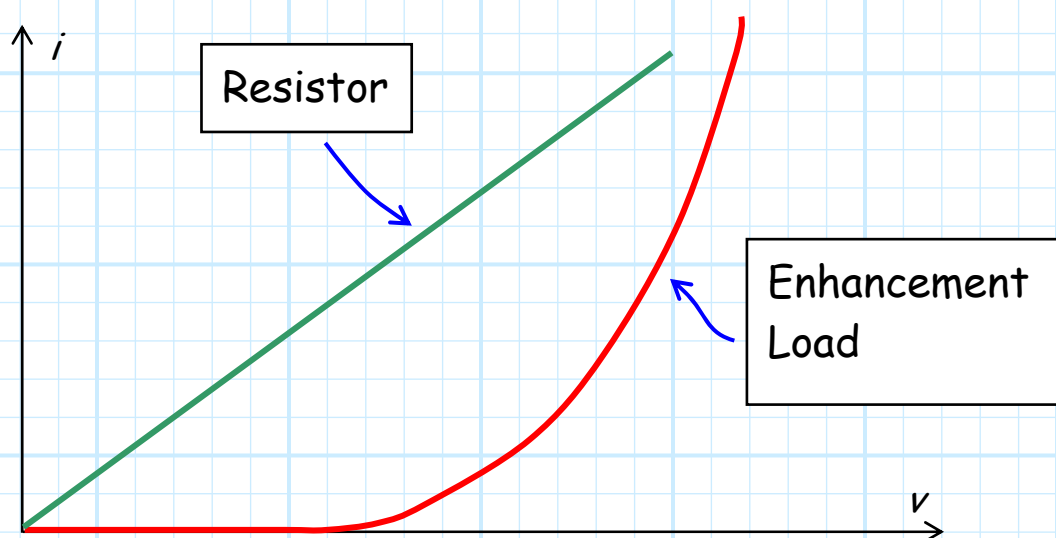
- 1) They **both** have  $i = 0$  when  $v = 0$ .
- 2) They **both** have increasing current  $i$  with increasing voltage  $v$ .



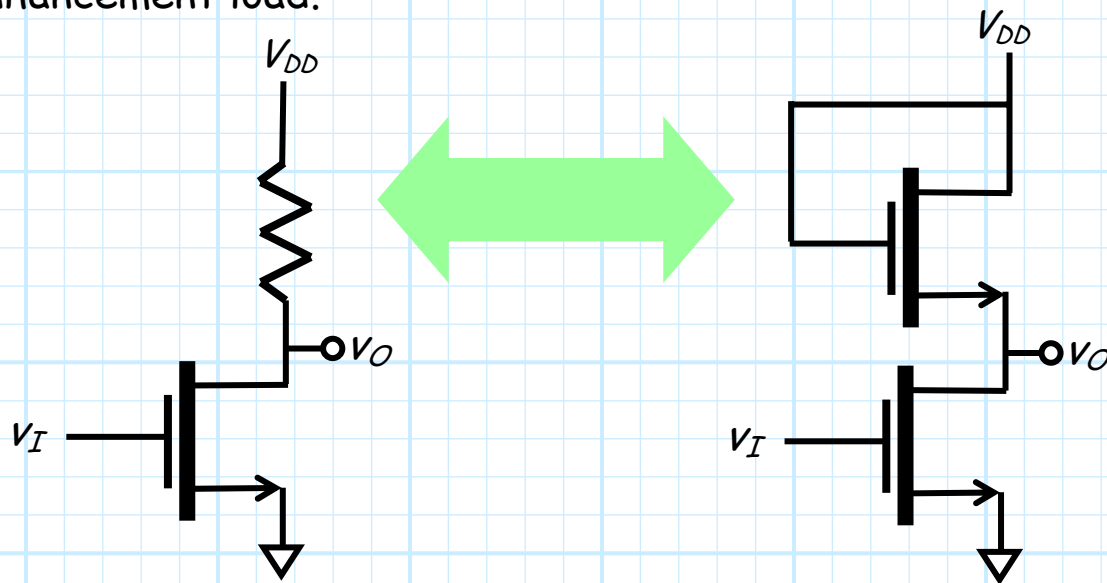
Therefore, we can build a **common source** amplifier with either a resistor, or in the case of an **integrated circuit**, an enhancement load.



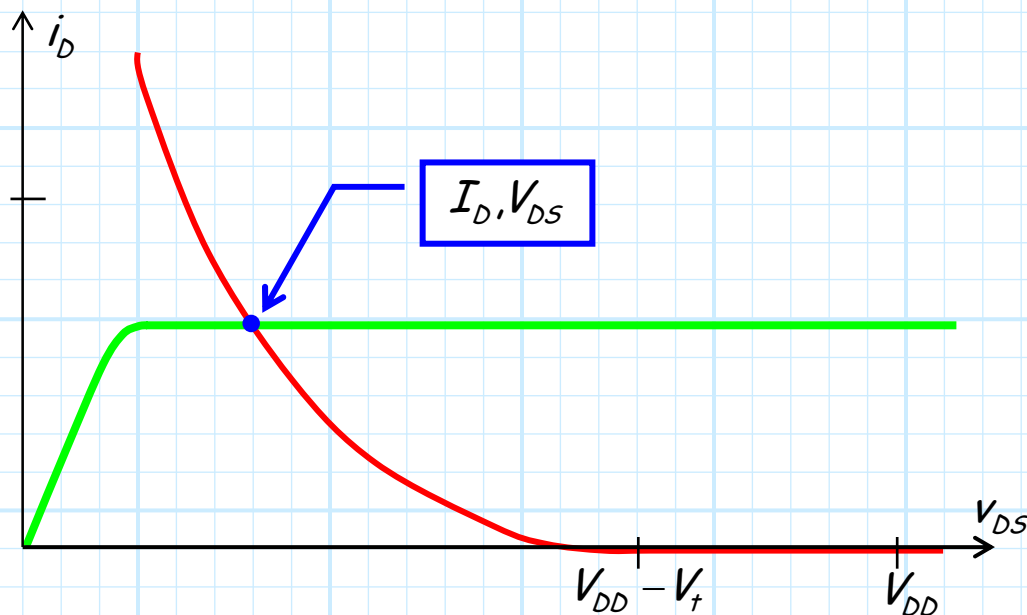For the enhancement load amplifier, the **load line** is replaced with a **load curve** ( $v = V_{DD} - v_{DS}$ )!



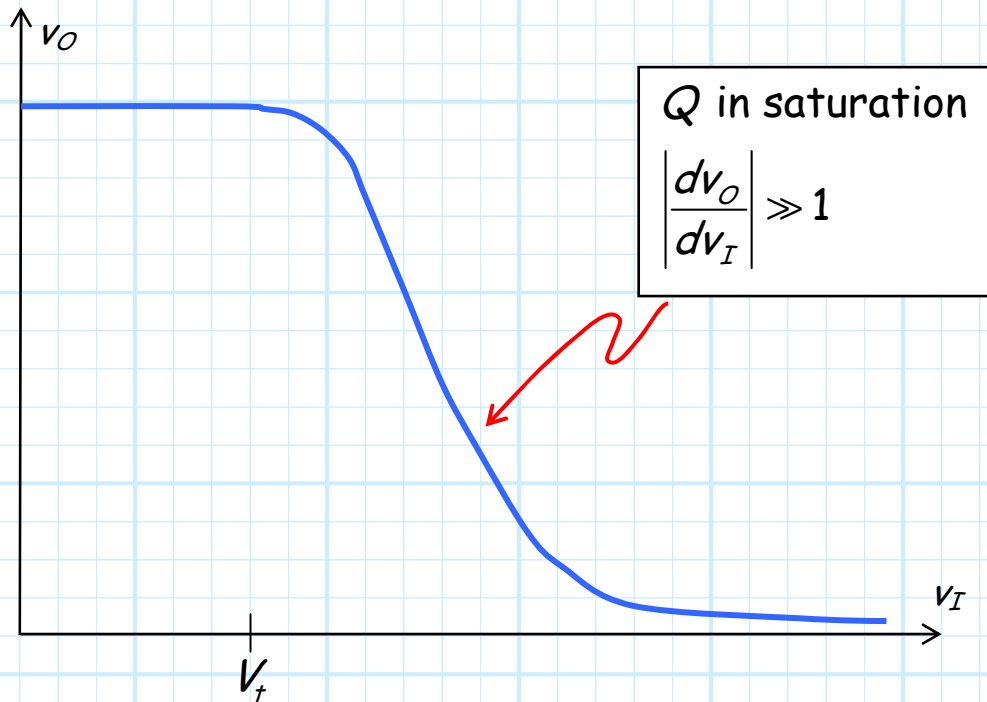And the **transfer function** of this circuit is:



**Q:** What is the *small signal* behavior of an enhancement load?


**A:** The enhancement load is made of a MOSFET device, and we **understand** the small-signal behavior for a MOSFET!

### Step 1 - DC Analysis

If  $V > V_t$ , then  $I = K(V - V_t)^2$

or:

$$V = \sqrt{\frac{I}{K}} + V_t$$

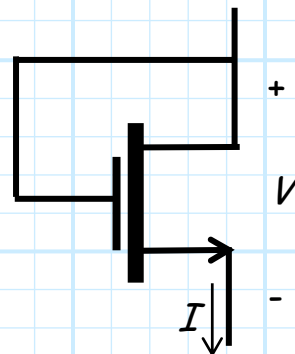


## Step 2 - Determine $g_m$ and $r_o$

$$g_m = 2K(V_{GS} - V_t) = 2K(V - V_t)$$


$$r_o = \frac{1}{\lambda I_D} = \frac{1}{\lambda I} = \frac{1}{\lambda K(V - V_t)^2}$$
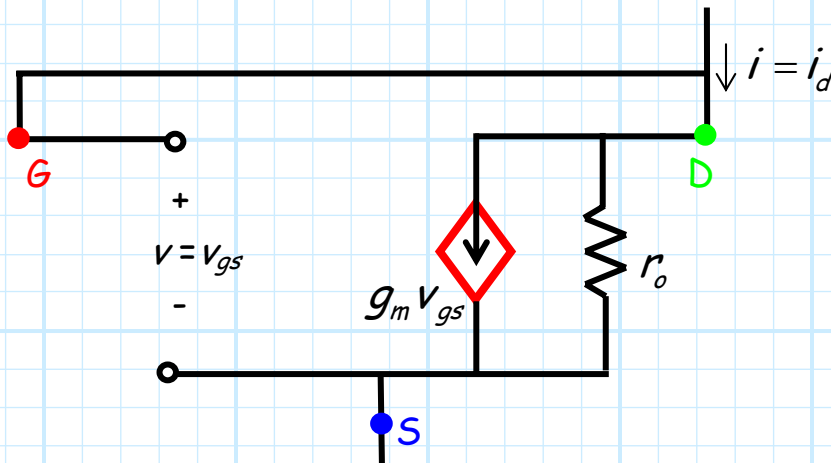
## Step 3 - Determine the small-signal circuit

Inserting the MOSFET small-signal model, we get:



Redrawing this circuit, we get:

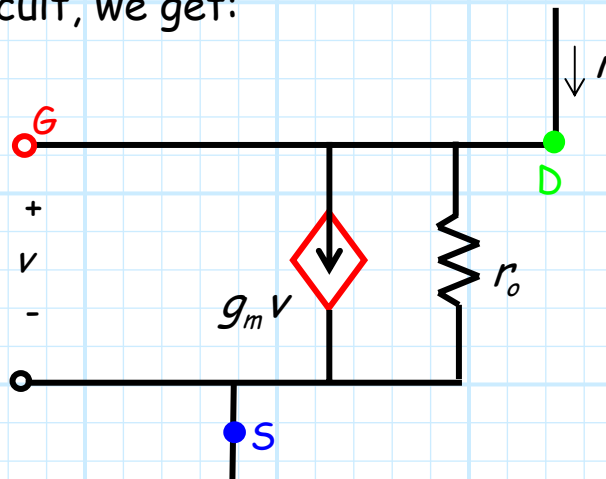





Or, simplifying further, we have the small-signal equivalent circuit for an enhancement load:

*It is imperative that you understand that the circuit to my right is the **small-signal equivalent circuit** for an enhancement load.*

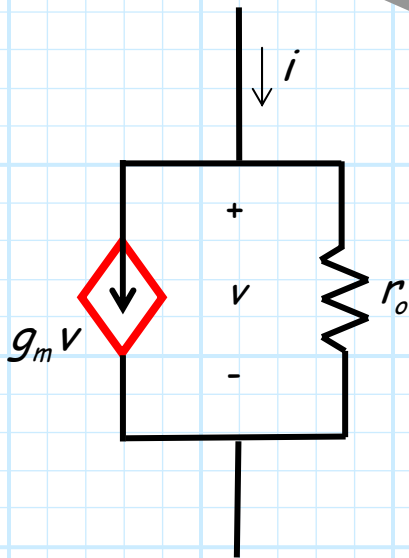*Please replace all **enhancement loads** with this small-signal model whenever you are attempting to find the **small-signal circuit** of any MOSFET amplifier.*




*Enhancement Load  
Small-Signal Model*

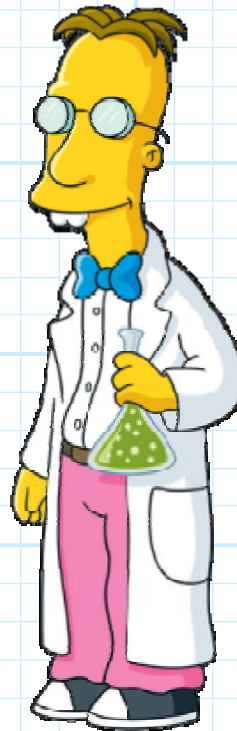
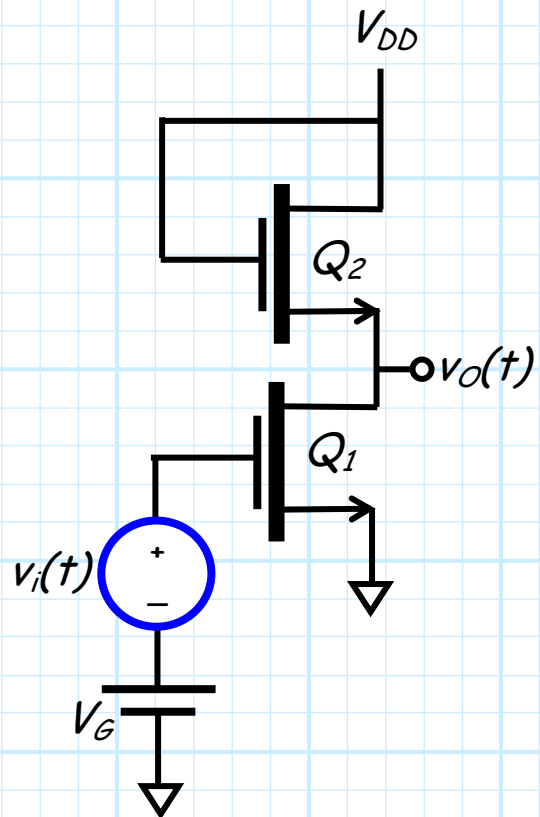
# The Common Source Amp with Enhancement Load

Consider this NMOS amplifier using an enhancement load.

- \* Note no resistors or capacitors are present!
- \* This is a common source amplifier.
- \*  $I_D$  stability could be a problem




**Q:** What is the small-signal open-circuit voltage gain, input resistance, and output resistance of this amplifier?

**A:** The values that we will determine when we follow precisely the same steps as before!!

## Step 1 - DC Analysis

The DC circuit of this amplifier is:

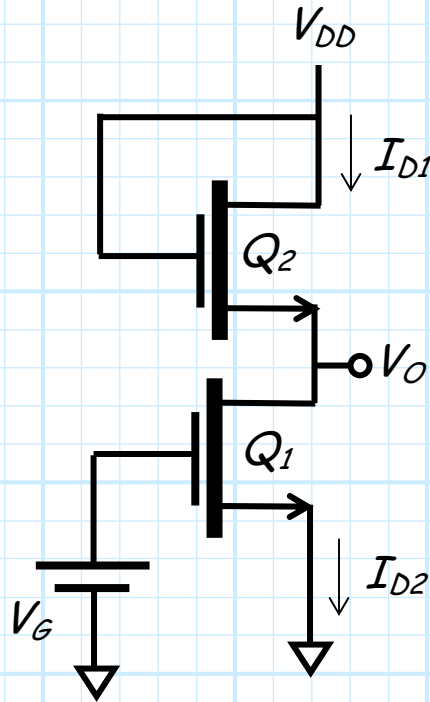

Note that:

$$I_{D1} = I_{D2} \doteq I_D$$

and that:

$$V_{GS1} = V_G - 0 = V_G$$

and also that:

$$V_{DS2} = V_{GS2}$$

and finally that:

$$V_{DS1} = V_{DD} - V_{DS2}$$

Let's of course **ASSUME** that both  $Q_1$  and  $Q_2$  are in saturation. Therefore we **ENFORCE**:

$$\begin{aligned} I_{D1} &= K_1 (V_{GS1} - V_{t1})^2 \\ &= K_1 (V_G - V_{t1})^2 \end{aligned}$$

Note that there are no unknowns in the previous equation. The drain current is explicitly determined from  $K_1$ ,  $V_G$ , and  $V_{t1}$ !

Continuing with the **ANALYSIS**, we can find the drain current through the enhancement load ( $I_{D2}$ ), since it is equal to the current through  $Q_1$ :

$$I_{D2} = I_{D1} = K_1 (V_G - V_{t1})^2$$

Yet we also know that  $V_{GS2}$  must be related to this drain current as:

$$I_{D2} = K_2 (V_{GS2} - V_{t2})^2$$

and therefore combining the above equations:

$$\begin{aligned} I_{D1} &= I_{D2} \\ K_1 (V_G - V_{t1})^2 &= K_2 (V_{GS2} - V_{t2})^2 \end{aligned}$$

Note this last equation has only one unknown ( $V_{GS2}$ )!

Rearranging, we find that:

$$V_{GS2} = \sqrt{\frac{K_1}{K_2}} (V_G - V_{t1}) + V_{t2}$$

Since  $V_{DS2} = V_{GS2}$  and  $V_{DS1} = V_{DD} - V_{DS2}$ , we can likewise state that:

$$V_{DS2} = \sqrt{\frac{K_1}{K_2}} (V_G - V_{t1}) + V_{t2}$$

and:

$$V_{DS1} = V_{DD} - V_{t2} - \sqrt{\frac{K_1}{K_2}} (V_G - V_{t1})$$

Now, we must **CHECK** to see if our assumption is correct.

The saturation assumption will be correct if:

$$\begin{aligned}V_{DS1} &> V_{GS1} - V_{t1} \\ &> V_G - V_{t1}\end{aligned}$$

and:

$$V_{GS1} > V_{t1} \quad \therefore \quad \text{if } V_G > V_{t1}$$

## Step 2 - Calculate small-signal parameters

We require the small-signal parameters for each of the transistors  $Q_1$  and  $Q_2$ . Therefore:


$$g_{m1} = 2K_1(V_G - V_{t1}) \quad \text{and} \quad g_{m2} = 2K_1(V_{GS2} - V_{t2})$$

and:


$$r_{o1} = \frac{1}{\lambda_1 I_D} \quad \text{and} \quad r_{o2} = \frac{1}{\lambda_2 I_D}$$

### Step 3 - Determine the small-signal circuit

First, let's turn off the DC sources:

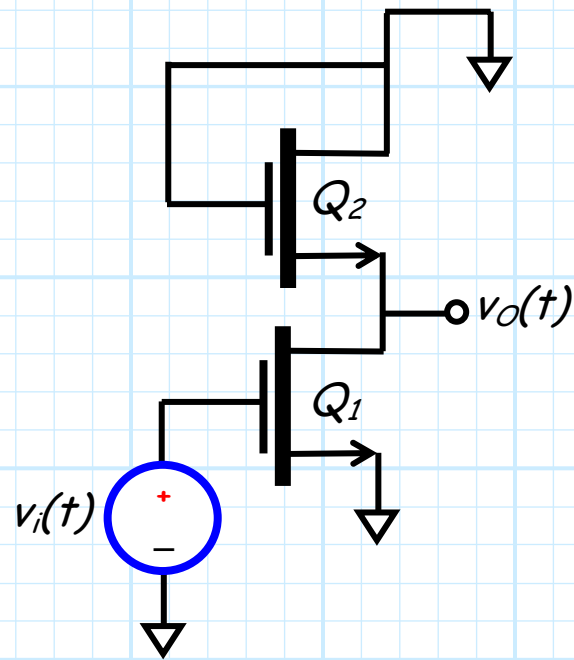


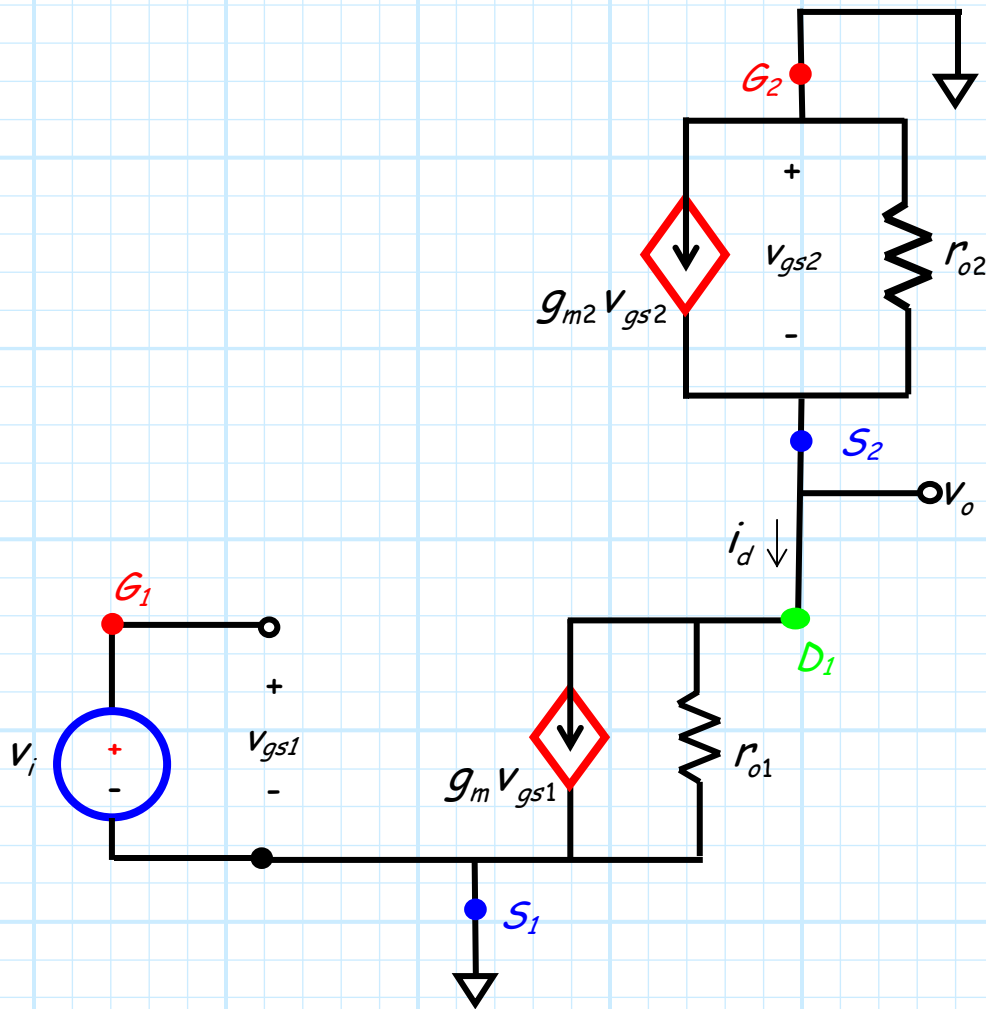We now replace **MOSFET**  $Q_1$  with its equivalent small-signal model, and replace the **enhancement load** with its equivalent small-signal model.




Note  $S_1$  and  $G_2$  are at **small-signal ground**!

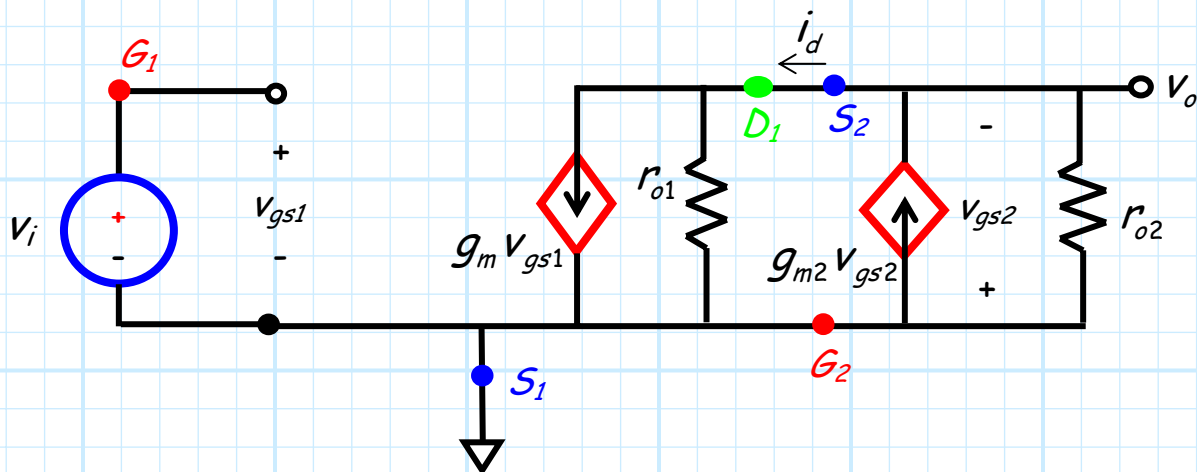Therefore, we can rewrite this circuit as:



Simplifying further, we find:

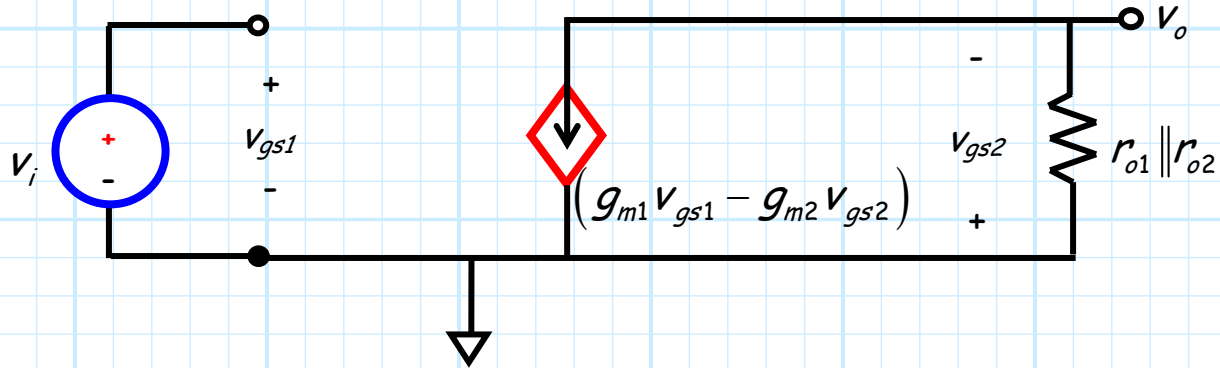

Therefore, we find that:

$$v_{gs1} = v_i$$

and that:

$$v_{gs2} = -v_o$$

as well as that:

$$\begin{aligned} v_o &= -(g_{m1} v_{gs1} - g_{m2} v_{gs2}) (r_{o1} \parallel r_{o2}) \\ &= -(g_{m1} v_i + g_{m2} v_o) (r_{o1} \parallel r_{o2}) \end{aligned}$$

Rearranging, we find:

$$A_{v_o} = \frac{v_o}{v_i} = \frac{-(r_{o1} \parallel r_{o2}) g_{m1}}{1 + (r_{o1} \parallel r_{o2}) g_{m2}} \approx \frac{-g_{m1}}{g_{m2}}$$

But recall that:

$$\begin{aligned} g_m &= 2K(V_{GS} - V_t) \\ &= 2\sqrt{K} \sqrt{I_D} \end{aligned}$$

where we have used the fact that  $I_D = K(V_{GS} - V_t)^2$  to determine that  $(V_{GS} - V_t) = \sqrt{I_D/K}$ .




Therefore:

$$A_{vo} = \frac{-g_{m1}}{g_{m2}} = \frac{2\sqrt{K_1}\sqrt{I_D}}{2\sqrt{K_2}\sqrt{I_D}} = \sqrt{\frac{K_1}{K_2}} = \frac{\sqrt{(W/L)_1}}{\sqrt{(W/L)_2}}$$

In other words, we adjust the MOSFET channel geometry to set the small-signal gain of this amplifier!

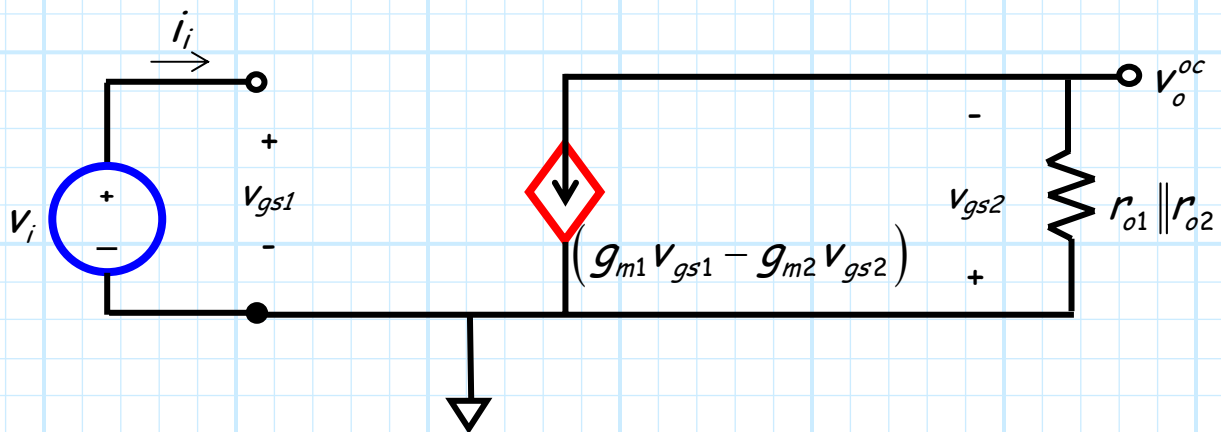Now let's determine the small-signal input and output resistances of this amplifier!




It is evident that since  $i_i = i_g = 0$ :

$$R_i = \frac{v_i}{i_i} = \infty \quad (\text{Great!!!})$$

Now for the output resistance, we know that the open-circuit output voltage is:
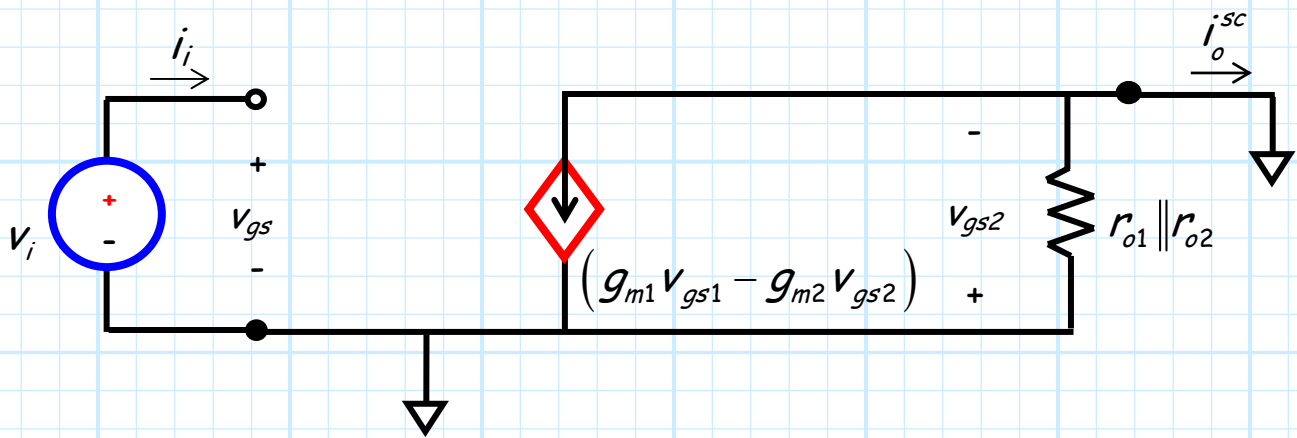
$$v_o^{oc} = -(g_{m1} v_{gs1} - g_{m2} v_{gs2}) (r_{o1} \parallel r_{o2})$$



Likewise, the short-circuit output current  $i_o^{sc}$  is:

$$i_{os} = -(g_{m1} v_{gs1} - g_{m2} v_{gs2})$$

Thus, the small-signal output resistance of this amplifier is equal to:

$$R_o = \frac{v_o^{oc}}{i_o^{sc}} = \frac{-(g_{m1} v_{gs1} - g_{m2} v_{gs2})(r_{o1} \parallel r_{o2})}{-(g_{m1} v_{gs1} - g_{m2} v_{gs2})} = (r_{o1} \parallel r_{o2}) \quad (\text{Doh!!!})$$

*The input resistance and open-circuit voltage gain of this common source amplifier are good, but the output resistance stinks!!*


*Smells like a common emitter amplifier!*



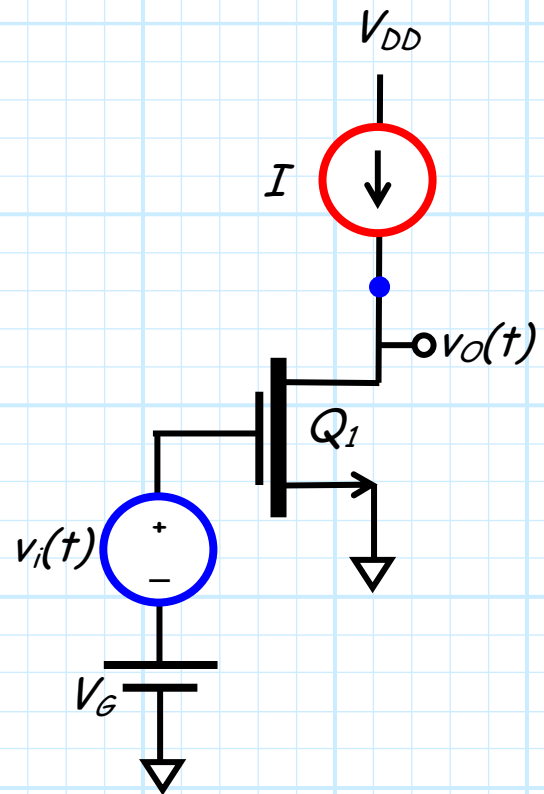
# The Common Source Amp with a Current Source

Now consider this NMOS amplifier using a **current source**.


- \* Note no resistors or capacitors are present!
- \* This is a **common source** amplifier.
- \*  $I_D$  stability is not a problem!



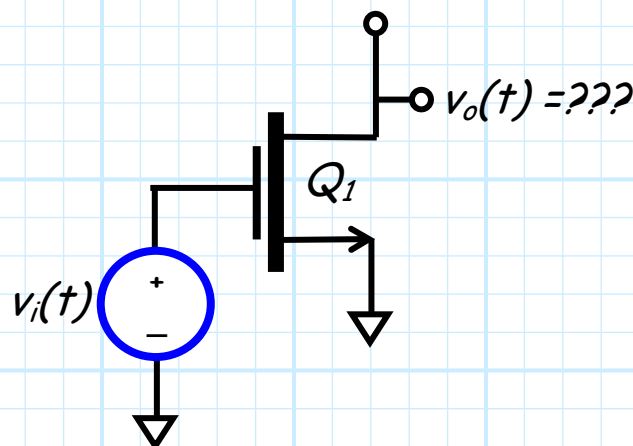**Q:** *I don't understand! Wouldn't the small-signal circuit be:*



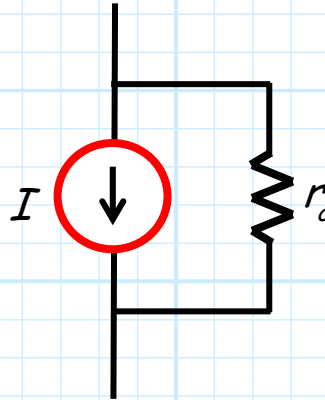
**A:** Remember, every **real** current source (as with every voltage source) has a **source resistance**  $r_o$ . A more **accurate** current source model is therefore:




**Ideally**,  $r_o = \infty$ . However, for good current sources, this output resistance is large (e.g.,  $r_o = 100\text{ K}\Omega$ ). Thus, we mostly **ignore** this value (i.e., approximate it as  $r_o = \infty$ ), but there are some circuits where this resistance makes quite a **difference**.

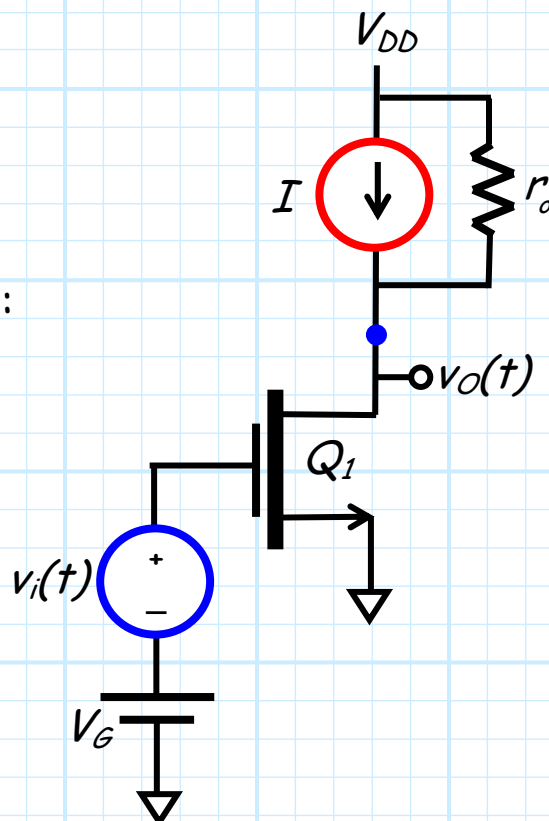**This is one of those circuits!**


Therefore, a more **accurate** amplifier circuit schematic is:



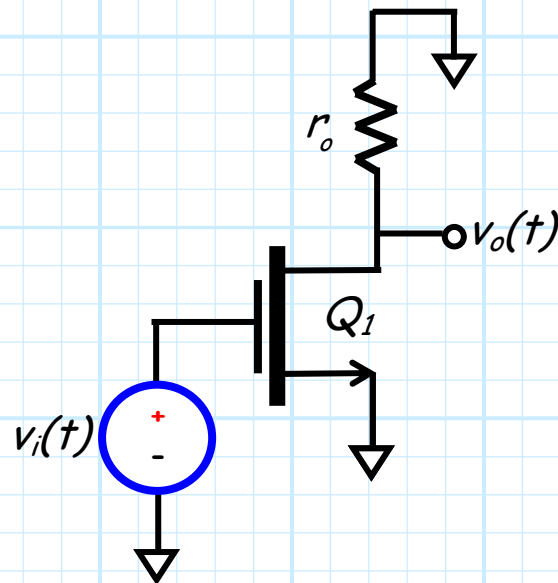And so the **small-signal circuit** becomes the familiar:




Therefore, with the hybrid-pi model:

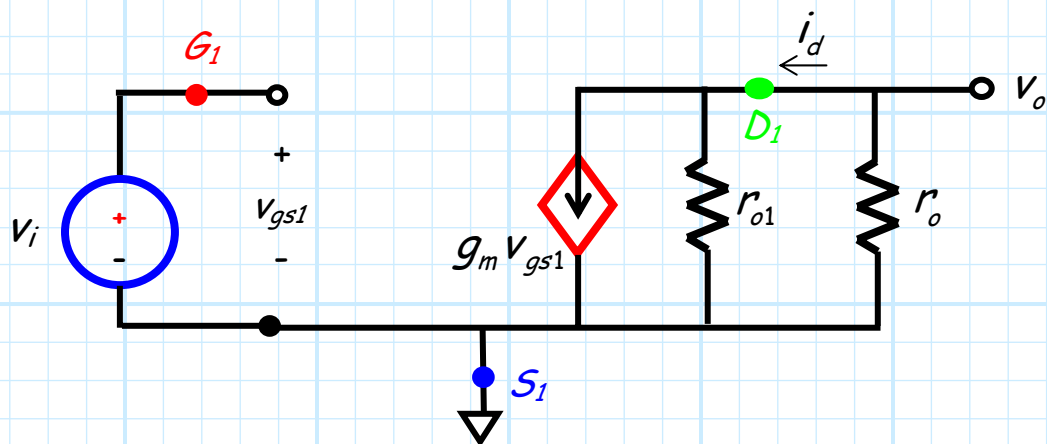


**Q:** But, we implement a current source using a **current mirror**. What is the **output resistance**  $r_o$  of a current mirror?

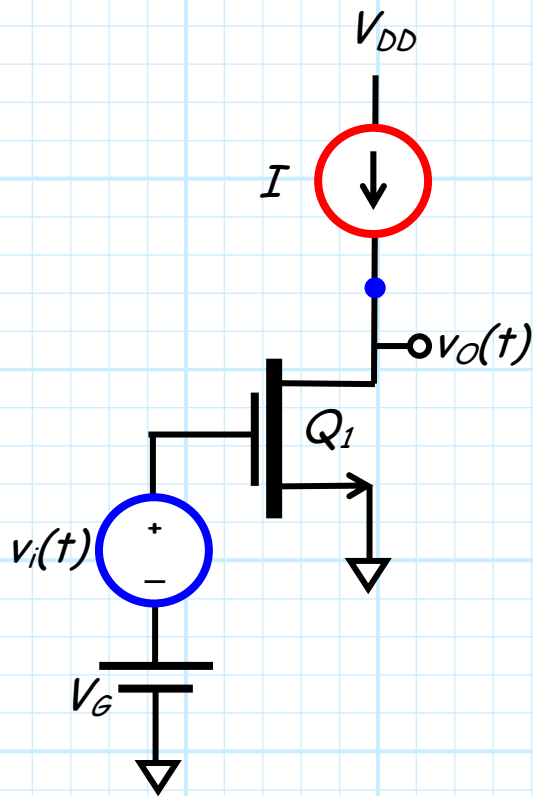**A:** Implementing a **PMOS** current mirror, we find that our amplifier circuit:



is specifically:

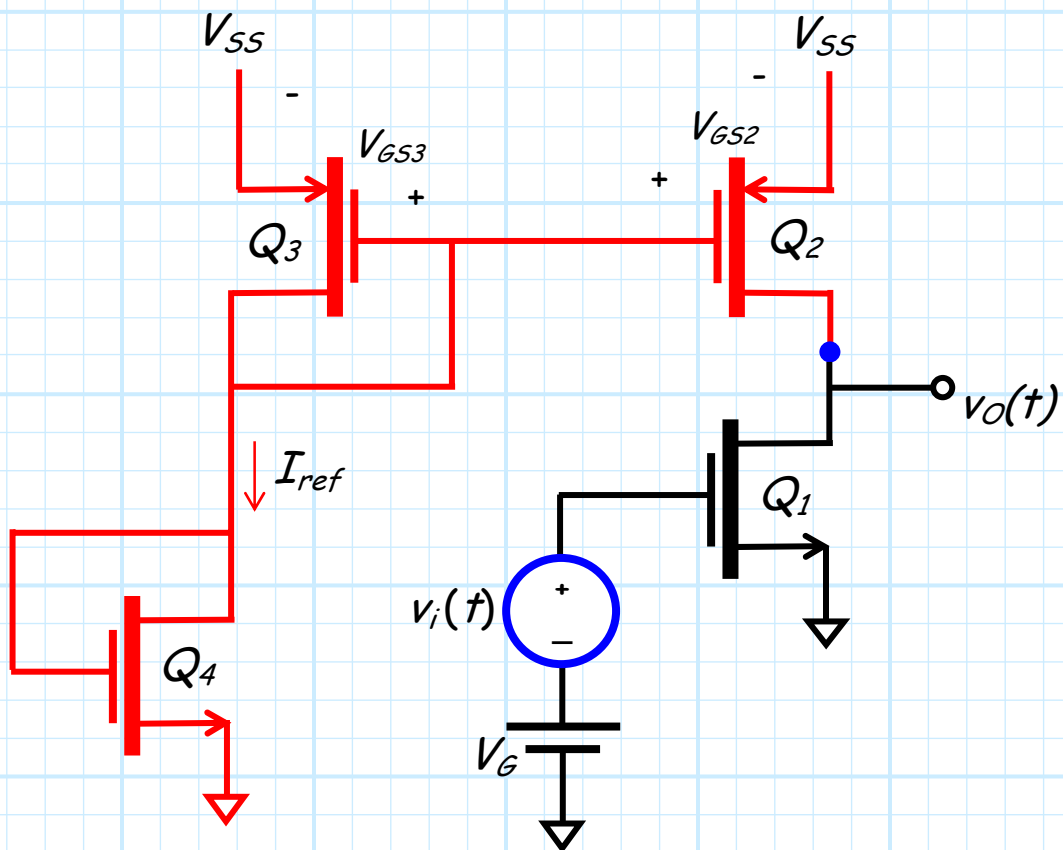

**Q:** *Yikes! Where did all those **transistors** come from? What is it that they **do**?*

**A:** Transistors  $Q_2$ ,  $Q_3$ , and  $Q_4$  form the **current mirror** that acts as the **current source**. Note that transistor  $Q_4$  is an **enhancement load**—it acts as the **resistor** in the current mirror circuit.

Note this amplifier circuit is **entirely** made of NMOS and PMOS **transistors**—we can “easily” implement this amplifier as an **integrated circuit**!

**Q:** *So again, what **is** the source resistance  $r_o$  of this current source?*

**A:** Let's determine the **small-signal circuit** for this integrated circuit amplifier and find out!

**Q:** *But there are **four** (count em') transistors in this circuit, determining the small-signal circuit must **take forever**!*

**A:** Actually no.

The important thing to realize when analyzing **this** circuit is that the gate-to-source voltage for transistors  $Q_2$ ,  $Q_3$ , and  $Q_4$  are **DC values**!

**Q:** ??


**A:** In other words, the small signal voltages  $v_{gs}$  for each transistor are equal to **zero**:

$$V_{gs2} = V_{gs3} = V_{gs4} = 0$$

**Q:** But doesn't the small-signal source  $v_i(t)$  **create** small-signal voltages and currents **throughout** the amplifier?

**A:** For **some** of the circuit yes, but for **most** of the circuit no!

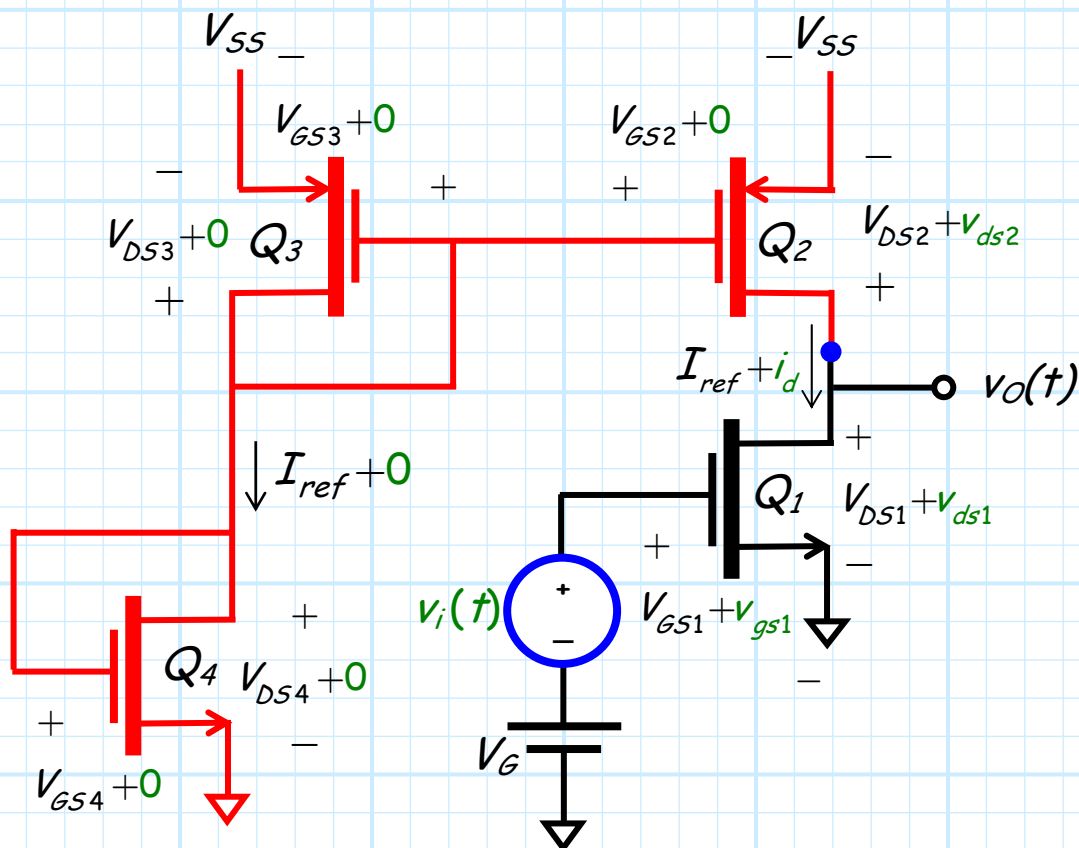Note that for transistor  $Q_1$  there will be **small-signal** voltages  $v_{gs1}(t)$  and  $v_{ds1}(t)$ , along with  $i_{d1}(t)$ . Likewise for transistor  $Q_2$ , a **small-signal** voltage  $v_{ds2}(t)$  and current  $i_{d2}(t)$  will occur.





But, for the remainder of the voltages and currents in this circuit (e.g.,  $V_{DS4}$ ,  $V_{GS2}$ ,  $I_{D3}$ ), the small-signal component is **zero!**

**Q:** *But wait! How can there be a small-signal drain current  $i_{d2}(t)$  through transistor  $Q_2$ , without a corresponding small-signal gate-to-source voltage  $v_{gs2}(t)$ ?*

**A:** Transistor  $Q_2$ , is the important device in this analysis.

Note its gate-to-source voltage is a **DC value** (no small-signal component!), yet there **must** be (by KCL) a **small-signal** drain current  $i_{d2}(t)$ !


This is a case where we **must** consider the **MOSFET output resistance**  $r_{o2}$ . The small-signal drain current for a **PMOS** device is:

$$i_{d2} = g_{m2} v_{gs2} - \frac{v_{ds2}}{r_{o2}}$$


Since  $v_{gs2}=0$ , this equation **simplifies** to:

$$i_{d2} = -\frac{v_{ds2}}{r_{o2}}$$

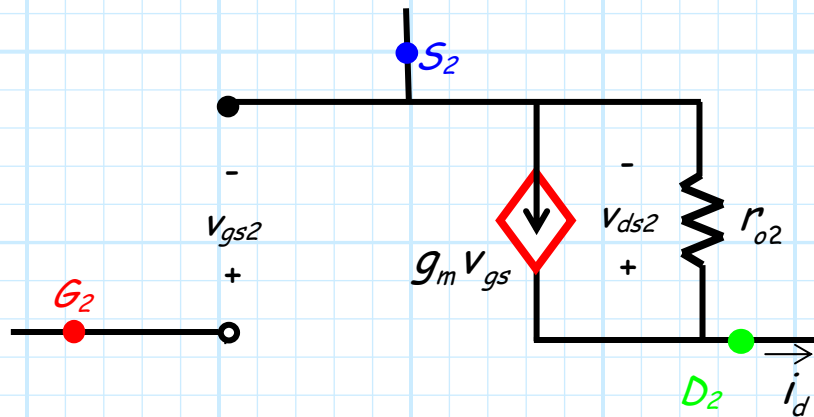
Equivalently, the small-signal PMOS model is:



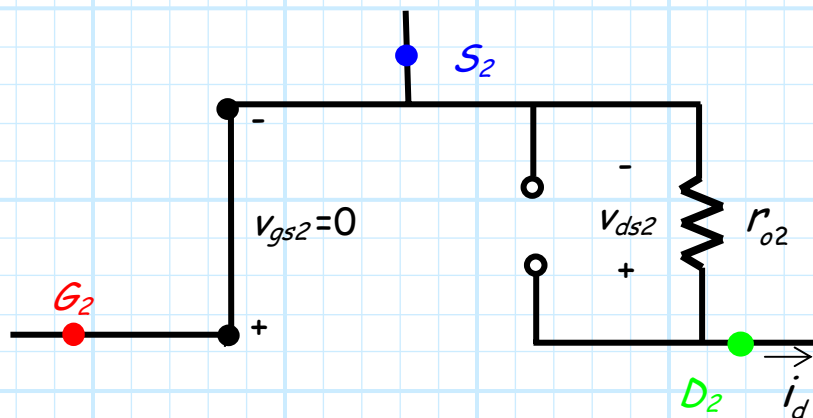
Thus for  $v_{gs2}=0$ , the small-signal model becomes:




Or, simplifying further:

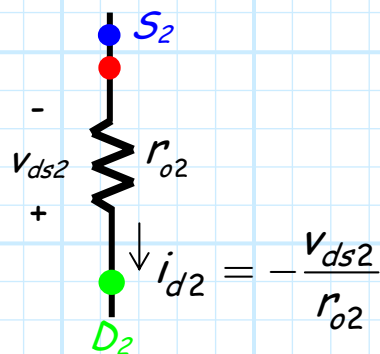

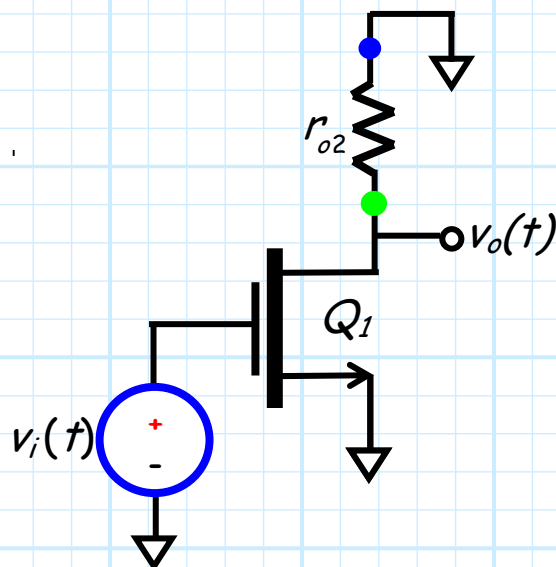Thus, the small-signal model of the entire current mirror is simply the output resistance of the MOSFET  $Q_2$  !



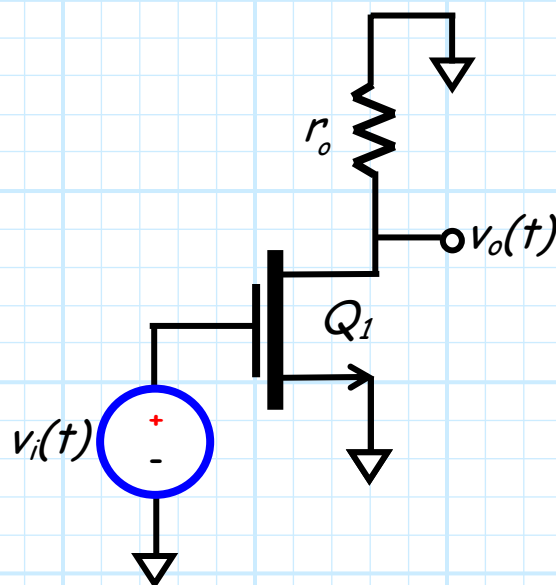
Comparing this to the earlier analysis--with a current source of output resistance  $r_o$ :




It is evident that the output resistance of the current mirror is simply equal to the output resistance of MOSFET  $Q_2$  !!!!

$$r_o = r_{o2}$$


And so **this** circuit:

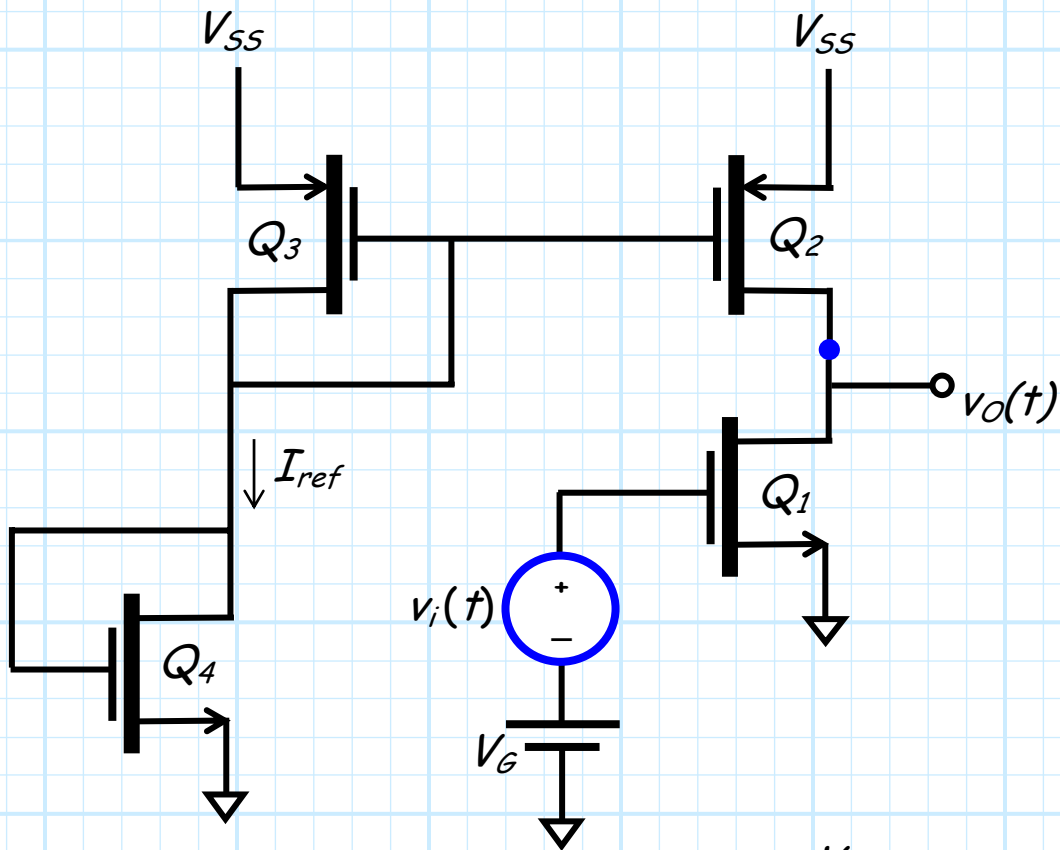

is equivalent to **this** circuit:

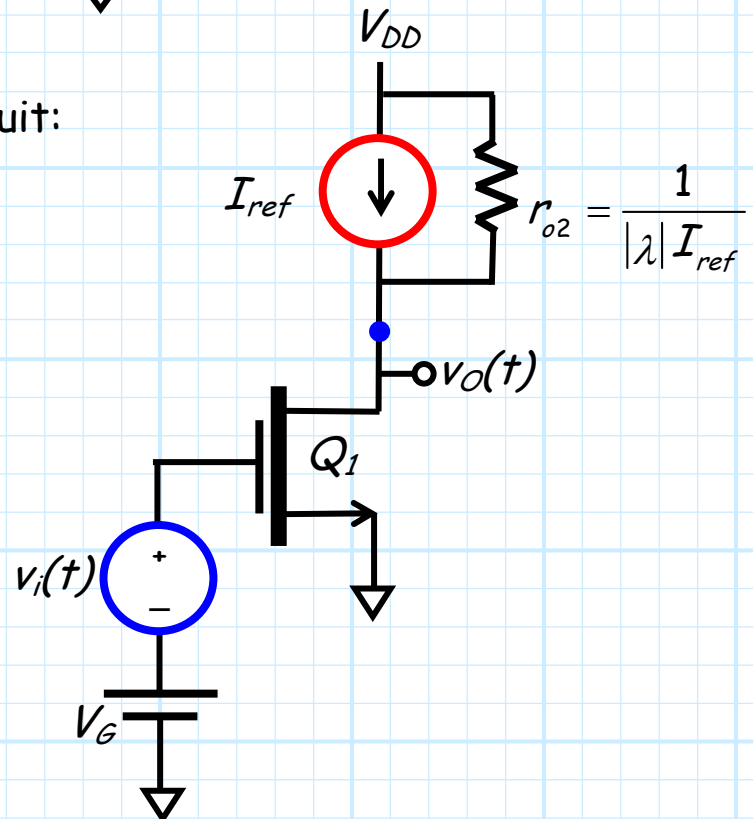

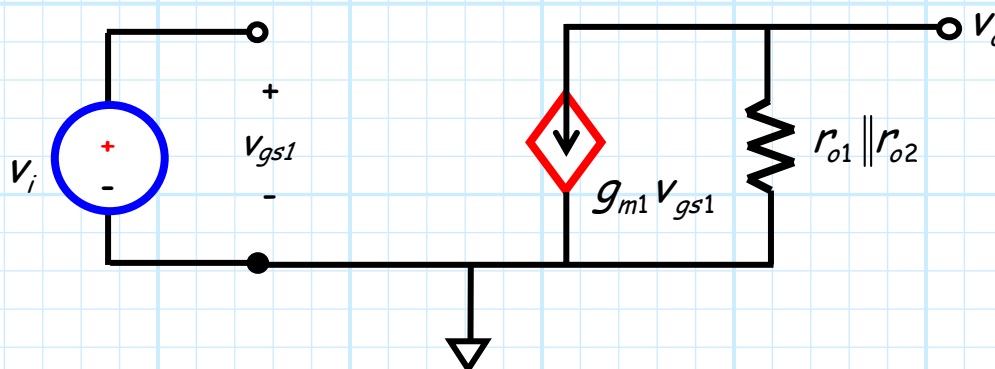The resulting small-signal circuit of this amp is:



And so the **open-circuit voltage gain** is:

$$A_{vo} = -g_{m1} (r_{o1} \parallel r_{o2}) = 2\sqrt{K_1} \sqrt{I_{ref}} (r_{o1} \parallel r_{o2})$$

Note **this** result is **far different** (i.e., larger) than the result when using the **enhancement load** for  $R_D$ :

$$A_{vo} = -\sqrt{\frac{K_1}{K_2}}$$

However, we find that the **output** and **input** resistances of this amplifier are the **same** as with the enhancement load:

$$R_i = \infty \qquad R_o = r_{o1} \parallel r_{o2}$$