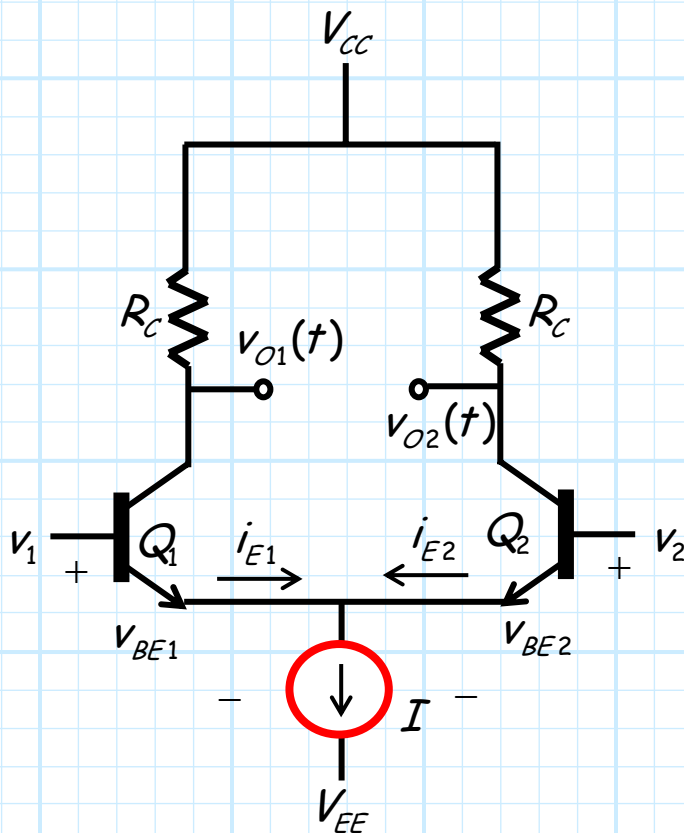


Large-Signal Operation of BJT Differential Pair

Consider the BJT differential pair:



Note:

$$V_{E1} = V_{E2} \doteq V_E$$

and:

$$i_{E1} + i_{E2} = I$$

Also, we know that:

$$i_{E1} = \frac{I_s}{\alpha} e^{V_{BE1}/V_T}$$

$$i_{E2} = \frac{I_s}{\alpha} e^{V_{BE2}/V_T}$$

where

$$V_{BE1} = V_1 - V_E$$

and

$$V_{BE2} = V_2 - V_E$$

Therefore, the **emitter currents** can be written in terms of the **base voltages** as:

$$i_{E1} = \left(\frac{I_s}{\alpha} e^{-v_E/V_T} \right) e^{v_1/V_T} \quad i_{E2} = \left(\frac{I_s}{\alpha} e^{-v_E/V_T} \right) e^{v_2/V_T} \quad (\text{A})$$

Of course, we know that $I = i_{E1} + i_{E2}$, thus:

$$I = \left(\frac{I_s}{\alpha} e^{-v_E/V_T} \right) \left(e^{v_1/V_T} + e^{v_2/V_T} \right)$$

And rearranging we find:

$$\frac{I_s}{\alpha} e^{-v_E/V_T} = \frac{I}{e^{v_1/V_T} + e^{v_2/V_T}} \quad (\text{B})$$

Now, we can insert equation **(B)** into equation **(A)** and find:

$$i_{E1} = \frac{I e^{v_1/V_T}}{e^{v_1/V_T} + e^{v_2/V_T}} = \frac{I}{1 + e^{-\frac{(v_1 - v_2)}{V_T}}}$$

as well as:

$$i_{E2} = \frac{I e^{v_2/V_T}}{e^{v_1/V_T} + e^{v_2/V_T}} = \frac{I}{1 + e^{+(v_1 - v_2)/V_T}}$$

Now, let's define a **differential voltage**:

$$v_D = v_1 - v_2$$

We can now (finally) write the emitter currents in terms of this differential voltage v_D **only!**

$$i_{E1} = \frac{I}{1 + e^{-v_D/V_T}}$$

$$i_{E2} = \frac{I}{1 + e^{+v_D/V_T}}$$


In other words, the emitter current in a differential pair is **independent** of the **common-mode** voltage $v_{cm} = (v_1 + v_2)/2$!

Now, let's examine this result more closely. We will consider **3 cases**, $v_D = 0$, $v_D \gg V_T$, and $v_D \ll -V_T$.

$$\underline{v_D = 0}$$

When $v_1 = v_2$ (i.e., $v_D = 0$), we find that the **emitter currents are equal**, with each taking **half** of the available current I :
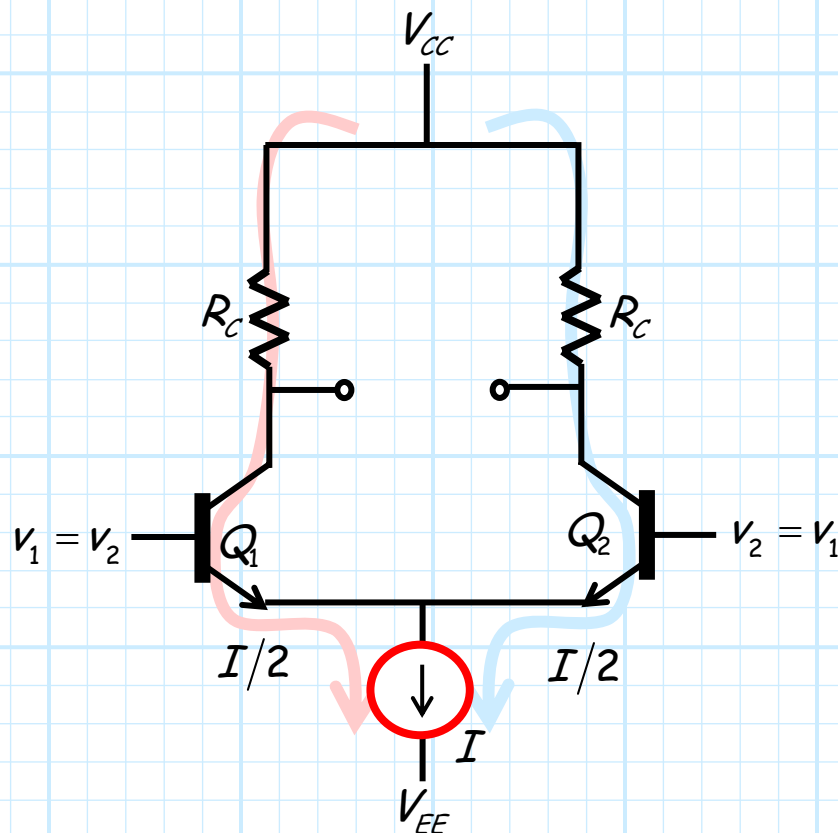
$$e^{v_D/V_T} = e^{-v_D/V_T} = 1, \quad \therefore i_{E1} = i_{E2} = \frac{I}{1+1} = \frac{I}{2}.$$




$$\underline{v_D \gg V_T}$$

When $v_D \gg V_T$ (i.e., $v_D \gg 25mV$), we find that the emitter current i_{E1} takes **all** the available current, leaving emitter current i_{E2} with **none**:

$$e^{-v_D/V_T} \approx 0, \quad \therefore \quad i_{E1} = \frac{I}{1+0} = I$$

and
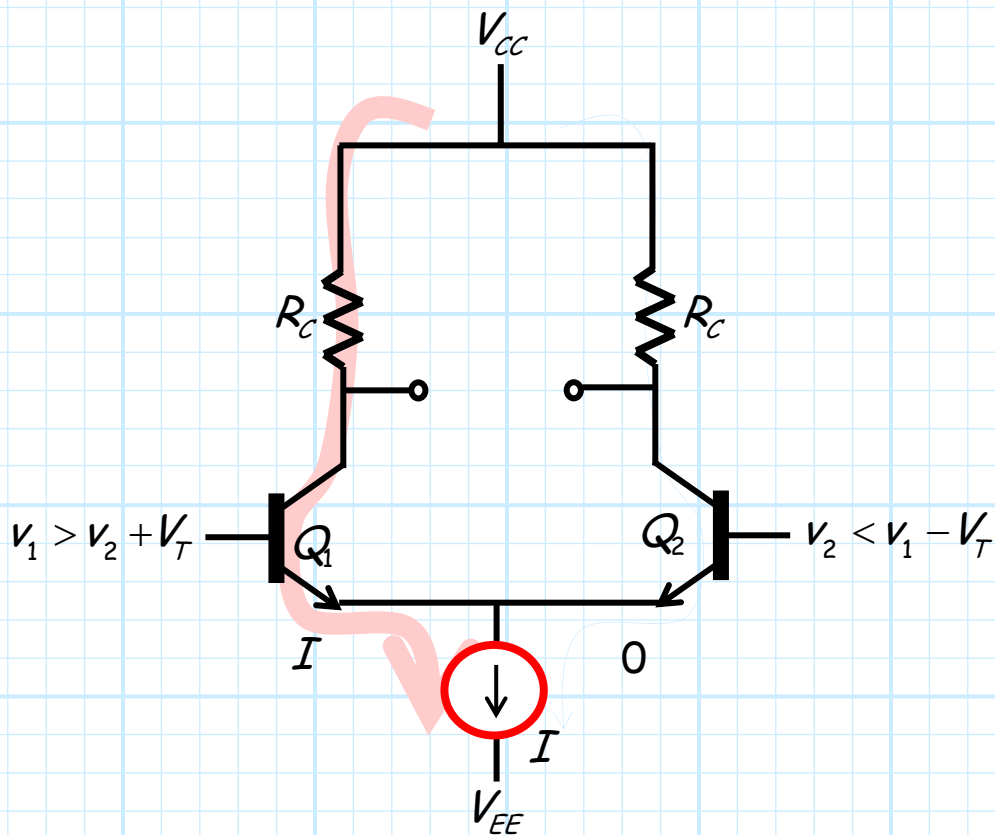
$$e^{v_D/V_T} \approx \infty, \quad \therefore \quad i_{E2} = \frac{I}{1+\infty} = 0$$




$$\underline{v_D \ll -V_T}$$

When $v_D \ll -V_T$ (i.e., $v_D \ll -25mV$), we find that the emitter current i_{E2} takes **all** the available current, leaving emitter current i_{E1} with **none**:

$$e^{-v_D/V_T} \approx \infty, \quad \therefore \quad i_{E1} = \frac{I}{1 + \infty} = 0$$


and
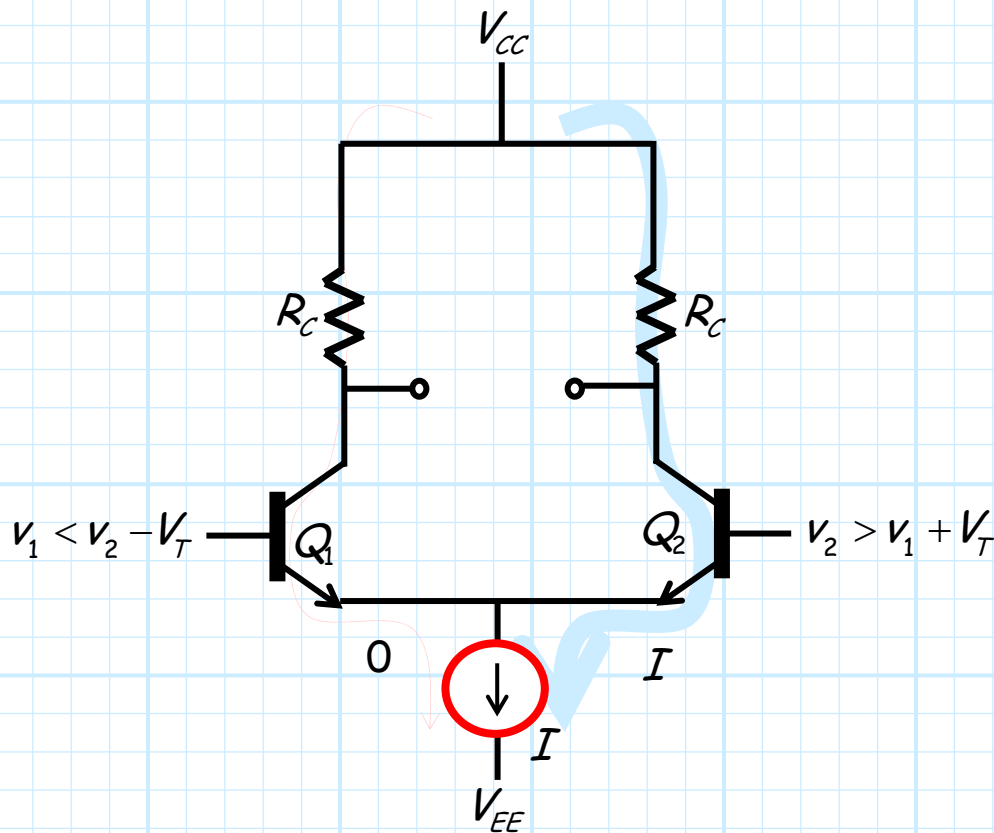
$$e^{v_D/V_T} \approx 0, \quad \therefore \quad i_{E2} = \frac{I}{1 + 0} = I$$



Recall that for BJTs in the active mode, the **collector** current is related to the emitter current by $i_C = \alpha i_E$.

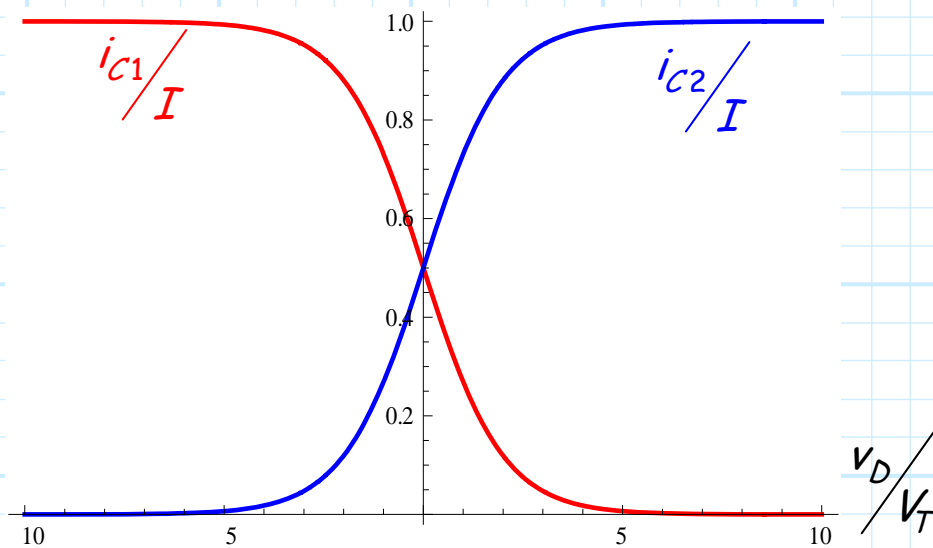Thus, we can **plot** the collector currents i_{C1} and i_{C2} as a function of differential voltage v_D :



Note for $|v_D| < \approx 2V_T$:

$$\left| \frac{di_C}{dv_D} \right| \gg 1$$

Q: *Is this important? What does this mean?*

A: