

Eigen Values of the Laplace Transform

Well, I fibbed a little when I stated that the Eigen function of linear, time-invariant systems (circuits) is:

$$\mathcal{L}\{e^{j\omega t}\} = G(\omega)e^{j\omega t}$$



Instead, the more **general** Eigen function is:

$$\mathcal{L}\{e^{st}\} = G(s)e^{st}$$

Where s is a **complex** (i.e., real and imaginary) frequency of the form:

$$s = \sigma + j\omega$$

such that:

$$e^{st} = e^{(\sigma + j\omega)t} = e^{\sigma t} e^{j\omega t}$$

Note then, if $\sigma = 0$, the Eigen function e^{st} becomes the previously described Eigen function $e^{j\omega t}$!


What does this function mean?

Q: *Yikes! I understand e^{st} even less than I understood $e^{j\omega t}$! What does this function mean?*

A: Remember, the function e^{st} is a **complex** function—it is actually an expression of **two real-value** functions.


These two real-valued functions could be its **real** and **imaginary** components:
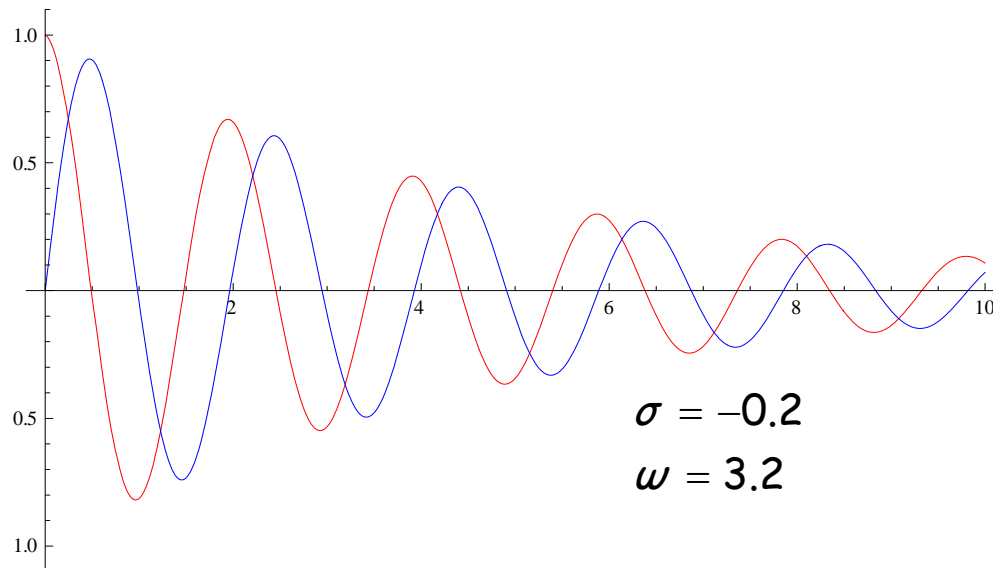
$$\begin{aligned} e^{st} &= e^{\sigma t} e^{+j\omega t} \\ &= e^{\sigma t} (\cos \omega t + j \sin \omega t) \\ &= e^{\sigma t} \cos \omega t + j e^{\sigma t} \sin \omega t \end{aligned}$$



Magnitude and phase

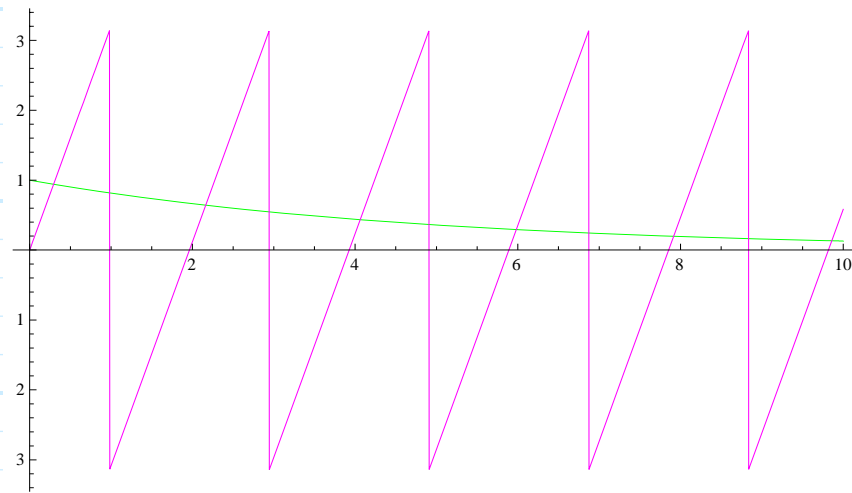
Or, the two real-valued functions could alternatively be the complex values **magnitude** and **phase**:



$$\sigma = -0.2$$

$$\omega = 3.2$$

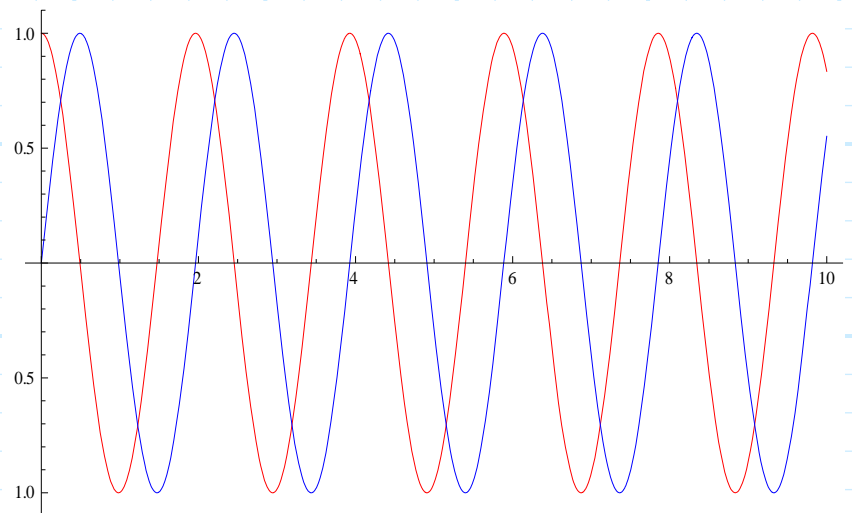If $\sigma = 0$, then $e^{st} = e^{+j\omega t}$, and we're back to the time-harmonic Eigen function:



$$\sigma = 0.0$$


$$\omega = 3.2$$

Can we use this as a basis?

Q: What about *basis functions*? Can we use these Eigen function to *expand* a signal?

A: Sure! Instead of the Fourier Transform, the result of expanding a signal with basis function e^{st} is the **Laplace Transform**.

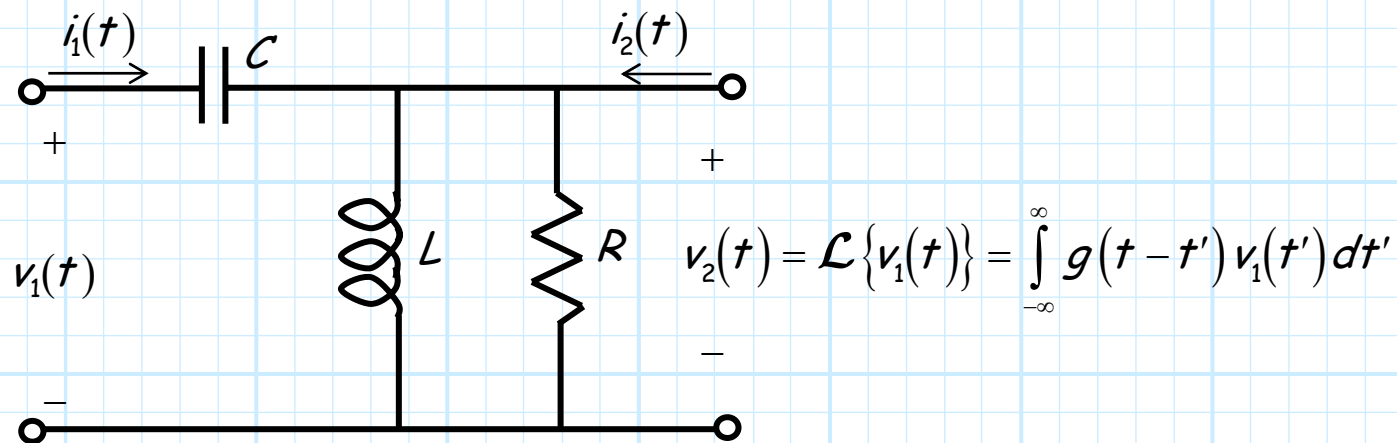For example, **again** consider the following linear circuit:



$$v_2(t) = \mathcal{L}\{v_1(t)\} = \int_{-\infty}^{\infty} g(t-t')v_1(t')dt'$$

A summary

Using the Laplace transform, we can determine the **output** voltage $v_2(t)$ by:

1. Expand the **input** signal $v_1(t)$ using the basis function e^{st} :

$$V_1(s) = \int_0^{+\infty} v_1(t) e^{-st} dt \quad (\text{or use a look-up table!})$$

2. Determine the **Eigen value** of the linear operator relating $v_1(t)$ to $v_2(t)$:

$$v_2(t) = \mathcal{L}\{v_1(t)\} = \int_{-\infty}^{\infty} g(t-t') v_1(t') dt'$$

$$\Rightarrow V_2(s) = G(s) V_1(s)$$

where:

$$G(s) = \int_{-\infty}^{+\infty} g(t) e^{-st} dt$$

3. Determine $v_2(t)$ from the **inverse** Laplace transform of $V_2(s)$ (**definitely** use a look-up table!).

The Eigen values of circuit elements

Q: But how do we determine $G(s)$?

A: It's just pretty darn simple!

Again, we determine the Eigen value of each linear operator of our **three** linear circuit elements—only **this** time we use the Eigen function e^{st} !

$$i_R(t) = \mathcal{L}_y^R[v_R(t)] = \frac{v_R(t)}{R}$$

$$\mathcal{L}_y^R[e^{st}] = \frac{e^{st}}{R}$$

$$I_R(s) = \frac{V_R(s)}{R}$$

$$i_C(t) = \mathcal{L}_y^C[v_C(t)] = C \frac{dv_C(t)}{dt}$$

$$\mathcal{L}_y^C[e^{st}] = C \frac{d e^{st}}{dt} = sC e^{st}$$


$$I_C(s) = sC V_C(s)$$

Just apply your circuits knowledge!


$$\mathcal{L}_y^L[v_L(t)] = i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t') dt'$$

$$\mathcal{L}_y^L[e^{st}] = \frac{1}{L} \int_{-\infty}^t e^{st'} dt' = \frac{1}{sL} e^{st}$$

$$I_L(s) = \frac{V_L(s)}{sL}$$

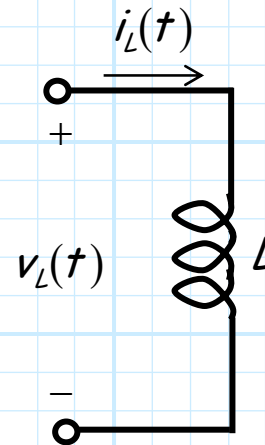

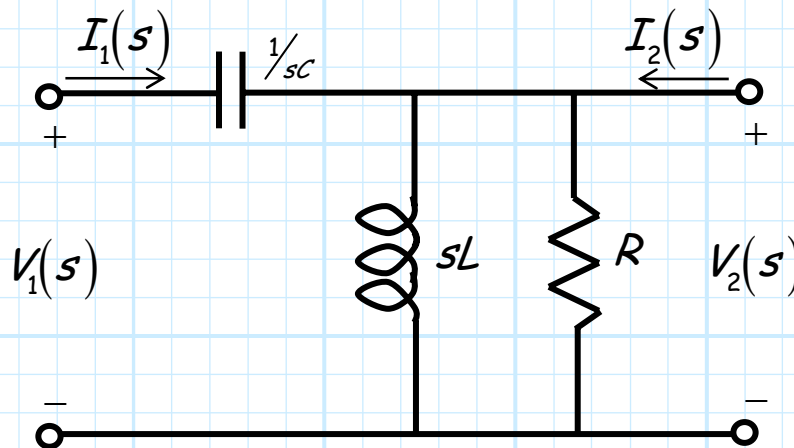As a result we can determine the Eigen value $G(s)$ of a linear circuit by applying our **circuit theory**:



$$\frac{V_2(s)}{V_1(s)} = G_{21}(s) = \frac{sL \parallel R}{\frac{1}{sC} + sL \parallel R}$$