




# Linear Circuit Elements

Most microwave devices can be described or modeled in terms of the **three** standard circuit elements:

1. RESISTANCE (R) 

2. INDUCTANCE (L) 


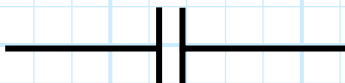
3. CAPACITANCE (C) 

For the purposes of circuit analysis, each of these three elements are **defined** in terms of the **mathematical** relationship between the difference in electric potential  $v(t)$  between the two terminals of the device (i.e., the **voltage** across the device), and the **current**  $i(t)$  flowing through the device.

We find that for these three circuit elements, the relationship between  $v(t)$  and  $i(t)$  can be expressed as a linear operator!

$$\mathcal{L}_y^R[v_R(t)] = i_R(t) = \frac{v_R(t)}{R}$$
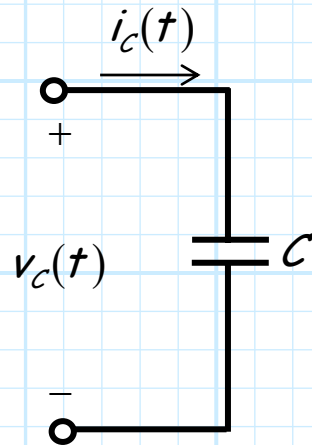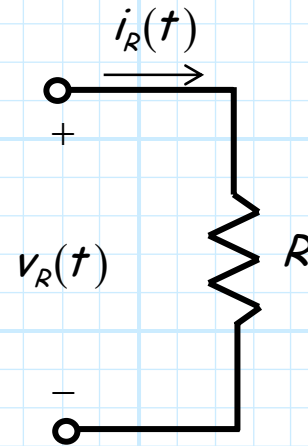
$$\mathcal{L}_z^R[i_R(t)] = v_R(t) = R i_R(t)$$




$$\mathcal{L}_y^C[v_C(t)] = i_C(t) = C \frac{dv_C(t)}{dt}$$

$$\mathcal{L}_z^C[i_C(t)] = v_C(t) = \frac{1}{C} \int_{-\infty}^t i_C(t') dt'$$

$$\mathcal{L}_y^L[v_L(t)] = i_L(t) = \frac{1}{L} \int_{-\infty}^t v_L(t') dt'$$
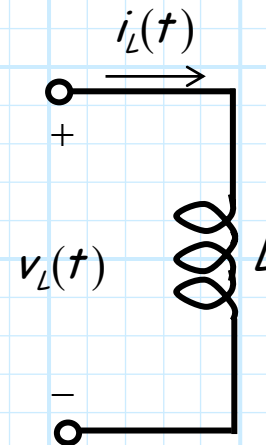
$$\mathcal{L}_z^L[i_L(t)] = v_L(t) = L \frac{di_L(t)}{dt}$$




Since the circuit behavior of these devices can be expressed with **linear** operators, these devices are referred to as **linear circuit elements**.
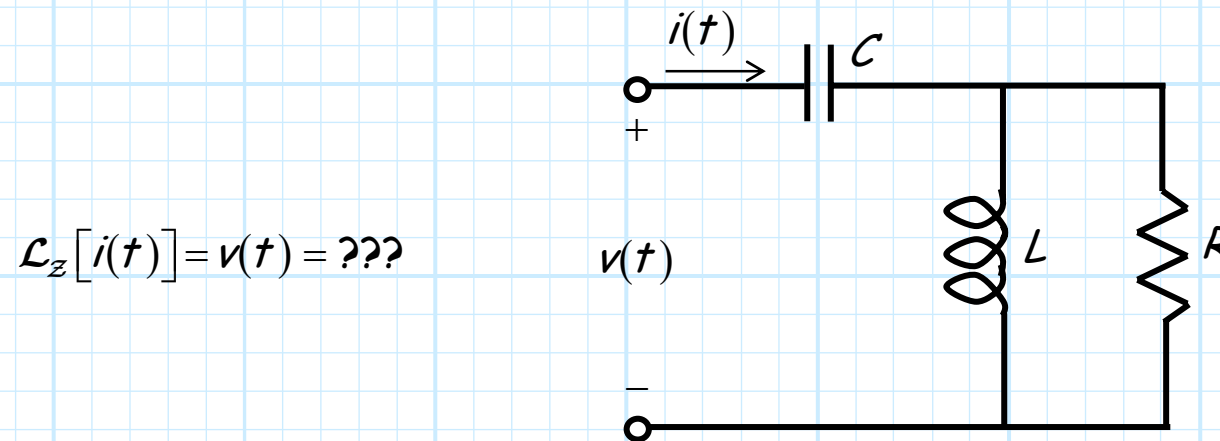
## A linear operator describes any relationship

**Q:** Well, that's simple enough, but what about an element formed from a **composite** of these fundamental elements?

For **example**, for example, how are  $v(t)$  and  $i(t)$  related in the circuit below??



**A:** It turns out that **any** circuit constructed **entirely** with linear circuit elements is **likewise** a linear system (i.e., a linear circuit).


As a result, we know that that there **must** be some linear operator that relates  $v(t)$  and  $i(t)$  in your example!

$$\mathcal{L}_Z[i(t)] = v(t)$$
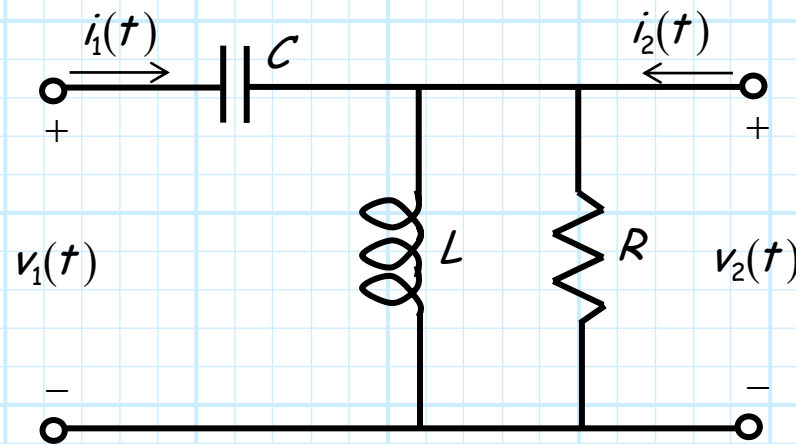
## This is very useful for multi-port networks

The circuit above provides a good example of a **single-port** (a.k.a. **one-port**) network.

We can of course construct networks with **two or more** ports; an example of a **two-port network** is shown below:



Since this circuit is **linear**, the relationship between **all** voltages and currents can likewise be expressed as **linear operators**, e.g.:

$$\mathcal{L}_{z_{21}}[v_1(t)] = v_2(t) \quad \mathcal{L}_{z_{21}}[i_1(t)] = v_2(t) \quad \mathcal{L}_{z_{22}}[i_2(t)] = v_2(t)$$

# The linear operator is a convolution integral


**Q:** *Yikes! What would these linear operators for this circuit be? How can we determine them?*

**A:** It turns out that linear operators for **all** linear circuits can all be expressed in precisely the **same** form!

For example, the linear operators of a single-port network are:

$$v(t) = \mathcal{L}_z[i(t)] = \int_{-\infty}^t g_z(t-t') i(t') dt'$$
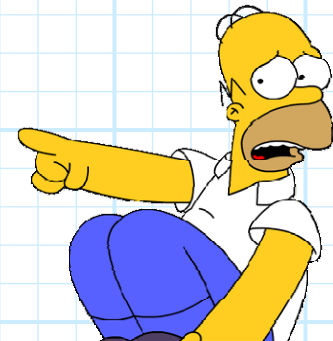
$$i(t) = \mathcal{L}_y[v(t)] = \int_{-\infty}^t g_y(t-t') v(t') dt'$$



In other words, the linear operator of linear circuits can always be expressed as a **convolution** integral—a convolution with a **circuit impulse function**  $g(t)$ .

# The impulse response

**Q:** *But just what is this "circuit impulse response"??*

**A:** An impulse response is simply the **response** of one circuit function (i.e.,  $i(t)$  or  $v(t)$ ) due to a **specific** stimulus by another.



That specific stimulus is the **impulse function**  $\delta(t)$ .

The impulse function **can** be defined as:

$$\delta(t) = \lim_{\tau \rightarrow 0} \frac{1}{\tau} \frac{\sin\left(\frac{\pi t}{\tau}\right)}{\left(\frac{\pi t}{\tau}\right)}$$

Such that it has the following two **properties**:

1.  $\delta(t) = 0$  for  $t \neq 0$

2.  $\int_{-\infty}^{\infty} \delta(t) dt = 1.0$

# We can define all sorts of impulse responses

The impulse responses of the **one-port example** are therefore defined as:

$$g_z(t) \doteq v(t) \Big|_{i(t)=\delta(t)}$$

and:

$$g_y(t) \doteq i(t) \Big|_{v(t)=\delta(t)}$$



Meaning simply that  $g_z(t)$  is equal to the **voltage** function  $v(t)$  when the circuit is "thumped" with a **impulse current** (i.e.,  $i(t) = \delta(t)$ ), and  $g_y(t)$  is equal to the **current**  $i(t)$  when the circuit is "thumped" with a **impulse voltage** (i.e.,  $v(t) = \delta(t)$ ).

## We can make convolution integrals simple!

Similarly, the relationship between the **input** and the **output** of a **two-port** network can be expressed as:

$$v_2(t) = \mathcal{L}_{21}[v_1(t)] = \int_{-\infty}^t g(t-t') v_1(t') dt'$$

where:

$$g(t) \doteq v_2(t) \Big|_{v_1(t)=\delta(t)}$$

Note that the circuit impulse response must be **causal** (nothing can occur at the output **until** something occurs at the input), so that:

$$g(t) = 0 \quad \text{for} \quad t < 0$$

**Q:** *Yikes! I recall evaluating convolution integrals to be messy, difficult and stressful. Surely there is an **easier** way to describe linear circuits!?!*

**A:** Nope! The convolution integral is **all** there is.

**However**, we can use our linear systems theory toolbox to greatly **simplify the evaluation** of a convolution integral!