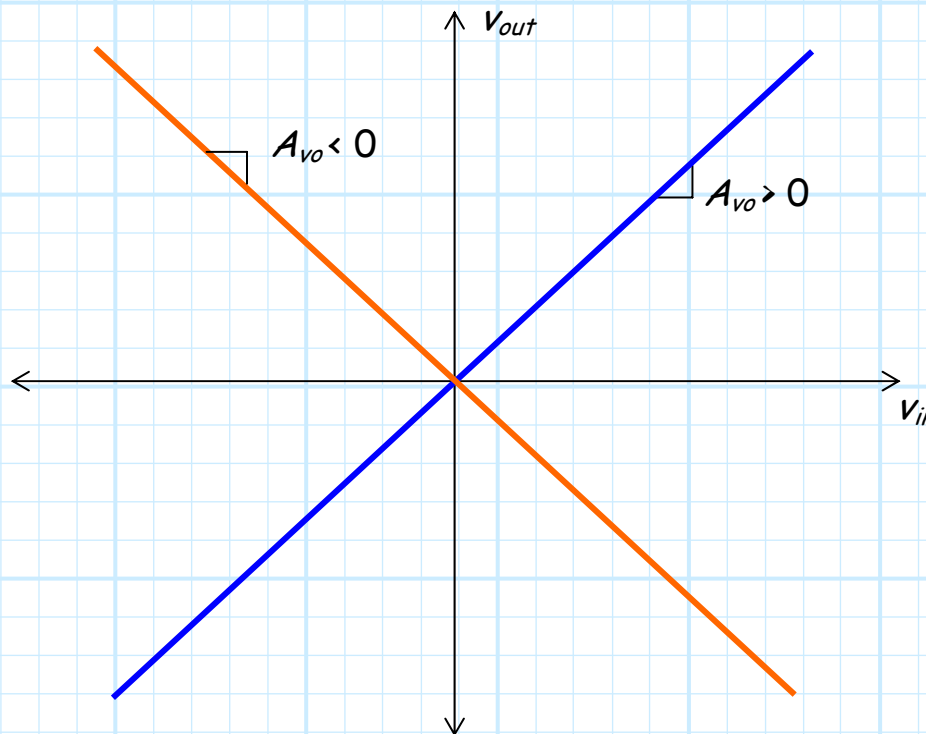


Non-Linear Behavior of Amplifiers

Note that the **ideal** amplifier transfer function:

$$v_{out}^{oc}(t) = A_{vo} v_i(t)$$

is an equation of a **line** (with slope = A_{vo} and y -intercept = 0).



The output voltage is limited

This **ideal** transfer function implies that the **output voltage** can be **very large**, provided that the gain A_{vo} and the input voltage v_{in} are large.

However, we find in a "real" amplifier that there are **limits** on how large the output voltage can become.

The transfer function of an amplifier is more **accurately** expressed as:

$$v_{out}(t) = \begin{cases} L_+ & v_{in}(t) > L_+^{in} \\ A_{vo} v_{in}(t) & L_-^{in} < v_{in}(t) < L_+^{in} \\ L_- & v_{in}(t) < L_-^{in} \end{cases}$$


Amplifier saturation

This expression is shown **graphically** as:

This expression (and graph) shows that electronic amplifiers have a **maximum** and **minimum** output voltage (L_+ and L_-).

If the **input** voltage is either too large or too small (too negative), then the amplifier **output** voltage will be equal to either L_+ or L_- .

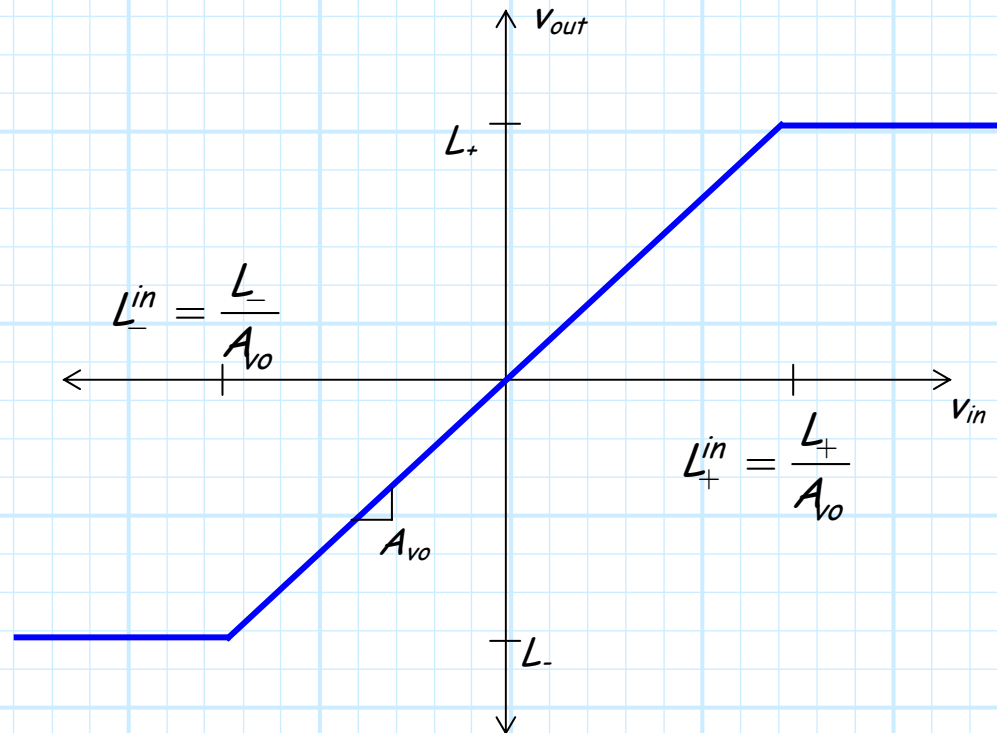If $v_{out} = L_+$ or $v_{out} = L_-$, we say the amplifier is in **saturation** (or compression).



Make sure the input isn't too large!

Amplifier saturation occurs when the **input** voltage is **greater** than:

$$v_{in} > \frac{L_+}{A_{vo}} \doteq L_+^{in}$$

or when the **input** voltage is **less** than:

$$v_{in} < \frac{L_-}{A_{vo}} \doteq L_-^{in}$$


Often, we find that these voltage limits are **symmetric**, i.e.:

$$L_- = -L_+ \quad \text{and} \quad L_-^{in} = -L_+^{in}$$

For example, the output limits of an amplifier might be $L_+ = 15$ V and $L_- = -15$ V.

However, we find that these limits are also often **asymmetric** (e.g., $L_+ = +15$ V and $L_- = +5$ V).

Saturation: Who really cares?

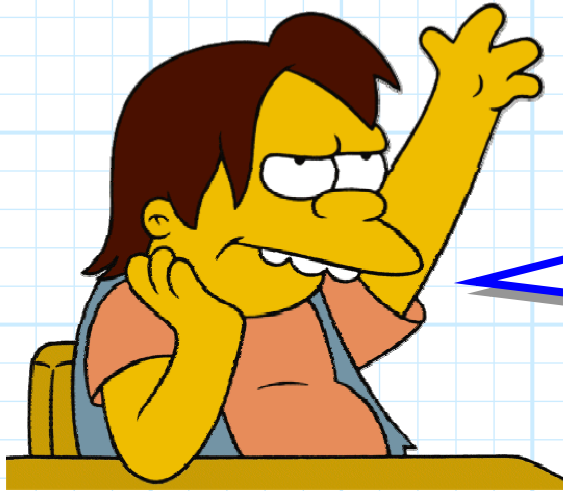


Q: *Why do we **care** if an amplifier saturates? Does it cause any **problems**, or otherwise result in performance **degradation**??*




A: **Absolutely!** If an amplifier saturates—even momentarily—the unavoidable result will be a **distorted** output signal.

A distortion free example

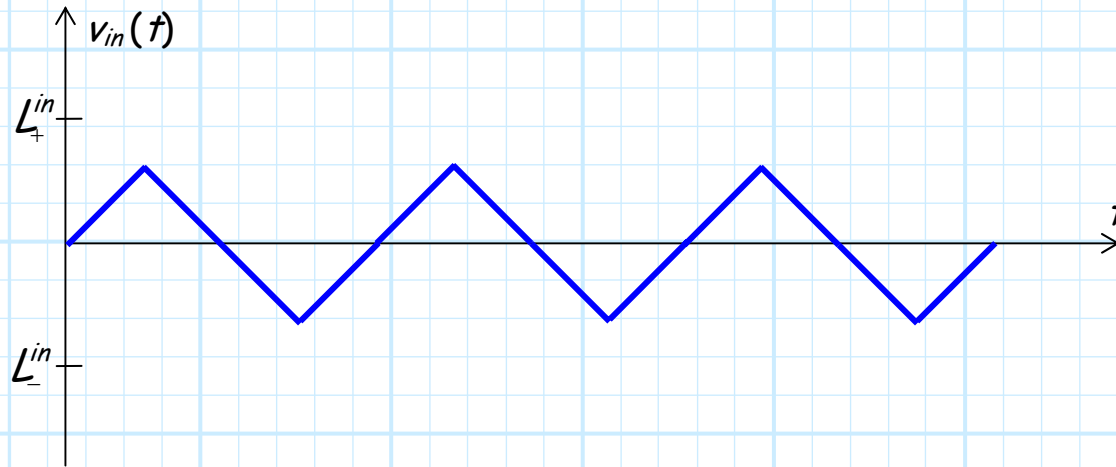For example, consider a case where the input to an amplifier is a **triangle wave**:




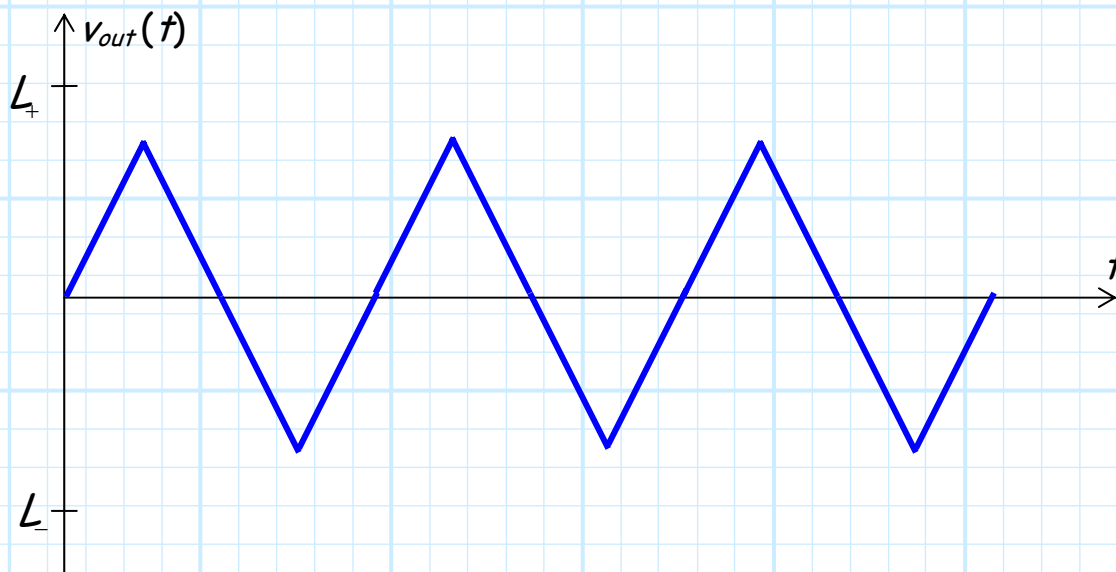Since $L_-^{in} < v_{in}(t) < L_+^{in}$ for all time t , the **output** signal will be within the limits L_+ and L_- for all time t , and thus the amplifier output will be $v_{out}(t) = A_{vo} v_{in}(t)$:



The input is too darn big!

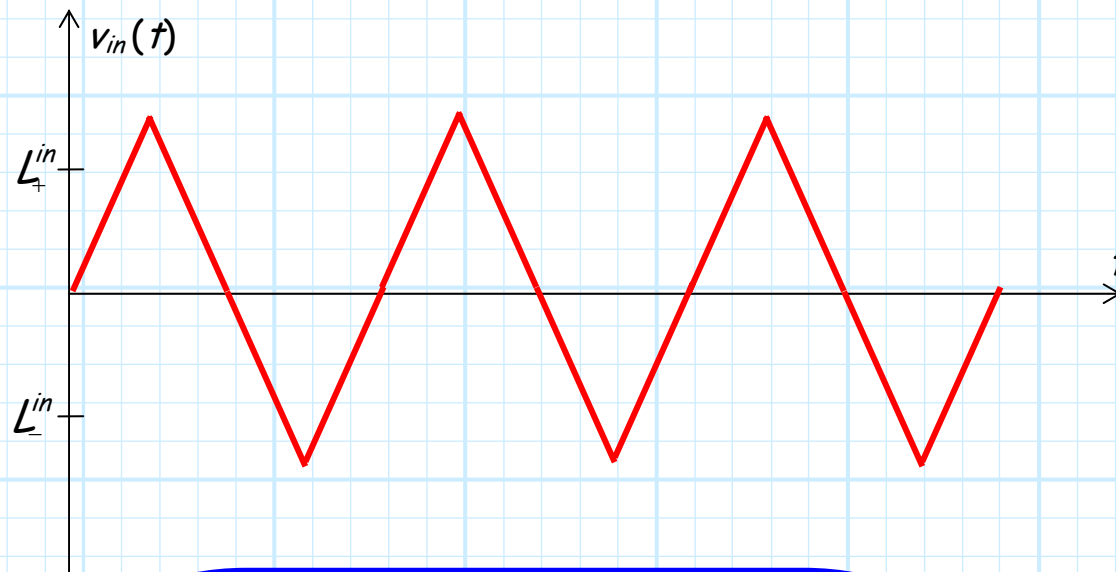Consider now the case where the input signal is much **larger**, such that $v_{in}(t) > L_+^{in}$ and $v_{in}(t) < L_-^{in}$ for some time t (e.g., the input triangle wave **exceeds** the voltage limits L_+^{in} and L_-^{in} some of the time):




*This is precisely the situation about which I earlier expressed **caution**.*

*We now must experience the palpable agony of **signal distortion!***



Palpable agony

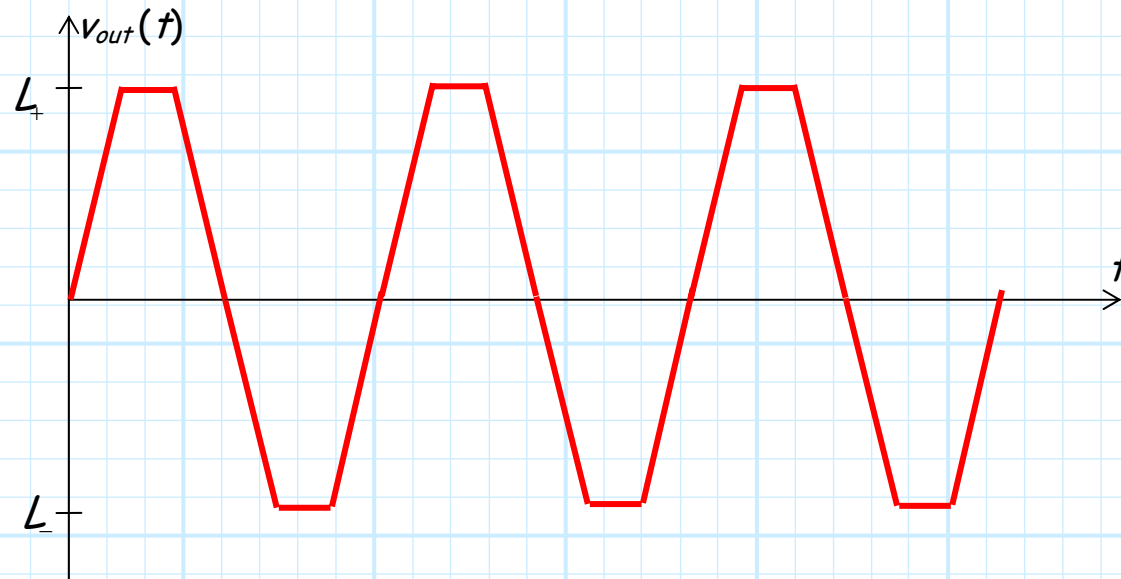

Note that this output signal is **not** a triangle wave!

For time t where $v_{in}(t) > L_+^{in}$ and $v_{in}(t) < L_-^{in}$, the value $A_{vo} v_{in}(t)$ is greater than L_+ and less than L_- , respectively.



Thus, the output voltage is limited to $v_{out}(t) = L_+$ and $v_{out}(t) = L_-$ for these times.

As a result, we find that output $v_{out}(t)$ does **not** equal $A_{vo} v_{in}(t)$ —the output signal is **distorted!**

"Soft" Saturation

In reality, the **saturation** voltages L_+ , L_- , L_+^{in} , and L_-^{in} are not so **precisely** defined.

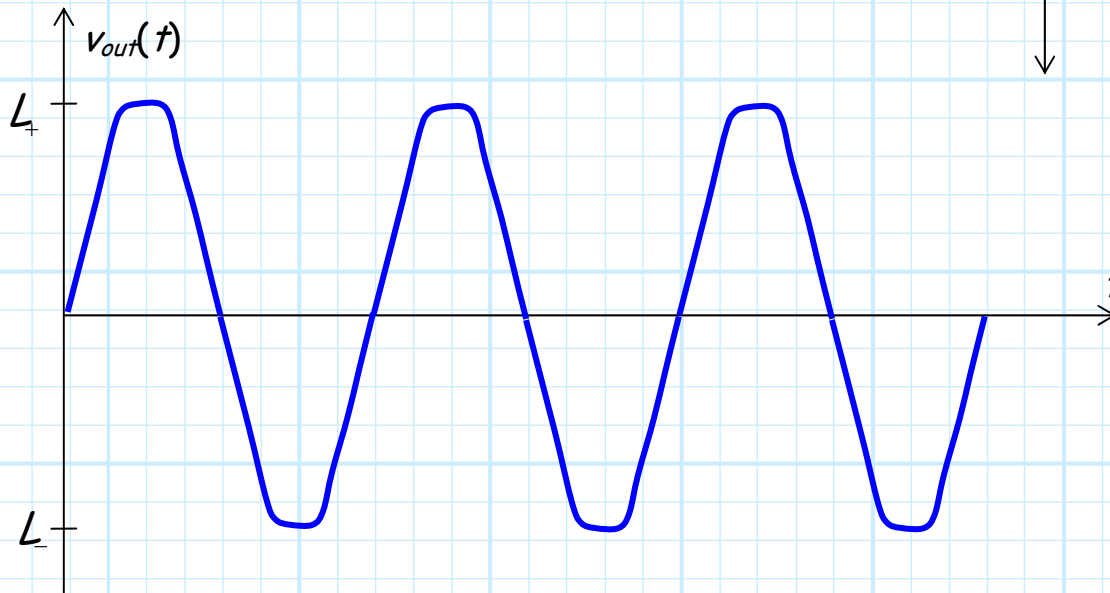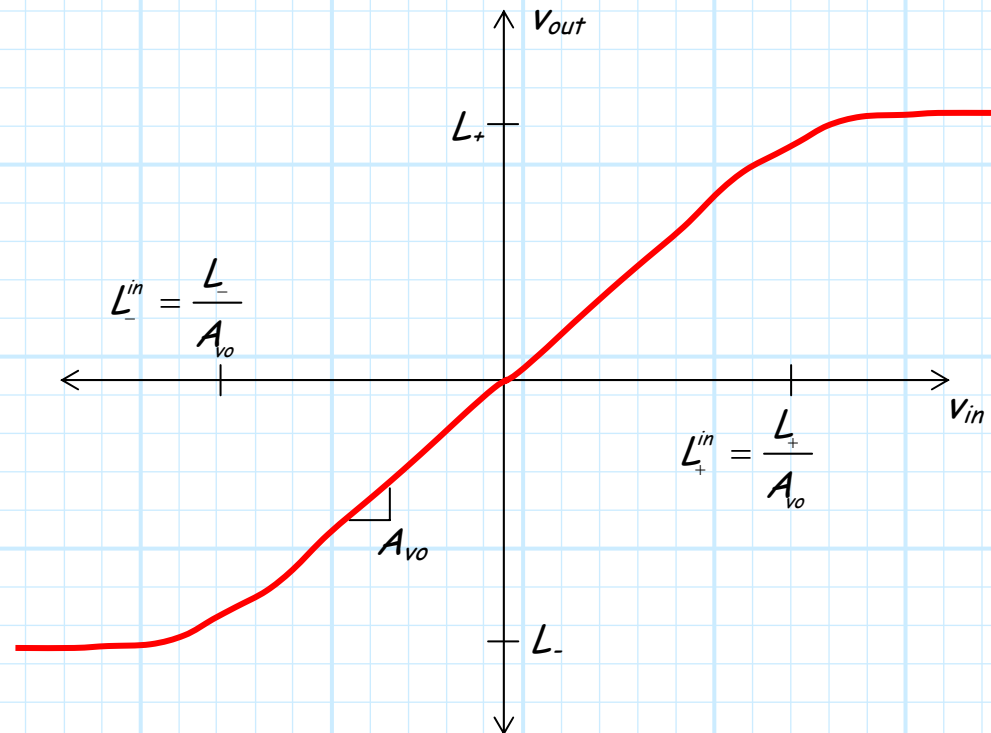
The transition from the linear amplifier region to the saturation region is **gradual**, and cannot be unambiguously defined at a precise point.



Yet another problem: DC offset

Now for another **non-linear** problem!

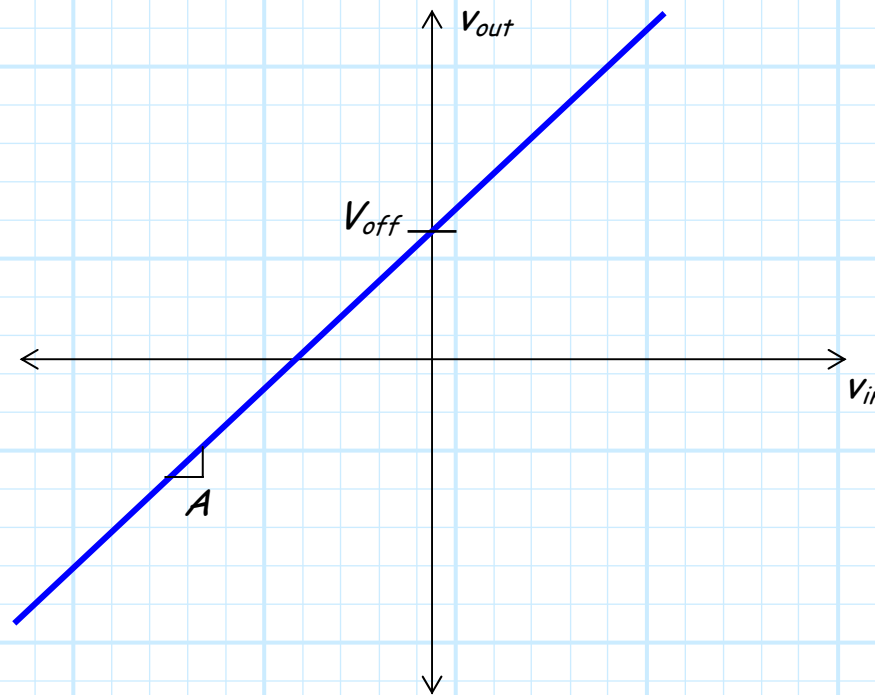We will find that many amplifiers exhibit a **DC offset** (i.e., a **DC bias**) at their output.



How do we define gain?

The output of these amplifiers can be expressed as:

$$v_{out}(t) = A v_{in}(t) + V_{off}$$

where A and V_{off} are constants.

It is evident that if the input is **zero**, the output voltage will **not** be (zero, that is)!

i.e., $v_{out} = V_{off}$ if $v_{in} = 0$



Q: *Yikes! How do we determine the **gain** of such an amplifier?*

If: $v_{out}(t) = A v_{in}(t) + V_{off}$

then what is:

$$\frac{v_{out}(t)}{v_{in}(t)} = \text{?????}$$

*The **ratio** of the output voltage to input voltage is **not a constant!***

Calculus: is there anything it can't do?

A: The gain of any amplifier can be defined more precisely using the **derivative** operator:

$$A_{vo} \doteq \frac{dv_{out}}{dv_{in}}$$

Thus, for an amplifier with an output DC offset, we find the voltage gain to be:

$$A_{vo} = \frac{dv_{out}}{dv_{in}} = \frac{d(Av_{in} + V_{off})}{dv_{in}} = A$$

In other words, the gain of an amplifier is determined by the **slope** of the transfer function!

This sort of makes sense!

For an amplifier with **no** DC offset (i.e., $v_o = A_{vo} v_i$), it is easy to see that the gain is **likewise** determined from this definition:

$$A_{vo} = \frac{dv_{out}}{dv_{in}} = \frac{dA_{vo}v_{in}}{dv_{in}} = A_{vo}$$

*Hey, hey! This definition makes sense if you think about it—gain is the **change** of the output voltage with respect to a **change** at the input.*

*For example, of small change Δv_{in} at the **input** will result in a change of $A_{vo} \Delta v_{in}$ at the **output**.*

*If A_{vo} is **large**, this change at the output will be **large**!*



Both problems collide

OK, here's **another** problem.

The derivative of the transfer curve for **real** amplifiers will **not be a constant**.

We find that the gain of a amplifier will often be **dependent** on the input voltage!

The main reason for this is amplifier **saturation**.

Consider again the transfer function of an amplifier that **saturates**:


$$v_{out} = \begin{cases} L_+ & v_{in} > L_+^{in} \\ Av_{in} + V_{off} & L_-^{in} < v_i < L_+^{in} \\ L_- & v_{in} < L_-^{in} \end{cases}$$

Gain is a function of v_{in}

We find the **gain** of this amplifier by taking the **derivative** with respect to v_{in} :

$$A_{vo} = \frac{dv_{out}}{dv_{in}} = \begin{cases} 0 & v_{in} > L_+^{in} \\ A & L_-^{in} < v_{in} < L_+^{in} \\ 0 & v_{in} < L_-^{in} \end{cases}$$

Graphically, this result is:

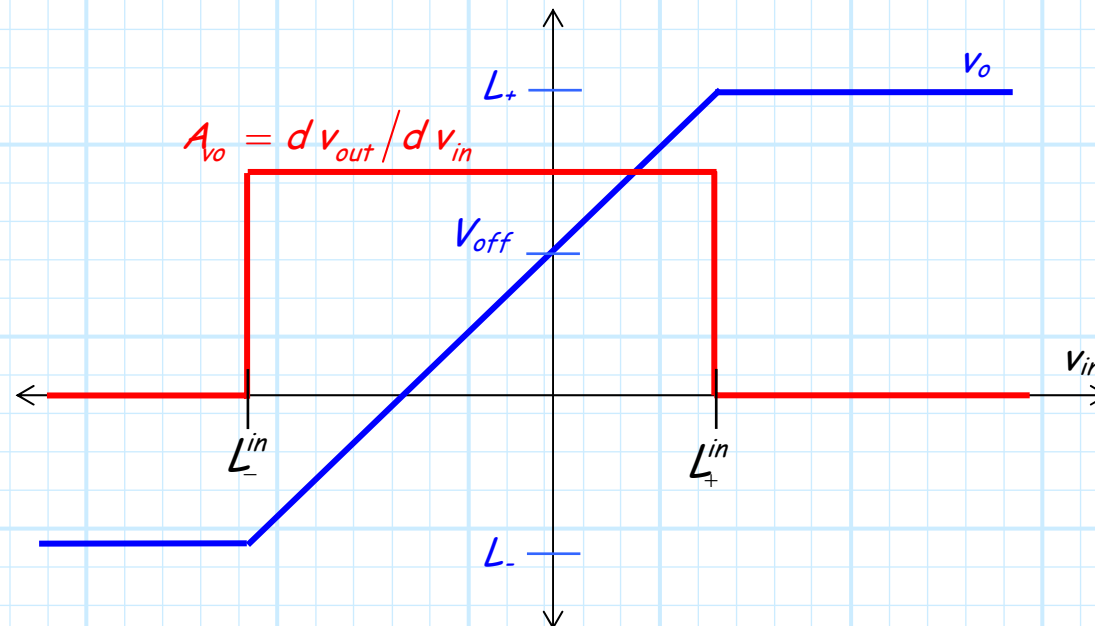

You'll see this transfer function again!

Thus, the gain of this amplifier when in saturation is **zero**. A change in the input voltage will result in **no change** on the output—the output voltage will simply be $v_o = V_{\pm}$.

Again, the transition into saturation is **gradual** for real amplifiers.

In fact, we will find that many of the amplifiers studied in this class have a **transfer function** that looks something like this→

We will find that the voltage gain of many amplifiers is **dependent** on the input voltage.

Thus, a **DC bias** at the input of the amplifier is often required to **maximize** the amplifier gain.

