

# The Eigen Values of Linear Circuits

Recall the linear operators that define a capacitor:

$$\mathcal{L}_y^c[v_c(t)] = i_c(t) = C \frac{dv_c(t)}{dt}$$

$$\mathcal{L}_z^c[i_c(t)] = v_c(t) = \frac{1}{C} \int_{-\infty}^t i_c(t') dt'$$

We now know that the **Eigen function** of these linear, time-invariant operators—like **all** linear, time-invariant operators—is  $\exp[j\omega t]$ .

The question now is: **what is the Eigen value** of each of these operators?

It is this value that **defines** the physical behavior of a given capacitor!

## The operator is linear

For  $v_c(t) = \exp[j\omega t]$ , we find:

$$\begin{aligned}i_c(t) &= \mathcal{L}_y^c[v_c(t)] \\ &= C \frac{d e^{j\omega t}}{dt} \\ &= (j\omega C) e^{j\omega t}\end{aligned}$$

Just as we expected, the Eigen function  $\exp[j\omega t]$  “survives” the linear operation **unscathed**—the current function  $i(t)$  has **precisely** the same form as the voltage function  $v(t) = \exp[j\omega t]$ .

The **only** difference between the **current** and **voltage** is the multiplication of the **Eigen value**, denoted as  $G_y^c(\omega)$ .

$$i_c(t) = \mathcal{L}_y^c[v(t) = e^{j\omega t}] = G_y^c(\omega) e^{j\omega t}$$

# The Eigen value of a capacitor

Since we **just** determined that for this case:

$$i_c(t) = (j\omega C) e^{j\omega t}$$

it is **evident** that the Eigen value of the linear operation:

$$i(t) = \mathcal{L}_y^C[v(t)] = C \frac{dv(t)}{dt}$$

is:

$$G_y^C(\omega) = j\omega C = \omega C e^{j\pi/2} \quad !!!$$

## Let's now consider real-valued functions

So for example, if:

$$\begin{aligned} v(t) &= V_m \cos(\omega_o t + \varphi) \\ &= \operatorname{Re} \left\{ (V_m e^{j\varphi}) e^{j\omega_o t} \right\} \end{aligned}$$

we will find that:

$$\begin{aligned} \mathcal{L}_y^{\mathcal{C}} \left[ (V_m e^{j\varphi}) e^{j\omega_o t} \right] &= \mathcal{G}_y^{\mathcal{C}}(\omega_o) (V_m e^{j\varphi}) e^{j\omega_o t} \\ &= \left( \omega C e^{j\pi/2} \right) (V_m e^{j\varphi}) e^{j\omega_o t} \\ &= \left( \omega C V_m e^{j(\pi/2 + \varphi)} \right) e^{j\omega_o t} \end{aligned}$$

Therefore:

$$\begin{aligned} i_c(t) &= \operatorname{Re} \left\{ \omega C V_m e^{j(\varphi + \pi/2)} e^{j\omega_o t} \right\} \\ &= \omega C V_m \cos\left(\omega_o t + \varphi + \pi/2\right) \\ &= -\omega C V_m \sin(\omega_o t + \varphi) \end{aligned}$$

## Remember what the complex value means

Hopefully, this example again emphasizes that these **real-valued** sinusoidal functions can be completely expressed in terms of **complex values**.

For **example**, the complex value:

$$V_C = V_m e^{j\varphi}$$

means that the magnitude of the sinusoidal **voltage** is  $|V_C| = V_m$ , and its relative phase is  $\angle V_C = \varphi$ . The complex value:

$$I_C = G_y^C(\omega) V_C = \left( \omega C e^{j\pi/2} \right) V_C$$

likewise means that the **magnitude** of the sinusoidal **current** is:

$$|I_C| = |G_y^C(\omega) V_C| = |G_y^C(\omega)| |V_C| = \omega C V_m$$


And the relative **phase** of the sinusoidal **current** is:

$$\angle I_C = \angle G_y^C(\omega) + \angle V_C = \frac{\pi}{2} + \varphi$$
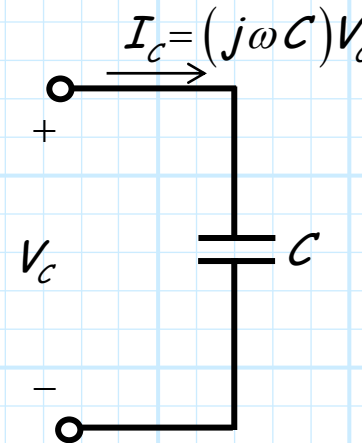
## Now find the voltage from the current

We can thus **summarize** the behavior of a capacitor with the simple **complex equation**:

$$\begin{aligned} I_c &= (j\omega C) V_c \\ &= \left( \omega C e^{j\pi/2} \right) V_c \end{aligned}$$



Now let's return to the **second** of the two linear operators that describe a capacitor:

$$v_c(t) = \mathcal{L}_z^C [i_c(t)] = \frac{1}{C} \int_{-\infty}^t i_c(t') dt'$$

Now, if the capacitor **current** is the Eigen function  $i_c(t) = \exp[j\omega t]$ , we find:

$$\mathcal{L}_z^C [e^{j\omega t}] = \frac{1}{C} \int_{-\infty}^t e^{j\omega t'} dt' = \left( \frac{1}{j\omega C} \right) e^{j\omega t}$$

where we assume  $i(t = -\infty) = 0$ .

# The Eigen value of this linear operator

Thus, we can conclude that:

$$\mathcal{L}_Z^C [e^{j\omega t}] = G_Z^C(\omega) e^{j\omega t} = \left( \frac{1}{j\omega C} \right) e^{j\omega t}$$

Hopefully, it is evident that the **Eigen value** of this linear operator is:

$$G_Z^C(\omega) = \frac{1}{j\omega C} = \frac{-j}{\omega C} = \frac{1}{\omega C} e^{j(3\pi/2)}$$

And so:

$$V_C = \left( \frac{1}{j\omega C} \right) I_C$$

## Impedance is simply an Eigen value!

**Q:** Wait a second! Isn't this essentially the **same** result as the one derived for operator  $\mathcal{L}_y^C$ ??

**A:** It's **precisely** the same! For both operators we find:

$$\frac{V_C}{I_C} = \frac{1}{j\omega C}$$

This should **not** be surprising, as **both** operators  $\mathcal{L}_y^C$  and  $\mathcal{L}_z^C$  relate the current through and voltage across the **same** device (a capacitor).

The **ratio** of complex voltage to complex current is of course referred to as the complex device **impedance**  $Z$ .


$$Z \doteq \frac{V}{I}$$

An **impedance** can be determined for **any** linear, time-invariant **one-port** network—but **only** for linear, time-invariant one-port networks!


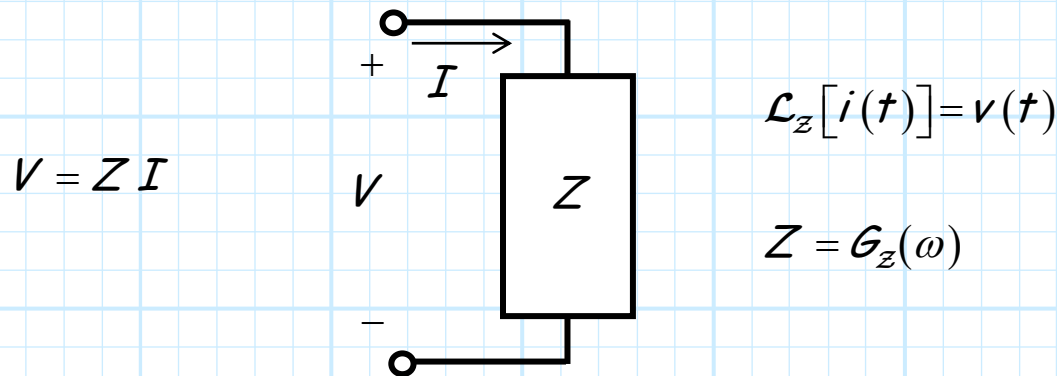
## Know what impedance tells you!

Generally speaking, impedance is a **function of frequency**. In fact, the impedance of a one-port network is simply the **Eigen value**  $G_Z(\omega)$  of the linear operator  $\mathcal{L}_Z$ :



Note that impedance is a **complex** value that provides us with **two** things:

1. The **ratio of the magnitudes** of the sinusoidal voltage and current:

$$|Z| = \frac{|V|}{|I|}$$

2. The **difference in phase** between the sinusoidal voltage and current:

$$\angle Z = \angle V - \angle I$$

# Admittance

**Q:** *What about the linear operator:*

$$\mathcal{L}_y[v(t)] = i(t) \quad ??$$

**A:** Hopefully it is now evident to **you** that:

$$G_y(\omega) = \frac{1}{G_z(\omega)} = \frac{1}{Z}$$

The inverse of impedance is **admittance**  $Y$ :

$$Y \doteq \frac{1}{Z} = \frac{I}{V}$$

## Inductors and resistors

Now, returning to the **other two** linear circuit elements, we find (and **you** can verify) that for resistors:

$$\mathcal{L}_y^R[v_R(t)] = i_R(t) \Rightarrow G_y^R(\omega) = 1/R$$

$$\mathcal{L}_z^R[i_R(t)] = v_R(t) \Rightarrow G_z^R(\omega) = R$$

and for inductors:

$$\mathcal{L}_y^L[v_L(t)] = i_L(t) \Rightarrow G_y^L(\omega) = \frac{1}{j\omega L}$$

$$\mathcal{L}_z^L[i_L(t)] = v_L(t) \Rightarrow G_z^L(\omega) = j\omega L$$

meaning:

$$Z_R = \frac{1}{Y_R} = R = R e^{j0} \quad \text{and} \quad Z_L = \frac{1}{Y_L} = j\omega L = \omega L e^{j(\pi/2)}$$

# All the rules of circuit theory apply to complex currents and voltages too

Now, note that the relationship

$$Z = \frac{V}{I}$$

forms a **complex "Ohm's Law"** with regard to complex currents and voltages.

Additionally, ICBST (It Can Be Shown That) **Kirchoff's Laws** are likewise valid for complex currents and voltages:

$$\sum_n I_n = 0 \qquad \sum_n V_n = 0$$


where of course the summation represents **complex addition**.

As a result, the impedance (i.e., the Eigen value) of **any** one-port device can be determined by simply applying a **basic** knowledge of **linear circuit analysis!**

# We can determine Eigen values without knowing the impulse response!

Returning to the example:

$$Z = \frac{V}{I}$$

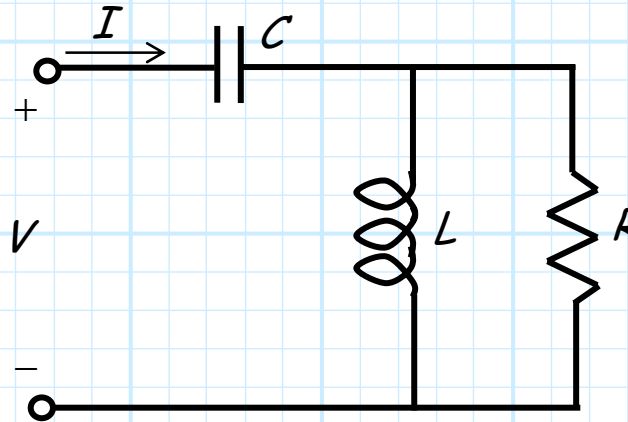

And thus using out **basic** circuits knowledge, we find:

$$Z = Z_C + Z_R \parallel Z_L = \frac{1}{j\omega C} + R \parallel j\omega L$$

Thus, the Eigen value of the linear operator:

$$\mathcal{L}_Z[i(t)] = v(t)$$

For **this** one-port network is:

$$G_Z(\omega) = \frac{1}{j\omega C} + R \parallel j\omega L$$

## No need for convolution!

**Look** what we did! We were able to determine  $G_z(\omega)$  **without** explicitly determining impulse response  $g_z(t)$ , or having to perform **any** integrations!

Now, if we actually **need** to determine the voltage function  $v(t)$  created by some **arbitrary** current function  $i(t)$ , we integrate:

$$\begin{aligned} v(t) &= \frac{1}{2\pi} \int_{-\infty}^{+\infty} G_z(\omega) I(\omega) e^{j\omega t} d\omega \\ &= \frac{1}{2\pi} \int_{-\infty}^{+\infty} \left( \frac{1}{j\omega C} + R \parallel j\omega L \right) I(\omega) e^{j\omega t} d\omega \end{aligned}$$

where:

$$I(\omega) = \int_{-\infty}^{+\infty} i(t) e^{-j\omega t} dt$$


Otherwise, if our current function is **time-harmonic** (i.e., sinusoidal with frequency  $\omega$ ), we can simply relate complex current  $I$  and complex voltage  $V$  with the equation:

$$\begin{aligned} V &= Z I \\ &= \left( \frac{1}{j\omega C} + R \parallel j\omega L \right) I \end{aligned}$$

## See how easy this is?

Similarly, for our **two-port** example, we can likewise determine from **basic** circuit theory the **Eigen value** of linear operator:

$$\mathcal{L}_{21}[v_1(t)] = v_2(t)$$

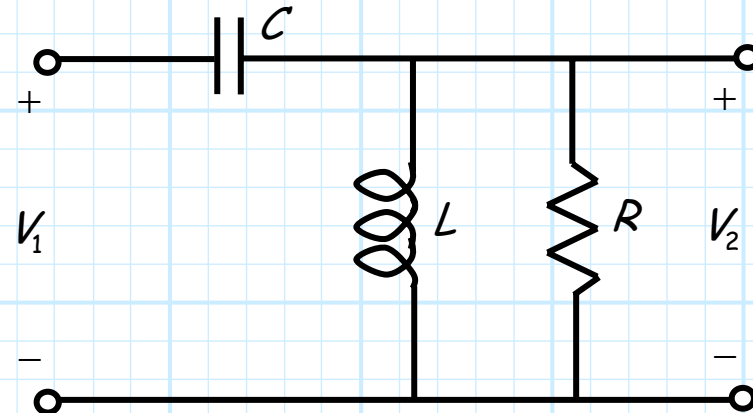

is:

$$G_{21}(\omega) = \frac{Z_L \parallel Z_R}{Z_C + Z_L \parallel Z_R} = \frac{j\omega L \parallel R}{\frac{1}{j\omega C} + j\omega L \parallel R}$$

so that:

$$V_2 = G_{21}(\omega) V_1$$

or more generally:

$$v_2(t) = \frac{1}{2\pi} \int_{-\infty}^{+\infty} G_{21}(\omega) V_1(\omega) e^{j\omega t} d\omega$$

where:

$$V_1(\omega) = \int_{-\infty}^{+\infty} v_1(t) e^{-j\omega t} dt$$