

DC Biasing of MOSFET Differential Pairs

Consider now the MOSFET differential pair:


Note:

$$V_{S1} = V_{S2} = V_S$$

and

$$i_{D1} + i_{D2} = I$$

Figure 7.1 The basic MOS differential-pair

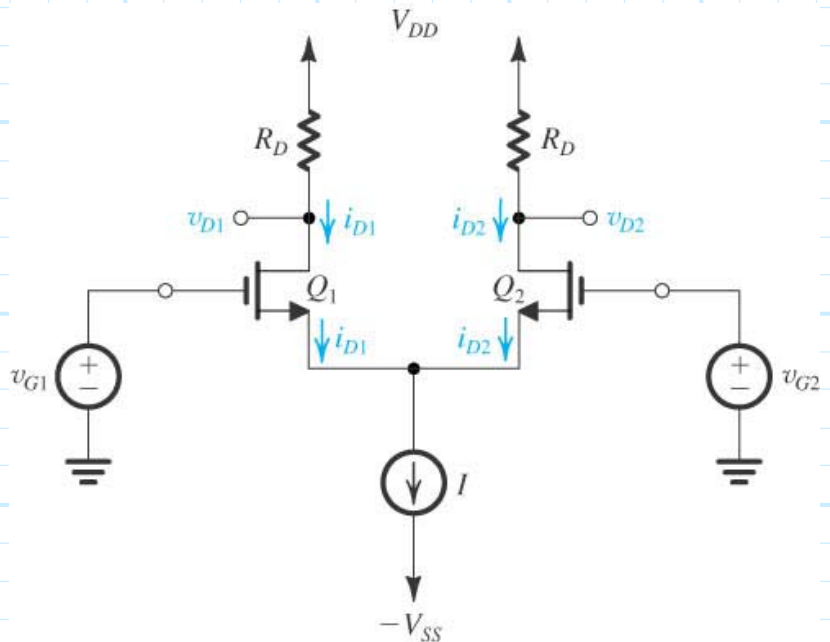

If each of the transistors are in saturation, then each drain current must be:

$$i_{D1} = K(v_{GS1} - V_t)^2 \quad \text{and} \quad i_{D2} = K(v_{GS2} - V_t)^2$$

where

$$v_{GS1} = v_1 - v_S \quad \text{and} \quad v_{GS2} = v_2 - v_S$$

Therefore, we define the differential input voltage as:

$$V_{GS1} - V_{GS2} = V_1 - V_2 \doteq V_D$$

Now, doing just a bunch of algebra, we can combine all of the above equations to find the drain current for each transistor:

$$i_{D1} = \frac{I}{2} + \sqrt{\frac{KI}{2}} v_D \sqrt{1 - \frac{K}{2I} v_D^2}$$

$$i_{D2} = \frac{I}{2} - \sqrt{\frac{KI}{2}} v_D \sqrt{1 - \frac{K}{2I} v_D^2}$$



*Note this result shows that the drain current of each transistor is dependent **only** on the **differential signal** $v_D = v_1 - v_2$ --the drain currents are **independent** of the **common-mode** (i.e., average) input signal!*

Note then, that if:

$$\underline{v_D = 0}$$

Both transistors will be in saturation and will share the available current evenly:

$$i_{D1} = i_{D2} = \frac{I}{2}$$

$$\underline{v_D < -\sqrt{\frac{2I}{K}}}$$

For this case, Q_1 is in cutoff and we find that:

$$i_{D1} = 0$$

whereas transistor Q_2 remains in saturation and "takes" all the available current:

$$i_{D2} = I$$

$$\underline{v_D > +\sqrt{\frac{2I}{K}}}$$

For this case, Q_2 is now in cutoff and we find that:

$$i_{D2} = 0$$


whereas Q_1 is the transistor that remains in saturation and "takes" all the available current:

$$i_{D1} = I$$

$$\underline{-\sqrt{\frac{2I}{K}} < v_D < +\sqrt{\frac{2I}{K}}}$$

In this region, both transistors are in saturation, and the drain current through each transistor is described using the two equations given earlier. Plotting these equations, we find:

Figure 7.6 Normalized plots of the currents in a MOSFET differential pair. Note that V_{OV} is the overdrive voltage at which Q_1 and Q_2 operate when conducting drain currents equal to $I/2$.

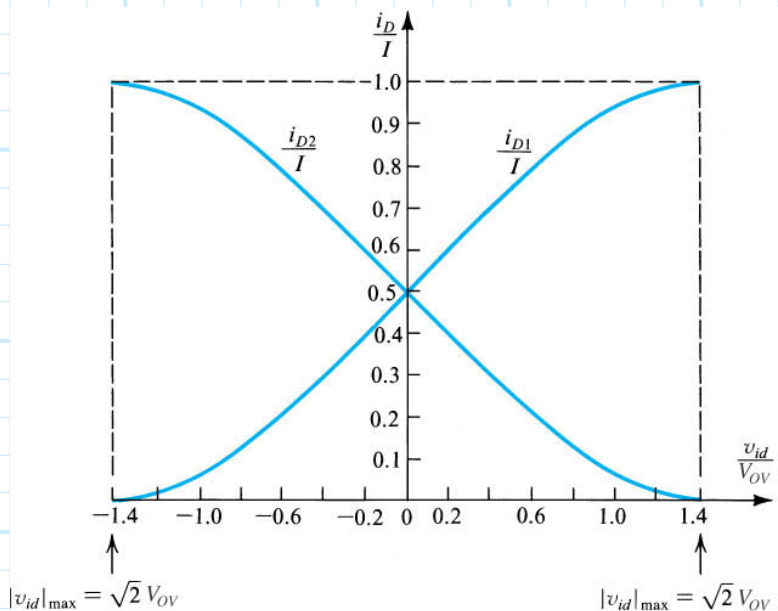

Note that the derivatives (i.e., slopes) of these curves are approximately constant in the center region of the plot (i.e., the region where $|v_D|$ is small).

This should not surprise us! If we look at the two equations for drain current:

$$i_{D1} = \frac{I}{2} + \sqrt{\frac{KI}{2}} v_D \sqrt{1 - \frac{K}{2I} v_D^2}$$

$$i_{D2} = \frac{I}{2} - \sqrt{\frac{KI}{2}} v_D \sqrt{1 - \frac{K}{2I} v_D^2}$$

we find that the last product term will approximately equal one:

$$\sqrt{1 - \frac{K}{2I} v_D^2} \approx 1 \quad \text{when} \quad |v_D| \ll \sqrt{\frac{2I}{K}}$$

Thus, we can approximate the drain currents for the case when the differential voltage $|v_D| \ll \sqrt{2I/K}$ as:

$$i_{D1} \approx \frac{I}{2} + \sqrt{\frac{KI}{2}} v_D$$

$$i_{D2} \approx \frac{I}{2} - \sqrt{\frac{KI}{2}} v_D$$

Now we can find the slope of the curves above by taking the derivative with respect to differential voltage v_D :

$$\frac{di_{D1}}{dv_D} \approx +\sqrt{\frac{KI}{2}}$$

$$\frac{di_{D2}}{dv_D} \approx -\sqrt{\frac{KI}{2}}$$

The slopes (derivatives) are approximately **constant** for small v_D -just as we **observed** they were in the plots above!

Q: *These **derivative** values likewise tell us something very important about the behavior of the MOSFET differential pair, do you know what these derivatives tell us?*

A: