

Special Problem 2.3-5

Determine **output voltage** $v_o(t)$ in terms of input voltage $v_I(t)$

