

5-2 Current-Voltage Characteristics

Reading Assignment: pp. 392 - 402

We will find that BJTs are in many ways similar and analogous to MOSFETs!

For example, we will find:


<u>BJT</u>		<u>MOSFET</u>
Base	is analogous to	Gate
Collector	"	Drain
Emitter	"	Source
Cutoff	"	Cutoff
Saturation	"	Triode
Active	"	Saturation
i_c	"	i_D
V_{BE}	"	V_{GS}
V_{DS}	"	V_{CE}

Look for these analogies to help you understand BJTs!


HO: BJT Symbols and Conventions

HO: A Mathematical Description of BJT Behavior

BJT Symbols and Conventions

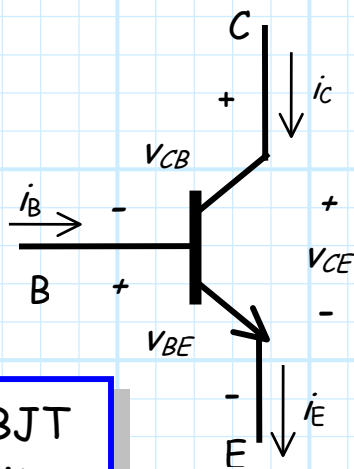

nnp BJT
Circuit
Symbol

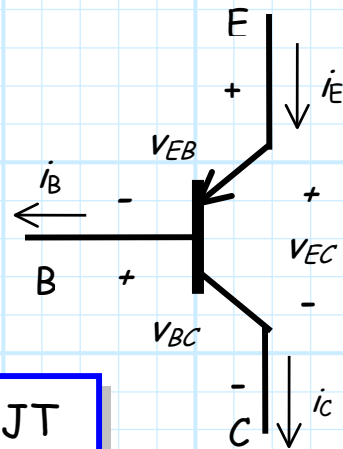

pnp BJT
Circuit
Symbol

From KCL only we find:

$$i_E = i_B + i_C$$

From KVL only we find:

$$V_{CE} = V_{CB} + V_{BE} \quad (npn)$$

$$V_{EC} = V_{EB} + V_{BC} \quad (pnp)$$

Note that:

- * The circuit **symbols** are very **similar** to MOSFETs, with *npn* like N-MOS and *pnp* like P-MOS.
- * Positive **current** is defined in **opposite** directions for *npn* and for *pnp* (just like N-MOS and PMOS!).
- * The **voltages** are of **opposite** polarity for *npn* and *pnp*. Specifically, for *npn* we use v_{BE} , v_{CE} and v_{CB} , whereas for *pnp* we use v_{EB} , v_{EC} and v_{BC} . This convention typically results in **positive** voltage values for **both** *npn* and *pnp* (**unlike** the MOSFET convention!).
- * The **base current** i_B is **not** equal to zero, therefore $i_E \neq i_C$ (**unlike** MOSFETS)!

A Mathematical Description of BJT Behavior

Now that we understand the **physical** behavior of a BJT—that is, the behavior for each of the three BJT **modes** (active, saturation, and cutoff)—we need to determine also the **mathematical** description of BJT behavior.

We will find that BJT behavior is in many ways **similar** to MOSFET behavior!

ACTIVE MODE

We found earlier that forward biasing the **emitter-base** junction (EBJ) results in **collector** (drift) current. The junction voltage for the EBJ is v_{BE} (for npn).

Thus, in active mode, the voltage **base-to-emitter** v_{BE} controls the **collector** current i_C . Specifically, we find that:

$$i_C = I_S e^{v_{BE}/V_T} \quad (\text{nnp})$$

$$i_C = I_S e^{v_{EB}/V_T} \quad (\text{pnp})$$

Here we should note **two** things:

1. *The active mode equation is very **similar** to the p-n junction diode equation.*

No surprise here! The collector current is directly proportional to the **diffusion** current across the EBJ. That's why the equation is just like the diffusion current equation for a *pn* junction.

In fact, I_S is **scale current** (a device parameter), and V_T is the **thermal voltage** (25 mV)—the same values used to describe junction diodes!

2. *A BJT in ACTIVE mode is **analogous** to a MOSFET in SATURATION mode.*

Recall that for a MOSFET in SATURATION, the **drain** current i_D is "**controlled**" by the **gate-to-source** voltage V_{GS} .


Likewise, for a BJT in ACTIVE mode, the **collector** current i_C is "**controlled**" by the **base-to-emitter** voltage V_{BE} .

Note the **analogies!**


i_D analogous to i_C

V_{BE} analogous to V_{GS}



ACTIVE analogous to SATURATION

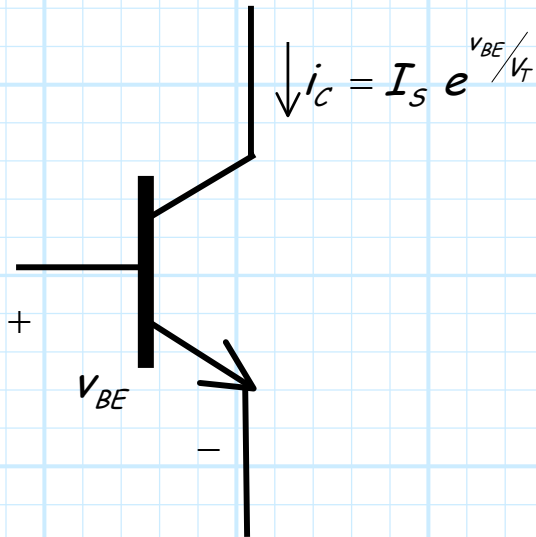

npn in ACTIVE mode

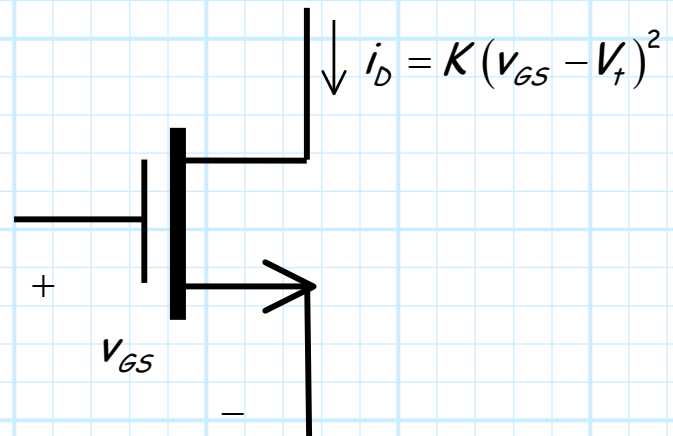

NMOS in SATURATION mode

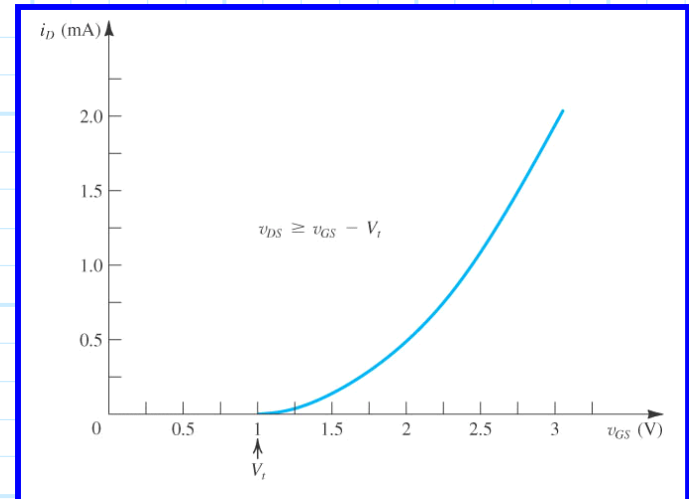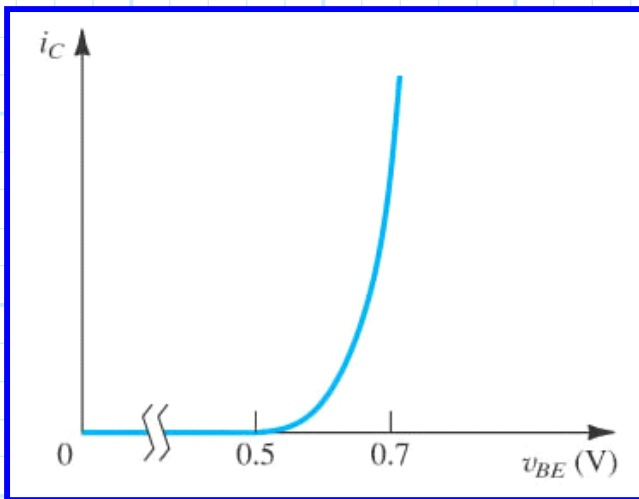

Note also that a **necessary** (but not sufficient) condition for a *npn* BJT to be in ACTIVE mode is that $v_{BE} > 0$ (i.e., the EBJ is forward biased).

This is **analogous** to an NMOS in SATURATION, where a **necessary** (but not sufficient) condition is that $v_{GS} > V_t$ (i.e., the channel is conducting).

Likewise, for a BJT to be in the **ACTIVE** mode, the **CBJ** must be in **reverse bias** (i.e., $v_{BC} < 0$). Assuming that the forward biased EBJ results in $v_{BE} \approx 0.7\text{V}$, we can use **KVL** to determine that the CBJ will be reverse biased only when:

$$v_{CE} > 0.7\text{V} \quad \text{for } npn \text{ in ACTIVE}$$

$$v_{EC} > 0.7\text{V} \quad \text{for } pnp \text{ in ACTIVE}$$

These statements above are **analogous** to the MOSFET inequality $v_{DS} > v_{GS} - V_t$ for MOSFET SAT. (more on this later!).

Now, we are tempted to make **another analogy** between base **current** i_B and gate **current** i_G , but here the analogies **end!**

Recall $i_G = 0$ **always**, but for BJTs we find that i_B is **not equal to zero** (generally).

Instead, we found that although **most** of the charge carriers (e.g., holes or free electrons) diffusing across the EBJ end up "drifting" across the CBJ into the **collector**, **some** charge carriers do "exit" the **base** terminal.

Recall, however, that for every **one** charge carrier that leaves the **base** terminal, there are typically **50 to 250** (depending on the BJT) charge carriers that drift into the collector.

As a result, the **collector current** for ACTIVE mode is typically 50 to 250 times **larger** than the **base current**! I.E.:

$$50 < \frac{i_C}{i_B} < 250 \quad \text{typically, for BJT ACTIVE}$$

The **precise** value of this ratio is the **device parameter** β (**beta**):

$$\beta \doteq \frac{i_C}{i_B} \quad \text{for BJT ACTIVE mode}$$

Thus, we find that the **base current** can be expressed as:

$$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{BE}/V_T} \quad (\text{nnp})$$

$$i_B = \frac{i_C}{\beta} = \frac{I_S}{\beta} e^{v_{EB}/V_T} \quad (\text{pnp})$$

Likewise, from **KCL**, we can determine the **emitter current** for a BJT in the **ACTIVE** mode:

$$\begin{aligned}i_E &= i_C + i_B \\ &= \beta i_B + i_B \\ &= (\beta + 1) i_B\end{aligned}$$

Or similarly,

$$\begin{aligned}i_E &= i_C + i_B \\ &= i_C + \frac{i_C}{\beta} \\ &= \left(1 + \frac{1}{\beta}\right) i_C \\ &= \left(\frac{\beta + 1}{\beta}\right) i_C\end{aligned}$$

An **alternative** to device parameter β is the **device parameter** α , defined as:

$$\alpha = \frac{\beta}{\beta + 1}$$

Note that the value of α will be just **slightly less than one**.

We can thus **alternatively** express the current relationships as:

$$i_C = \alpha i_E \quad i_B = (1 - \alpha) i_E$$

And therefore:

$$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{BE}/V_T} \quad (\text{npn})$$

$$i_E = \frac{i_C}{\alpha} = \frac{I_S}{\alpha} e^{v_{EB}/V_T} \quad (\text{pnp})$$

Recall that the **exponential** expression for a *pn* junction turned out to be of **limited** use, as it typically led to unsolvable **transcendental equations**.

The **same** is true for **these** exponential equations! We will thus generally use the equations below to **approximate** the behavior of a BJT in the **ACTIVE** mode:

$$v_{BE} \approx 0.7 \quad i_C = \beta i_B \quad v_{CE} > 0.7 \quad (\text{npn in ACTIVE})$$

$$v_{EB} \approx 0.7 \quad i_C = \beta i_B \quad v_{EC} > 0.7 \quad (\text{pnp in ACTIVE})$$

SATURATION MODE

Recall for BJT **SATURATION** mode that **both** the CBJ and the EBJ are **forward biased**.

Thus, the collector current is due to **two** physical mechanisms, the **first** being charge carriers (holes or free-electrons) that

drift across the CBJ (just like ACTIVE mode), and the **second** being charge carriers that **diffuse** across the forward biased CBJ!

As a result, a **second term** appears in our mathematical description of **collector current** (when the BJT is in SATURATION):

$$i_C = I_S e^{v_{BE}/V_T} - \left(\frac{I_S}{\alpha_R} \right) e^{v_{BC}/V_T} \quad (\text{npn})$$

$$i_C = I_S e^{v_{EB}/V_T} - \left(\frac{I_S}{\alpha_R} \right) e^{v_{CB}/V_T} \quad (\text{pnp})$$

where α_R represents the **same** device parameter α discussed earlier (for ACTIVE mode), with the only difference that it specifies the value of α specifically for the **CBJ**.

This second term describes the current due to **diffusion** across the CBJ. Note that this current is in the **opposite** direction of the drift current (the first term), hence the **minus** sign in the second term.

Now using **KVL** (i.e., $v_{CE} = v_{CB} + v_{BE}$), we can write this collector current equation as:

$$\begin{aligned}
 i_C &= I_S e^{v_{BE}/V_T} - \left(\frac{I_S}{\alpha_R} \right) e^{(v_{BE}-v_{CE})/V_T} \\
 &= I_S e^{v_{BE}/V_T} \left(1 - \frac{e^{-v_{CE}/V_T}}{\alpha_R} \right)
 \end{aligned}$$

Thus, we can conclude:

$$i_C = I_S e^{v_{BE}/V_T} \left(1 - \frac{e^{-v_{CE}/V_T}}{\alpha_R} \right) \quad \text{for } npn \text{ in SAT.}$$

$$i_C = I_S e^{v_{EB}/V_T} \left(1 - \frac{e^{-v_{EC}/V_T}}{\alpha_R} \right) \quad \text{for } pnp \text{ in SAT.}$$


It is thus clear that for a BJT in SATURATION, the collector current i_C is dependent on **both** v_{BE} and v_{CE} .

This is precisely **analogous** to the TRIODE mode for MOSFETS!


Recall for **triode** mode, drain current i_D is dependent on both v_{GS} and v_{DS} . We thus have discovered **two** new analogies:

V_{CE} analogous to V_{DS}



SATURATION analogous to TRIODE

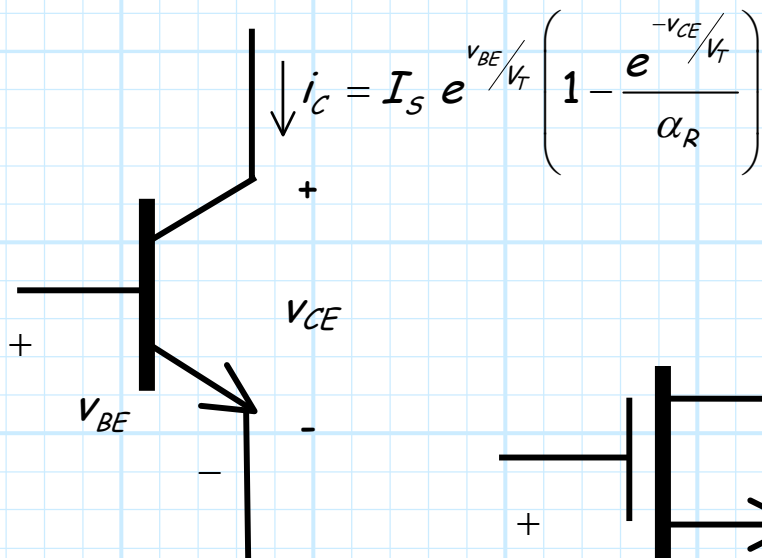

npn in SAT. mode

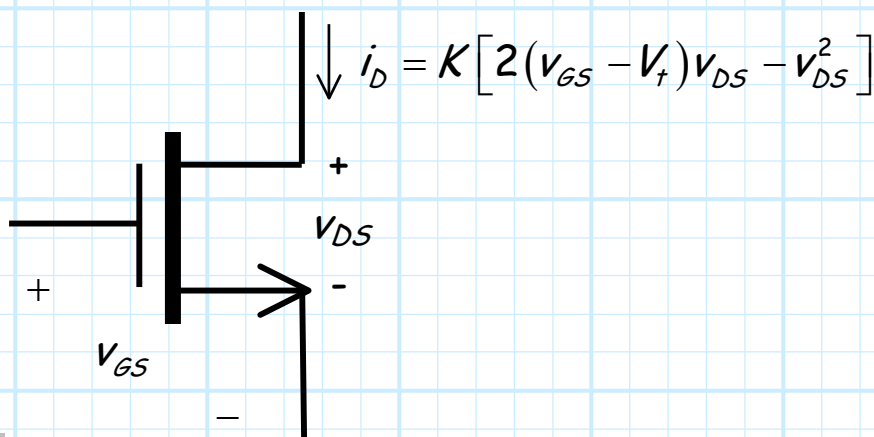

NMOS in TRIODE mode

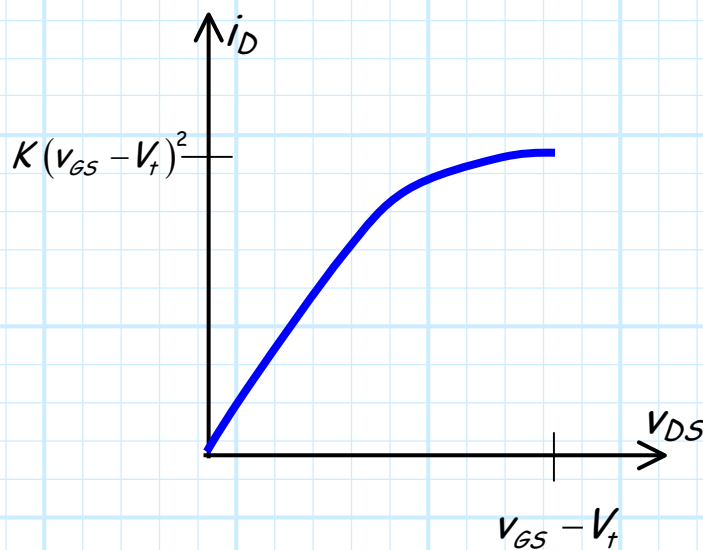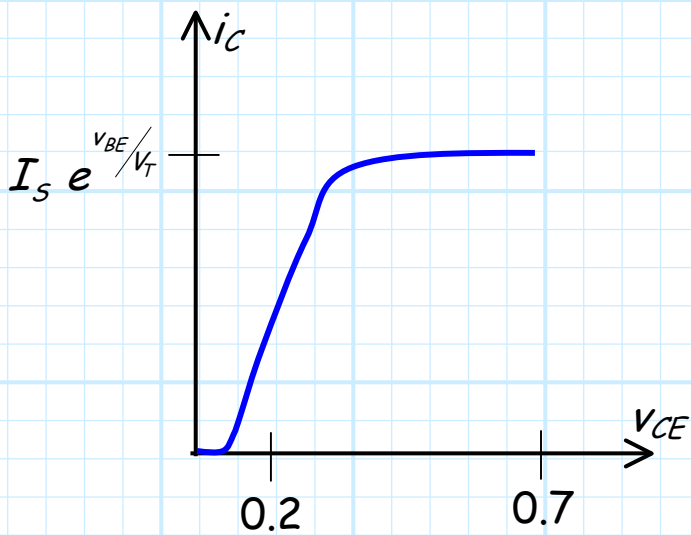

Now, a BJT is in SATURATION mode if **both** the CBJ and the EBJ are **forward biased**. Assuming that $v_{BE} \approx 0.7V$ if the EBJ is forward biased, the CBJ voltage v_{BC} will be positive **only** if (using KVL):

$$\begin{aligned}v_{BC} &> 0 \\v_{BE} - v_{CE} &> 0 \\0.7 - v_{CE} &> 0 \\v_{CE} &< 0.7\end{aligned}$$

Thus, we can conclude that a **necessary** (but not sufficient) condition for a BJT to be in SATURATION is:

$$v_{CE} < 0.7 \quad \text{for } npn \text{ in SAT.}$$

$$v_{EC} < 0.7 \quad \text{for } pnp \text{ in SAT.}$$

These inequalities are **analogous** to the MOSFET inequalities:

$$v_{DS} < v_{GS} - V_t \quad \text{for NMOS in Triode}$$

$$v_{DS} > v_{GS} - V_t \quad \text{for PMOS in Triode}$$

Now, we note for the BJT SATURATION mode that the **collector current will always be less** than that in ACTIVE mode with the same value of v_{BE} :

$$I_S e^{v_{BE}/V_T} \left(1 - \frac{e^{-v_{CE}/V_T}}{\alpha_R} \right) < I_S e^{v_{BE}/V_T} \text{ for all } v_{CE}$$

Thus, we can **equivalently** state that the collector current in SATURATION will be **less** than the value βi_B :

$$i_C < \beta i_B \text{ for BJT in SAT.}$$

This of course means that the **base** current in SAT. is **greater** than i_C/β (i.e., the base current in active):

$$i_B > \frac{i_C}{\beta} \text{ for BJT in SAT.}$$

Likewise, this means that:

$$i_E < (\beta + 1)i_B \text{ and } i_C < \alpha i_E \text{ for BJT in SAT.}$$

But remember KCL is still valid for BJTs in SATURATION (it's **always** valid!):

$$i_E = i_B + i_C \text{ (KCL)}$$

Finally, we should again note that the **exponential** equations presented for SATURATION mode are **not** particularly useful for analyzing BJT circuits (that **transcendental** equation thing again!).

Thus, we describe a BJT in SATURATION with some **approximate** equations. Since both CBJ and EBJ are forward biased, we assume that $v_{BE} \approx 0.7V$ and that $v_{BC} \approx 0.5V$, resulting in the following **approximate** description for a BJT in SATURATION:

$$v_{BE} \approx 0.7V \quad v_{CE} \approx 0.2V \quad i_C < \beta i_B \quad \text{for } npn \text{ in SAT.}$$

$$v_{EB} \approx 0.7V \quad v_{EC} \approx 0.2V \quad i_C < \beta i_B \quad \text{for } pnp \text{ in SAT.}$$

CUTOFF MODE

Cutoff mode for BJTs is obviously **analogous** to cutoff mode for MOSFETS.

In both cases the transistor currents are **zero!**

$$i_E = i_B = i_C = 0 \quad \text{for BJTs in CUTOFF}$$

Note that a BJT is in cutoff if **both** EBJ and CBJ are in **reverse bias**. This is true if:

$v_{BE} < 0$ and $v_{BC} < 0$ for *npn* in CUTOFF

$v_{EB} < 0$ and $v_{CB} < 0$ for *pnp* in CUTOFF