

**Special Problem 2.3-2**

An amplifier with an open-circuit voltage gain of  $A_{vo} = 10$  and an output resistance of  $R_o = 1\text{K}$  is connected in series to an inverting amplifier, as shown below.

Find the value of  $R_1$  so that  $V_o/V_I = -100$ .

