

Special Problem 2.3-3

Determine the **output voltage** $v_o(t)$ of the circuit below:

