

**Special Problem 2.3-5**

Determine **output voltage**  $v_o(t)$  in terms of input voltage  $v_I(t)$

