

Special Problem 2.6-4

Determine the complex transfer function $T(\omega) = v_o(\omega)/v_i(\omega)$ for this circuit.

