

Special Problem 2.6-5

Determine the time-domain output signal $v_o(t)$ in terms of the two input signals $v_1(t)$ and $v_2(t)$.

