

Special Problem 2.7-3

Homer S. constructed the following circuit in his garage.

He determined that the **3dB frequency** (f_{3dB}) of this circuit is **1 MHz** -- exactly the bandwidth he wanted.

In order to generate more gain, Homer now decides to **change** the value of R_2 to $R_2 = 19K..$

1) What is the **new 3dB frequency** Homer's circuit (i.e., when $R_2 = 19 K$)?

2) (optional, no credit) What did Homer **say** when he measured this new 3dB frequency?

