

### Special Problem 2.8-5

The op-amp in the circuit below has a **slew rate** of 10 volts/ $\mu$ sec.

Its **output** voltage is **limited** to  $-15 < v_o(t) < 15$  (otherwise the output **saturates**).

The **input** signal is:

$$v_i(t) = 0.25t^2 \quad \text{V}$$

where time  $t$  is in **microseconds**.

Determine the **time**  $t$  (in microseconds) when the output signal  $v_o(t)$  begins to **distort** for **any reason**, if:

a)  $R_2 = 3K$

b)  $R_2 = 15K$

