

Special Problem 4.6-11

Assume **both** transistors are in active mode.

1) Based on these assumptions, determine the collector currents i_c , and collector voltages V_C for each transistor.

2) Determine if the original **assumptions** were correct.

