

Special Problem 4.6-12

Assume the BJT is in **active** mode.

- 1) Based on this assumption, find collector current i_c and collector voltage V_c
- 2) Determine if the original **assumption** was correct.

