

Special Problem 4.6-13

Assume the BJT is in **active** mode.

1) Based on this assumption, find collector current i_c , collector voltage V_c and emitter voltage V_E .

2) Determine **if** the original **assumption** was correct.

