

Special Problem 4.6-15

Assume that both BJTs are in **active** mode.

Find the **collector voltage** for **each BJT**.

Check to see if the active assumption is correct.

