

Special Problem 4.6-2

Assume that both transistors are in **active** mode.

Find then the **base currents** and **collector voltages** for each transistor.

Determine whether the active assumption for **each** transistor was correct.

