

Special Problem 4.12 -5

It is known that the emitter voltage of the transistor in this circuit is at 2 volts with respect to ground (i.e., $V_E = 2.0\text{ V}$).

What then, is the value of resistor R?

