

Special Problem 4.6-6

Assuming that Q_1 and Q_2 are both in the active mode, determine the **base currents** i_B and **collector voltages** V_C of each transistor.

Are the active assumptions correct? Provide **complete** numerical justification for your answer.

