

Special Problem 4.6-7

Assume the transistor below is in **active region** ($\beta = 49$).

- 1) Determine the **emitter current** and **voltage collector to emitter**.
- 2) **Check** the assumption and **determine** if it is valid.

