

Special Problem 4.6-8

In the circuit below, the collector-to-emitter voltage is $V_{CE} = 5.8 \text{ V}$.

The transistor is in the **active** region.

What is β for this transistor?

